

Special Problem 4.6-9

For the circuit below, **assume** that the BJT is in the **active** region.

Determine the **base current** and the **collector voltage**.

Determine **whether** the active assumption was correct.

