

Special Problem 4.7-3

Bart has created a **new kind** of transistor for Springfield Elementary's science fair.

This transistor has **three terminals**, named Homer (H), Lisa (L), and Marge (M).

Bart has discovered in the lab that i_H (in mA) is related to v_{LM} (in volts) as:

$$i_H = 3 (v_{LM})^2 - 2 v_{LM} \quad (\text{mA})$$

He has also discovered that i_L (in mA) is related to v_{LM} (in volts) as:

$$i_L = 0.2 (v_{LM})^2 + 0.3 v_{LM} \quad (\text{mA})$$

Note that Bart's transistor is **completley unrelated** to either a BJT or a MOSFET.

Say that Bart has placed a **DC bias voltage** between terminals L and M of $V_{LM}=3.0$ V.

For this bias point, determine the **numeric values** of **small-signal** parameters g_h and r_l , that Bart has **defined** as:

$$g_h \doteq \frac{i_h}{v_{lm}} \quad \text{and} \quad r_l \doteq \frac{v_{lm}}{i_l}$$

where v_{lm} is a **small-signal voltage** and i_h, i_l are **small-signal currents**.

