

Special Problem 5.4-1

Assume the transistor Q_1 is in saturation.

- 1) Find the **drain current** (i_D).
- 2) **Check the assumption** and determine if it is valid.

