

Special Problem 5.4-2

The gate voltage of this circuit is at -1.0 volt ($V_G = -1.0$ V).

Note the MOSFET is a **depletion** type.

Find the value of **resistor R**.

