

Special Problem 5.4-4

In the circuit below, find the **values** of the drain-to-source voltage V_{DS} and the gate-to-source voltage V_{GS} .

Note that the MOSFET in the circuit is a **depletion** type.

