

Special Problem 5.4-5

The PMOS transistor in the circuit below is known to have a gate-to-source voltage of $V_{GS} = -4\text{ V}$.

1) Find the value of resistor **R**.

2) Find the value of V_{DS} .

