

Special Problem 5.4-6

The MOSFET in the circuit below is a **depletion** type.

Determine the **drain current** and **voltage drain to source**.

