

Special Problem - 5.5-8

The capacitors in this circuit are very large.

Determine the small-signal voltage gain $A_v = v_o/v_i$ of this amplifier.

Determine the small-signal input resistance of this amplifier.

