

### Special Problem - 5.5-8

The capacitors in this circuit are very large.

Determine the small-signal voltage gain  $A_v = v_o/v_i$  of this amplifier.

Determine the small-signal input resistance of this amplifier.

