

Special Problem 2.3-1

Find an expression for V_O in terms of V_I for the circuit shown below.

