

**Special Problem 2.4-1**

The input  $V_A(\omega)$  is a signal expressed as its Fourier Transform.

You of course recall that the impedance of an inductor is  $Z = j\omega L$ .

Note both resistors have the same value.

Determine  $V_O(\omega)$  in terms of  $V_A(\omega)$ .

