

**Special Problem 2.5-1**

For the following circuit, **determine**  $v_O$  in terms of  $v_I$ .

