

**Special Problem 2.6-1**

For the circuit below, find  $v_o$  in terms of inputs  $v_1$  and  $v_2$ .

Find both the **differential** and **common-mode** gains of this amplifier.

Determine CMRR.

