

Special Problem 2.6-3

Determine the open-circuit voltage gain of this amplifier.

