

Special Problem 4.6-14

Assume the BJT in the circuit below is in **active mode**.

- 1) Determine **base current I_B** and **collector voltage V_C**
- 2) Determine if the active mode **assumption** is correct.

