

Special Problem 4.6-4

Assume the transistor is in the **active** region and determine **collector voltage V_C** .

Was the active assumption correct? **Clearly** state why or why not.

