

### Problem 3 - 15 points


Bart has created a **new kind** of transistor for Springfield Elementary's science fair.

This transistor has **three terminals**, named Homer (**H**), Lisa (**L**), and Marge (**M**).

Bart has discovered in the lab that  $i_H$  (in mA) is related to  $v_{LM}$  (in volts) as:

$$i_H = 3 (v_{LM})^2 - 2 v_{LM} \quad (\text{mA})$$

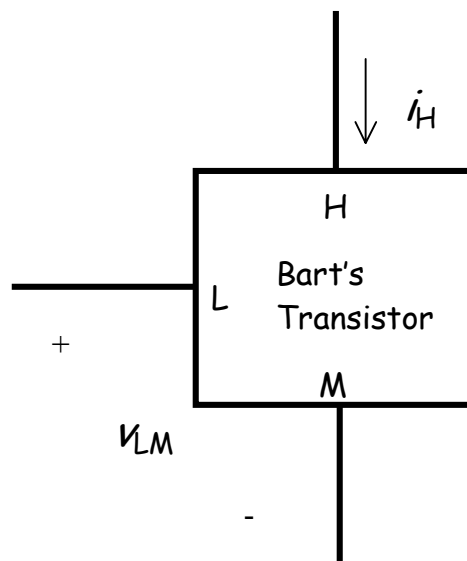Note that Bart's transistor is **completley unrelated** to either a BJT or a MOSFET.



Determine the **DC current** ( $I_H$ ) and **small signal current** ( $i_H(t)$ ) flowing into terminal **H** if the total voltage between terminals **L** and **M** is:

$$v_{LM} = 1 + 0.01 \cos \omega t$$