

Special Problem 4.8-1

The capacitors in the circuit below are very large.

The signal $v_i(t)$ is small.

Determine the small-signal voltage gain $A_v = v_o/v_i$

