

Special Problem 4.8-2

Determine:

- the small-signal gain $A_o = v_o/v_i$ of the amplifier.
- the small-signal input resistance of the amplifier

