

Special Problem 5.4 - 3

For the circuit shown below, determine the value of resistor R_D .

