

Special Problem 5.5 - 4

The threshold voltage of the transistor is $V_T = 2.0$ Volts, $K = 0.125$ mA/V².

The capacitors are **very** large.

Find the **small-signal gain** $A_v = v_o/v_i$ of this amplifier.

