

Special Problem 5.5-6

The A.C signal $v_i(t)$ is very small.

The capacitors in the circuit are very large.

Find the small-signal voltage gain $A_v = v_o/v_i$ of the amplifier below.

