

Special Problem 5.6-1

In the circuit below, Q_1 has $K_1=2 \text{ mA/V}^2$ and $V_t = 2.0 \text{ V}$.

But, Q_2 has $K_2 = 1 \text{ mA/V}^2$ and $V_t = 2.0 \text{ V}$.

In other words Q_1 and Q_2 are **not** identical!

1) **Determine R** so that the **drain current of Q_1 is 8 mA**.

2) What then is the **drain voltage of Q_2** ?

