

Special Problem 6.6-1

For the **differential amplifier** shown below, the **DC** components of v_{I1} and v_{I2} are **equal**.

Both transistors Q_1 and Q_2 are in **saturation**.

The transistors are identical, with $K = 1 \text{ mA/V}^2$ and $V_f = 1.0 \text{ V}$

Find the **small signal differential gain** $A_d = v_{o1}/v_d$ for the differential amplifier shown below.

