

5. Circulators and Isolators

Q: *All the devices we have studied thus far are **reciprocal**. Are there such things as **non-reciprocal** microwave devices?*

A:

HO: The Circulator

HO: The Isolator

Circulators

A circulator is a matched, lossless but **non-reciprocal** 3-port device, whose scattering matrix is **ideally**:



$$\bar{\bar{\mathbf{S}}} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

Circulators use anisotropic **ferrite** materials, which are often "biased" by a permanent magnet! → The result is a **non-reciprocal** device!

First, we note that for a circulator, the power incident on port 1 will exit **completely** from port 2:


$$P_2^- = P_1^+$$

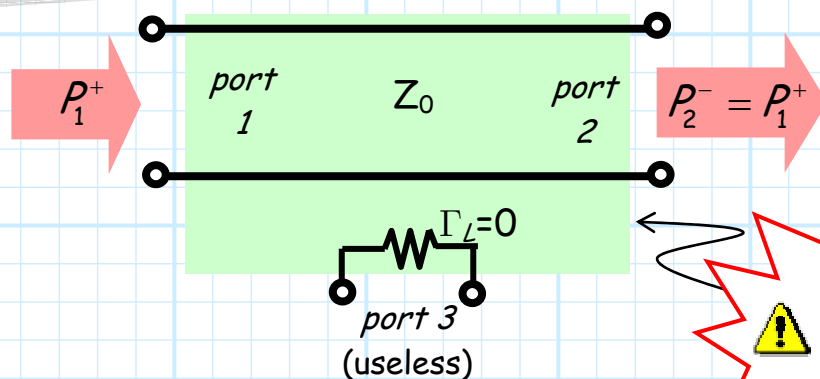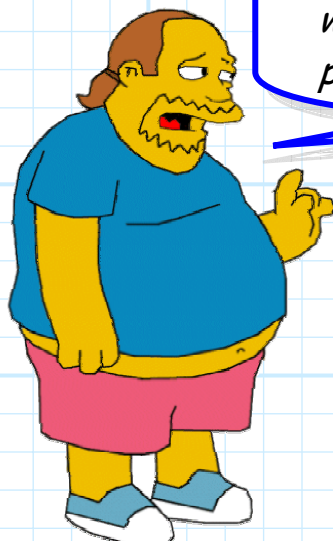Pardon me while I sarcastically yawn. This unremarkable behavior is likewise true for the simple circuit below, which requires just a length of transmission line. Oh please, continue to waste our valuable time.



This is **not** a circulator!

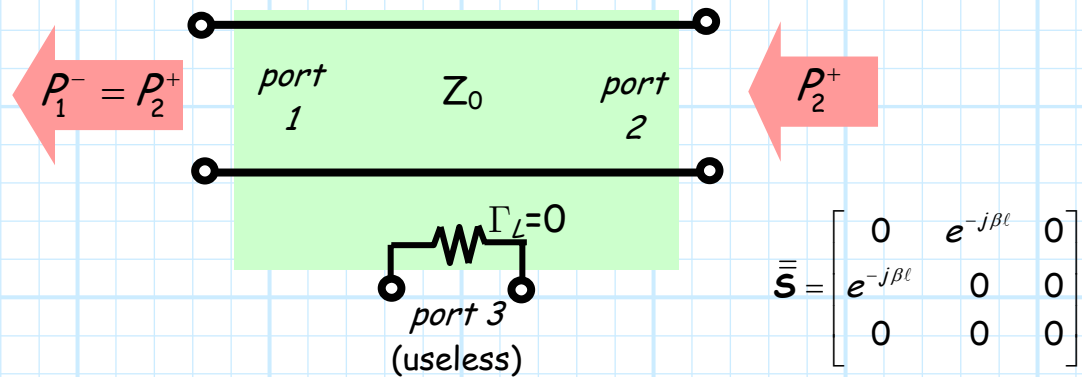True! But a transmission line, being a **reciprocal** device, will likewise result in the power incident on **port 2** of your simple circuit to **exit** completely from **port 1** ($P_1^- = P_2^+$):



But, this is **not** true for a circulator! If power is incident on port 2, then **no power** will exit port 1!




Q: You have been *surprisingly* successful in regaining my interest. Please tell us then, just *where* does the power incident on port 2 go?

A: It will exit from port 3!


Likewise, power flowing into **port 3** will exit—**port 1**!

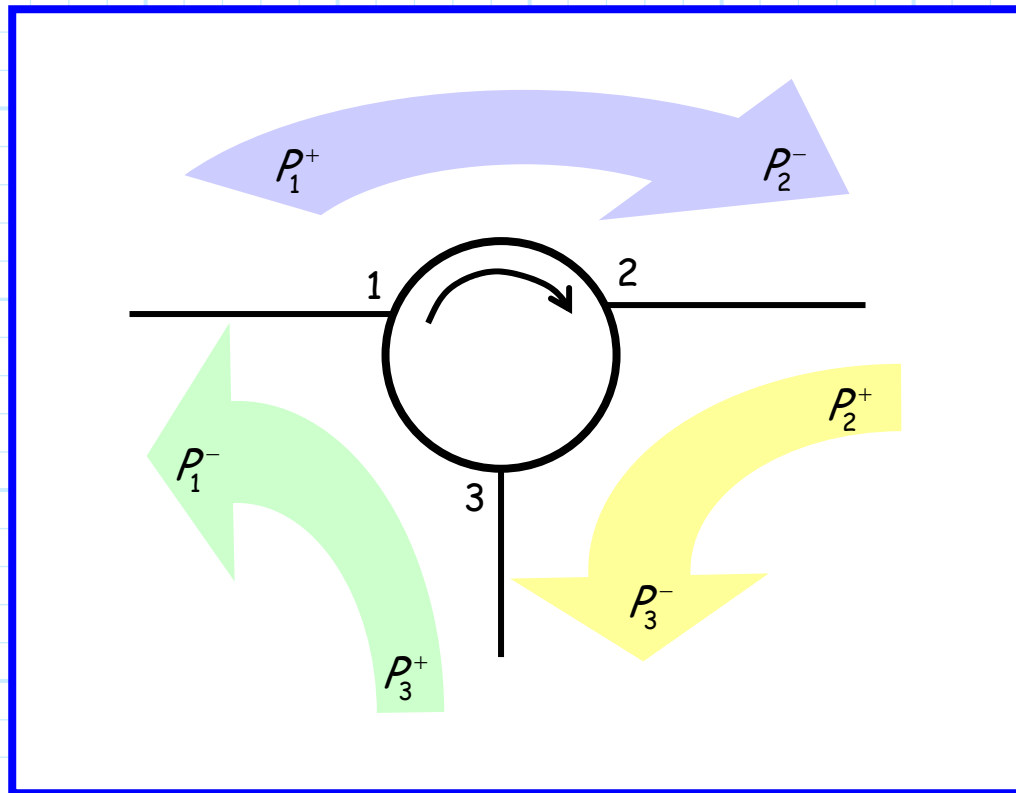It is evident, then how the circulator gets its **name**: power appears to **circulate** around the device, a behavior that is emphasized by its device **symbol**:



We can see that, for example, a **source** at port 2 “thinks” it is attached to a **load** at port 3, while a **load** at port 2 “thinks” it is attached to a **source** at port 1!

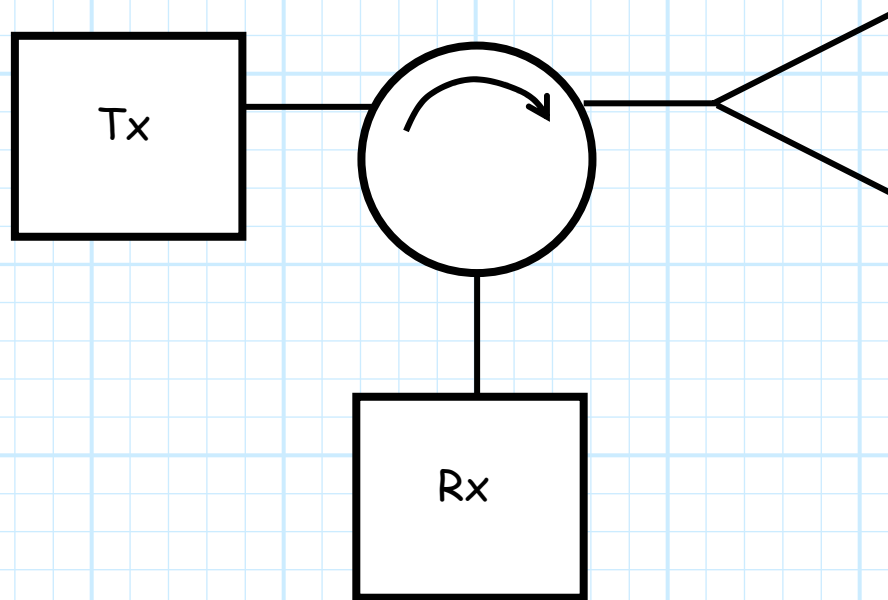This behavior is useful when we want to use **one** antenna as **both** the transmitter and receiver antenna. The transmit antenna (i.e., the load) at port 2 **gets** its power from the transmitter at **port 1**. However, the receive antenna (i.e., the source) at port 2 **delivers** its power to the receiver at **port 3**!




It is **particularly** important to keep the transmitter power from getting to the receiver. To accomplish this, the **antenna** must be **matched** to the transmission line. Do **you** see why?

Finally, we should note some major **drawbacks** with a circulator:

1. They're **expensive**.
2. They're **heavy**.
3. They generally produce a large, static **magnetic field**.
4. They typically exhibit a large **insertion loss** (e.g., $|S_{21}|^2 = |S_{32}|^2 = |S_{13}|^2 \approx 0.75$).

Isolators

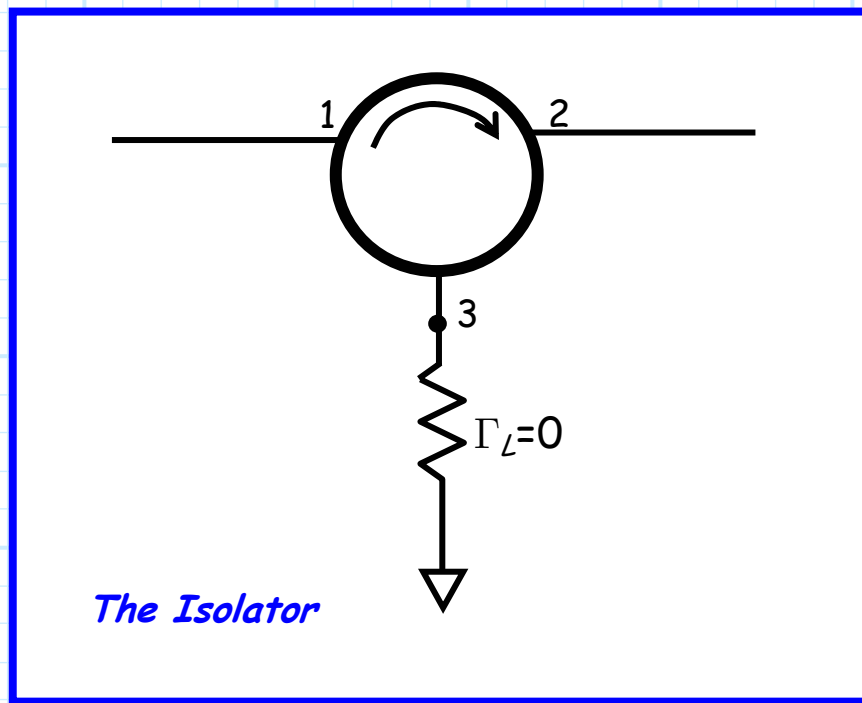An **isolator** is simply a **circulator**, with port 3 terminated in a **matched** load!




The matched load at port 3 insures that $P_3^+ = 0$ **always**. As a result we know that $P_1^- = P_3^+ = 0$ **--always!**

An ideal isolator is thus a **two-port** device with an **odd** looking scattering matrix:

$$\bar{\bar{S}} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$


Therefore, $P_2^- = P_1^+$, but $P_1^- = 0$ regardless of P_2^+ --an ideal isolator is matched, but is also non-reciprocal and **lossy**!

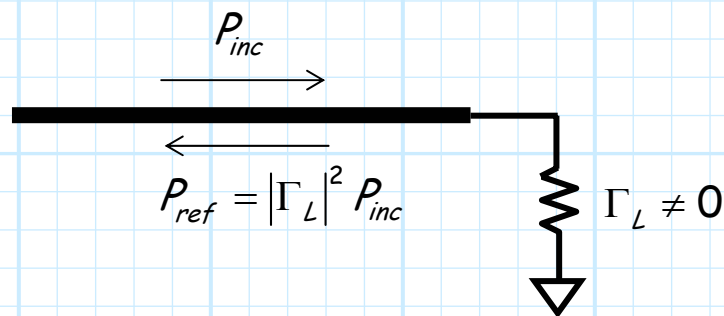An isolator is useful for **isolating** a load from a source. For example, consider an **unmatched** load at the end of a transmission line:



Plenty of power is reflected back toward the source!

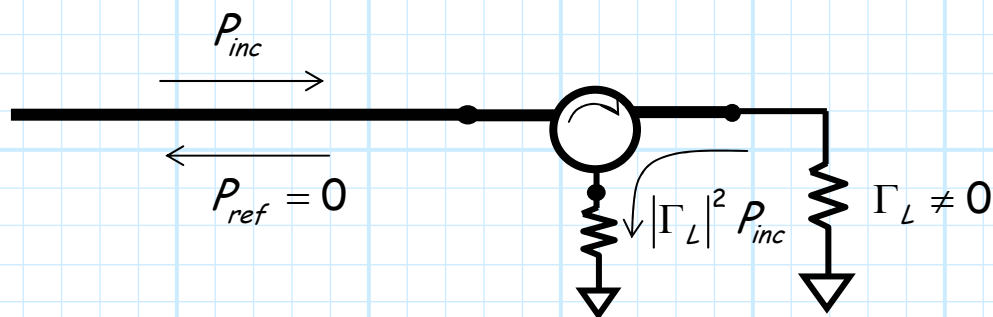Now, let's **insert** an isolator between the source and load:



There is **no power** reflected back to the source! Instead, power reflected by the load is **absorbed** by the isolator.

To the source, the circuit appears **matched**—but it's **not**!

If the isolator was truly a matching network, then the **absence** of reflected power would indicate that **all** the incident power was absorbed by the **load**. Instead, there is no reflected power because this power is instead absorbed by the **isolator**—the isolator is **lossy**!