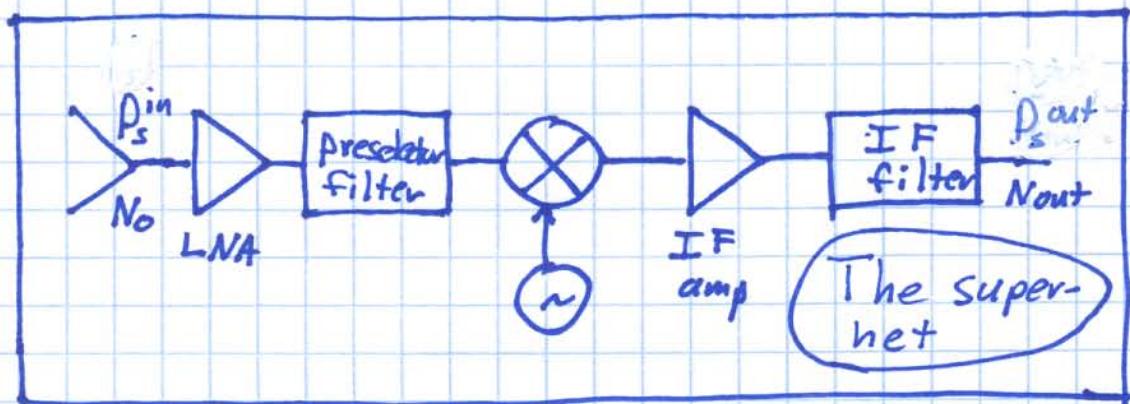


# Rx Gain and Noise Figure

We can now determine the overall gain and noise figure for a super-het receiver!!

Consider the following example:



Let's look at each device:

## 1) Antenna

We assume the antenna temperature

$$T_A = T_0 = 290^\circ K, \text{ and } N_0 = -174 \text{ dB/Hz}$$

Also, the antenna couples in signal with power  $\underline{P_s}$ .

2) Low Noise Amplifier (LNA)

Say this device has gain  $G_1 = 10$   
and noise figure  $F_1 = 1.5$

3) Preselector Filter

Say this device has an insertion loss of 1dB.

$$\text{so } G_2 = -1\text{dB} = 0.8$$

$$\text{and } F_2 = 1\text{dB} = 1.26$$

4) Mixer

Say this device has a conversion loss of 6dB.

$$\text{so } G_3 = -6\text{dB} = 0.25$$

$$\text{and } F_3 = 6\text{dB} = 4$$

5) IF Amp

Say this device has gain of

30 dB and a noise figure of 6 dB

$$\therefore G_4 = 30 \text{ dB} = 1000$$

$$F_4 = 6 \text{ dB} = 4$$

### 6) I F Filter

Say this device has an insertion loss of 2 dB

$$\therefore G_5 = -2 \text{ dB} = 0.63$$

$$F_5 = 2 \text{ dB} = 1.58$$

The gain of the receiver is

$$G = G_1 G_2 G_3 G_4 G_5$$

$$= (10)(0.8)(0.25)(1000)(0.63)$$

$$= 1260 = 31 \text{ dB}$$


The noise figure of this Rx  
is  $\text{oo}$

$$\begin{aligned}
 F &= F_1 + \frac{(F_2 - 1)}{G_1} + \frac{(F_3 - 1)}{G_1 G_2} + \frac{(F_4 - 1)}{G_1 G_2 G_3} + \frac{(F_5 - 1)}{G_1 G_2 G_3 G_4} \\
 &= 1.5 + \frac{0.26}{10} + \frac{3}{10(0.6)} + \frac{3}{10(0.6)(0.25)} + \frac{0.58}{10(0.6)(0.25)(1000)} \\
 &= 1.5 + 0.026 + 0.375 + 0.094 + 3 \times 10^{-4} \\
 &= 2.0
 \end{aligned}$$

$\text{oo}$  The noise at the output of  
the IF filter is:

$$\begin{aligned}
 P_n^{\text{out}} &= FGKT_0B \\
 &= (2.0)(1260) KT_0 B \\
 &= \underline{\underline{10^{-17} B \text{ Watts}}}
 \end{aligned}$$

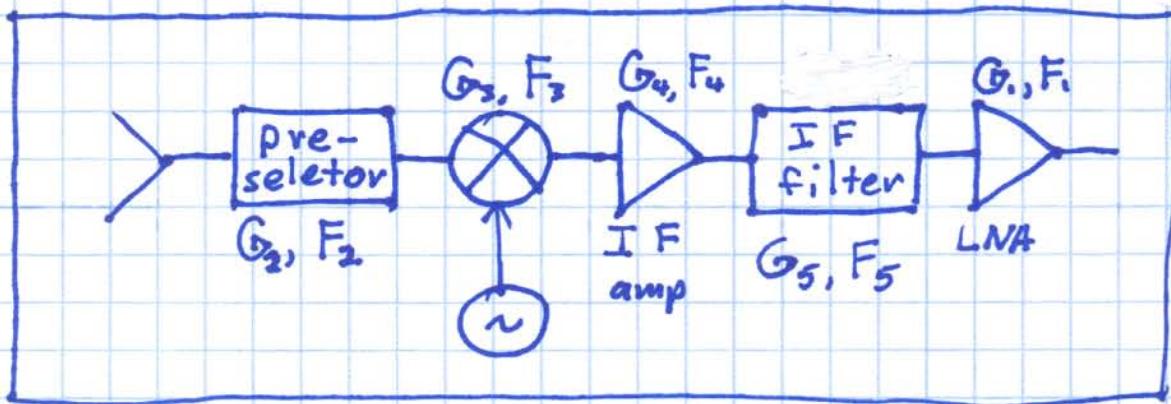Let's see what happens if we move the LNA:



$$G = G_2 G_3 G_4 G_5 G_1 = 1260 = 31 \text{ dB}$$

As before !!

But, noise figure  $F$  is:

$$\begin{aligned}
 F &= F_2 + \frac{(F_3 - 1)}{G_2} + \frac{(F_4 - 1)}{G_2 G_3} + \frac{(F_5 - 1)}{G_2 G_3 G_4} + \frac{(F_1 - 1)}{G_2 G_3 G_4 G_5} \\
 &= 1.26 + \frac{3}{0.8} + \frac{3}{0.8(0.25)} + \frac{0.58}{0.8(0.25)10^3} + \frac{0.5}{0.8(0.25)10^3 0.63} \\
 &= 1.26 + 3.75 + 15 + 0.003 + 0.004 \\
 &= \underline{\underline{20}} = 13 \text{ dB}
 \end{aligned}$$

Much bigger  
than before !!!

$$\begin{aligned}
 P_n^{\text{out}} &= FG K T_0 B \\
 &= (20)(1260) K T_0 B \\
 &= \underline{\underline{10^{-16} B \text{ Watts}}}
 \end{aligned}$$

$10 \times$  more noise than before!!

This example shows how important the LNA is for low-noise receiver design!