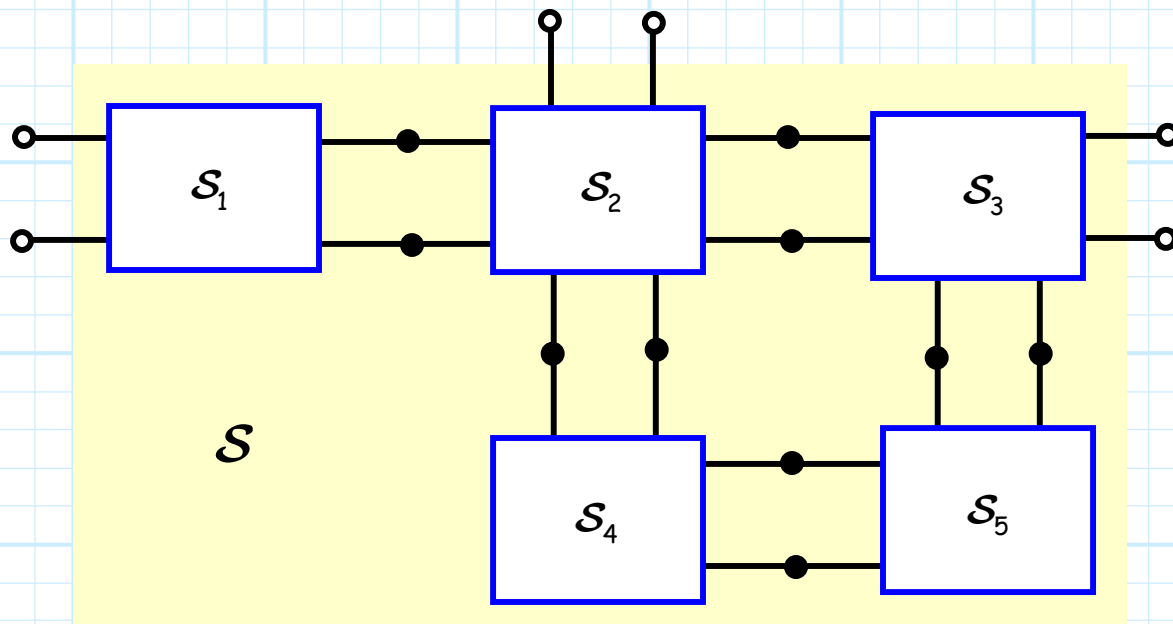


Signal Flow Graphs

Consider a complex **3-port** microwave network, constructed of **5** simpler microwave devices:



where S_n is the **scattering matrix** of each device (I've **changed** notations— $S_1 = \overline{\overline{S_1}}$!), and S is the **overall** scattering matrix of the **entire** 3-port network.

Q: *Is there any way to determine this **overall** network scattering matrix S from the **individual** device scattering matrices S_n ?*

A: **Definitely!** Note the wave **exiting** one port of a device is a wave **entering** (i.e., incident on) another (and vice versa). This is a **boundary condition** at the port connection between devices.

Add to this the scattering parameter equations from each individual device, and we have a **sufficient** amount of math to determine the relationship between the incident and exiting waves of the remaining three ports—in other words, the scattering matrix of the **3-port network**!

Q: *Yikes! Wouldn't that require a lot of **tedious** algebra!*

A: It sure would! We might use a **computer** to assist us, or we might use a tool employed since the early days of microwave engineering—the **signal flow graph**.


A signal flow graph of a microwave network is useful for **two** reasons:

- 1)** It provides a **graphical** representation of a microwave network, allowing for a **qualitative** analysis and interpretation of the network.
- 2)** It provides a method for **simplifying** (i.e., reducing) a microwave network to a more **fundamental** form, such an easier **quantitative** analysis can be achieved.

Included in this quantitative analysis can be the determination of the network's **scattering matrix**; but more on that **later**.

But first, some **definitions**!

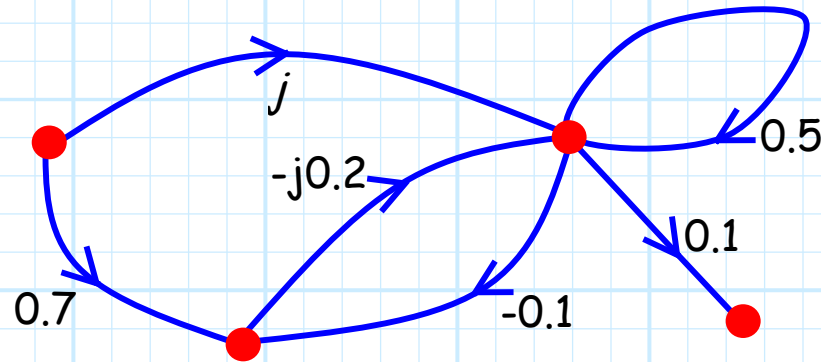Every signal flow graph consists of a set of **nodes**. These nodes are connected by **branches**, which are simply contours with a specified **direction**. Each branch likewise has a complex **value**.



Q: What could this possibly have to do with **microwave engineering**?

A: Each **port** of a microwave device is represented by **two nodes**—the “a” node and the “b” node. The “a” node simply represents the value of the **incident** wave on that port, evaluated **at** the plane of that port:

$$a_n \doteq V_n^+ (z_n = z_{nP})$$


Likewise, the “b” node simply represents the value of the **exiting** wave from that port, evaluated **at** the plane of that port:

$$b_n \doteq V_n^- (z_n = z_{nP})$$

Note then that the **total voltage** at a port is simply:

$$V_n (z_n = z_{nP}) = V_n^+ (z_n = z_{nP}) + V_n^- (z_n = z_{nP}) = a_n + b_n$$

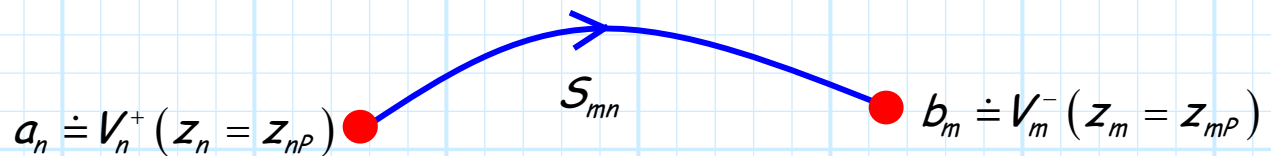The value of the **branch** connecting two nodes is simply the value of the **scattering parameter** relating these two voltage values:




The signal flow graph above is simply a **graphical** representation of the equation:

$$V_m^-(z_m = z_{mP}) = S_{mn} V_n^+(z_n = z_{nP})$$

$$b_m = S_{mn} a_n$$

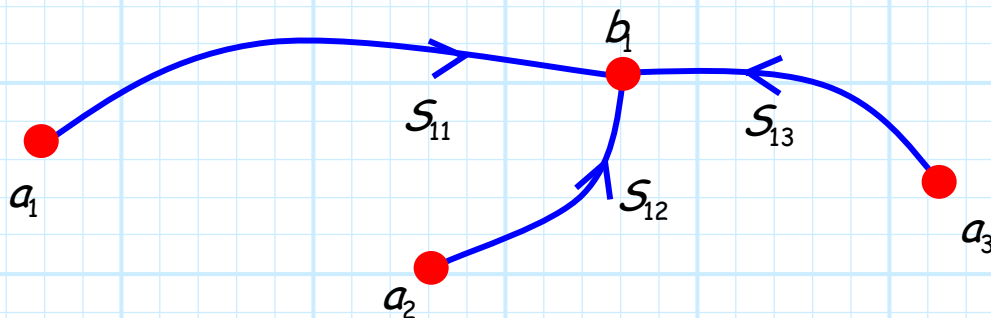Moreover, if **multiple** branches enter a node, then the voltage represented by that node is the **sum** of the values from each branch. For example, the signal flow graph:



is a **graphical** representation of the equation:

$$b_1 = S_{11} a_1 + S_{12} a_2 + S_{13} a_3$$

Now, consider a **two-port device** with a scattering matrix \mathcal{S} :


$$\mathcal{S} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

So that:


$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

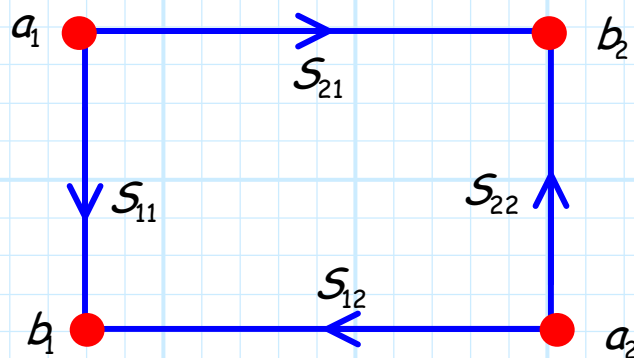We can thus **graphically** represent a **two-port device** as:



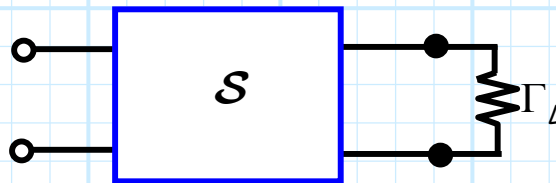Now, consider a case where the second port is **terminated** by some load Γ_L :




We now have yet **another** equation:


$$V_2^+(z_2 = z_{2p}) = \Gamma_L V_2^-(z_2 = z_{2p})$$

$$a_2 = \Gamma_L b_2$$

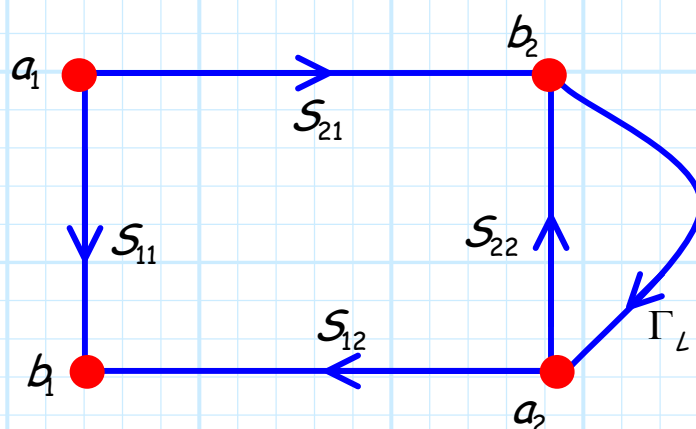Therefore, the signal flow graph of this **terminated** network is:



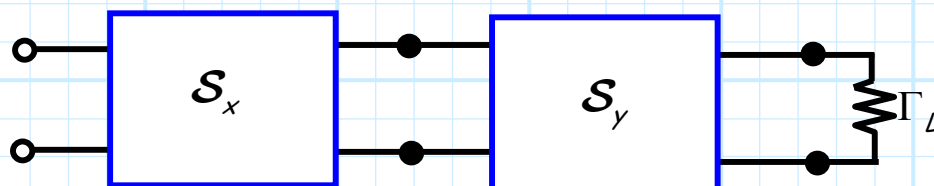
Now let's cascade **two different** two-port networks



Here, the output port of the first device is **directly** connected to the input port of the second device. We describe this mathematically as:

$$a_1^y = b_2^x \quad \text{and} \quad b_1^y = a_2^x$$

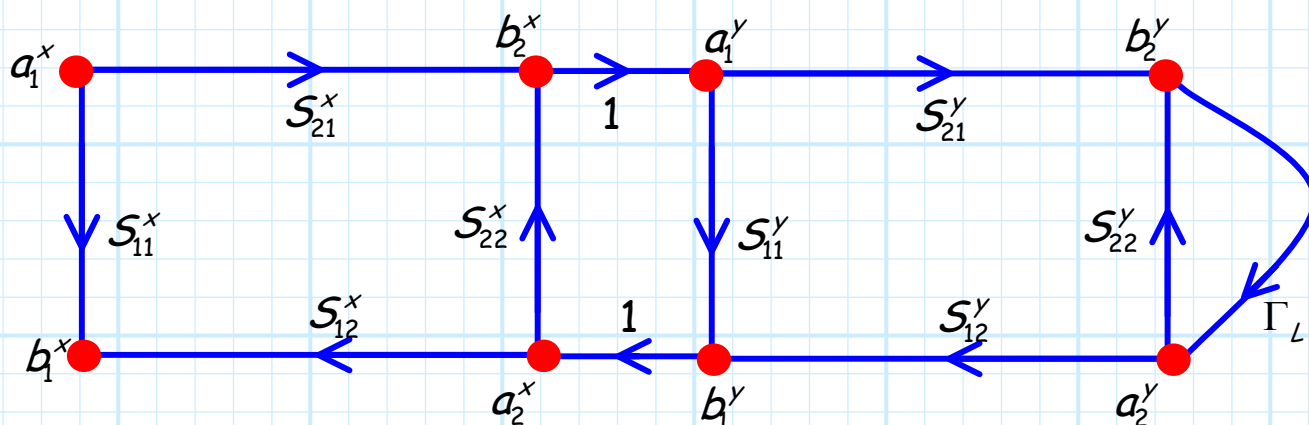Thus, the signal flow graph of this network is:




Q: But what happens if the networks are connected with *transmission lines*?

A: Recall that a length ℓ of transmission line with characteristic impedance Z_0 is likewise a **two-port** device. Its scattering matrix is:

$$\mathcal{S} = \begin{bmatrix} 0 & e^{-j\beta\ell} \\ e^{-j\beta\ell} & 0 \end{bmatrix}$$

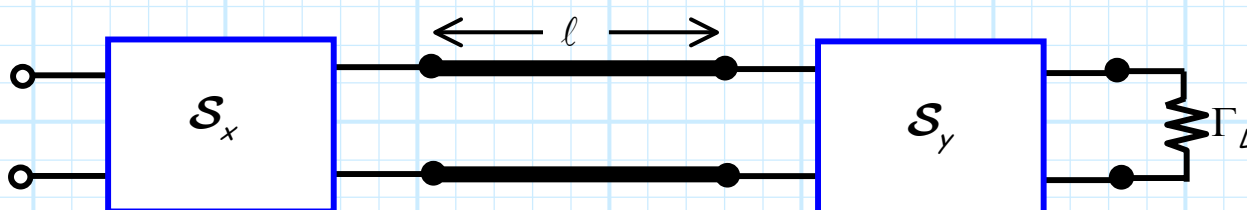Thus, if the two devices are connected by a length of **transmission line**:



the signal flow graph is:

