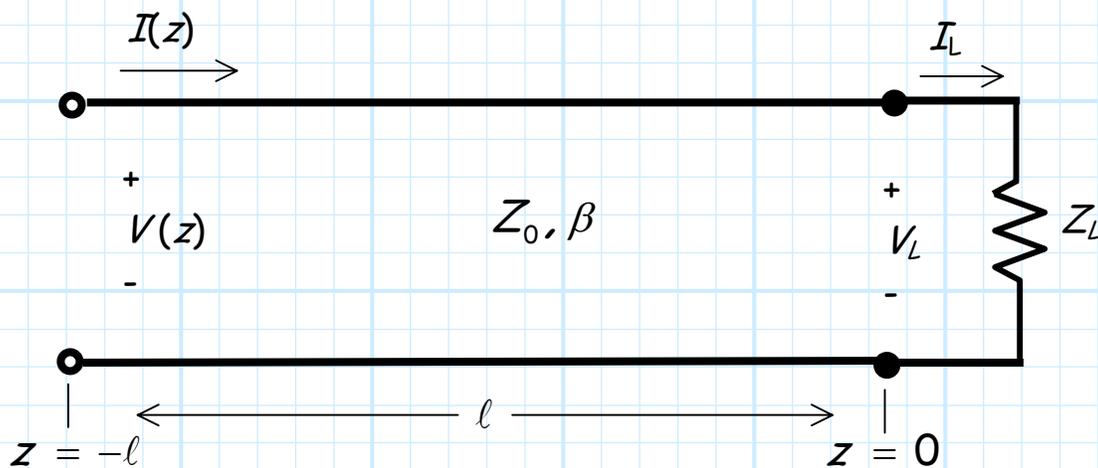


# Transmission Line Input Impedance

Consider a lossless line, length  $\ell$ , terminated with a load  $Z_L$ .



Let's determine the **input impedance** of this line!

**Q:** *Just what do you mean by **input impedance**?*

**A:** The input impedance is simply the line impedance seen at the **beginning** ( $z = -\ell$ ) of the transmission line, i.e.:

$$Z_{in} = Z(z = -\ell) = \frac{V(z = -\ell)}{I(z = -\ell)}$$

Note  $Z_{in}$  equal to **neither** the load impedance  $Z_L$  nor the characteristic impedance  $Z_0$ !

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$

To determine exactly what  $Z_{in}$  is, we first must determine the voltage and current at the **beginning** of the transmission line ( $z = -\ell$ ).

$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Therefore:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left( \frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right)$$

We can explicitly write  $Z_{in}$  in terms of load  $Z_L$  using the previously determined relationship:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Combining these two expressions, we get:

$$\begin{aligned} Z_{in} &= Z_0 \frac{(Z_L + Z_0)e^{+j\beta\ell} + (Z_L - Z_0)e^{-j\beta\ell}}{(Z_L + Z_0)e^{+j\beta\ell} - (Z_L - Z_0)e^{-j\beta\ell}} \\ &= Z_0 \left( \frac{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) + Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})}{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) - Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})} \right) \end{aligned}$$

Now, recall **Euler's equations**:

$$e^{+j\beta\ell} = \cos \beta\ell + j \sin \beta\ell$$

$$e^{-j\beta\ell} = \cos \beta\ell - j \sin \beta\ell$$

Using Euler's relationships, we can likewise write the input impedance without the **complex** exponentials:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right) \end{aligned}$$

Note that depending on the values of  $\beta$ ,  $Z_0$  and  $l$ , the input impedance can be **radically** different from the load impedance  $Z_L$ !

### Special Cases

Now let's look at the  $Z_{in}$  for some important **load** impedances and **line lengths**.

→ You should commit these results to **memory**!

1.  $l = \lambda/2$

If the length of the transmission line is exactly **one-half** wavelength ( $l = \lambda/2$ ), we find that:

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{2} = \pi$$


meaning that:

$$\cos \beta l = \cos \pi = -1 \quad \text{and} \quad \sin \beta l = \sin \pi = 0$$

and therefore:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_L (-1) + j Z_L (0)}{Z_0 (-1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

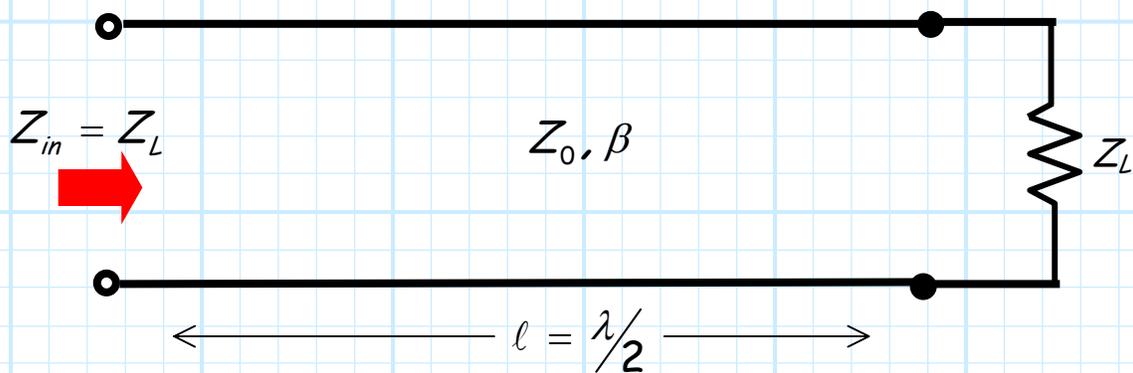In other words, if the transmission line is precisely **one-half wavelength** long, the **input impedance** is equal to the **load impedance**, regardless of  $Z_0$  or  $\beta$ .



2.  $l = \lambda/4$

If the length of the transmission line is exactly **one-quarter wavelength** ( $l = \lambda/4$ ), we find that:

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

meaning that:

$$\cos \beta l = \cos \pi/2 = 0 \quad \text{and} \quad \sin \beta l = \sin \pi/2 = 1$$

and therefore:


$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_L (0) + j Z_0 (1)}{Z_0 (0) + j Z_L (1)} \right) \\ &= \frac{(Z_0)^2}{Z_L} \end{aligned}$$

In other words, if the transmission line is precisely **one-quarter wavelength** long, the **input impedance** is **inversely** proportional to the **load impedance**.

Think about what this means! Say the load impedance is a **short circuit**, such that  $Z_L = 0$ . The **input impedance** at beginning of the  $\lambda/4$  transmission line is therefore:

$$Z_{in} = \frac{(Z_0)^2}{Z_L} = \frac{(Z_0)^2}{0} = \infty$$

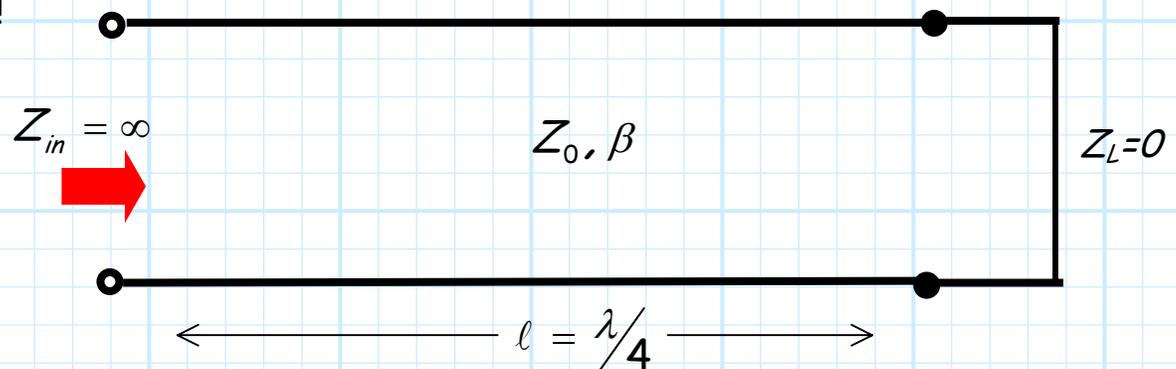$Z_{in} = \infty$  ! This is an **open circuit**! The quarter-wave transmission line **transforms** a short-circuit into an open-circuit—and vice versa!




$$3. \quad Z_L = Z_0$$

If the load is **numerically equal** to the characteristic impedance of the transmission line (a real value), we find that the input impedance becomes:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_0 \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_0 \sin \beta l} \right) \\ &= Z_0 \end{aligned}$$

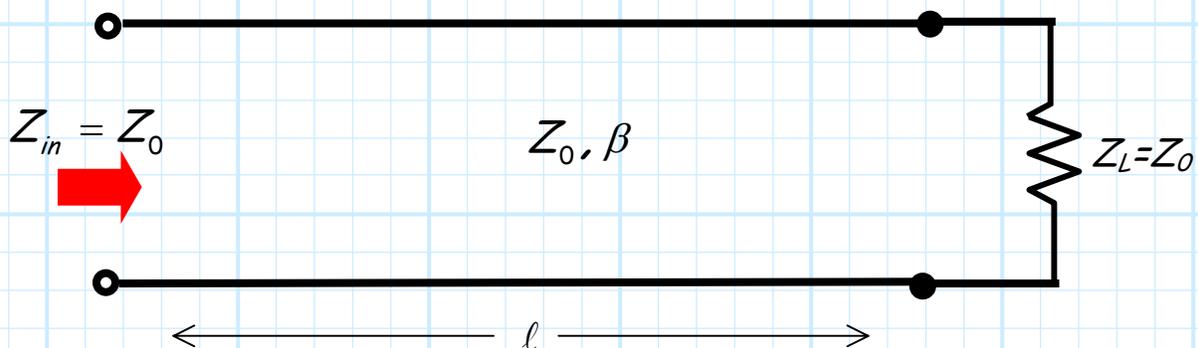In other words, if the **load** impedance is equal to the transmission line **characteristic** impedance, the **input** impedance will be likewise be equal to  $Z_0$  regardless of the transmission line length  $l$ .




$$4. \quad Z_L = j X_L$$

If the load is **purely reactive** (i.e., the resistive component is zero), the input impedance is:

$$\begin{aligned}
 Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\
 &= Z_0 \left( \frac{j X_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j^2 X_L \sin \beta l} \right) \\
 &= j Z_0 \left( \frac{X_L \cos \beta l + Z_0 \sin \beta l}{Z_0 \cos \beta l - X_L \sin \beta l} \right)
 \end{aligned}$$

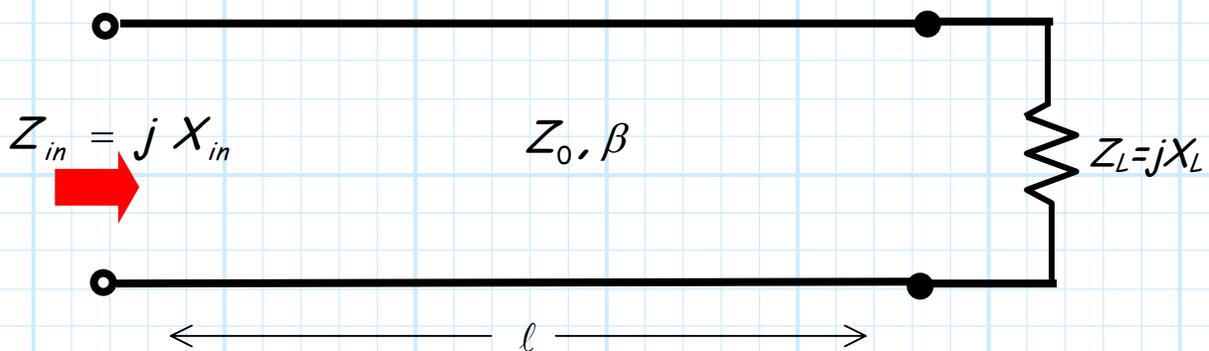In other words, if the load is purely reactive, then the input impedance will **likewise** be purely reactive, **regardless** of the line length  $l$ .



Note that the **opposite** is **not** true: even if the load is **purely resistive** ( $Z_L = R$ ), the input impedance will be **complex** (both resistive and reactive components).

**Q:** *Why is this?*

**A:**

## 5. $l \ll \lambda$

If the transmission line is **electrically small**—its length  $l$  is small with respect to signal wavelength  $\lambda$ --we find that:

$$\beta l = \frac{2\pi}{\lambda} l = 2\pi \frac{l}{\lambda} \approx 0$$

and thus:

$$\cos \beta l = \cos 0 = 1 \quad \text{and} \quad \sin \beta l = \sin 0 = 0$$

so that the input impedance is:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left( \frac{Z_L (1) + j Z_L (0)}{Z_0 (1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

In other words, if the transmission line length is much smaller than a wavelength, the **input** impedance  $Z_{in}$  will **always** be equal to the **load** impedance  $Z_L$ .

**This** is the assumption we used in all previous circuits courses (e.g., EECS 211, 212, 312, 412)! In those courses, we assumed that the signal frequency  $\omega$  is relatively **low**, such that the signal wavelength  $\lambda$  is **very large** ( $\lambda \gg l$ ).

Note also for this case ( the electrically short transmission line), the voltage and current at each end of the transmission line are approximately the **same!**

$$V(z = -l) \approx V(z = 0) \quad \text{and} \quad I(z = -l) \approx I(z = 0) \quad \text{if} \quad l \ll \lambda$$

If  $l \ll \lambda$ , our "wire" behaves **exactly** as it did in EECS 211 !