

II Transmitter and Receiver Design

We design radio systems using **RF/microwave** components.

Q: Why don't we use the "usual" circuit components (e.g., resistors, capacitors, op-amps, transistors) ??

A: We **do** use these! But we require new devices because:

1. _____
2. _____

A. Microwave Components

Let's carefully examine each of the microwave devices that are useful for radio design:

- 1)
- 2)
- 3)
- 4)
- 5)
- 6)
- 7)
- 8)

1. Transmission Lines

Q: *So just what is a transmission line?*

A:

→

Q: *Oh, so it's simply a conducting wire, right?*

A:

HO: The Telegraphers Equations

HO: Time-Harmonic Solutions for Linear Circuits

a) Basic Transmission Line Theory

Q: *So, what complex functions $I(z)$ and $V(z)$ do satisfy both telegrapher equations?*

A:

HO: The Transmission Line Wave Equations

Q: *Are the solutions for $I(z)$ and $V(z)$ completely independent, or are they related in any way?*

A:

HO: The Transmission Line Characteristic Impedance

Q: *So what is the significance of the constant β ? What does it tell us?*

A:

HO: The Propagation Constant

Q: *Is characteristic impedance Z_0 the same as the concept of impedance I learned about in **circuits** class?*

A:

HO: Line Impedance

Q: *These **wave** functions $V^+(z)$ and $V^-(z)$ seem to be important. How are **they** related?*

A:

HO: The Reflection Coefficient

HO: V, I, Z or V^+, V^-, Γ ??

b) The Terminated, Lossless Transmission Line

We now know that a **lossless** transmission line is **completely** characterized by **real** constants Z_0 and β .

Likewise, the **2 waves** propagating on a transmission line are **completely** characterized by **complex** constants V_0^+ and V_0^- .

Q: Z_0 and β are determined from L, C , and ω . How do we find V_0^+ and V_0^- ?

A: _____

Every transmission line has 2 "boundaries"

1)

2) _____

Typically, there is a **source** at one end of the line, and a **load** at the other.

→ _____

Let's apply the **load** boundary condition!

HO: The Terminated, Lossless Transmission Line

HO: Special Values of Load Impedance

Q: So what is the significance of the constant β ? What does it tell us?

A: _____

HO: The Propagation Constant

Q: So the line impedance at the **end** of a line must be load impedance Z_L (i.e., $Z(z = z_L) = Z_L$); what is the line impedance at the **beginning** of the line (i.e., $Z(z = z_L - \ell) = ?$)?

A: _____

HO: Transmission Line Input Impedance

Q: You said the purpose of the transmission line is to transfer **E.M. energy** from the source to the load. Exactly how much **power** is flowing in the transmission line, and how much is **delivered** to the load?

A: HO: Power Flow and Return Loss

Note that we can **specify** a load with:

- 1)
- 2)
- 3)


A fourth alternative is VSWR.

HO: VSWR

c) A second boundary condition: Applying a generator to the transmission line

Q: A passive load Z_L specifies $Z(z)$ and $\Gamma(z)$, but we still don't explicitly know $V(z)$, $I(z)$, $V'(z)$, or $V''(z)$. How are these functions determined?

A:

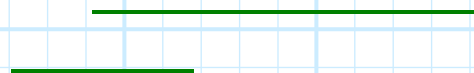

HO: A Transmission Line Connecting Source and Load

Q: OK, we can *finally* ask the question that we have been concerned with since the very beginning: How much **power** is delivered to the load by the source?

A: HO: Delivered Power

Q: *So the power transferred depends on the **source**, the **transmission line**, and the **load**. What combination of these devices will result in **maximum** power transfer?*

A: *HO: Special Cases of Source and Input Impedances*

Q: *Yikes! The signal source is generally a Thevenin's equivalent of the **output** of some **useful device**, while the load impedance is generally the **input** impedance of some other **useful device**. I do **not** want to—nor typically can I—**change** these devices or **alter** their characteristics.*

*Must I then just **accept** the fact that I will achieve **suboptimum** power transfer?*

A:

HO: Matching Networks

Q: But in microwave circuits, a source and load are connected by a transmission line. Can we implement matching networks in transmission line circuits?

A: *HO: Matching Networks and Transmission Lines*

Q: *Matching networks seem almost too good to be true; can we really design and construct them to provide a perfect match?*

A: It is relatively easy to provide a near perfect match at precisely **one frequency!**

But, since lossless matching networks are made entirely of **reactive** elements (not to mention the reactive components of the source and load impedance), we find that changing the signal frequency will typically "**mismatch**" our circuit!

Thus a difficult challenge for any microwave component designer is to provide a **wideband** match to a transmission line with characteristic impedance Z_0 .




d) Scattering Parameters

Note that a passive load is a one-port device—a device that can be characterized (at one frequency) by impedance Z_L or load reflection coefficient Γ_L .

However, many microwave devices have **multiple** ports!

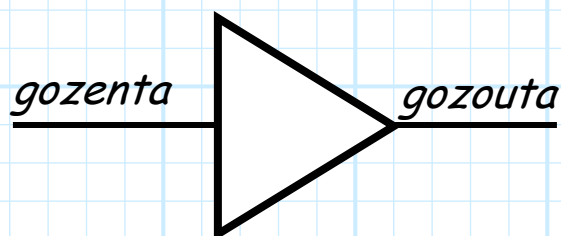Most common are **two-port devices** (e.g., amplifiers and filters), devices with both a gozenta and a gozouta.



Note that a transmission line is also two-port device!

Q: *Are there any known ways to characterize a **multi-port** device?*

A: Yes! **Two** methods are:

1.

2.

HO: The Impedance Matrix

Q: *You say that the impedance matrix characterizes a multi-port device. But is this characterization helpful? Can we actually use it to solve real problems?*

A: Example: Using the Impedance Matrix

Q: The impedance matrix relates the quantities $V(z)$ and $I(z)$, is there an equivalent matrix that relates $V(z)$ and $V(z)$?

A: _____

HO: The Scattering Matrix

Q: Can the scattering matrix likewise be used to solve real problems?

A: Of course!

Example: The Scattering Matrix

Example: Scattering Parameters

Q: *But, can the scattering matrix by itself tell us anything about the device it characterizes?*

A: Yes! It can tell us if the device is matched, or lossless, or reciprocal.

HO: Matched, Lossless, Reciprocal

e) *Types of Transmission Lines*

Perhaps the most common transmission line structure is coaxial transmission line.

HO: Coaxial Transmission Lines

Coaxial transmission lines are used with connectorized devices.


HO: Coax Connectors

We can also construct transmission lines on printed circuit boards.

HO: Printed Circuit Board Transmission Lines

The Telegrapher Equations

Consider a section of "wire":

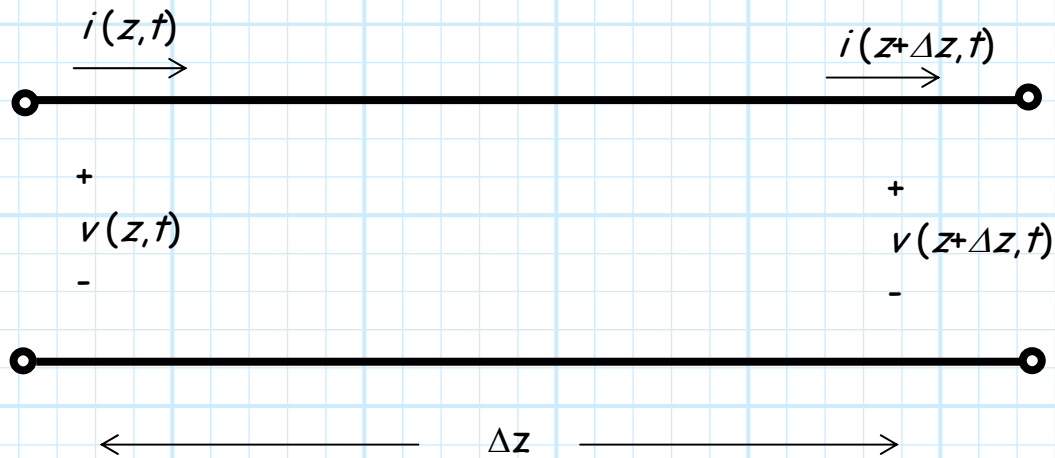


Q: Huh?! Current i and voltage v are a function of position z ??
Shouldn't $i(z,t) = i(z + \Delta z, t)$ and $v(z,t) = v(z + \Delta z, t)$?

A: NO! Because a wire is never a **perfect** conductor.

A "wire" will have:

- 1) Inductance
- 2) Resistance
- 3) Capacitance
- 4) Conductance

i.e.,

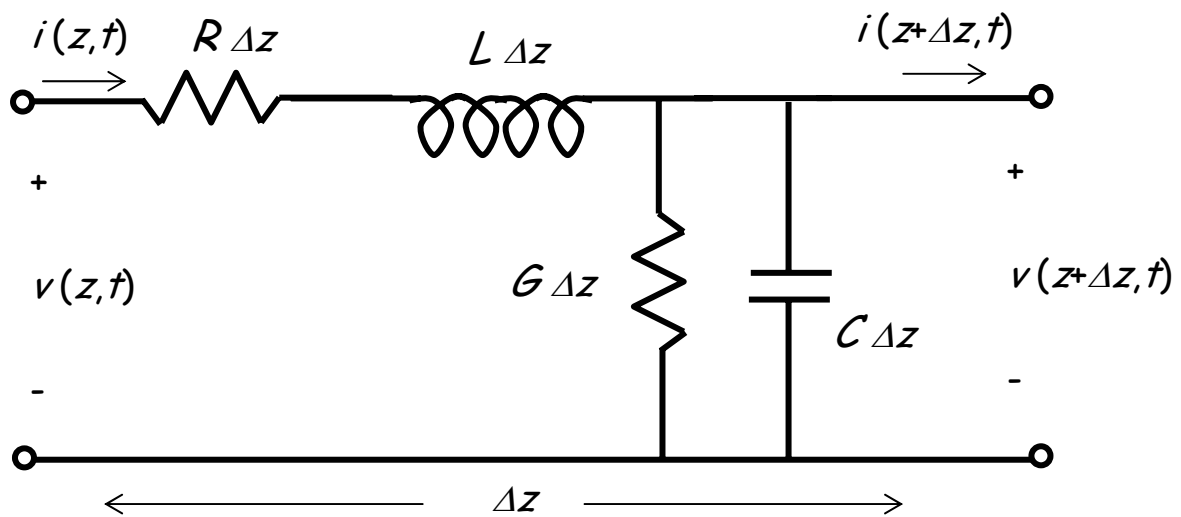

Where:

R = resistance/unit length

L = inductance/unit length

C = capacitance/unit length

G = conductance/unit length

\therefore resistance of wire length Δz is $R\Delta z$.

Using KVL, we find:

$$v(z + \Delta z, t) - v(z, t) = -R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t}$$

and from KCL:

$$i(z + \Delta z, t) - i(z, t) = -G\Delta z v(z, t) - C\Delta z \frac{\partial v(z, t)}{\partial t}$$

Dividing the first equation by Δz , and then taking the limit as $\Delta z \rightarrow 0$:

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

These equations are known as the **telegrapher's equations** !

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

Time-Harmonic Solutions for Linear Circuits

There are an unaccountably **infinite** number of solutions $v(z,t)$ and $i(z,t)$ for the telegrapher's equations! However, we can simplify the problem by assuming that the function of time is **time harmonic** (i.e., sinusoidal), oscillating at some **radial frequency** ω (e.g., $\cos \omega t$).

Q: *Why on earth would we assume a **sinusoidal** function of time? Why not a **square wave**, or **triangle wave**, or a "sawtooth" function?*

A: We assume **sinusoids** because they have a **very** special property!

Sinusoidal time functions—and **only** a sinusoidal time functions—are the **eigen functions** of **linear, time-invariant** systems.

Q: ???

A: If a sinusoidal voltage source with frequency ω is used to excite a linear, time-invariant circuit (and a transmission line is **both** linear **and** time invariant!), then the voltage at each and **every** point with the circuit will likewise vary sinusoidally—at the same frequency ω !

Q: *So what? Isn't that obvious?*

A: Not at all! If you were to excite a linear circuit with a **square wave**, or **triangle wave**, or **sawtooth**, you would find that—generally speaking—**nowhere** else in the circuit is the voltage a perfect square wave, triangle wave, or sawtooth. The linear circuit will effectively **distort** the input signal into something **else!**

Q: *Into what function will the input signal be distorted?*

A: It depends—both on the original form of the **input signal**, and the parameters of the **linear circuit**. At **different** points within the circuit we will discover **different** functions of time—**unless**, of course, we use a **sinusoidal** input. Again, for a sinusoidal excitation, we find at **every** point within circuit an **undistorted** sinusoidal function!

Q: *So, the sinusoidal function at every point in the circuit is exactly the same as the input sinusoid?*

A: Not quite **exactly** the same. Although at every point within the circuit the voltage will be precisely sinusoidal (with frequency ω), the **magnitude** and **relative phase** of the sinusoid will generally be different at each and every point within the circuit.

Thus, the voltage along a transmission line—when excited by a sinusoidal source—**must** have the form:

$$v(z, t) = v(z) \cos(\omega t + \varphi(z))$$

Thus, at some arbitrary location z along the transmission line, we **must** find a time-harmonic oscillation of **magnitude** $v(z)$ and **relative phase** $\varphi(z)$.

Now, consider Euler's equation, which states:

$$e^{j\psi} = \cos \psi + j \sin \psi$$

Thus, it is apparent that:

$$\operatorname{Re}\{e^{j\psi}\} = \cos \psi$$

and so we conclude that the voltage on a transmission line can be expressed as:

$$\begin{aligned} v(z, t) &= v(z) \cos(\omega t + \varphi(z)) \\ &= \operatorname{Re}\{v(z) e^{j(\omega t + \varphi(z))}\} \\ &= \operatorname{Re}\{v(z) e^{+j\varphi(z)} e^{j\omega t}\} \end{aligned}$$

Thus, we can specify the time-harmonic voltage at each and every location z along a transmission line with the **complex** function $V(z)$:

$$V(z) = v(z) e^{-j\varphi(z)}$$

where the **magnitude** of the complex function is the **magnitude** of the sinusoid:

$$v(z) = |V(z)|$$

and the phase of the complex function is the relative phase of the sinusoid :

$$\varphi(z) = \arg\{V(z)\}$$

Q: *Hey wait a minute! What happened to the time-harmonic function $e^{j\omega t}$??*

A: There really is no reason to **explicitly** write the complex function $e^{j\omega t}$, since we know in fact (being the eigen function of linear systems and all) that if this is the time function at any **one** location (such as at the excitation source) then this must be time function at **all** transmission line locations z !

The only **unknown** is the **complex** function $V(z)$. Once we determine $V(z)$, we can always (if we so desire) "recover" the **real** function $v(z, t)$ as:

$$v(z, t) = \operatorname{Re}\{V(z)e^{j\omega t}\}$$

Thus, if we assume a **time-harmonic source**, finding the transmission line solution $v(z, t)$ reduces to solving for the **complex function** $V(z)$.

The Transmission Line Wave Equation

Let's assume that $v(z,t)$ and $i(z,t)$ each have the time-harmonic form:

$$v(z,t) = \text{Re}\{V(z)e^{j\omega t}\} \quad \text{and} \quad i(z,t) = \text{Re}\{I(z)e^{j\omega t}\}$$

The time-derivative of these functions are:

$$\frac{\partial v(z,t)}{\partial t} = \text{Re}\left\{V(z)\frac{\partial e^{j\omega t}}{\partial t}\right\} = \text{Re}\{j\omega V(z)e^{j\omega t}\}$$

$$\frac{\partial i(z,t)}{\partial t} = \text{Re}\left\{I(z)\frac{\partial e^{j\omega t}}{\partial t}\right\} = \text{Re}\{j\omega I(z)e^{j\omega t}\}$$

The telegrapher's equations thus become:

$$\text{Re}\left\{\frac{\partial V(z)}{\partial z} e^{j\omega t}\right\} = \text{Re}\{-(R + j\omega L)I(z)e^{j\omega t}\}$$

$$\text{Re}\left\{\frac{\partial I(z)}{\partial z} e^{j\omega t}\right\} = \text{Re}\{-(G + j\omega C)V(z)e^{j\omega t}\}$$


And then simplifying, we have the **complex** form of **telegrapher's equations**:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(\mathcal{G} + j\omega \mathcal{C})V(z)$$

Note that these complex differential equations are **not** a function of time t !

- * The functions $I(z)$ and $V(z)$ are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function $e^{j\omega t}$.
- * Thus, $I(z)$ and $V(z)$ describe the current and voltage along the transmission line, as a function as position z .
- * **Remember**, not just **any** function $I(z)$ and $V(z)$ can exist on a transmission line, but rather **only** those functions that satisfy the **telegraphers equations**.

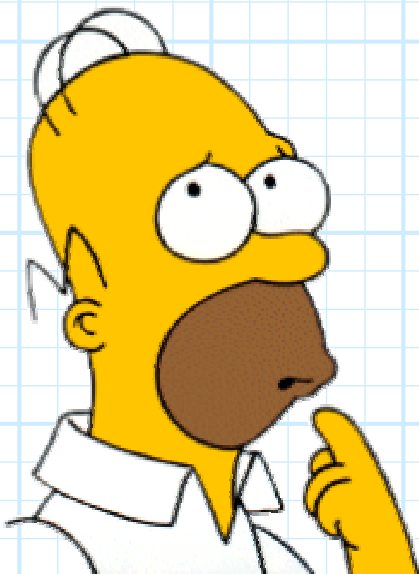

Our task, therefore, is to **solve** the telegrapher equations and find **all** solutions $I(z)$ and $V(z)$!

Q: So, what functions $I(z)$ and $V(z)$ do satisfy both telegrapher's equations??

A: To make this easier, we will combine the telegrapher equations to form **one** differential equation for $V(z)$ and **another** for $I(z)$.

First, take the **derivative** with respect to z of the **first** telegrapher equation:

$$\frac{\partial}{\partial z} \left\{ \frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z) \right\}$$

$$= \frac{\partial^2 V(z)}{\partial z^2} = -(R + j\omega L) \frac{\partial I(z)}{\partial z}$$

Note that the **second** telegrapher equation expresses the derivative of $I(z)$ in terms of $V(z)$:

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$

Combining these two equations, we get an equation involving $V(z)$ **only**:

$$\frac{\partial^2 V(z)}{\partial z^2} = (R + j\omega L)(G + j\omega C) V(z)$$

Now, we find at high frequencies that:

$$R \ll j\omega L \quad \text{and} \quad G \ll j\omega C$$

and so we can **approximate** the differential equation as:

$$\frac{\partial^2 V(z)}{\partial z^2} = (j\omega L)(j\omega C)V(z) = \omega^2 LC V(z) = \beta^2 V(z)$$

where it is apparent that:

$$\beta^2 \doteq \omega^2 LC$$

In a **similar** manner (i.e., begin by taking the derivative of the **second** telegrapher equation), we can derive the differential equation:

$$\frac{\partial^2 I(z)}{\partial z^2} = \beta^2 I(z)$$

We have **decoupled** the telegrapher's equations, such that we now have **two** equations involving **one** function only:

$$\frac{\partial^2 V(z)}{\partial z^2} = \beta^2 V(z)$$

$$\frac{\partial^2 I(z)}{\partial z^2} = \beta^2 I(z)$$

These are known as the **transmission line wave equations**.

Note only **special** functions satisfy these equations: if we take the double derivative of the function, the result is the **original function** (to within a constant)!



Q: *Yeah right! Every function that I know is **changed** after a double differentiation. What kind of "magical" function could possibly satisfy this differential equation?*

A: Such functions **do** exist !

For example, the functions $V(z) = e^{-j\beta z}$ and $V(z) = e^{+j\beta z}$ each satisfy this transmission line wave equation (**insert** these into the differential equation and see for **yourself!**).

Likewise, since the transmission line wave equation is a **linear** differential equation, a weighted **superposition** of the two solutions is **also a solution** (again, **insert** this solution to and see for **yourself!**):

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

In fact, it turns out that **any** and **all** possible solutions to the differential equations can be expressed in **this** simple form!

Therefore, the **general** solution to these wave equations (and thus the telegrapher equations) are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

where V_0^+ , V_0^- , I_0^+ , and I_0^- are **complex constants**.

→ It is **unfathomably** important that **you** understand what this result means!

It means that the functions $V(z)$ and $I(z)$, describing the current and voltage at **all** points z along a transmission line, can **always** be **completely** specified with just **four complex constants** (V_0^+ , V_0^- , I_0^+ , I_0^-)!!

We can **alternatively** write these solutions as:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = I^+(z) + I^-(z)$$

where:


$$V^+(z) \doteq V_0^+ e^{-j\beta z}$$

$$V^-(z) \doteq V_0^- e^{+j\beta z}$$

$$I^+(z) \doteq I_0^+ e^{-j\beta z}$$

$$I^-(z) \doteq I_0^- e^{+j\beta z}$$

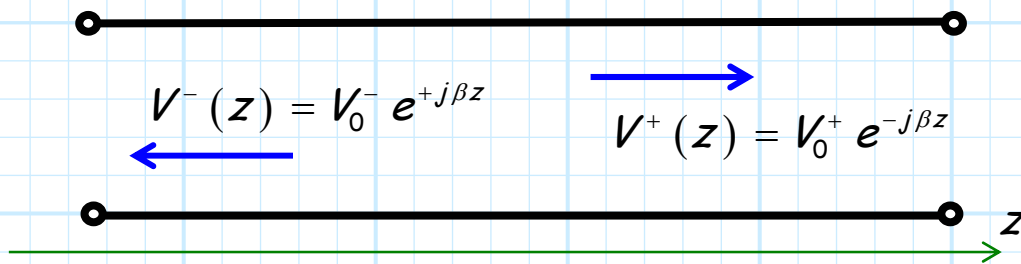The two terms in each solution describe **two waves** propagating in the transmission line, **one wave** ($V^+(z)$ or $I^+(z)$) propagating in one direction ($+z$) and the **other wave** ($V^-(z)$ or $I^-(z)$) propagating in the **opposite** direction ($-z$).



Q: So just what **are** the complex values V_0^+ , V_0^- , I_0^+ , I_0^- ?

A: Consider the wave solutions at **one** specific point on the transmission line—the point $z = 0$. For example, we find that:

$$\begin{aligned} V^+(z=0) &= V_0^+ e^{-j\beta(z=0)} \\ &= V_0^+ e^{-(0)} \\ &= V_0^+ (1) \\ &= V_0^+ \end{aligned}$$

In other words, V_0^+ is simply the **complex** value of the wave function $V^+(z)$ at the point $z=0$ on the transmission line!

Likewise, we find:

$$V_0^- = V^-(z = 0)$$


$$I_0^+ = I^+(z = 0)$$

$$I_0^- = I^-(z = 0)$$

Again, the four complex values V_0^+ , I_0^+ , V_0^- , I_0^- are **all** that is needed to determine the voltage and current at any and all points on the transmission line.

More specifically, **each** of these four complex constants completely specifies **one** of the four transmission line wave functions $V^+(z)$, $I^+(z)$, $V^-(z)$, $I^-(z)$.

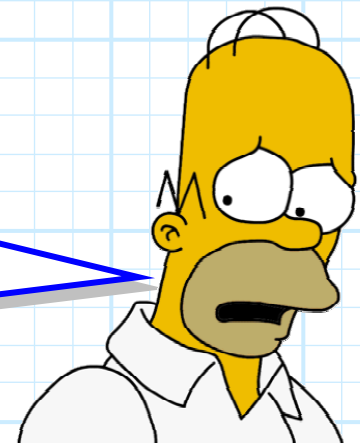Q: *But what **determines** these wave functions? How do we **find** the values of constants V_0^+ , I_0^+ , V_0^- , I_0^- ?*



A: As you might expect, the voltage and current on a transmission line is determined by the devices **attached** to it on either end (e.g., active sources and/or passive loads)!

The precise values of V_0^+ , I_0^+ , V_0^- , I_0^- are therefore determined by satisfying the **boundary conditions** applied at **each end** of the transmission line—much more on this **later!**

The Characteristic Impedance of a Transmission Line

So, from the telegrapher's differential equations, we know that the complex current $I(z)$ and voltage $V(z)$ must have the form:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

Let's insert the expression for $V(z)$ into the first telegrapher's equation, and **see what happens!**

$$\frac{dV(z)}{dz} = -j\beta V_0^+ e^{-j\beta z} + j\beta V_0^- e^{+j\beta z} = -j\omega L I(z)$$


Therefore, rearranging, $I(z)$ must be:

$$I(z) = \frac{\beta}{\omega L} (V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z})$$

Q: *But wait! I thought we already knew current $I(z)$. Isn't it:*

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} \quad ??$$

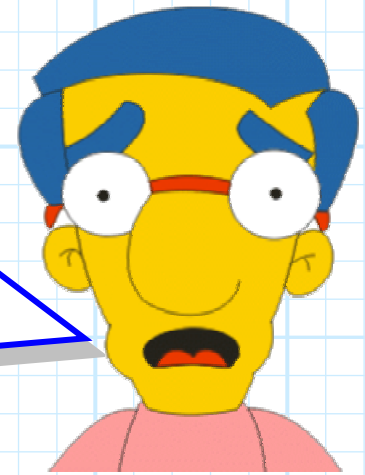How can both expressions for $I(z)$ be true??



A: Easy! Both expressions for current are **equal** to each other.

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} = \frac{\beta}{\omega L} (V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z})$$

For the above equation to be true for **all** z , I_0 and V_0 must be related as:

$$I_0^+ e^{-\gamma z} = \left(\frac{\beta}{\omega L} \right) V_0^+ e^{-\gamma z} \quad \text{and} \quad I_0^- e^{+\gamma z} = \left(\frac{-\beta}{\omega L} \right) V_0^- e^{+\gamma z}$$

Or—recalling that $V_0^+ e^{-j\beta z} = V^+(z)$ (etc.)—we can express this in terms of the **two propagating waves**:

$$I^+(z) = \left(\frac{\beta}{\omega L} \right) V^+(z) \quad \text{and} \quad I^-(z) = \left(\frac{-\beta}{\omega L} \right) V^-(z)$$

Now, we note that since:

$$\beta = \omega \sqrt{LC}$$

We find that:

$$\frac{\beta}{\omega L} = \frac{\omega \sqrt{LC}}{\omega L} = \sqrt{\frac{C}{L}}$$

Thus, we come to the **startling** conclusion that:

$$\frac{V^+(z)}{I^+(z)} = \sqrt{\frac{L}{C}} \quad \text{and} \quad \frac{-V^-(z)}{I^-(z)} = \sqrt{\frac{L}{C}}$$

Q: *What's so startling about **this** conclusion?*

A: Note that although the magnitude and phase of each propagating wave is a **function** of transmission line **position** z (e.g., $V^+(z)$ and $I^+(z)$), the **ratio** of the voltage and current of **each wave** is independent of position—a **constant** with respect to position z !

Although V_0^\pm and I_0^\pm are determined by **boundary conditions** (i.e., what's connected to either end of the transmission line), the **ratio** V_0^\pm/I_0^\pm is determined by the parameters of the transmission line **only** (R, L, G, C).

→ This ratio is an important **characteristic** of a transmission line, called its **Characteristic Impedance** Z_0 .

$$Z_0 \doteq \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} = \sqrt{\frac{L}{C}}$$

We can therefore describe the current and voltage along a transmission line as:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

or equivalently:

$$V(z) = Z_0 I_0^+ e^{-j\beta z} - Z_0 I_0^- e^{+j\beta z}$$


$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

Note that instead of characterizing a transmission line with **real** parameters L and C , we can (and typically do!) describe a lossless transmission line using real parameters Z_0 and β .

Line Impedance

Now let's define **line impedance** $Z(z)$, a **complex** function which is simply the ratio of the complex line **voltage** and complex line **current**:

$$Z(z) = \frac{V(z)}{I(z)}$$

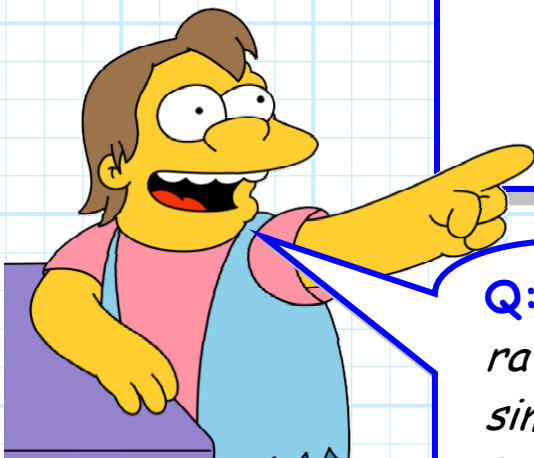

Q: *Hey! I know what this is! The ratio of the voltage to current is simply the **characteristic impedance** Z_0 , right ???*

A: **NO!** The line impedance $Z(z)$ is (generally speaking) **NOT** the transmission line **characteristic impedance** Z_0 !!!

→ It is **unfathomably important** that you understand this!!!!

To see why, recall that:

$$V(z) = V^+(z) + V^-(z)$$

And that:

$$I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

Therefore:


$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left(\frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right) \neq Z_0$$

Or, more specifically, we can write:

$$Z(z) = Z_0 \left(\frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}} \right)$$

Q: *I'm confused! Isn't:*

$$V^+(z)/I^+(z) = Z_0 ???$$

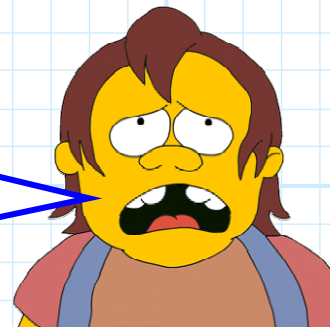

A: Yes! That **is** true! The ratio of the voltage to current for **each** of the two propagating waves is $\pm Z_0$. However, the ratio of the **sum** of the two voltages to the **sum** of the two currents is **not** equal to Z_0 (generally speaking)!

This is actually confirmed by the equation above. Say that $V^-(z) = 0$, so that only **one** wave ($V^+(z)$) is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance** Z_0 !

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left(\frac{V^+(z)}{I^+(z)} \right) = \frac{V^+(z)}{I^+(z)} = Z_0 \quad (\text{when } V^-(z) = 0)$$

Q: *So, it appears to me that characteristic impedance Z_0 is a **transmission line parameter**, depending **only** on the transmission line values L and C .*

*Whereas **line impedance** is $Z(z)$ depends the magnitude and phase of the two propagating waves $V^+(z)$ and $V^-(z)$ --values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!*

Right !?



A: **Exactly!** Moreover, note that characteristic impedance Z_0 is simply a **number**, whereas line impedance $Z(z)$ is a **function** of position (z) on the transmission line.

The Reflection Coefficient


So, we know that the transmission line **voltage** $V(z)$ and the transmission line **current** $I(z)$ can be related by the **line impedance** $Z(z)$:

$$V(z) = Z(z) I(z)$$

or equivalently:

$$I(z) = \frac{V(z)}{Z(z)}$$

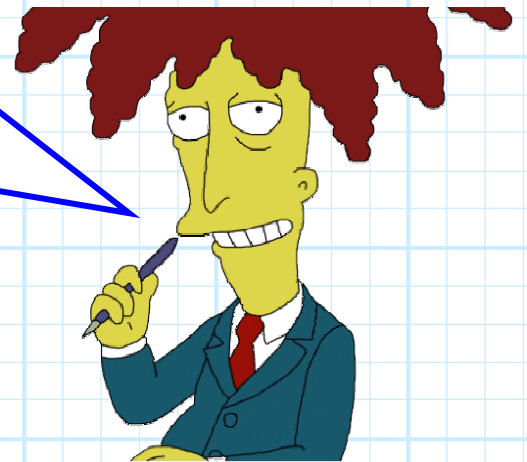Q: *Piece of cake! I fully understand the concepts of voltage, current and impedance from my circuits classes. Let's move on to something more important (or, at the very least, more interesting).*



Expressing the "activity" on a transmission line in terms of **voltage, current and impedance** is of course **perfectly valid**.


However, let us look **closer** at the expression for each of these quantities:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

$$Z(z) = Z_0 \left(\frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right)$$

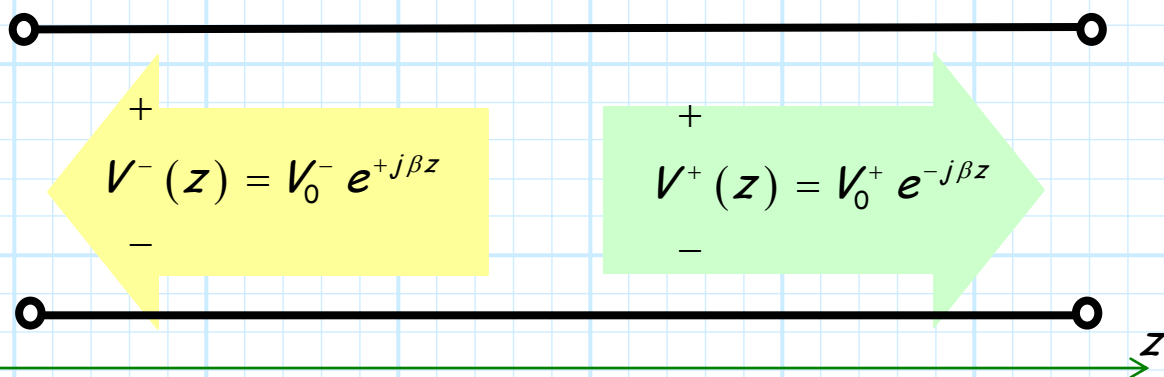It is evident that we can **alternatively** express all "activity" on the transmission line in terms of the two transmission line waves $V^+(z)$ and $V^-(z)$.



Q: I know $V(z)$ and $I(z)$ are related by line impedance $Z(z)$:

$$Z(z) = \frac{V(z)}{I(z)}$$

But how are $V^+(z)$ and $V^-(z)$ related?

A: Similar to line impedance, we can define a new parameter—the **reflection coefficient** $\Gamma(z)$ —as the **ratio** of the two quantities:

$$\Gamma(z) \doteq \frac{V^-(z)}{V^+(z)} \Rightarrow V^-(z) = \Gamma(z)V^+(z)$$

More specifically, we can express $\Gamma(z)$ as:

$$\Gamma(z) = \frac{V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Note then, the value of the reflection coefficient at $z=0$ is:

$$\Gamma(z=0) = \frac{V^-(z=0)}{V^+(z=0)} e^{+j2\beta(0)} = \frac{V_0^-}{V_0^+}$$

We define this value as Γ_0 , where:

$$\Gamma_0 \doteq \Gamma(z=0) = \frac{V_0^-}{V_0^+}$$

Note then that we can alternatively write $\Gamma(z)$ as:

$$\Gamma(z) = \Gamma_0 e^{+j2\beta z}$$

So now we have **two different** but equivalent ways to describe transmission line activity!

We can use (total) **voltage** and **current**, related by **line impedance**:

$$Z(z) = \frac{V(z)}{I(z)} \quad \therefore \quad V(z) = Z(z) I(z)$$

Or, we can use the two propagating **voltage waves**, related by the **reflection coefficient**:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} \quad \therefore \quad V^-(z) = \Gamma(z) V^+(z)$$

These are **equivalent** relationships—we can use **either** when describing a transmission line.



*Based on your **circuits** experience, you might well be **tempted** to always use the **first** relationship. However, we will find it useful (as well as simple) indeed to describe activity on a transmission line in terms of the **second** relationship—in terms of the **two** propagating transmission line **waves**!*

V, I, Z or V^+ , V^- , Γ ?

Q: How do I choose *which* relationship to use when describing/analyzing transmission line activity? What if I make the *wrong* choice? How will I know if my analysis is correct?

A: Remember, the two relationships are **equivalent**. There is **no** explicitly wrong or right choice—**both** will provide you with precisely the **same** correct answer!



For example, we know that the total voltage and current can be determined from knowledge wave representation:

$$\begin{aligned} V(z) &= V^+(z) + V^-(z) \\ &= V^+(z)(1 + \Gamma(z)) \end{aligned}$$

$$\begin{aligned} I(z) &= \frac{V^+(z) - V^-(z)}{Z_0} \\ &= \frac{V^+(z)(1 - \Gamma(z))}{Z_0} \end{aligned}$$

Or explicitly using the wave solutions $V^+(z) = V_0^+ e^{-j\beta z}$ and $V^-(z) = V_0^- e^{+j\beta z}$:

$$\begin{aligned} V(z) &= V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \\ &= V_0^+ (e^{-j\beta z} + \Gamma_0 e^{+j\beta z}) \end{aligned}$$

$$\begin{aligned} I(z) &= \frac{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}{Z_0} \\ &= \frac{V_0^+ (e^{-j\beta z} - \Gamma_0 e^{+j\beta z})}{Z_0} \end{aligned}$$

More importantly, we find that **line impedance** $Z(z) = V(z)/I(z)$ can be expressed as:

$$\begin{aligned} Z(z) &= Z_0 \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \\ &= Z_0 \left(\frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right) \end{aligned}$$

Look what happened—the line impedance can be **completely** and unambiguously expressed in terms of **reflection coefficient** $\Gamma(z)$!

More explicitly:

$$Z(z) = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

$$= Z_0 \frac{1 + \Gamma_0 e^{+j2\beta z}}{1 - \Gamma_0 e^{+j2\beta z}}$$

With a little algebra, we find likewise that the wave functions can be determined from $V(z)$, $I(z)$ and $Z(z)$:

$$V^+(z) = \frac{V(z) + I(z)Z_0}{2}$$

$$= \frac{V(z)}{Z(z)} \left(\frac{Z(z) + Z_0}{2} \right)$$

$$V^-(z) = \frac{V(z) - I(z)Z_0}{2}$$

$$= \frac{V(z)}{Z(z)} \left(\frac{Z(z) - Z_0}{2} \right)$$

From this result we easily find that the reflection coefficient $\Gamma(z)$ can **likewise** be written directly in terms of **line impedance**:

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

Thus, the values $\Gamma(z)$ and $Z(z)$ are **equivalent** parameters—if we know **one**, then we can directly determine the **other**!



Q: *So, if they are equivalent, why wouldn't I **always** use the current, voltage, line impedance representation? After all, I am more **familiar** and more confident those quantities. The **wave** representation sort of **scares** me!*

A: Perhaps I can **convince** you of the value of the **wave** representation.

Remember, the time-harmonic solution to the telegraphers equation simply boils down to **two complex constants**— V_0^+ and V_0^- . Once these complex values have been determined, we can describe **completely** the activity **all** points along our transmission line.

For the **wave** representation we find:

$$V^+(z) = V_0^+ e^{-j\beta z}$$

$$V^-(z) = V_0^- e^{+j\beta z}$$

$$\Gamma(z) = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Note that the **magnitudes** of the complex functions are in fact **constants** (with respect to position z):

$$|V^+(z)| = |V_0^+|$$

$$|V^-(z)| = |V_0^-|$$

$$|\Gamma(z)| = \left| \frac{V_0^-}{V_0^+} \right|$$

While the **relative phase** of these complex functions are expressed as a **simple** linear relationship with respect to z :

$$\mathit{arg} \{V^+(z)\} = -\beta z$$

$$\mathit{arg} \{V^-(z)\} = +\beta z$$

$$\mathit{arg} \{\Gamma(z)\} = +2\beta z$$

Now, **contrast** this with the complex current, voltage, impedance functions:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}{Z_0}$$

$$Z(z) = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

With magnitude:

$$|V(z)| = |V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}| = ??$$

$$|I(z)| = \frac{|V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}|}{Z_0} = ??$$

$$|Z(z)| = Z_0 \frac{|V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}|}{|V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}|} = ??$$

and phase:

$$\arg\{V(z)\} = \arg\{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}\} = ??$$

$$\arg\{I(z)\} = \arg\{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}\} = ??$$

$$\begin{aligned} \arg\{Z(z)\} &= \arg\{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}\} \\ &\quad - \arg\{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}\} \\ &= ?? \end{aligned}$$




Q: *It appears to me that when attempting to describe the activity along a transmission line—as a function of **position** z —it is much **easier** and more **straightforward** to use the **wave** representation. Is my insightful conclusion **correct** (nyuck, nyuck, nyuck)?*

A: Yes it is! However, this does **not** mean that we **never** determine $V(z)$, $I(z)$, or $Z(z)$; these quantities are still **fundamental** and very important—particularly at each **end** of the transmission line!

The Terminated, Lossless Transmission Line

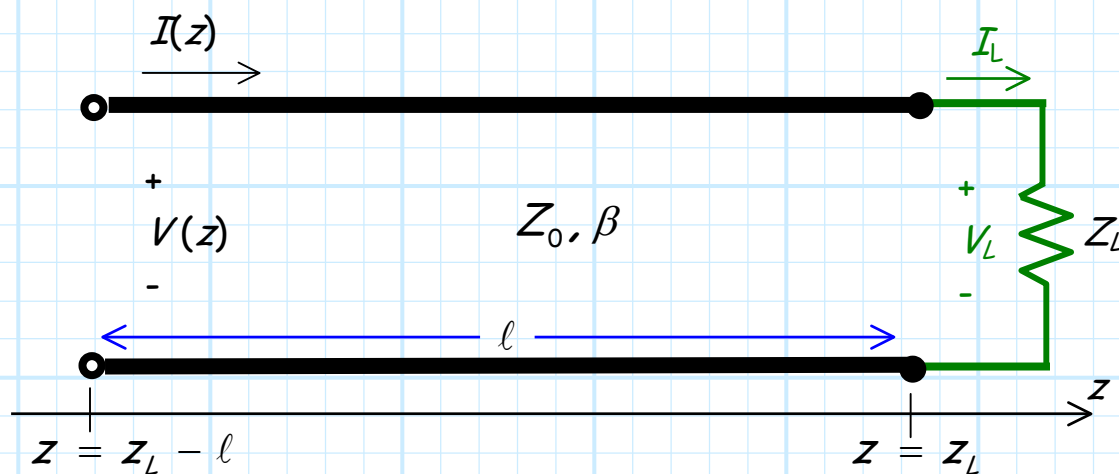Now let's **attach** something to our transmission line. Consider a lossless line, length ℓ , terminated with a load Z_L .



Q: What is the **current and voltage** at each and **every** point on the transmission line (i.e., what is $I(z)$ and $V(z)$ for **all** points z where $z_L - \ell \leq z \leq z_L$?)?

A: To find out, we must apply **boundary conditions!**

In other words, at the **end** of the transmission line ($z = z_L$)—where the load is **attached**—we have **many** requirements that **all** must be satisfied!

1. To begin with, the voltage and current ($I(z = z_L)$ and $V(z = z_L)$) must be consistent with a valid **transmission line solution**:


$$\begin{aligned} V(z = z_L) &= V^+(z = z_L) + V^-(z = z_L) \\ &= V_0^+ e^{-j\beta z_L} + V_0^- e^{+j\beta z_L} \end{aligned}$$

$$\begin{aligned} I(z = z_L) &= \frac{V_0^+(z = z_L)}{Z_0} - \frac{V_0^-(z = z_L)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta z_L} - \frac{V_0^-}{Z_0} e^{+j\beta z_L} \end{aligned}$$

2. Likewise, the load voltage and current must be related by **Ohm's law**:

$$V_L = Z_L I_L$$

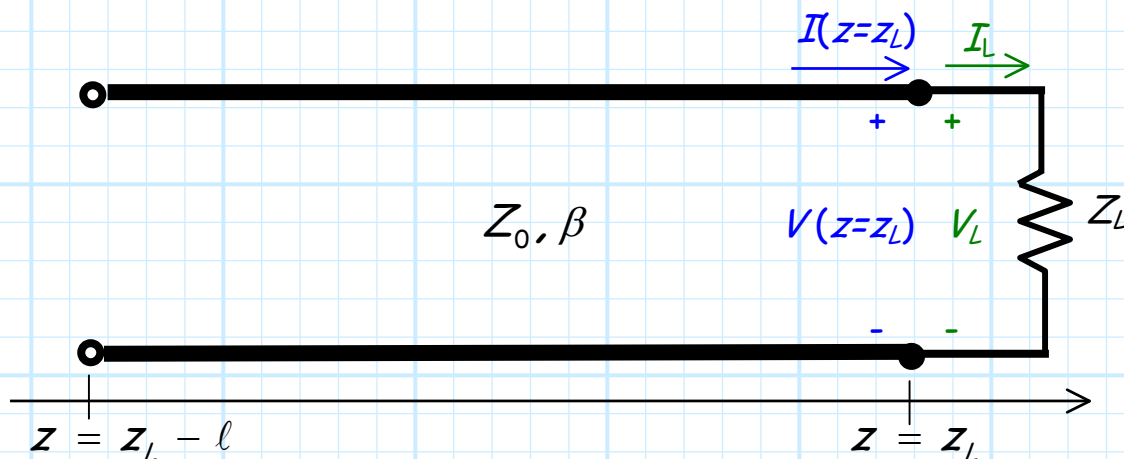3. Most importantly, we recognize that the values $I(z = z_L)$, $V(z = z_L)$ and I_L , V_L are **not** independent, but in fact are strictly related by **Kirchoff's Laws**!




From KVL and KCL we find these requirements:

$$V(z = z_L) = V_L$$

$$I(z = z_L) = I_L$$

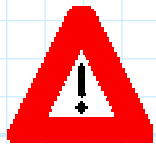These are the **boundary conditions** for **this** particular problem.



→ **Careful!** Different transmission line problems lead to **different** boundary conditions—you must access each problem **individually** and **independently!**

Combining these equations and boundary conditions, we find that:

$$V_L = Z_L I_L$$

$$V(z = z_L) = Z_L I(z = z_L)$$

$$V^+(z = z_L) + V^-(z = z_L) = \frac{Z_L}{Z_0} (V^+(z = z_L) - V^-(z = z_L))$$

Rearranging, we can conclude:

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Q: *Hey wait as second! We earlier defined $V^-(z)/V^+(z)$ as reflection coefficient $\Gamma(z)$. How does this relate to the expression above?*

A: Recall that $\Gamma(z)$ is a **function** of transmission line position z . The value $V^-(z = z_L)/V^+(z = z_L)$ is simply the value of function $\Gamma(z)$ **evaluated** at $z = z_L$ (i.e., evaluated at the **end** of the line):

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

This value is of **fundamental** importance for the terminated transmission line problem, so we provide it with its **own** special symbol (Γ_L)!

$$\Gamma_L \doteq \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Q: *Wait! We earlier determined that:*

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

so it would seem that:

$$\Gamma_L = \Gamma(z = z_L) = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

Which expression is correct??

A: They **both** are! It is evident that the two expressions:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and} \quad \Gamma_L = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

are **equal** if:

$$Z(z = z_L) = Z_L$$

And since we know that from **Ohm's Law**:

$$Z_L = \frac{V_L}{I_L}$$

and from **Kirchoff's Laws**:

$$\frac{V_L}{I_L} = \frac{V(z = z_L)}{I(z = z_L)}$$

and that **line impedance** is:


$$\frac{V(z = z_L)}{I(z = z_L)} = Z(z = z_L)$$

we find it apparent that the **line impedance** at the **end** of the transmission line is **equal** to the **load impedance**:

$$Z(z = z_L) = Z_L$$

The above expression is essentially **another** expression of the **boundary condition** applied at the **end** of the transmission line.

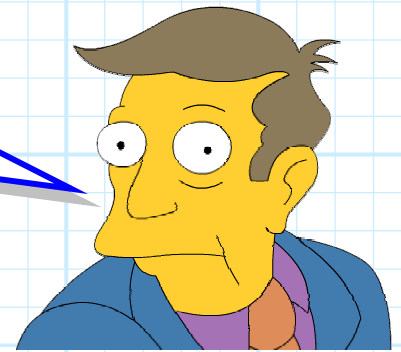Q: *I'm confused! Just what are we trying to accomplish in this handout?*



A: We are trying to find $V(z)$ and $I(z)$ when a lossless transmission line is terminated by a load Z_L !

We can now determine the value of V_0^- in terms of V_0^+ . Since:

$$\Gamma_L = \frac{V^-(z=z_L)}{V^+(z=z_L)} = \frac{V_0^- e^{+j\beta z_L}}{V_0^+ e^{-j\beta z_L}}$$

We find:

$$V_0^- = e^{-2j\beta z_L} \Gamma_L V_0^+$$

And therefore we find:

$$V^-(z) = (e^{-2j\beta z_L} \Gamma_L V_0^+) e^{+j\beta z}$$

$$V(z) = V_0^+ \left[e^{-j\beta z} + (e^{-2j\beta z_L} \Gamma_L) e^{+j\beta z} \right]$$


$$I(z) = \frac{V_0^+}{Z_0} \left[e^{-j\beta z} - (e^{-2j\beta z_L} \Gamma_L) e^{+j\beta z} \right]$$

where:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\underline{z_L = 0}$$

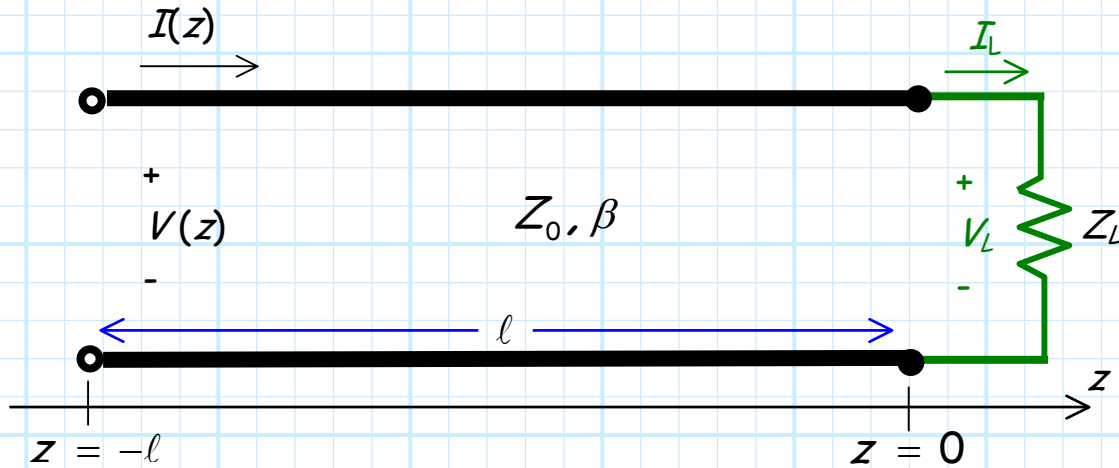Now, we can further **simplify** our analysis by **arbitrarily** assigning the end point z_L a **zero** value (i.e., $z_L = 0$):



If the load is located at $z=0$ (i.e., if $z_L = 0$), we find that:

$$\begin{aligned} V(z=0) &= V^+(z=0) + V^-(z=0) \\ &= V_0^+ e^{-j\beta(0)} + V_0^- e^{+j\beta(0)} \\ &= V_0^+ + V_0^- \end{aligned}$$

$$\begin{aligned} I(z=0) &= \frac{V_0^+(z=0)}{Z_0} - \frac{V_0^-(z=0)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta(0)} - \frac{V_0^-}{Z_0} e^{+j\beta(0)} \\ &= \frac{V_0^+ - V_0^-}{Z_0} \end{aligned}$$

$$Z(z=0) = Z_0 \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right)$$

Likewise, it is apparent that if $z_L = 0$, Γ_L and Γ_0 are the same:

$$\Gamma_L = \Gamma(z = z_L) = \frac{V^-(z = 0)}{V^+(z = 0)} = \frac{V_0^-}{V_0^+} = \Gamma_0$$

Therefore:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_0$$

Thus, we can write the line current and voltage simply as:

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_L e^{+j\beta z}]$$

[for $z_L = 0$]

Q: *But, how do we determine V_0^+ ??*

A: We require a **second** boundary condition to determine V_0^+ . The only boundary left is at the **other end** of the transmission line. Typically, a **source** of some sort is located there. This makes physical sense, as something must generate the **incident wave**!

Special Values of Load Impedance

It's interesting to note that the load Z_L enforces a boundary condition that explicitly determines neither $V(z)$ nor $I(z)$ —but **completely specifies line impedance $Z(z)$!**

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \Gamma_L e^{+j\beta z}}{e^{-j\beta z} - \Gamma_L e^{+j\beta z}} = Z_0 \frac{Z_L \cos \beta z - jZ_0 \sin \beta z}{Z_0 \cos \beta z - jZ_L \sin \beta z}$$

$$\Gamma(z) = \Gamma_L e^{+j2\beta z} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{+j2\beta z}$$

Likewise, the load boundary condition leaves $V^+(z)$ and $V^-(z)$ undetermined, but **completely determines reflection coefficient function $\Gamma(z)$!**

Let's look at some **specific** values of load impedance $Z_L = R_L + jX_L$ and see what functions $Z(z)$ and $\Gamma(z)$ result!

- $Z_L = Z_0$

In this case, the **load impedance is numerically equal to the characteristic impedance** of the transmission line. Assuming the line is **lossless**, then Z_0 is **real**, and thus:

$$R_L = Z_0 \quad \text{and} \quad X_L = 0$$

It is evident that the resulting load reflection coefficient is **zero**:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

This result is very interesting, as it means that there is **no reflected wave** $V^-(z)$!

Thus, the **total** voltage and current along the transmission line is simply voltage and current of the **incident** wave:

$$V(z) = V^+(z) = V_0^+ e^{-j\beta z}$$

$$I(z) = I^+(z) = \frac{V_0^+}{Z_0} e^{-j\beta z}$$

Meaning that the **line** impedance is likewise **numerically** equal to the **characteristic** impedance of the transmission line for **all** line position z .

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_0^+ e^{-j\beta z}}{V_0^+ e^{-j\beta z}} = Z_0$$

And likewise, the reflection coefficient is **zero** at **all** points along the line:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{0}{V^+(z)} = 0$$

We call this condition (when $Z_L = Z_0$) the **matched** condition, and the load $Z_L = Z_0$ a **matched load**.

2. $Z_L = jX_L$

For this case, the load impedance is **purely reactive** (e.g. a capacitor or inductor), the real (resistive) portion of the load is zero:

$$R_L = 0$$

The resulting load reflection coefficient is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX_L - Z_0}{jX_L + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient is generally some **complex** number.

We can rewrite this value explicitly in terms of its **real** and **imaginary** part as:

$$\Gamma_L = \frac{jX_L - Z_0}{jX_L + Z_0} = \left(\frac{X_L^2 - Z_0^2}{X_L^2 + Z_0^2} \right) + j \left(\frac{2Z_0 X_L}{X_L^2 + Z_0^2} \right)$$

Yuck! This isn't much help!

Let's **instead** write this complex value Γ_L in terms of its **magnitude** and **phase**. For **magnitude** we find a much more straightforward result!

$$|\Gamma_L|^2 = \frac{|jX_L - Z_0|^2}{|jX_L + Z_0|^2} = \frac{X_L^2 + Z_0^2}{X_L^2 + Z_0^2} = 1$$

Its magnitude is **one!** Thus, we find that for reactive loads, the reflection coefficient can be simply expressed as:

$$\Gamma_L = e^{j\theta_\Gamma}$$

where

$$\theta_\Gamma = \tan^{-1} \left[\frac{2Z_0 X_L}{X_L^2 - Z_0^2} \right]$$

We can therefore conclude that for a **reactive load**:

$$V_0^- = e^{j\theta_\Gamma} V_0^+$$

As a result, the **total** voltage and current along the transmission line is simply (assuming $z_L = 0$):

$$\begin{aligned} V(z) &= V_0^+ (e^{-j\beta z} + e^{+j\theta_\Gamma} e^{+j\beta z}) \\ &= V_0^+ e^{+j\theta_\Gamma/2} (e^{-j(\beta z + \theta_\Gamma/2)} + e^{+j(\beta z + \theta_\Gamma/2)}) \\ &= 2V_0^+ e^{+j\theta_\Gamma/2} \cos(\beta z + \theta_\Gamma/2) \end{aligned}$$

$$\begin{aligned}
 I(z) &= \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{+j\beta z}) \\
 &= \frac{V_0^+}{Z_0} e^{+j\theta_L/2} (e^{-j(\beta z + \theta_L/2)} - e^{+j(\beta z + \theta_L/2)}) \\
 &= -j \frac{2V_0^+}{Z_0} e^{+j\theta_L/2} \sin(\beta z + \theta_L/2)
 \end{aligned}$$

Meaning that the **line impedance** can be written in terms of a trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = j Z_0 \cot(\beta z + \theta_r/2)$$

Note that this impedance is **purely reactive**— $V(z)$ and $I(z)$ are 90° out of phase!

We also note that the line impedance at the **end** of the transmission line is:

$$Z(z=0) = jZ_0 \cot(\theta_r/2)$$

With a little trigonometry, we can show (trust me!) that:

$$\cot(\theta_r/2) = \frac{X_L}{Z_0}$$

and therefore:

$$Z(z=0) = jZ_0 \cot(\theta_r/2) = j X_L = Z_L$$

Just as we **expected** (and our boundary condition **demanded**)!

Finally, the reflection coefficient **function** is:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V_0^+ e^{+j\theta_r} e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = e^{+j2(\beta z + \theta_r/2)}$$

Meaning that for purely reactive loads:

$$|\Gamma(z)| = \left| e^{+j2(\beta z + \theta_r/2)} \right| = 1$$

In other words, the **magnitude** reflection coefficient function is equal to one—at each and **every** point on the transmission line.

3. $Z_L = R_L$

For this case, the load impedance is **purely real** (e.g. a **resistor**), and thus there is no reactive component:

$$X_L = 0$$

The resulting **load reflection coefficient** is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R - Z_0}{R + Z_0}$$

Given that Z_0 is real (i.e., the line is **lossless**), we find that this load reflection coefficient must be a purely **real** value! In other words:

$$\operatorname{Re}\{\Gamma_L\} = \frac{R - Z_0}{R + Z_0} \quad \operatorname{Im}\{\Gamma_L\} = 0$$

So a real-valued load Z_L results in a real valued load reflection coefficient Γ_L .

Now let's consider the line impedance $Z(z)$ and reflection coefficient function $\Gamma(z)$.

Q: *I bet I know the answer to this one! We know that a purely imaginary (i.e., reactive) load results in a purely reactive line impedance.*

Thus, a purely real (i.e., resistive) load will result in a purely resistive line impedance, right??

A: NOPE! The line impedance resulting from a real load is complex—it has both real and imaginary components!

Thus the line impedance, as well as reflection coefficient function, **cannot** be further simplified for the case where $Z_L = R_L$.

Q: *Why is that?*

A: Remember, a **lossless** transmission line has series inductance and shunt capacitance **only**. In other words, a length of lossless transmission line is a **purely reactive** device (it absorbs **no** energy!).

* If we attach a **purely reactive** load at the end of the transmission line, we still have a **completely** reactive system (load and transmission line). Because this system has **no** resistive (i.e., real) component, the general expressions for line impedance, line voltage, etc. can be significantly **simplified**.

* However, if we attach a **purely real** load to our reactive transmission line, we now have a **complex** system, with **both** real and imaginary (i.e., resistive and reactive) components. This **complex** case is exactly what our general expressions **already** describes—**no** further simplification is possible!

$$4. Z_L = R_L + jX_L$$

Now, let's look at the **general** case, where the **load** has both a **real** (resistive) and **imaginary** (reactive) component.

Q: *Haven't we **already** determined all the **general** expressions (e.g., $\Gamma_L, V(z), I(z), Z(z), \Gamma(z)$) for this general case? Is there **anything** else left to be determined?*

A: There is **one** last thing we need to discuss. It seems trivial, but its ramifications are **very** important!

For you see, the "general" case is **not**, in reality, quite so general. Although the reactive component of the load can be **either** positive or negative ($-\infty < X_L < \infty$), the resistive component of a passive load **must** be positive ($R_L > 0$)—there's **no** such thing as **negative** resistor!

This leads to one **very** important and useful result. Consider the **load reflection coefficient**:

$$\begin{aligned}\Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{(R_L + jX_L) - Z_0}{(R_L + jX_L) + Z_0} \\ &= \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L}\end{aligned}$$

Now let's look at the **magnitude** of this value:

$$\begin{aligned}
 |\Gamma_L|^2 &= \left| \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L} \right|^2 \\
 &= \frac{(R_L - Z_0)^2 + X_L^2}{(R_L + Z_0)^2 + X_L^2} \\
 &= \frac{(R_L^2 - 2R_L Z_0 + Z_0^2) + X_L^2}{(R_L^2 + 2R_L Z_0 + Z_0^2) + X_L^2} \\
 &= \frac{(R_L^2 + Z_0^2 + X_L^2) - 2R_L Z_0}{(R_L^2 + Z_0^2 + X_L^2) + 2R_L Z_0}
 \end{aligned}$$

It is apparent that since both R_L and Z_0 are **positive**, the **numerator** of the above expression must be **less** than (or equal to) the **denominator** of the above expression.

→ In other words, the magnitude of the load reflection coefficient is always **less** than or equal to one!

$$|\Gamma_L| \leq 1 \quad (\text{for } R_L \geq 0)$$

Moreover, we find that this means the reflection coefficient **function** likewise always has a magnitude **less** than or equal to one, for **all** values of position z .

$$|\Gamma(z)| \leq 1 \quad (\text{for all } z)$$

Which means, of course, that the **reflected** wave will always have a magnitude **less** than that of the **incident** wave magnitude:

$$|V^-(z)| \leq |V^+(z)| \quad (\text{for all } z)$$

We will find out later that this result is consistent with **conservation of energy**—the reflected wave from a passive load **cannot** be larger than the wave incident on it.

The Propagation Constant β

Recall that the activity along a transmission line can be expressed in terms of two functions, functions that we have described as **wave functions**:

$$V^+(z) = V_0^+ e^{-j\beta z}$$

$$V^-(z) = V_0^- e^{+j\beta z}$$

where β is a real constant with value:

$$\beta = \omega\sqrt{LC}$$

Q: *What is this constant β ? What does it **physically** represent?*

A: Remember, a complex function can be expressed in terms of its **magnitude** and **phase**:

$$f(z) = |f(z)| e^{j\phi_f(z)}$$

Thus:

$$|V^+(z)| = |V_0^+| \quad \phi^+(z) = -\beta z + \phi_0^+$$

$$|V^-(z)| = |V_0^-| \quad \phi^-(z) = +\beta z + \phi_0^-$$

Therefore, $-\beta z + \phi_0^+$ represents the relative **phase** of wave $V^+(z)$; a **function** of transmission line **position** z . Since phase ϕ is expressed in **radians**, and z is distance (in meters), the value β must have **units** of:

$$\beta = \frac{\phi}{z} \quad \frac{\text{radians}}{\text{meter}}$$

The **wavelength** λ of the propagating wave is defined as the **distance** $\Delta z_{2\pi}$ over which the relative phase changes by 2π **radians**. So:

$$2\pi = \phi(z + \Delta z_{2\pi}) - \phi(z) = \beta \Delta z_{2\pi} = \beta \lambda$$

or, rearranging:

$$\beta = \frac{2\pi}{\lambda}$$

Thus, the value β is thus essentially a **spatial frequency**, in the same way that ω is a temporal frequency:

$$\omega = \frac{2\pi}{T}$$

where T is the **time** required for the phase of the oscillating signal to change by a value of 2π radians, i.e.:

$$\omega T = 2\pi$$

Note that this time is the **period** of a sinewave, and related to its **frequency** in Hertz (cycles/second) as:

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

Q: *So, just how fast does this wave propagate down a transmission line?*

We describe wave velocity in terms of its **phase velocity**—in other words, how **fast** does a specific value of absolute phase ϕ seem to **propagate** down the transmission line.

Since velocity is change in distance with respect to **time**, we need to first express our propagating wave in its real form:

$$\begin{aligned} v^+(z, t) &= \text{Re} \{ V^+(z) e^{-j\omega t} \} \\ &= |V_0^+| \cos(\omega t - \beta z + \phi_0^+) \end{aligned}$$

Thus, the absolute phase is a function of **both** time and frequency:

$$\phi^+(z, t) = \omega t - \beta z + \phi_0^+$$

Now let's set this phase to some **arbitrary** value of ϕ_c radians.

$$\omega t - \beta z + \phi_0^+ = \phi_c$$

For **every** time t , there is **some** location z on a transmission line that has this phase value ϕ_c . That location is evidently:

$$z = \frac{\omega t + \phi_0^+ - \phi_c}{\beta}$$

Note as **time increases**, so too does the **location** z on the line where $\phi^+(z, t) = \phi_c$.

The **velocity** v_p at which this phase point moves down the line can be determined as:

$$v_p = \frac{dz}{dt} = \frac{d\left(\frac{\omega t + \phi_0^+ - \phi_c}{\beta}\right)}{dt} = \frac{\omega}{\beta}$$

This wave velocity is the **velocity of the propagating wave!**

Note that the value:

$$\frac{v_p}{\lambda} = \frac{\omega}{\beta} \frac{\beta}{2\pi} = \frac{\omega}{2\pi} = f$$

and thus we can conclude that:

$$v_p = f\lambda$$

as well as:

$$\beta = \frac{\omega}{v_p}$$

Q: *But these results were derived for the $V^+(z)$ wave; what about the **other** wave ($V^-(z)$)?*

A: The results are essentially the **same**, as each wave depends on the same value β .

The only **subtle difference** comes when we evaluate the phase velocity. For the wave $V^-(z)$, we find:

$$\phi^-(z, t) = \omega t + \beta z + \phi_0^-$$

Note the **plus sign** associated with βz !

We thus find that some arbitrary phase value will be located at location:

$$z = \frac{-\phi_0^- + \phi_c - \omega t}{\beta}$$

Note now that an **increasing time** will result in a **decreasing** value of **position** z . In other words this wave is propagating in the direction of decreasing position z —in the **opposite** direction of the $V^+(z)$ wave!


This is **further** verified by the derivative:

$$v_p = \frac{dz}{dt} = \frac{d\left(\frac{-\phi_0^- + \phi_c - \omega t}{\beta}\right)}{dt} = -\frac{\omega}{\beta}$$

Where the **minus sign** merely means that the wave propagates in the $-z$ direction. Otherwise, the **wavelength** and **velocity** of the two waves are **precisely** the same!

Transmission Line Input Impedance

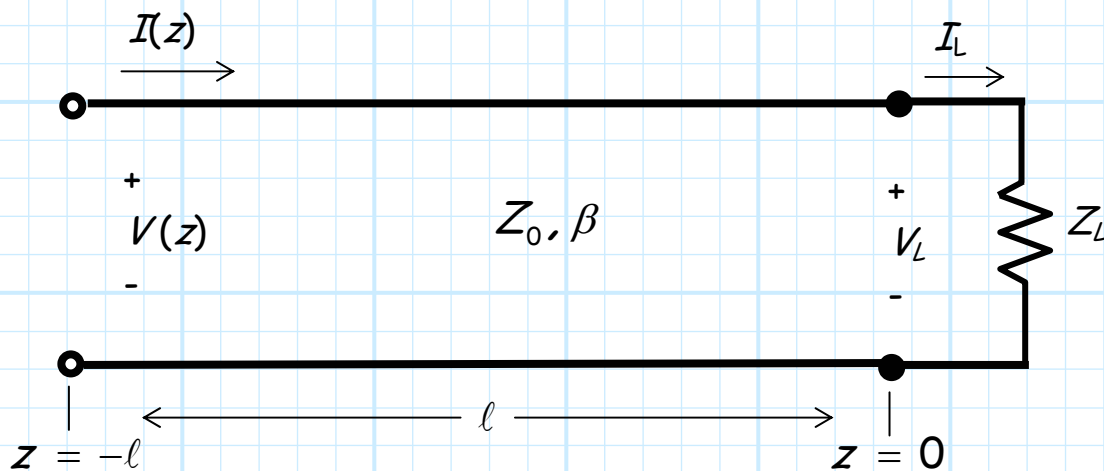Consider a lossless line, length ℓ , terminated with a load Z_L .



Let's determine the **input impedance** of this line!

Q: *Just what do you mean by **input impedance**?*

A: The input impedance is simply the line impedance seen at the **beginning** ($z = -\ell$) of the transmission line, i.e.:

$$Z_{in} = Z(z = -\ell) = \frac{V(z = -\ell)}{I(z = -\ell)}$$

Note Z_{in} equal to **neither** the load impedance Z_L **nor** the characteristic impedance Z_0 !

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$

To determine exactly what Z_{in} is, we first must determine the voltage and current at the **beginning** of the transmission line ($z = -\ell$).

$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Therefore:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left(\frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right)$$

We can explicitly write Z_{in} in terms of load Z_L using the previously determined relationship:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Combining these two expressions, we get:

$$\begin{aligned} Z_{in} &= Z_0 \frac{(Z_L + Z_0)e^{+j\beta\ell} + (Z_L - Z_0)e^{-j\beta\ell}}{(Z_L + Z_0)e^{+j\beta\ell} - (Z_L - Z_0)e^{-j\beta\ell}} \\ &= Z_0 \left(\frac{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) + Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})}{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) - Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})} \right) \end{aligned}$$

Now, recall **Euler's equations**:

$$e^{+j\beta\ell} = \cos \beta\ell + j \sin \beta\ell$$

$$e^{-j\beta\ell} = \cos \beta\ell - j \sin \beta\ell$$

Using Euler's relationships, we can likewise write the input impedance without the **complex** exponentials:

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right) \end{aligned}$$

Note that depending on the values of β , Z_0 and l , the input impedance can be **radically** different from the load impedance Z_L !

Q: *So is there a similar concept of input reflection coefficient?*

A: There sure is! As you might expect, it is simply the value of reflection coefficient function $\Gamma(z)$ evaluated at the beginning of the transmission line (i.e., at $z = -l$):


$$\Gamma_{in} \doteq \Gamma(z = -l) = \Gamma_0 e^{-j2\beta l}$$

Note that the input impedance and input reflection coefficient are related in the same way as Z and Γ are at every other point on the transmission line:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Power Flow and Return Loss

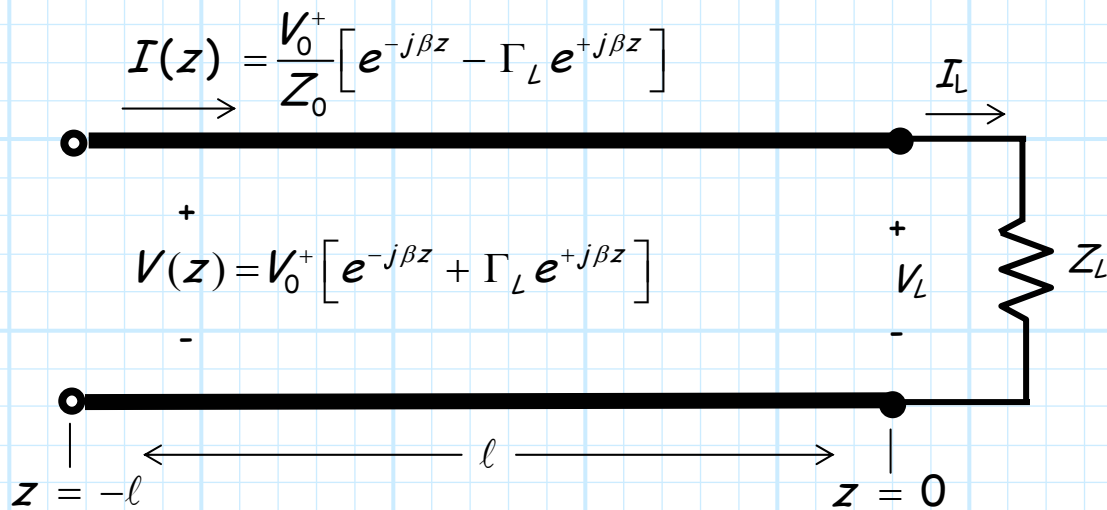We have discovered that **two waves propagate** along a transmission line, one in each direction ($V^+(z)$ and $V^-(z)$).



The result is that electromagnetic energy flows along the transmission line at a given rate (i.e., **power**).

Q: *How much power flows along a transmission line, and where does that power go?*

A: We can answer that question by determining the power **absorbed** by the load!

The **time average** power absorbed by an impedance Z_L is:

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} \\
 &= \frac{1}{2} \operatorname{Re}\{V(z=0) I(z=0)^*\} \\
 &= \frac{1}{2 Z_0} \operatorname{Re}\left\{ \left(V_0^+ [e^{-j\beta 0} + \Gamma_L e^{+j\beta 0}] \right) \left(V_0^+ [e^{-j\beta 0} - \Gamma_L e^{+j\beta 0}] \right)^* \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} \operatorname{Re}\left\{ 1 - (\Gamma_L^* - \Gamma_L) - |\Gamma_L|^2 \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)
 \end{aligned}$$

The significance of this result can be seen by **rewriting** the expression as:

$$\begin{aligned}
 P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^+ \Gamma_L|^2}{2 Z_0} \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^-|^2}{2 Z_0}
 \end{aligned}$$

The two terms in above expression have a very definite **physical meaning**. The first term is the time-averaged **power of the wave** propagating along the transmission line **toward the load**.

We say that this wave is **incident** on the load:

$$P_{inc} = P_+ = \frac{|V_0^+|^2}{2Z_0}$$

Likewise, the second term of the P_{abs} equation describes the **power of the wave** moving in the other direction (**away from the load**). We refer to this as the wave **reflected** from the load:

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma_L|^2 |V_0^+|^2}{2Z_0} = |\Gamma_L|^2 P_{inc}$$

Thus, the power **absorbed** by the load is simply:


$$P_{abs} = P_{inc} - P_{ref}$$

or, rearranging, we find:

$$P_{inc} = P_{abs} + P_{ref}$$

This equation is simply an expression of the **conservation of energy** !

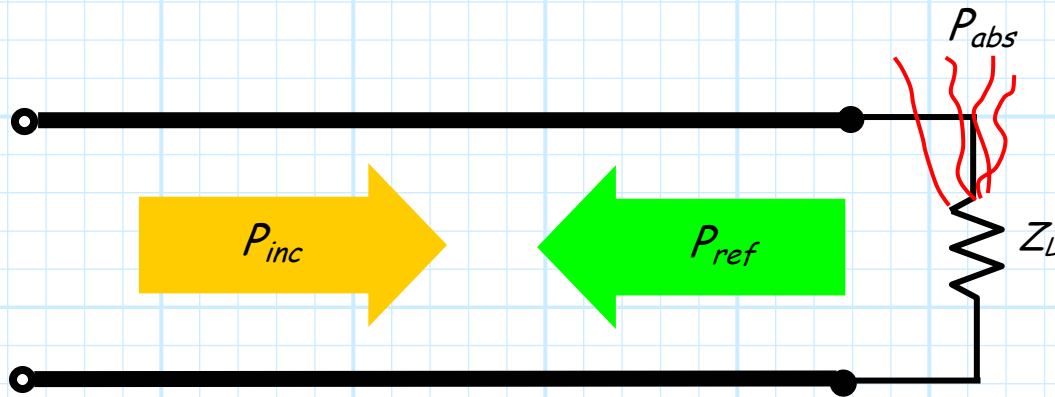It says that power flowing **toward** the load (P_{inc}) is either **absorbed** by the load (P_{abs}) or **reflected** back from the load (P_{ref}).



Note that if $|\Gamma_L|^2 = 1$, then $P_{inc} = P_{ref}$, and therefore **no power** is absorbed by the load.

This of course **makes sense** !

The magnitude of the reflection coefficient ($|\Gamma_L|$) is equal to one **only** when the load impedance is **purely reactive** (i.e., purely imaginary).

Of course, a purely reactive element (e.g., capacitor or inductor) **cannot** absorb any power—**all** the power **must** be reflected!

Return Loss

The **ratio** of the reflected power to the incident power is known as **return loss**. Typically, return loss is expressed in **dB**:

$$R.L. = -10 \log_{10} \left[\frac{P_{ref}}{P_{inc}} \right] = -10 \log_{10} |\Gamma_L|^2$$

For **example**, if the return loss is **10dB**, then **10%** of the incident power is **reflected** at the load, with the remaining **90%** being **absorbed** by the load—we “lose” 10% of the incident power

Likewise, if the return loss is **30dB**, then **0.1 %** of the incident power is **reflected** at the load, with the remaining **99.9%** being **absorbed** by the load—we “lose” 0.1% of the incident power.

Thus, a **larger** numeric value for return loss **actually** indicates **less** lost power! An **ideal** return loss would be ∞ dB, whereas a return loss of 0 dB indicates that $|\Gamma_L| = 1$ --the load is **reactive!**

VSWR

Consider again the **voltage** along a terminated transmission line, as a function of **position** z :

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

Recall this is a **complex** function, the magnitude of which expresses the **magnitude** of the **sinusoidal signal** at position z , while the phase of the complex value represents the relative **phase** of the sinusoidal signal.

Let's look at the **magnitude** only:

$$\begin{aligned} |V(z)| &= |V_0^+| |e^{-j\beta z} + \Gamma_L e^{+j\beta z}| \\ &= |V_0^+| |e^{-j\beta z}| |1 + \Gamma_L e^{+j2\beta z}| \\ &= |V_0^+| |1 + \Gamma_L e^{+j2\beta z}| \end{aligned}$$

ICBST the **largest** value of $|V(z)|$ occurs at the location z where:

$$\Gamma_L e^{+j2\beta z} = |\Gamma_L| + j0$$

while the **smallest** value of $|V(z)|$ occurs at the location z where:

$$\Gamma_L e^{+j2\beta z} = -|\Gamma_L| + j0$$

As a result we can conclude that:

$$|V(z)|_{\max} = |V_0^+| (1 + |\Gamma_L|)$$

$$|V(z)|_{\min} = |V_0^+| (1 - |\Gamma_L|)$$

The ratio of $|V(z)|_{\max}$ to $|V(z)|_{\min}$ is known as the **Voltage Standing Wave Ratio (VSWR)**:

$$VSWR \doteq \frac{|V(z)|_{\max}}{|V(z)|_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \therefore \quad 1 \leq VSWR \leq \infty$$

Note if $|\Gamma_L| = 0$ (i.e., $Z_L = Z_0$), then $VSWR = 1$. We find for this case:

$$|V(z)|_{\max} = |V(z)|_{\min} = |V_0^+|$$


In other words, the voltage magnitude is a **constant** with respect to position z .

Conversely, if $|\Gamma_L| = 1$ (i.e., $Z_L = jX$), then $VSWR = \infty$. We find for **this** case:

$$|V(z)|_{\min} = 0 \quad \text{and} \quad |V(z)|_{\max} = 2|V_0^+|$$

In other words, the voltage magnitude varies **greatly** with respect to position z .


As with **return loss**, VSWR is dependent on the **magnitude** of Γ_L (i.e., $|\Gamma_L|$) **only** !

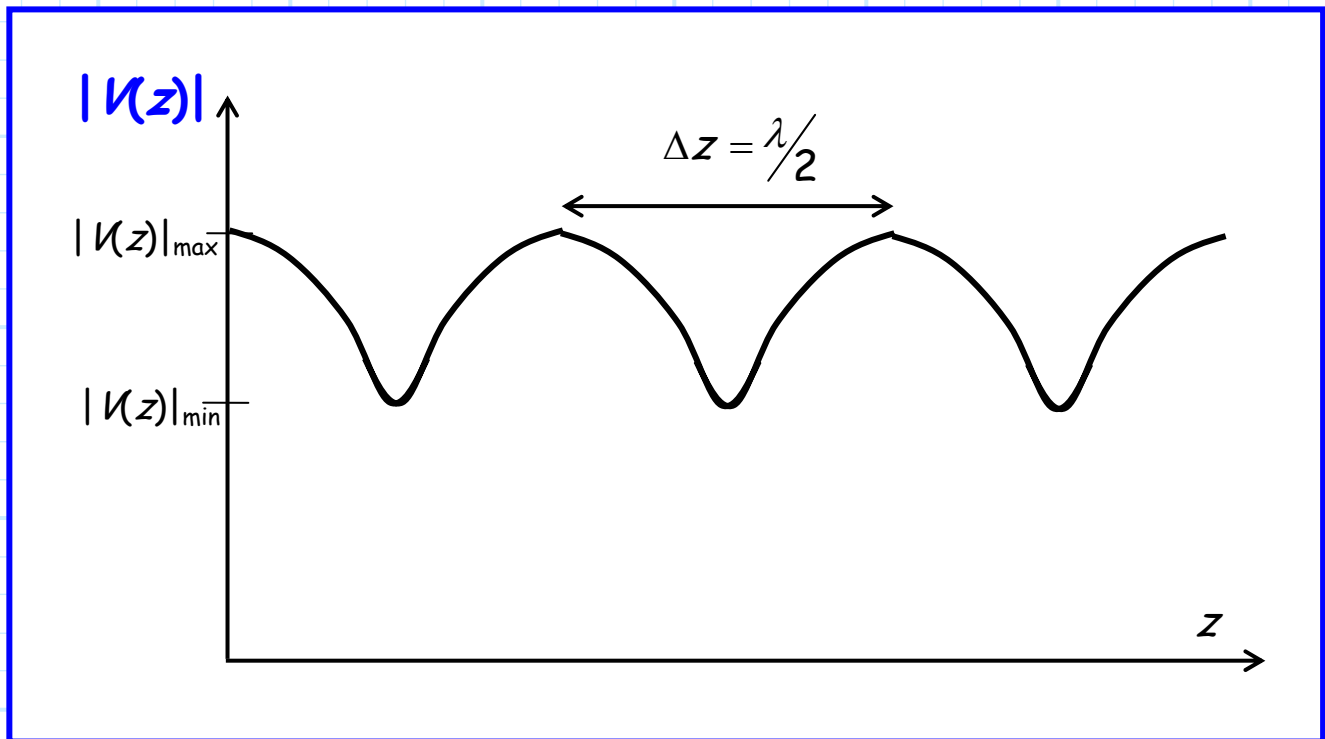


A Transmission Line Connecting Source & Load

We can think of a transmission line as a conduit that allows **power** to flow from an **output** of one device/network to an **input** of another.

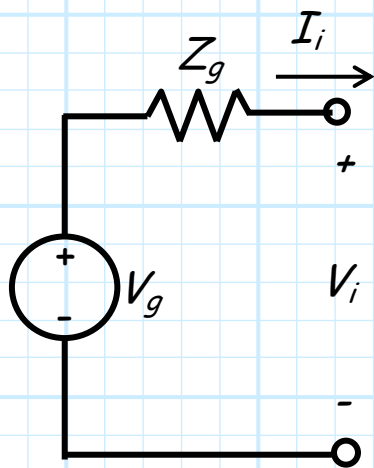To simplify our analysis, we can model the **input** of the device **receiving** the power with its input impedance (e.g., Z_L), while we can model the device **output delivering** the power with its Thevenin's or Norton's equivalent circuit.




$$V_g = V_i + Z_g I_i$$

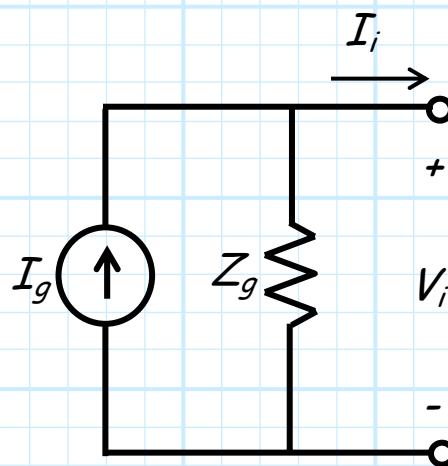

$$I_g = \frac{V_i}{Z_g} + I_i$$

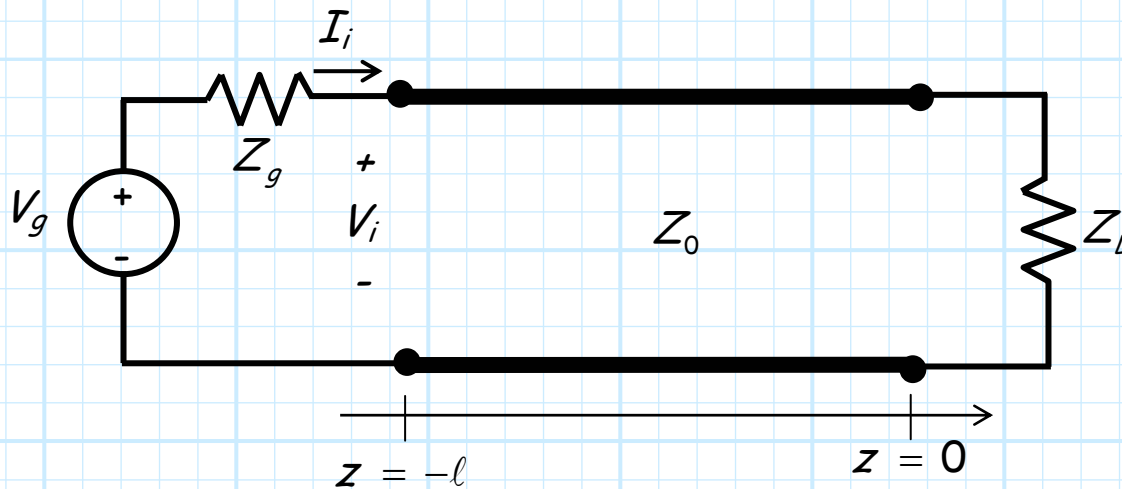Typically, the power source is modeled with its **Thevenin's** equivalent; however, we will find that the **Norton's** equivalent circuit is useful if we express the remainder of the circuit in terms of its **admittance** values (e.g., $Y_0, Y_L, Y(z)$).



Recall from the telegrapher's equations that the current and voltage along the transmission line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

At $z = 0$, we enforced the **boundary condition** resulting from Ohm's Law:

$$Z_L = \frac{V_L}{I_L} = \frac{V(z=0)}{I(z=0)} = \frac{(V_0^+ + V_0^-)}{\left(\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}\right)}$$

Which resulted in:

$$\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \doteq \Gamma_L$$

So therefore:

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_L e^{+j\beta z}]$$

We are left with the **question**: just what is the **value** of complex constant V_0^+ ?!?

This constant depends on the signal source! To determine its exact **value**, we must now apply **boundary conditions** at $z = -\ell$.

We know that at the **beginning** of the transmission line:


$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Likewise, we know that the **source** must satisfy:

$$V_g = V_i + Z_g I_i$$

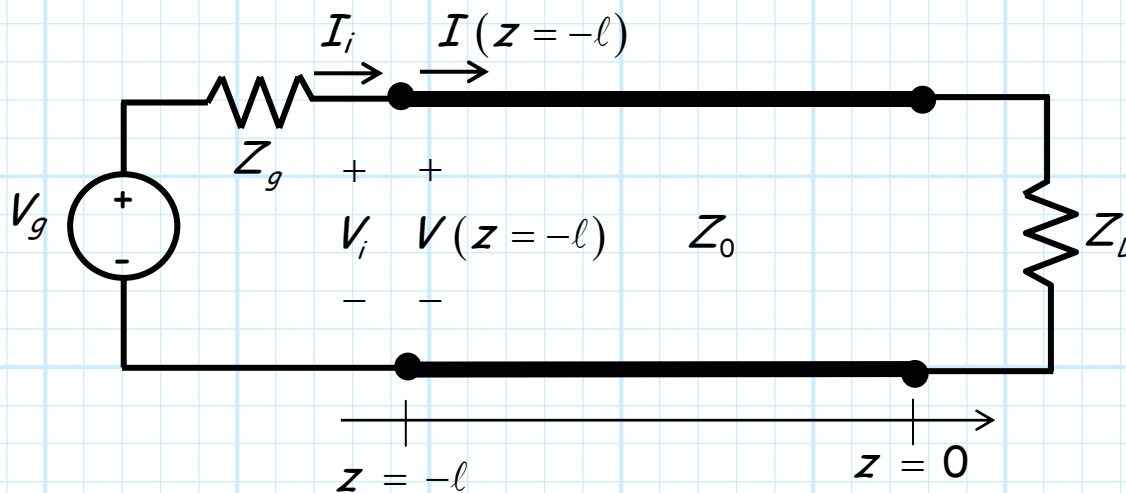To relate these **three** expressions, we need to apply **boundary conditions** at $z = -\ell$:



From **KVL** we find:

$$V_i = V(z = -\ell)$$

And from **KCL**:

$$I_i = I(z = -\ell)$$

Combining these equations, we find:

$$V_g = V_i + Z_g I_i$$

$$V_g = V_0^+ \left[e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right] + Z_g \frac{V_0^+}{Z_0} \left[e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right]$$

One equation \rightarrow **one unknown** (V_0^+)!!

Solving, we find the value of V_0^+ :



$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

where:

$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$

There is one **very important** point that must be made about the result:

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

And that is—the wave $V_0^+(z)$ **incident** on the load Z_L is actually dependent on the value of load Z_L !!!!

Remember:


$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$

We tend to think of the incident wave $V_0^+(z)$ being “**caused**” by the source, and it is certainly true that $V_0^+(z)$ **depends** on the source—after all, $V_0^+(z) = 0$ if $V_g = 0$. However, we find from the equation above that it **likewise** depends on the value of the load!

Thus we **cannot**—in general—consider the incident wave to be the “**cause**” and the reflected wave the “**effect**”. Instead, each wave must obtain the proper **amplitude** (e.g., V_0^+, V_0^-) so that the boundary conditions are satisfied at **both** the beginning and end of the transmission line.

Delivered Power

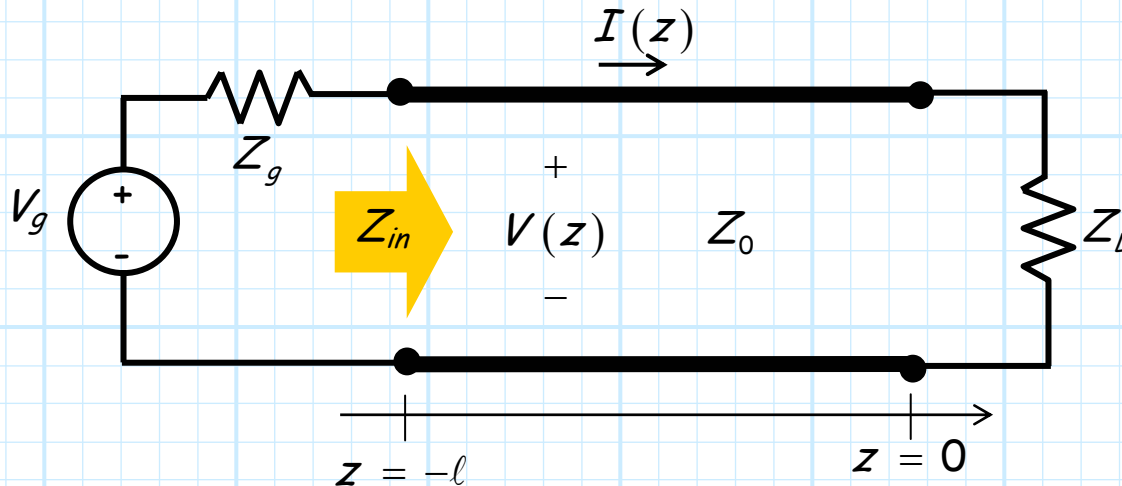Q: If the purpose of a transmission line is to transfer **power** from a source to a load, then exactly how much power is **delivered** to Z_L for the circuit shown below ??



A: We of course **could** determine V_0^+ and V_0^- , and then determine the power absorbed by the load (P_{abs}) as:


$$P_{abs} = \frac{1}{2} \operatorname{Re} \{ V(z=0) I^*(z=0) \}$$

However, if the transmission line is **lossless**, then we know that the power delivered to the load must be **equal** to the power "delivered" to the **input** (P_{in}) of the transmission line:

$$P_{abs} = P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z=-l) I^*(z=-l) \}$$

However, we can determine this power **without** having to solve for V_0^+ and V_0^- (i.e., $V(z)$ and $I(z)$). We can simply use our knowledge of **circuit theory!**

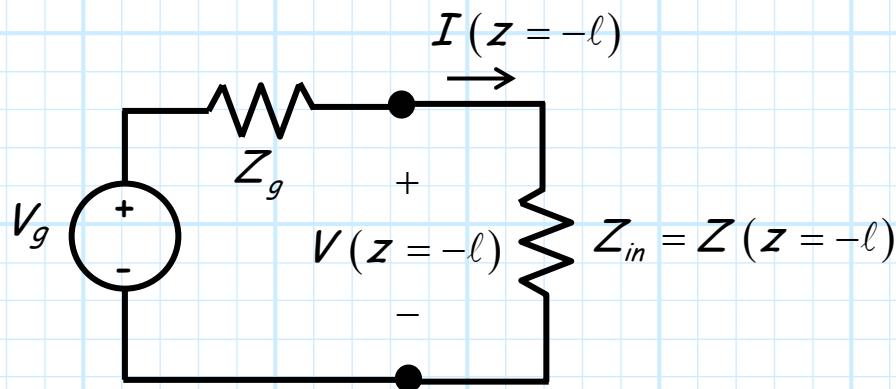We can **transform** load Z_L to the beginning of the transmission line, so that we can replace the transmission line with its **input impedance** Z_{in} :



Note by **voltage division** we can determine:

$$V(z = -l) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from **Ohm's Law** we conclude:

$$I(z = -l) = \frac{V_g}{Z_g + Z_{in}}$$

And thus, the **power** P_{in} delivered to Z_{in} (and thus the **power** P_{abs} delivered to the load Z_L) is:

$$\begin{aligned}
 P_{abs} &= P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{V_g^*}{(Z_g + Z_{in})^*} \right\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \} \\
 &= \frac{1}{2} |V_g|^2 \frac{|Z_{in}|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ y_{in} \}
 \end{aligned}$$

Note that we could **also** determine P_{abs} from our **earlier** expression:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

But we would of course have to **first** determine V_0^+ (!):

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

Special Cases of Source and Load Impedance

Let's look at **specific cases** of Z_g and Z_L , and determine how they affect V_0^+ and P_{abs} .

$$Z_g = Z_0$$

For this case, we find that V_0^+ **simplifies** greatly:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_0(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{1}{1 + \Gamma_{in} + 1 - \Gamma_{in}} \\ &= \frac{1}{2} V_g e^{-j\beta\ell} \end{aligned}$$

Look at what **this** says!

It says that the incident wave in this case is **independent** of the load attached at the other end!

Thus, for the **one** case $Z_g = Z_0$, we in fact can consider $V^+(z)$ as being the source wave, and then the reflected wave $V^-(z)$ as being the result of this stimulus.

Remember, the complex value V_0^+ is the value of the incident wave evaluated at the end of the transmission line ($V_0^+ = V^+(z=0)$). We can likewise determine the value of the incident wave at the **beginning** of the transmission line (i.e., $V^+(z=-\ell)$). For this case, where $Z_g = Z_0$, we find that this value can be very simply stated (!):

$$\begin{aligned} V^+(z=-\ell) &= V_0^+ e^{-j\beta(z=-\ell)} \\ &= \left(\frac{1}{2} V_g e^{-j\beta\ell} \right) e^{+j\beta\ell} \\ &= \frac{V_g}{2} \end{aligned}$$

Likewise, we find that the delivered power for this case can be simply stated as:

$$\begin{aligned} P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\ &= \frac{|V_g|^2}{8 Z_0} (1 - |\Gamma_L|^2) \end{aligned}$$

$$Z_{in} = Z_g^*$$

For this case, we find Z_L takes on whatever value required to make $Z_{in} = Z_g^*$. This is a **very** important case!

First, using the fact that:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_g^* - Z_0}{Z_g^* + Z_0}$$

We can show that (trust me!):

$$V_0^+ = V_g e^{-j\beta l} \frac{Z_g^* + Z_0}{4\text{Re}\{Z_g\}}$$

Not a particularly interesting result, but let's look at the absorbed power.

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_g^*|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|2\operatorname{Re}\{Z_g^*\}|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} |V_g|^2 \frac{1}{4\operatorname{Re}\{Z_g^*\}} = P_{avl}
 \end{aligned}$$


Although this result does not look particularly interesting **either**, we find the result is **very** important!

It can be shown that—for a **given** V_g and Z_g —the value of input impedance Z_{in} that will absorb the **largest possible** amount of power is the value $Z_{in} = Z_g^*$.

This case is known as the **conjugate match**, and is essentially the goal of every transmission line problem—to deliver the largest possible power to Z_{in} , and thus to Z_L as well!


This maximum delivered power is known as the **available power** (P_{avl}) of the source.

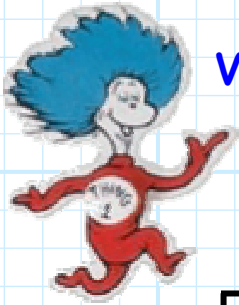There are **two** very important things to understand about this result!



Very Important Thing #1

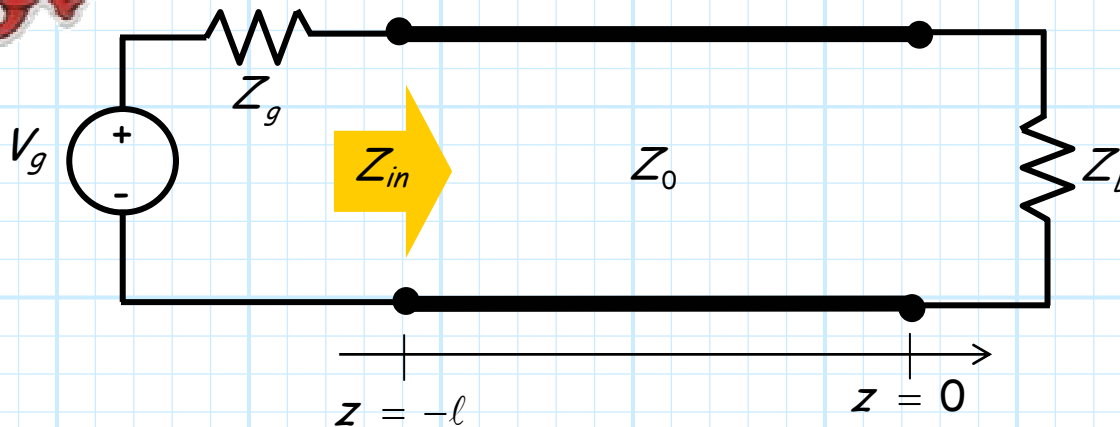Consider again the terminated transmission line:



Recall that if $Z_L = Z_0$, the **reflected** wave will be **zero**, and the absorbed power will be:

$$P_{abs} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2}$$

But note if $Z_L = Z_0$, the input impedance $Z_{in} = Z_0$ —but then $Z_{in} \neq Z_g^*$ (generally)! In other words, $Z_L = Z_0$ does **not** (generally) result in a **conjugate match**, and thus setting $Z_L = Z_0$ does **not** result in maximum power absorption!

Q: *Huh!? This makes no sense! A load value of $Z_L = Z_0$ will minimize the reflected wave ($P^- = 0$)—all of the incident power will be absorbed. Any other value of $Z_L \neq Z_0$ will result in some of the incident wave being reflected—how in the world could this increase absorbed power?*

After all, just look at the expression for absorbed power:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

Clearly, this value is maximized when $\Gamma_L = 0$ (i.e., when $Z_L = Z_0$)!!!

A: You are forgetting one very important fact! Although it is true that the load impedance Z_L affects the **reflected** wave power P^- , the value of Z_L —as we have shown in this handout—**likewise** helps determine the value of the **incident** wave (i.e., the value of P^+) as well.

Thus, the value of Z_L that minimizes P^- will **not** generally maximize P^+ , **nor** will the value of Z_L that maximizes P^+ likewise minimize P^- .

Instead, the value of Z_L that maximizes the **absorbed** power is, by definition, the value that maximizes the **difference** $P^+ - P^-$.

We find that this value of Z_L is the value that makes Z_{in} as "close" as possible to the **ideal** case of $Z_{in} = Z_g^*$.

Q: *Yes, but what about the case where $Z_g = Z_0$? For that case, we determined that the incident wave is independent of Z_L . Thus, it would seem that at least for that case, the*

delivered power would be maximized when the reflected power was minimized (i.e., $Z_L = Z_0$).

A: True! But think about what the **input** impedance would be in that case— $Z_{in} = Z_0$. Oh by the way, that provides a **conjugate match** ($Z_{in} = Z_0 = Z_g^*$)!

Thus, in some ways, the case $Z_g = Z_0 = Z_L$ (i.e., **both** source and load impedances are numerically equal to Z_0) is **ideal**. A **conjugate match** occurs, the incident wave is **independent** of Z_L , there is **no** reflected wave, and all the math **simplifies** quite nicely:

$$V_0^+ = \frac{1}{2} V_g e^{-j\beta\ell} \qquad P_{abs} = \frac{|V_g|^2}{8 Z_0}$$



Very Important Thing #2

Note the conjugate match criteria **says**:

Given V_g and Z_g , maximum power transfer occurs when $Z_{in} = Z_g^$.*

It does **NOT** say:

Given V_g and Z_{in} , maximum power transfer occurs when $Z_g^ = Z_{in}$.*

This last statement is in fact **false!**

A **factual** statement is this:

Given V_g and Z_{in} , maximum power transfer occurs when $Z_g = 0$.

A fact that is **evident** when observing the expression for **available power**:


$$P_{available} = \frac{1}{2} |V_g|^2 \frac{1}{4 \operatorname{Re}\{Z_g^*\}} = \frac{|V_g|^2}{8R_g}$$

In other words, given a choice, use a source with the **smallest** possible **output resistance** (given that V_g remains **constant**).

This will maximize the **available power** from your source!

Matching Networks

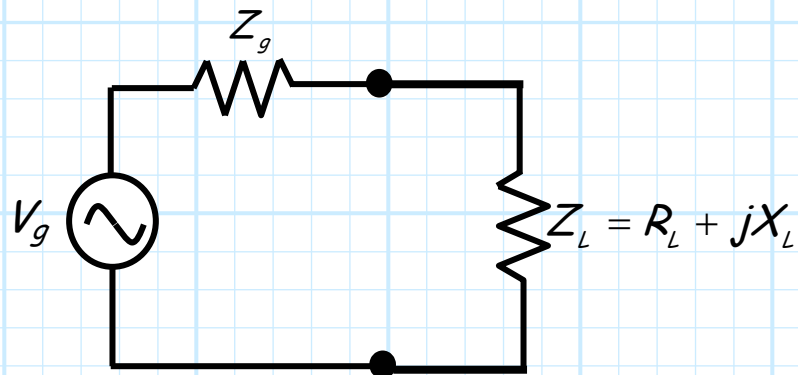Consider again the problem where a **passive load** is attached to an **active source**:



The load will **absorb power**—power that is **delivered** to it by the **source**.

$$\begin{aligned}
 P_L &= \frac{1}{2} \operatorname{Re} \{ V_L I_L^* \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ \left(V_g \frac{Z_L}{Z_g + Z_L} \right) \left(\frac{V_g}{Z_g + Z_L} \right)^* \right\} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re} \{ Z_L \}}{|Z_g + Z_L|^2} \\
 &= \frac{1}{2} |V_g|^2 \frac{R_L}{|Z_g + Z_L|^2}
 \end{aligned}$$

Recall that the power delivered to the load will be **maximized** (for a given V_g and Z_g) if the load impedance is equal to the **complex conjugate** of the source impedance ($Z_L = Z_g^*$).

We call this maximum power the **available power** P_{avl} of the **source**—it is, after all, the **largest** amount of power that the source can **ever** deliver!

$$P_L^{max} \doteq P_{avl} = \frac{|V_g|^2}{8 R_g}$$

- * Note the available power of the **source** is dependent on **source** parameters **only** (i.e., V_g and R_g). This makes sense! Do you see why?
- * Thus, we can say that to “take full advantage” of all the available power of the source, we must to make the load impedance the complex conjugate of the source impedance.
- * Otherwise, the power delivered to the load will be less than power made available by the source! In other “words”:


$$P_L \leq P_{avl}$$

Q: *But, you said that the load impedance typically models the input impedance of some useful device. We **don't** typically get to “select” or adjust this impedance—it is what it is. Must we then simply **accept** the fact that the delivered power will be less than the available power?*




A: NO! We can in fact modify our circuit such that all available source power is delivered to the load—**without** in any way **altering** the impedance value of that load!

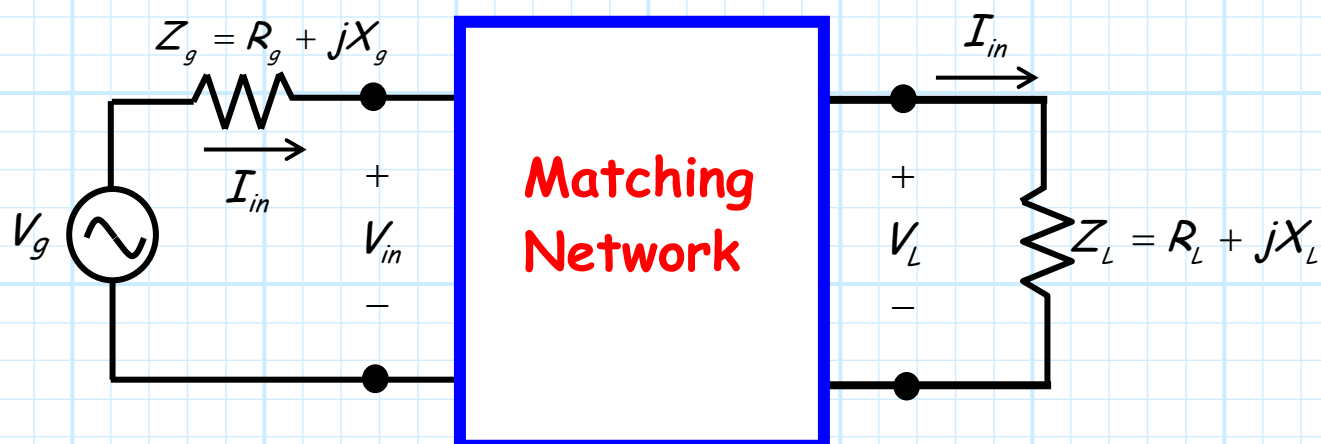To accomplish this, we must insert a **matching network** between the source and the load:




The sole purpose of this matching network is to “transform” the load impedance into an input impedance that is **conjugate matched** to the source! I.E.:
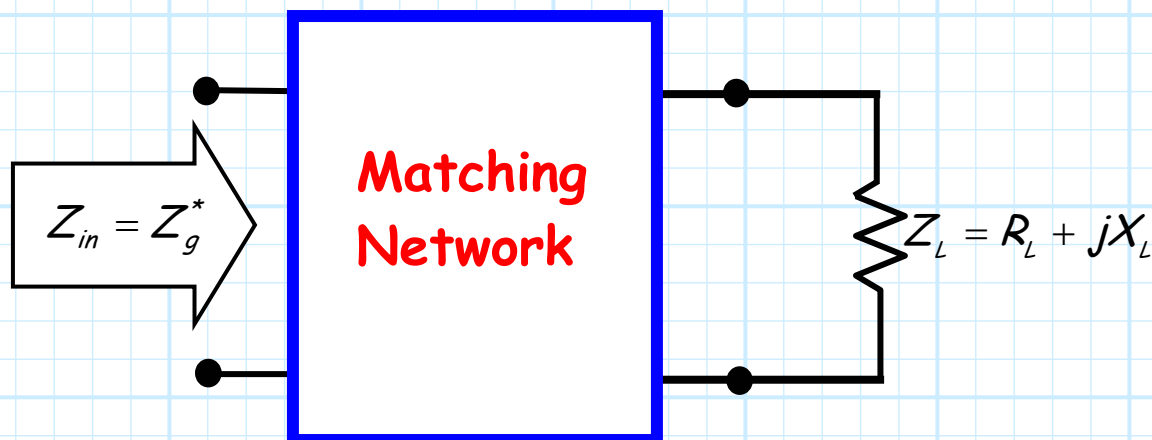
$$Z_{in} = \frac{V_{in}}{I_{in}} = Z_g^*$$




Because of this, **all** available source power is delivered to the input of the matching network (i.e., delivered to Z_{in}):

$$P_{in} = P_{avl}$$

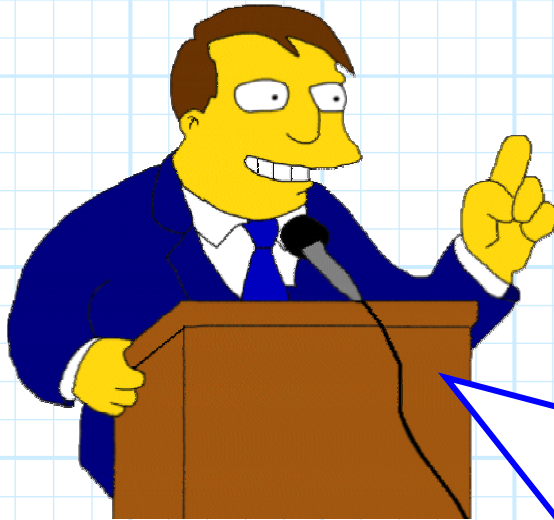

Q: *Wait just one second! The matching network ensures that **all** available power is delivered to the **input** of the matching network, but that does **not** mean (necessarily) that this power will be delivered to the **load** Z_L . The power delivered to the load **could** still be **much less** than the available power!*

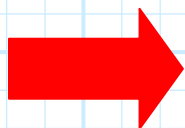A: True! To ensure that the **available power** delivered to the input of the matching network is **entirely** delivered to the **load**, we must construct our matching network such that it **cannot absorb any power**—the matching network must be **lossless!**



We must construct our matching network entirely with **reactive elements!**


Examples of reactive elements include inductors, capacitors, transformers, as well as lengths of **lossless transmission lines**.

Thus, constructing a proper lossless matching network will lead to the **happy** condition where:


$$P_L = P_{in} = P_{avl}$$

- * Note that the design and construction of this lossless network will depend on **both** the value of source impedance Z_g and load impedance Z_L .
- * However, the matching network does **not physically alter** the values of either of these two quantities—the source and load are left physically unchanged!

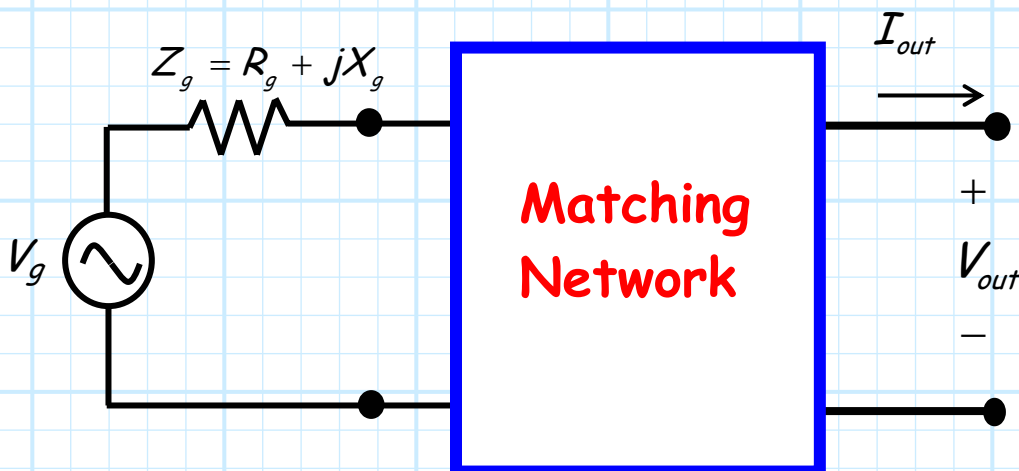
Now, let's consider the matching network from a **different perspective**. Instead of defining it in terms of its **input impedance** when attached the load, let's describe it in terms of its **output impedance** when attached to the **source**:



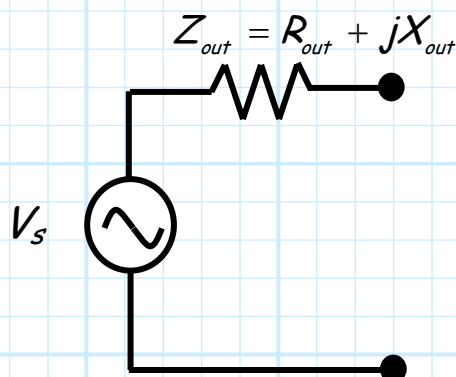
This "new" source (i.e., the original source with the matching network attached) can be expressed in terms of its **Thevenin's equivalent circuit**:



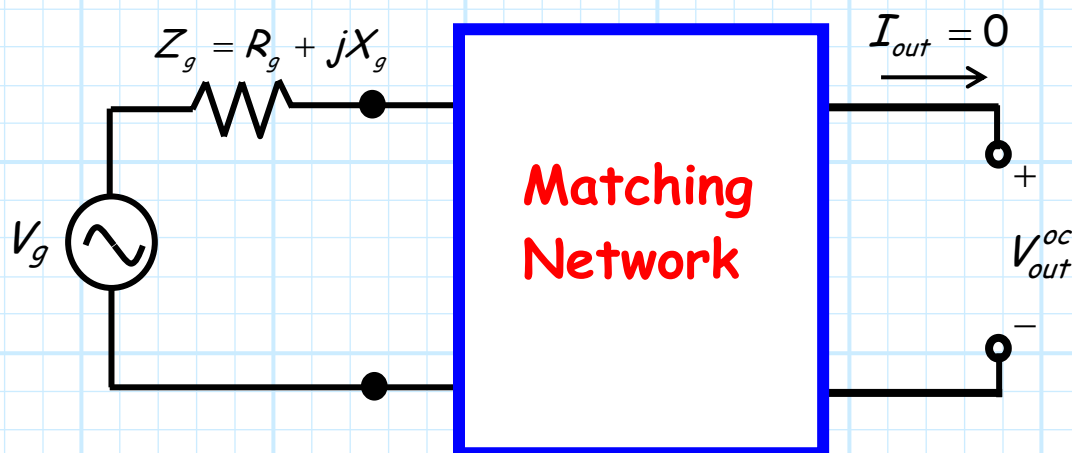This equivalent circuit can be determined by first evaluating (or measuring) the **open-circuit output voltage** V_{out}^{oc} :



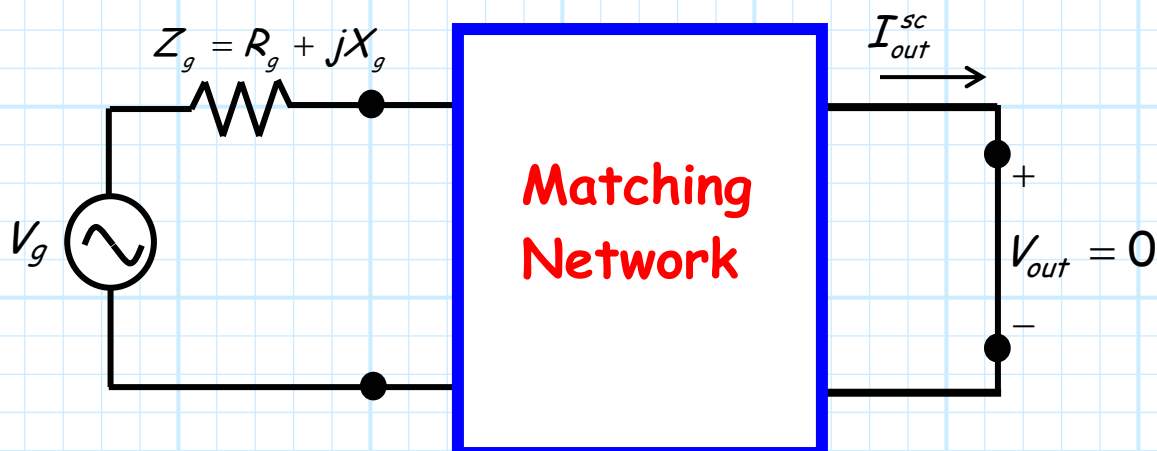And likewise evaluating (or measuring) the **short-circuit output current** I_{out}^{sc} :



From these two values (V_{out}^{oc} and I_{out}^{sc}) we can determine the **Thevenin's equivalent source**:

$$V_s = V_{out}^{oc} \quad Z_{out} = \frac{V_{out}^{oc}}{I_{out}^{oc}}$$

Note that in general that $V_s \neq V_g$ and $Z_{out} \neq Z_g$ —the matching network “transforms” **both** the values of both the impedance **and** the voltage source.




Q: Arrrrgg! Doesn't that mean that the **available power** of this “transformed” source will be **different** from the original?

A: Nope. **If** the matching network is **lossless**, the available power of this equivalent source is **identical** to the available power of the original source—the lossless matching network does **not** alter the available power!


$$P_{avl} = \frac{|V_g|^2}{8R_g} = \frac{|V_s|^2}{8R_{out}}$$

Now, for a **properly** designed, **lossless** matching network, it turns out that (as you might have expected!) the output impedance Z_{out} is equal to the **complex conjugate** of the load impedance. I.E.:


$$Z_{out} = Z_L^*$$

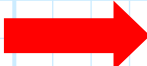 The source and load are again matched!

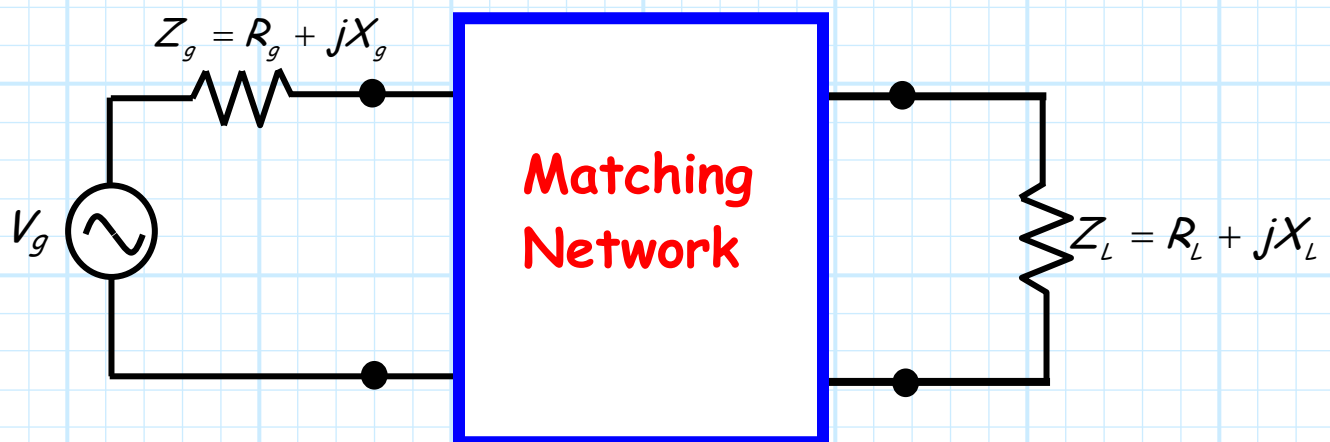
Thus, we can look at the matching network in two equivalent ways:



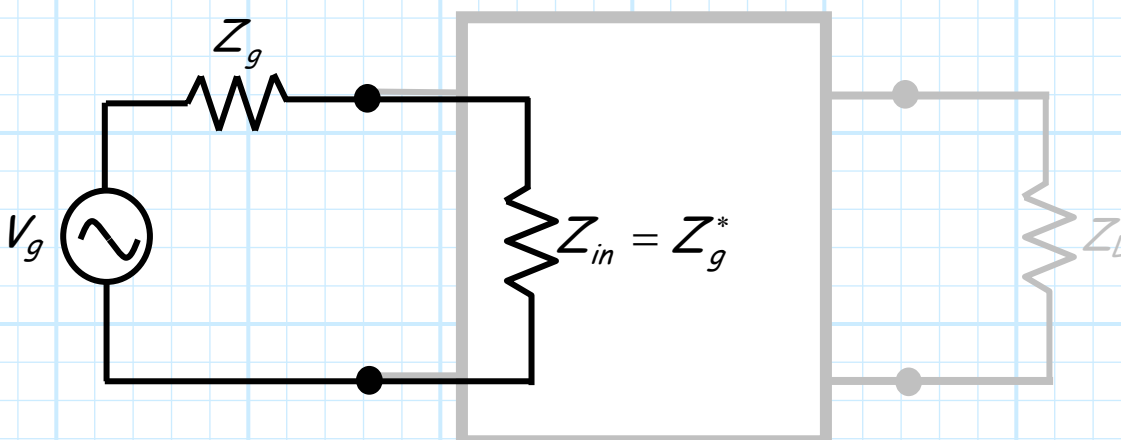1. As a network attached to a load, one that "transforms" its impedance to Z_{in} —a value matched to the source impedance Z_g :




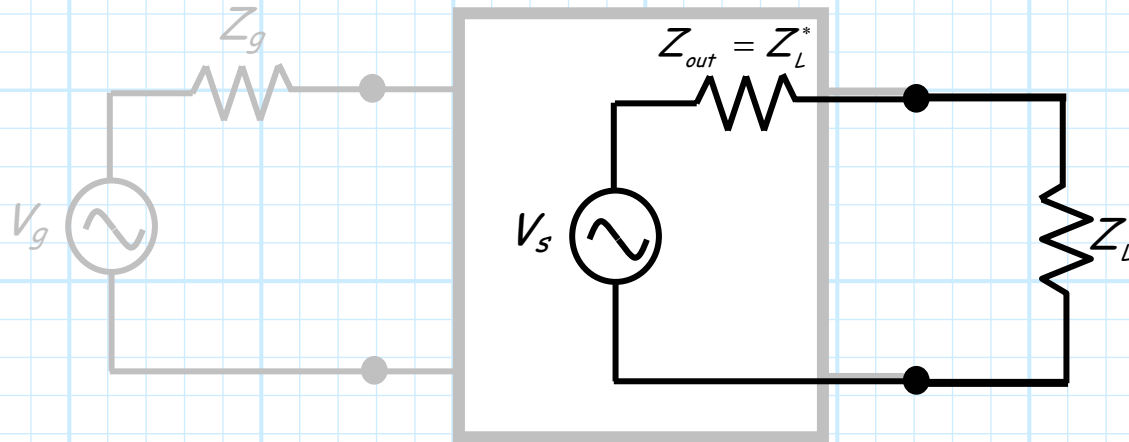2. Or, as network attached to a source, one that "transforms" its impedance to Z_{out} —a value matched to the load impedance Z_L :



Either way, the source and load impedance are conjugate matched—**all** the available power is delivered to the load!

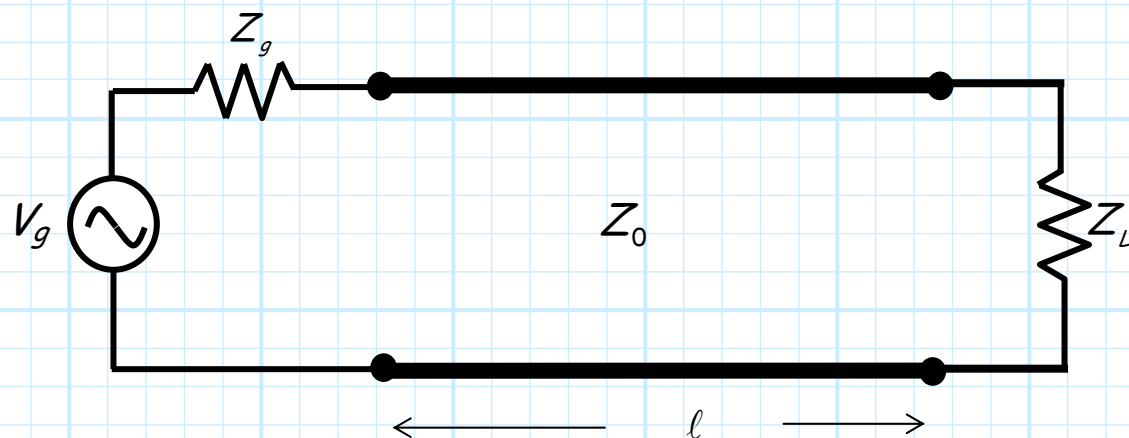Recall that a primary purpose of a transmission line is to allow the transfer of power from a source to a load.




Recall that the **efficacy** of this power transfer depends on:

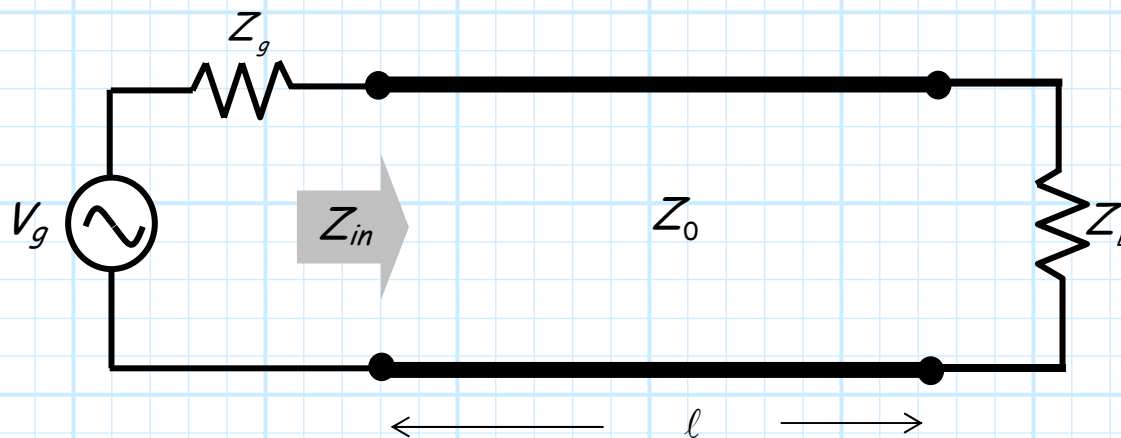1. the source impedance Z_g .
2. load impedance Z_L .
3. the transmission line characteristic impedance Z_0 .
4. the transmission line length ℓ .

Matching Networks and Transmission Lines

Recall that a primary purpose of a transmission line is to allow the transfer of **power** from a source to a load.



Q: So, say we directly connect an **arbitrary** source to an **arbitrary** load via a length of transmission line. Will the power delivered to the load be equal to the **available power** of the source?

A: Not likely! Remember we determined earlier that the efficacy of power transfer depends on:

1. the source impedance Z_g .
2. load impedance Z_L .
3. the transmission line characteristic impedance Z_0 .

4. the transmission line length ℓ .


Recall that **maximum** power transfer occurred only when these four parameters resulted in the **input impedance** of the transmission line being equal to the **complex conjugate** of the **source impedance** (i.e., $Z_{in}^* = Z_g$).

It is of course **unlikely** that the very **specific** conditions of a **conjugate match** will occur if we simply connect a length of transmission line between an **arbitrary** source and load, and thus the power delivered to the load will generally be **less** than the **available power** of the source.

Q: *Is there any way to use a **matching network** to fix this problem? Can the power delivered to the load be increased to **equal** the available power of the source if there is a transmission line connecting them?*


A: There sure is! We **can** likewise construct a matching network for the case where the source and load are connected by a **transmission line**.

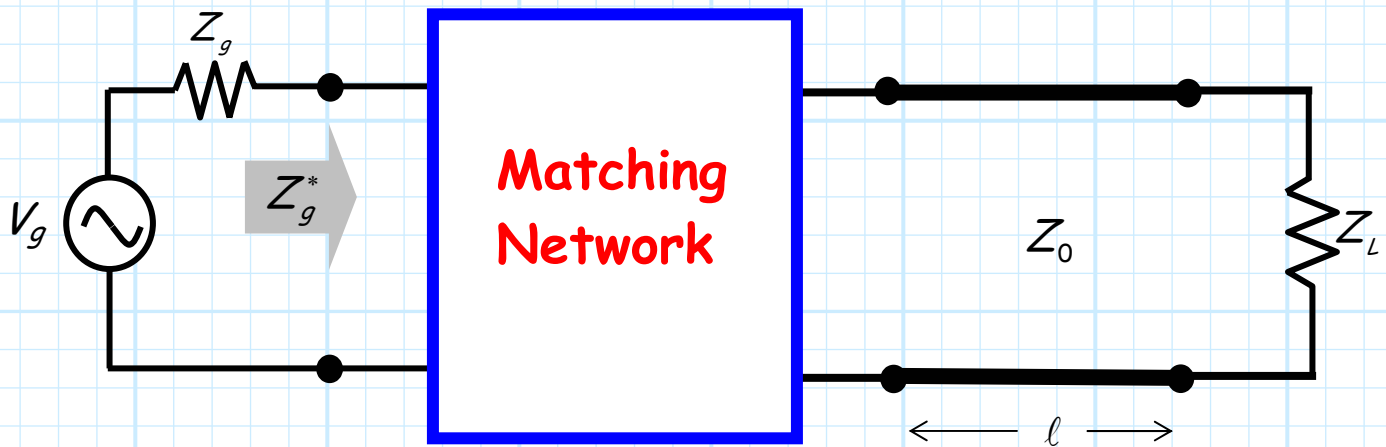For example, we can construct a network to transform the **input impedance** of the transmission line into the complex conjugate of the **source impedance**.




Q: *But, do we have to place the matching network between the source and the transmission line?*

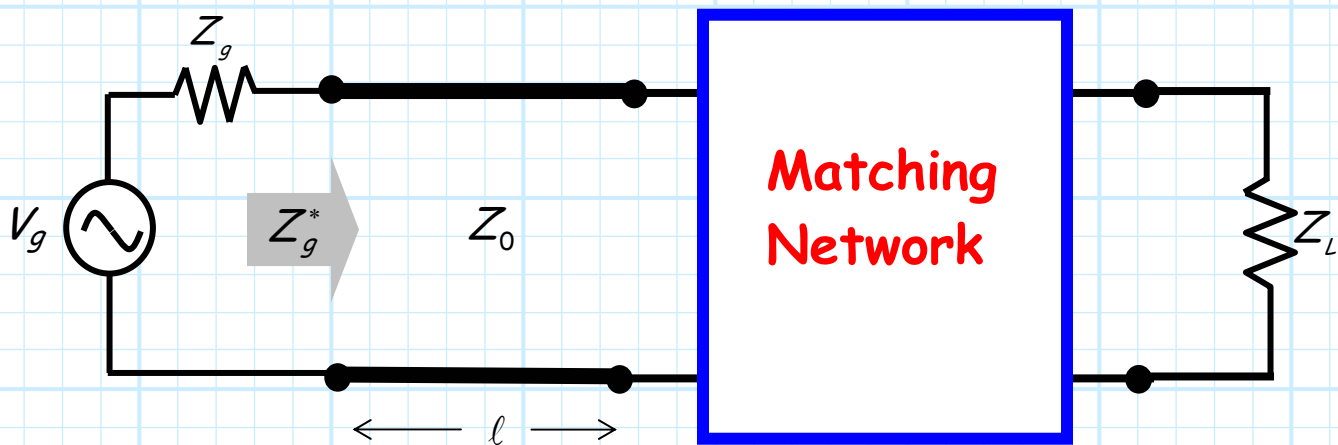A: Nope! We could also place a (different) matching network between the transmission line and the load.



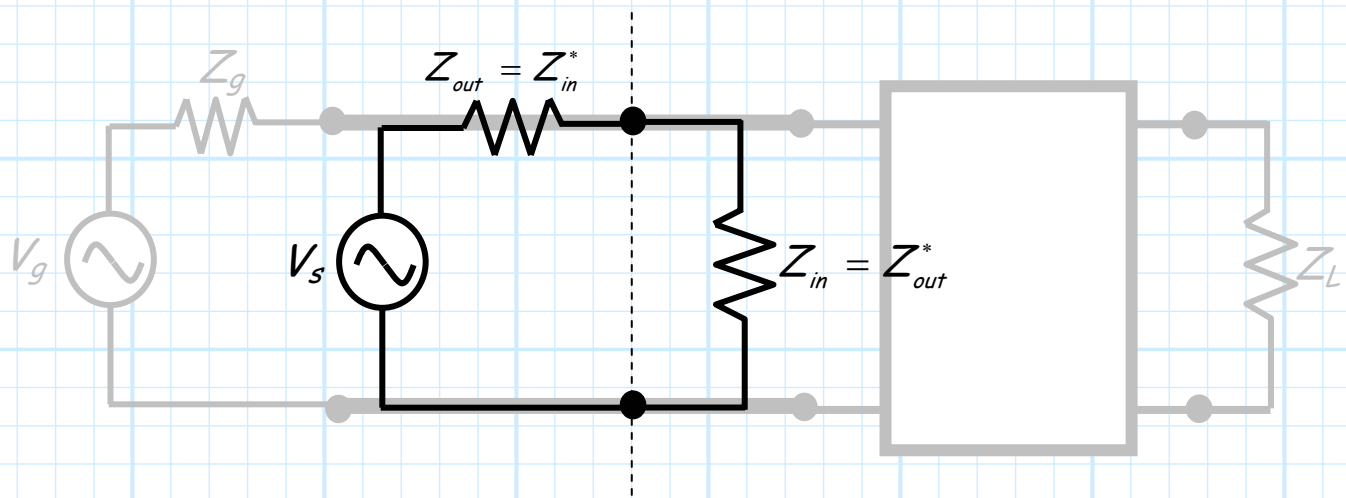
In either case, we find that at **any** and **all** points along this matched circuit, the output impedance of the equivalent **source** (i.e., looking left) will be equal to the **complex conjugate** of the **input impedance** (i.e., looking right).




Q: So which method should we choose? Do engineers typically place the matching network between the source and the transmission line, or place it between the transmission line and the load?

A: Actually, the typical solution is to do **both**!

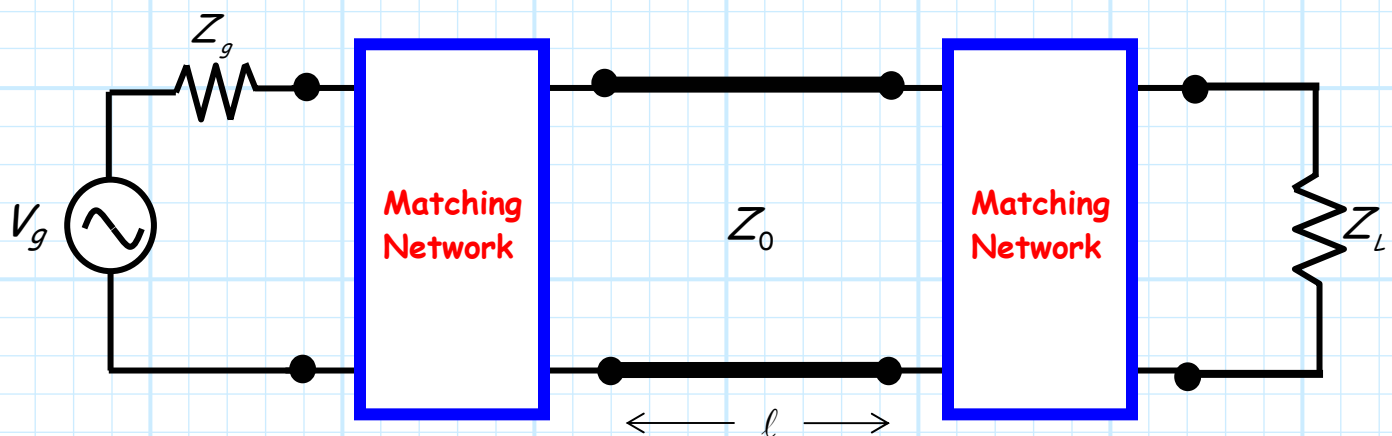
We find that often there is a matching network between the a source and the transmission line, **and** between the line and the load.



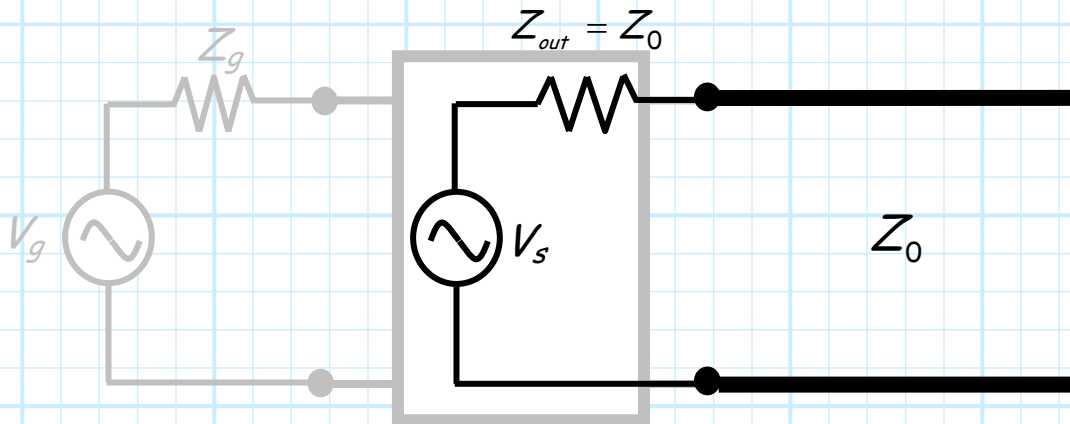The first network matches the **source** to the **transmission line**—in other words, it transforms the **output impedance** of the equivalent source to a value numerically equal to **characteristic impedance Z_0** :



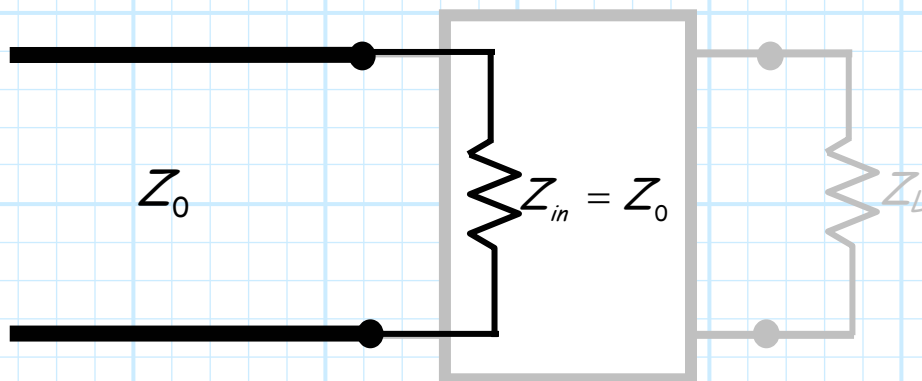The second network matches the **load** to the **transmission line**—in other words it transforms the **load impedance** to a value numerically equal to **characteristic impedance Z_0** :



Q: *Yikes! Why would we want to build **two** separate matching networks, instead of just **one**?*

A: By using two separate matching networks, we can **decouple** the design problem. Recall again that the design of a **single** matching network solution would depend on four separate parameters:

1. the source impedance Z_g .
2. load impedance Z_L .
3. the transmission line characteristic impedance Z_0 .
4. the transmission line length ℓ .

Alternatively, the design of the network matching the **source** and **transmission line** depends on **only**:

1. the source impedance Z_g .
2. the transmission line characteristic impedance Z_0 .

Whereas, the design of the network matching the **load** and **transmission line** depends on **only**:

1. the source impedance Z_L .
2. the transmission line characteristic impedance Z_0 .

Note that **neither** design depends on the transmission line **length** ℓ !


Q: *How is that possible?*

A: Remember the case where $Z_g = Z_0 = Z_L$. For that **special** case, we found that a conjugate match was the result—**regardless** of the transmission line length.

Thus, by matching the source to line impedance Z_0 **and** likewise matching the load to the line impedance, a conjugate match is **assured**—but the **length** of the transmission line does **not** matter!


In fact, the typically problem for microwave engineers is to match a load (e.g., device input impedance) to a **standard** transmission line impedance (typically $Z_0 = 50\Omega$); **or** to independently match a source (e.g., device output impedance) to a **standard** line impedance.

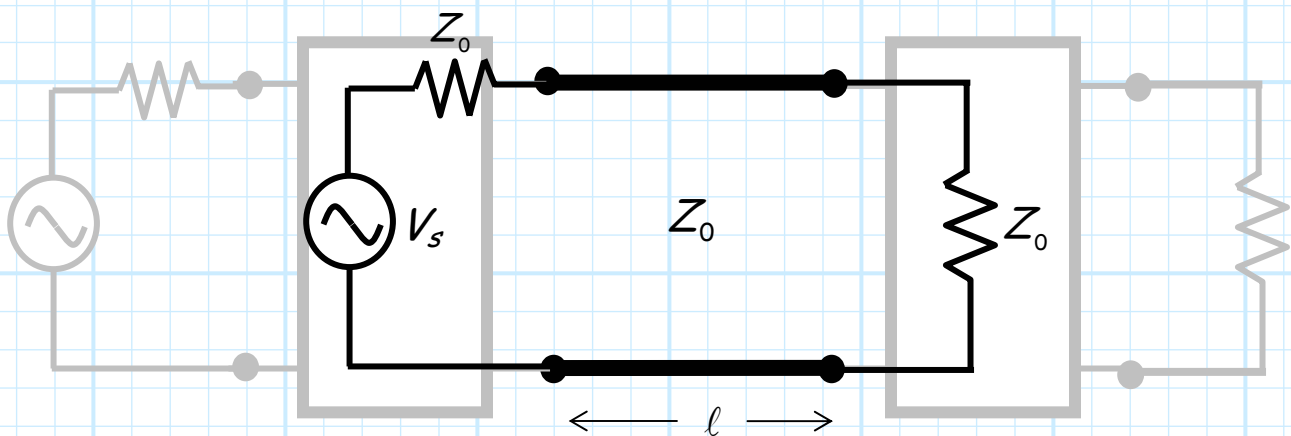A **conjugate match** is thus obtained by connecting the two with a transmission line of **any length**!



The Impedance Matrix

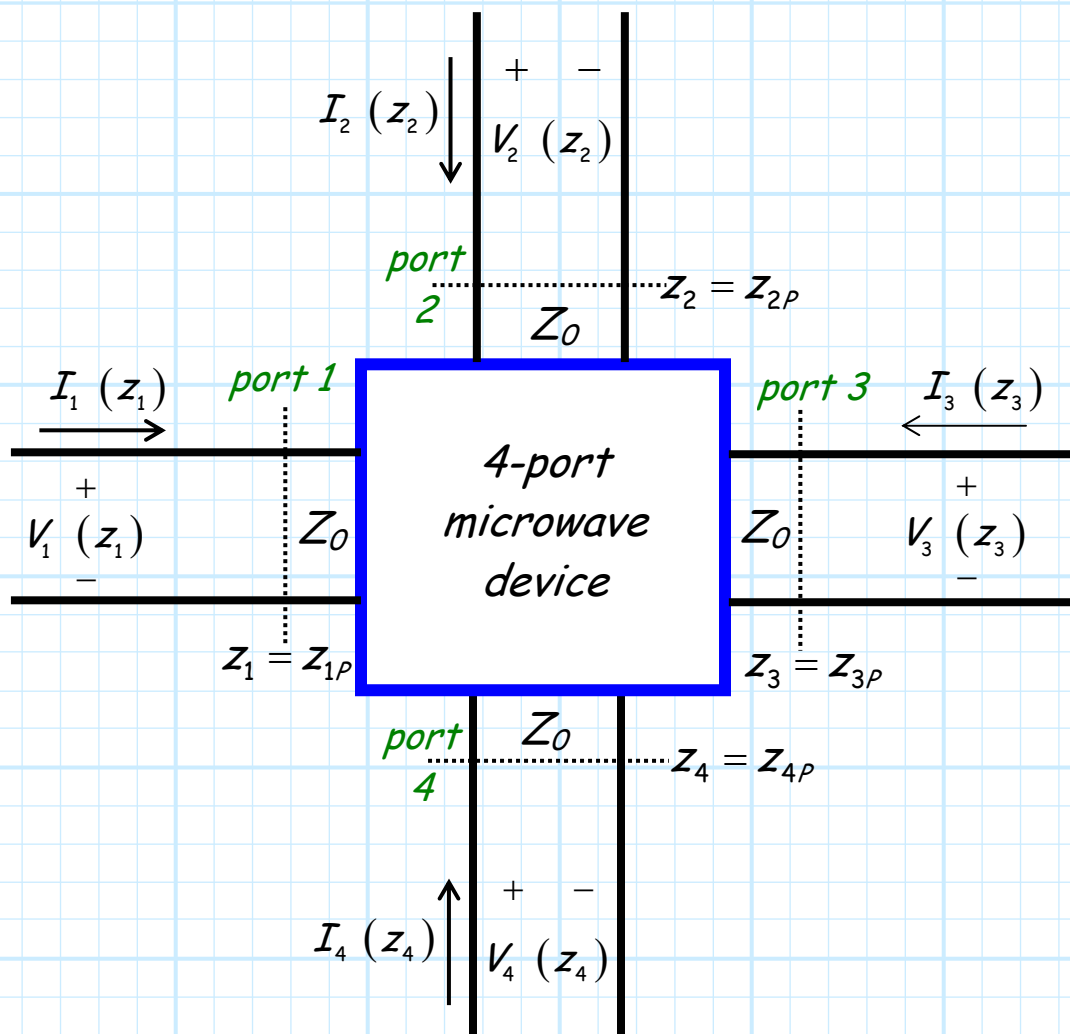Consider the **4-port** microwave device shown below:



Note in this example, there are four **identical** transmission lines connected to the same "box". Inside this box there may be a very **simple** linear device/circuit, or it might contain a very large and **complex** linear microwave system.

→ Either way, the "box" can be fully characterized by its **impedance matrix!**

First, note that each transmission line has a specific **location** that effectively defines the **input** to the device (i.e., z_{1P} , z_{2P} , z_{3P} , z_{4P}). These often arbitrary positions are known as the **port locations**, or **port planes** of the device.

Thus, the **voltage** and **current** at port n is:

$$V_n(z_n = z_{nP}) \quad I_n(z_n = z_{nP})$$

We can **simplify** this cumbersome notation by simply **defining** port n current and voltage as I_n and V_n :

$$V_n = V_n(z_n = z_{nP}) \quad I_n = I_n(z_n = z_{nP})$$

For **example**, the current at port **3** would be $I_3 = I_3(z_3 = z_{3P})$.

Now, say there exists a non-zero current at **port 1** (i.e., $I_1 \neq 0$), while the current at all **other** ports are known to be **zero** (i.e., $I_2 = I_3 = I_4 = 0$).

Say we measure/determine the **current** at port **1** (i.e., determine I_1), and we then measure/determine the **voltage** at the port **2** plane (i.e., determine V_2).

The complex ratio between V_2 and I_1 is known as the **trans-impedance parameter** Z_{21} :

$$Z_{21} = \frac{V_2}{I_1}$$

Likewise, the trans-impedance parameters Z_{31} and Z_{41} are:

$$Z_{31} = \frac{V_3}{I_1} \quad \text{and} \quad Z_{41} = \frac{V_4}{I_1}$$

We of course could **also** define, say, trans-impedance parameter Z_{34} as the ratio between the complex values I_4 (the current into port 4) and V_3 (the voltage at port 3), given that the current at all other ports (1, 2, and 3) are zero.


Thus, more **generally**, the ratio of the current into port n and the voltage at port m is:

$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that } I_k = 0 \text{ for all } k \neq n)$$

Q: But how do we ensure that all but **one** port current is zero?



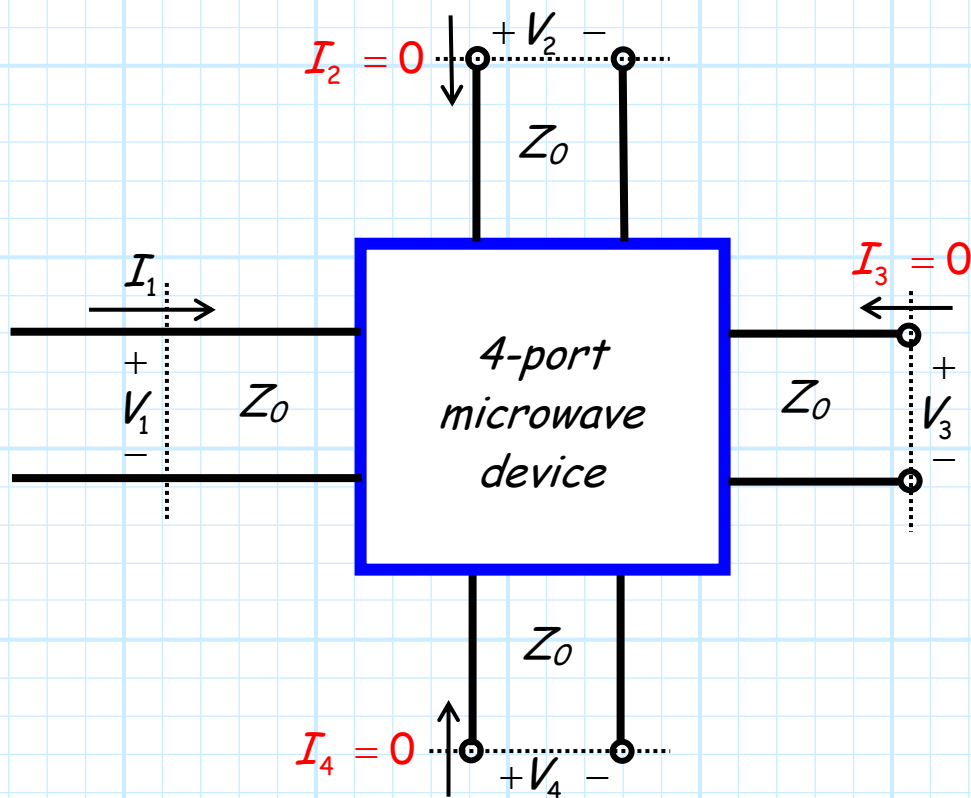
A: Place an **open circuit** at those ports!



Placing an **open** at a port (and it must be **at the port!**) enforces the condition that $I = 0$.

Now, we can thus **equivalently** state the definition of trans-impedance as:
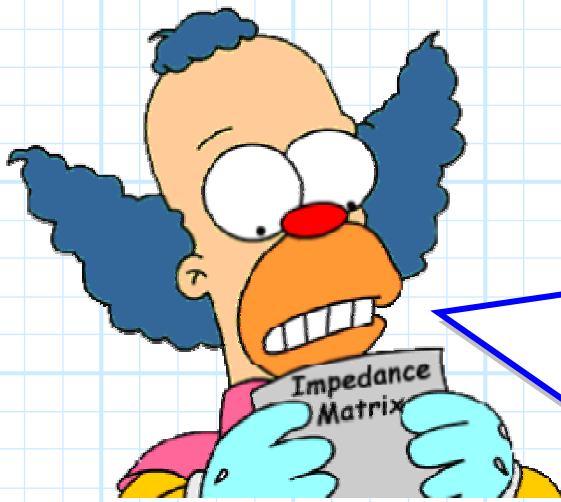
$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that all ports } k \neq n \text{ are open})$$



Q: *As impossible as it sounds, this handout is even more **boring** and **pointless** than any of your previous efforts. **Why** are we studying this? After all, what is the likelihood that a device will have an **open** circuit on **all** but one of its ports?!*

A: OK, say that **none** of our ports are **open-circuited**, such that we have currents **simultaneously** on **each** of the **four** ports of our device.

Since the device is **linear**, the voltage at any **one** port due to **all** the port currents is simply the coherent **sum** of the voltage at that port due to **each** of the currents!

For example, the voltage at port 3 can be determined by:

$$V_3 = Z_{34} I_4 + Z_{33} I_3 + Z_{32} I_2 + Z_{31} I_1$$

More generally, the voltage at port m of an N -port device is:

$$V_m = \sum_{n=1}^N Z_{mn} I_n$$

This expression can be written in **matrix** form as:

$$\bar{\mathbf{V}} = \bar{\mathbf{Z}} \bar{\mathbf{I}}$$

Where $\bar{\mathbf{I}}$ is the **vector**:

$$\bar{\mathbf{I}} = [I_1, I_2, I_3, \dots, I_N]^T$$

and $\bar{\mathbf{V}}$ is the **vector**:

$$\bar{\mathbf{V}} = [V_1, V_2, V_3, \dots, V_N]^T$$

And the matrix $\bar{\mathbf{Z}}$ is called the **impedance matrix**:

$$\bar{\mathbf{Z}} = \begin{bmatrix} Z_{11} & \dots & Z_{1n} \\ \vdots & \ddots & \vdots \\ Z_{m1} & \dots & Z_{mn} \end{bmatrix}$$

The impedance matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the impedance matrix describes a multi-port device the way that Z_L describes a single-port device (e.g., a load)!




But **beware!** The values of the impedance matrix for a particular device or network, just like Z_L , are **frequency dependent!** Thus, it may be more instructive to **explicitly** write:

$$\bar{\bar{\mathbf{Z}}}(\omega) = \begin{bmatrix} Z_{11}(\omega) & \cdots & Z_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ Z_{m1}(\omega) & \cdots & Z_{mn}(\omega) \end{bmatrix}$$

Example: Using the Impedance Matrix

Consider the following circuit:

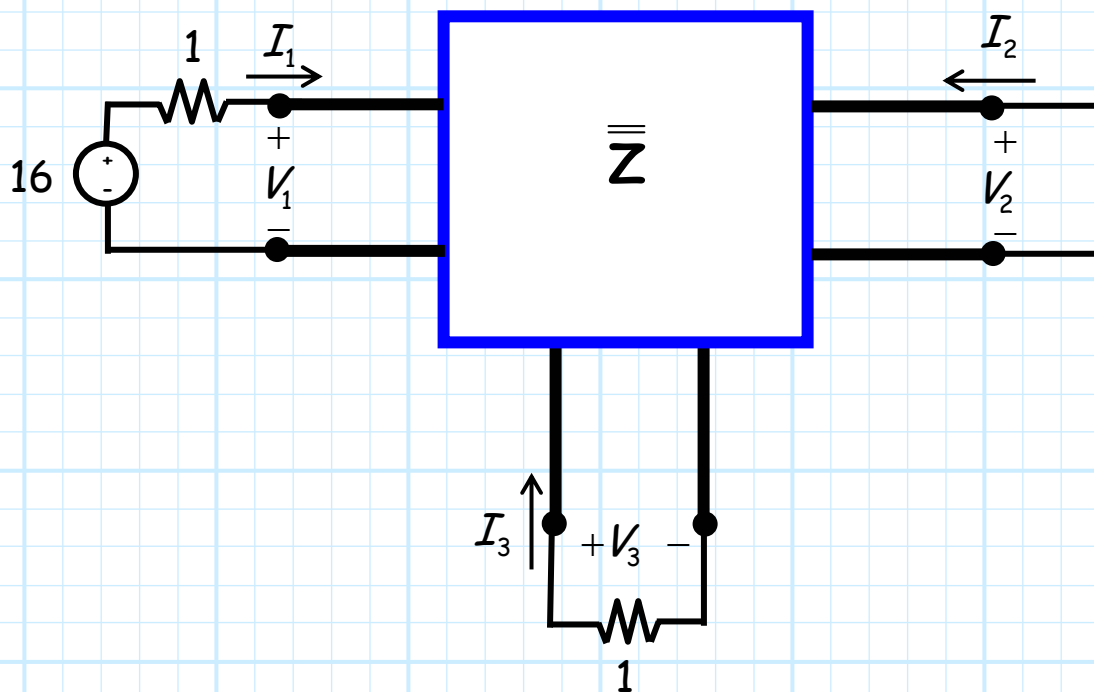

Where the 3-port **device** is characterized by the **impedance matrix**:

$$\bar{Z} = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix}$$

Let's now determine all port **voltages** V_1, V_2, V_3 and all **currents** I_1, I_2, I_3 .



Q: *How can we do that—we **don't** know what the device is made of! What's inside that box?*

A: We **don't** need to know what's inside that box! We know its impedance matrix, and that **completely** characterizes the device (or, at least, characterizes it at **one** frequency).

Thus, we have enough information to solve this problem. From the impedance matrix we know:

$$V_1 = 2 I_1 + I_2 + 2 I_3$$

$$V_2 = I_1 + I_2 + 4 I_3$$

$$V_3 = 2 I_1 + 4 I_2 + I_3$$

Q: *Wait! There are only **3** equations here, yet there are **6** unknowns!?*



A: True! The impedance matrix describes the device in the box, but it does **not** describe the devices **attached** to it. We require **more** equations to describe them.

1. The **source** at port 1 is described by the equation:

$$V_1 = 16.0 - (1)I_1$$

2. The **short** circuit on port 2 means that:

$$V_2 = 0$$

3. While the **load** on port 3 leads to:

$$V_3 = -(1)I_3 \quad (\text{note the minus sign!})$$

Now we have **6** equations and **6** unknowns! Combining equations, we find:

$$V_1 = 16 - I_1 = 2I_1 + I_2 + 2I_3$$

$$\therefore 16 = 3I_1 + I_2 + 2I_3$$

$$V_2 = 0 = I_1 + I_2 + 4I_3$$

$$\therefore 0 = I_1 + I_2 + 4I_3$$

$$V_3 = -I_3 = 2I_1 + 4I_2 + I_3$$

$$\therefore 0 = 2I_1 + 4I_2 + 2I_3$$

Solving, we find (I'll let you do the algebraic details!):

$$I_1 = 7.0$$

$$I_2 = -3.0$$

$$I_3 = -1.0$$

$$V_1 = 9.0$$

$$V_2 = 0.0$$

$$V_3 = 1.0$$

The Scattering Matrix

At “**low**” frequencies, we can completely characterize a **linear** device or network using an **impedance** matrix, which relates the currents and voltages at **each** device terminal to the currents and voltages at **all** other terminals.


But, at microwave frequencies, it is **difficult** to measure **total** currents and voltages!



- * Instead, we can measure the **magnitude** and **phase** of each of the two transmission line **waves** $V^+(z)$ and $V^-(z)$.
- * In other words, we can determine the relationship between the incident and reflected wave at **each** device terminal to the incident and reflected waves at **all** other terminals.

These relationships are completely represented by the **scattering matrix**. It **completely** describes the behavior of a linear, multi-port device at a **given frequency** ω .

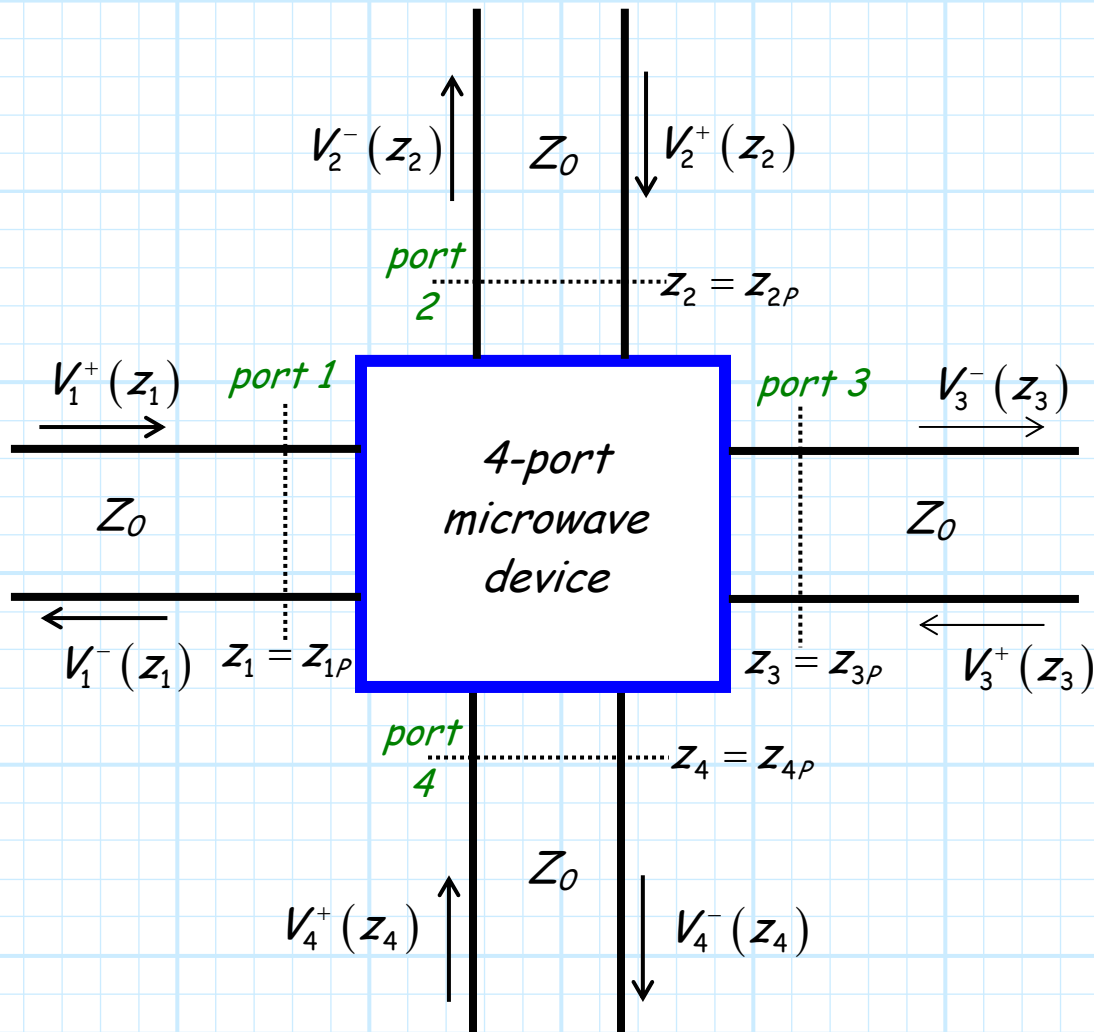Consider the **4-port** microwave device shown below:



Note in this example, there are four **identical** transmission lines connected to the same "box". Inside this box there may be a very **simple** linear device/circuit, or it might contain a very large and **complex** linear microwave system.

→ Either way, the "box" can be fully characterized by its **scattering parameters!**

First, note that each transmission line has a specific **location** that effectively defines the **input** to the device (i.e., z_{1p} , z_{2p} , z_{3p} , z_{4p}). These often arbitrary positions are known as the **port locations**, or port **planes** of the device.

Say there exists an **incident wave on port 1** (i.e., $V_1^+(z_1) \neq 0$), while the incident waves on all other ports are known to be **zero** (i.e., $V_2^+(z_2) = V_3^+(z_3) = V_4^+(z_4) = 0$).

Say we measure/determine the voltage of the wave flowing **into port 1**, at the port 1 **plane** (i.e., determine $V_1^+(z_1 = z_{1p})$).

Say we then measure/determine the voltage of the wave flowing **out of port 2**, at the port 2 plane (i.e., determine $V_2^-(z_2 = z_{2p})$).

The complex ratio between $V_1^+(z_1 = z_{1p})$ and $V_2^-(z_2 = z_{2p})$ is known as the **scattering parameter** S_{21} :

$$S_{21} = \frac{V_2^-(z = z_2)}{V_1^+(z = z_1)} = \frac{V_{02}^- e^{+j\beta z_{2p}}}{V_{01}^+ e^{-j\beta z_{1p}}} = \frac{V_{02}^-}{V_{01}^+} e^{+j\beta(z_{2p} + z_{1p})}$$

Likewise, the scattering parameters S_{31} and S_{41} are:

$$S_{31} = \frac{V_3^-(z_3 = z_{3p})}{V_1^+(z_1 = z_{1p})} \quad \text{and} \quad S_{41} = \frac{V_4^-(z_4 = z_{4p})}{V_1^+(z_1 = z_{1p})}$$

We of course could **also** define, say, scattering parameter S_{34} as the ratio between the complex values $V_4^+(z_4 = z_{4p})$ (the wave **into** port 4) and $V_3^-(z_3 = z_{3p})$ (the wave **out of** port 3), given that the input to all other ports (1,2, and 3) are zero.


Thus, more **generally**, the ratio of the wave incident on port n to the wave emerging from port m is:

$$S_{mn} = \frac{V_m^-(z_m = z_{mp})}{V_n^+(z_n = z_{np})} \quad (\text{given that } V_k^+(z_k) = 0 \text{ for all } k \neq n)$$

Note that frequently the port positions are assigned a **zero** value (e.g., $z_{1p} = 0$, $z_{2p} = 0$). This of course **simplifies** the scattering parameter calculation:

$$S_{mn} = \frac{V_m^-(z_m = 0)}{V_n^+(z_n = 0)} = \frac{V_{0m}^- e^{+j\beta_0}}{V_{0n}^+ e^{-j\beta_0}} = \frac{V_{0m}^-}{V_{0n}^+}$$

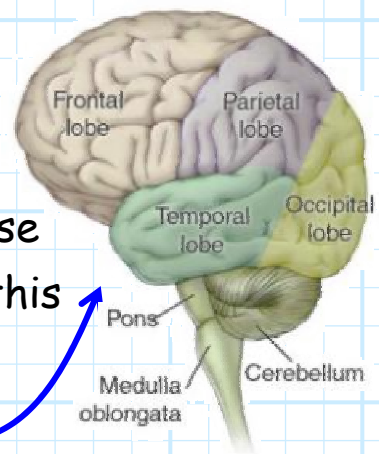
We will **generally assume** that the port locations are defined as $z_{np} = 0$, and thus use the **above** notation. But **remember** where this expression came from!



Q: *But how do we ensure that only one incident wave is non-zero?*




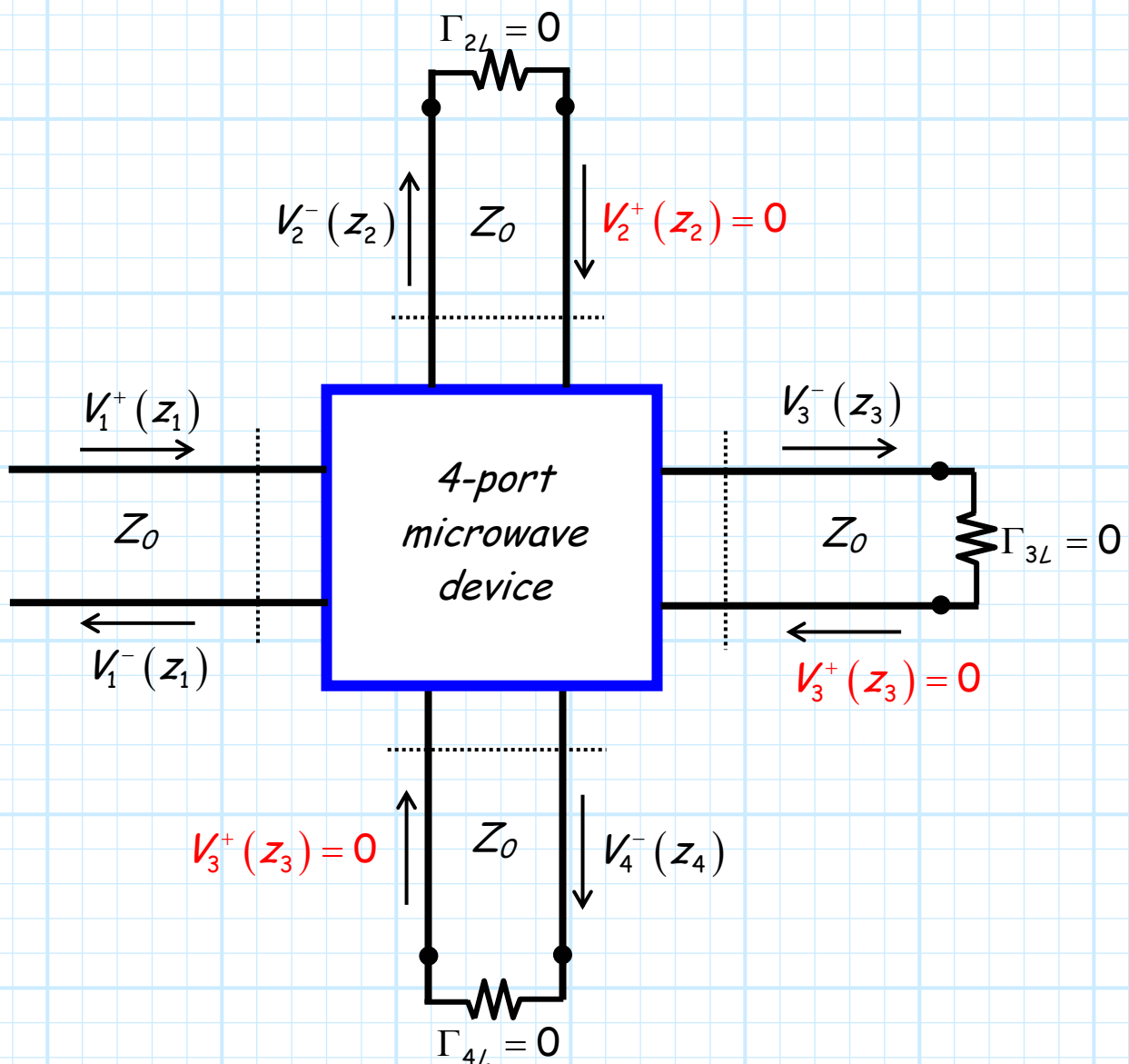A: **Terminate all other ports with a matched load!**



Note that if the ports are terminated in a **matched load** (i.e., $Z_L = Z_0$), then $\Gamma_{nL} = 0$ and therefore:

$$V_n^+(z_n) = 0$$

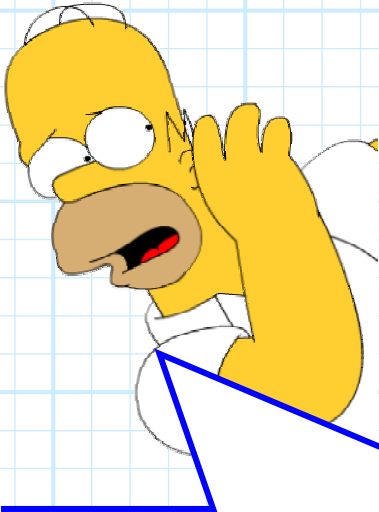

In other words, terminating a port ensures that there will be **no signal** incident on that port!

Q: *Just between you and me, I think you've messed this up! In all previous handouts you said that if $\Gamma_L = 0$, the wave in the **minus** direction would be zero:*

$$V^-(z) = 0 \quad \text{if} \quad \Gamma_L = 0$$


*but just **now** you said that the wave in the **positive** direction would be zero:*

$$V^+(z) = 0 \quad \text{if} \quad \Gamma_L = 0$$

*Of course, there is **no way** that **both** statements can be correct!*


A: Actually, **both** statements are correct! You must be careful to understand the **physical definitions** of the plus and minus directions—in other words, the propagation directions of waves $V_n^+(z_n)$ and $V_n^-(z_n)$!

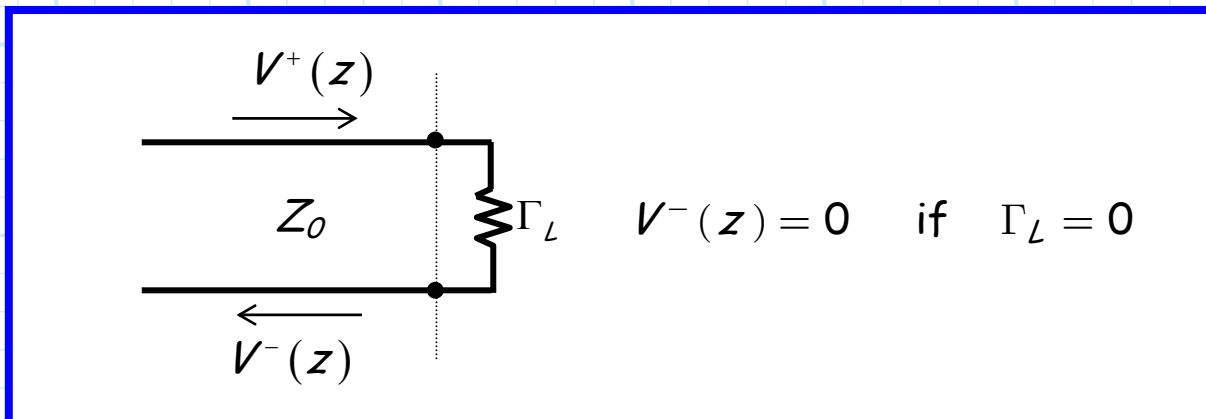For example, we **originally** analyzed this case:



In this original case, the wave **incident** on the load is $V^+(z)$ (**plus** direction), while the **reflected** wave is $V^-(z)$ (**minus** direction).

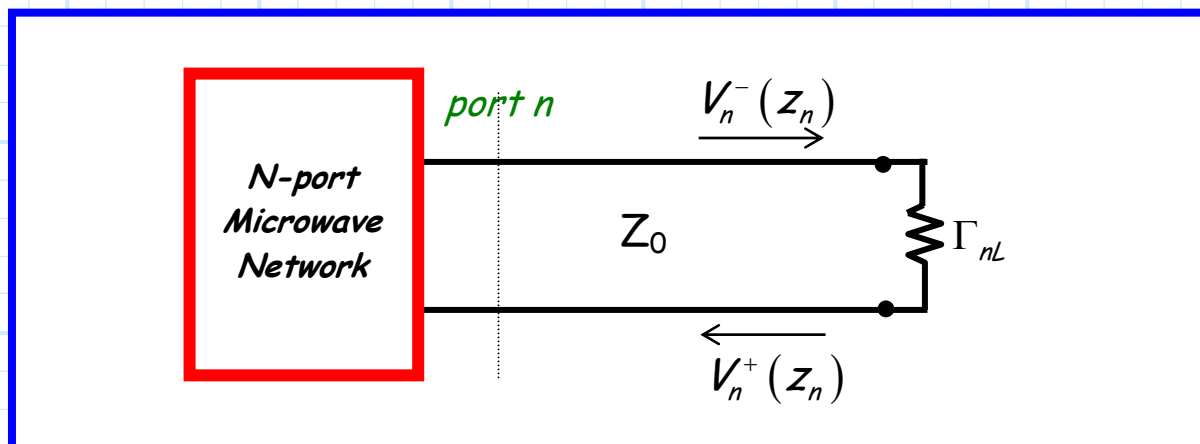Contrast this with the case we are **now** considering:




For this current case, the situation is **reversed**. The wave incident on the load is **now** denoted as $V_n^-(z_n)$ (coming **out** of port n), while the wave reflected off the load is **now** denoted as $V_n^+(z_n)$ (going **into** port n).

As a result, $V_n^+(z_n) = 0$ when $\Gamma_{nL} = 0$!

Perhaps we could more **generally** state that:
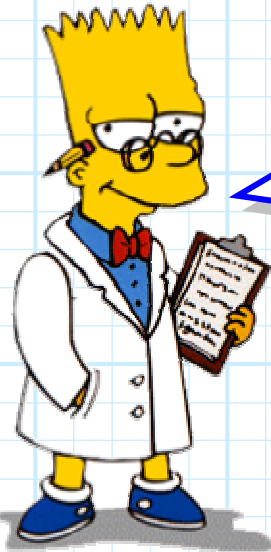
$$V^{\text{reflected}} (z = z_L) = \Gamma_L V^{\text{incident}} (z = z_L)$$



*For each case, you must be able to correctly identify the mathematical statement describing the wave **incident** on, and **reflected** from, some passive load.*


*Like most equations in engineering, the **variable names can change**, but the **physics described by the mathematics will not!***

Now, **back** to our discussion of **S-parameters**. We found that if $z_{nP} = 0$ for all ports n , the scattering parameters could be directly written in terms of wave **amplitudes** V_{0n}^+ and V_{0m}^- .

$$S_{mn} = \frac{V_{0m}^-}{V_{0n}^+} \quad (\text{given that } V_k^+(z_k) = 0 \text{ for all } k \neq n)$$

Which we can now **equivalently** state as:
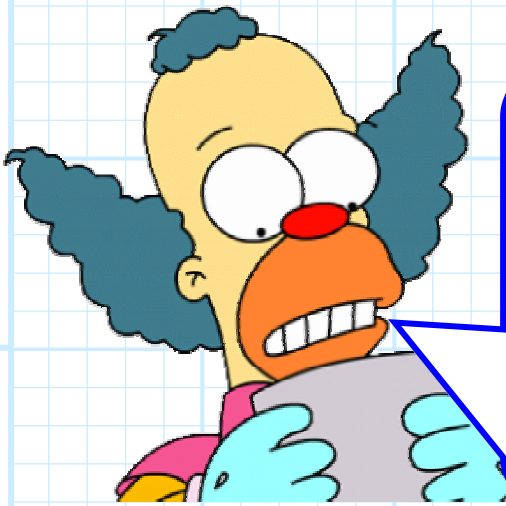
$$S_{mn} = \frac{V_{0m}^-}{V_{0n}^+} \quad (\text{given that all ports, except port } n, \text{ are matched})$$



*Q: As impossible as it sounds, this handout is even more **boring** and **pointless** than any of your previous efforts. Why are we studying this? After all, what is the likelihood that a microwave network will have only **one** incident wave—that **all** of the ports will be matched?!*

A: OK, say that our ports are **not** matched, such that we have waves **simultaneously** incident on **each** of the **four** ports of our device.

Since the device is **linear**, the output at any port due to **all** the incident waves is simply the coherent **sum** of the output at that port due to **each** input wave!

For example, the output wave at port 3 can be determined by (assuming $z_{nP} = 0$):

$$V_{03}^- = S_{34} V_{04}^+ + S_{33} V_{03}^+ + S_{32} V_{02}^+ + S_{31} V_{01}^+$$

More generally, the output wave voltage at port m of an N -port device is:

$$V_{0m}^- = \sum_{n=1}^N S_{mn} V_{0n}^+ \quad (z_{nP} = 0)$$

This expression can be written in **matrix** form as:

$$\bar{\mathbf{V}}^- = \bar{\bar{\mathbf{S}}} \bar{\mathbf{V}}^+$$

Where $\bar{\mathbf{V}}^-$ is the **vector**:

$$\bar{\mathbf{V}}^- = [V_{01}^-, V_{02}^-, V_{03}^-, \dots, V_{0N}^-]^T$$

and $\bar{\mathbf{V}}^+$ is the **vector**:

$$\bar{\mathbf{V}}^+ = [V_{01}^+, V_{02}^+, V_{03}^+, \dots, V_{0N}^+]^T$$

Therefore $\bar{\bar{\mathbf{S}}}$ is the **scattering matrix**:

$$\bar{\bar{\mathbf{S}}} = \begin{bmatrix} S_{11} & \dots & S_{1n} \\ \vdots & \ddots & \vdots \\ S_{m1} & \dots & S_{mn} \end{bmatrix}$$

The scattering matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the scattering matrix describes a multi-port device the way that Γ_L describes a single-port device (e.g., a load)!



But **beware!** The values of the scattering matrix for a particular device or network, just like Γ_L , are **frequency dependent!** Thus, it may be more instructive to **explicitly** write:


$$\bar{\bar{\mathbf{S}}}(\omega) = \begin{bmatrix} S_{11}(\omega) & \dots & S_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ S_{m1}(\omega) & \dots & S_{mn}(\omega) \end{bmatrix}$$

Example: The Scattering Matrix

Say we have a 3-port network that is completely characterized at some frequency ω by the **scattering matrix**:

$$\bar{S} = \begin{bmatrix} 0.0 & 0.2 & 0.5 \\ 0.5 & 0.0 & 0.2 \\ 0.5 & 0.5 & 0.0 \end{bmatrix}$$

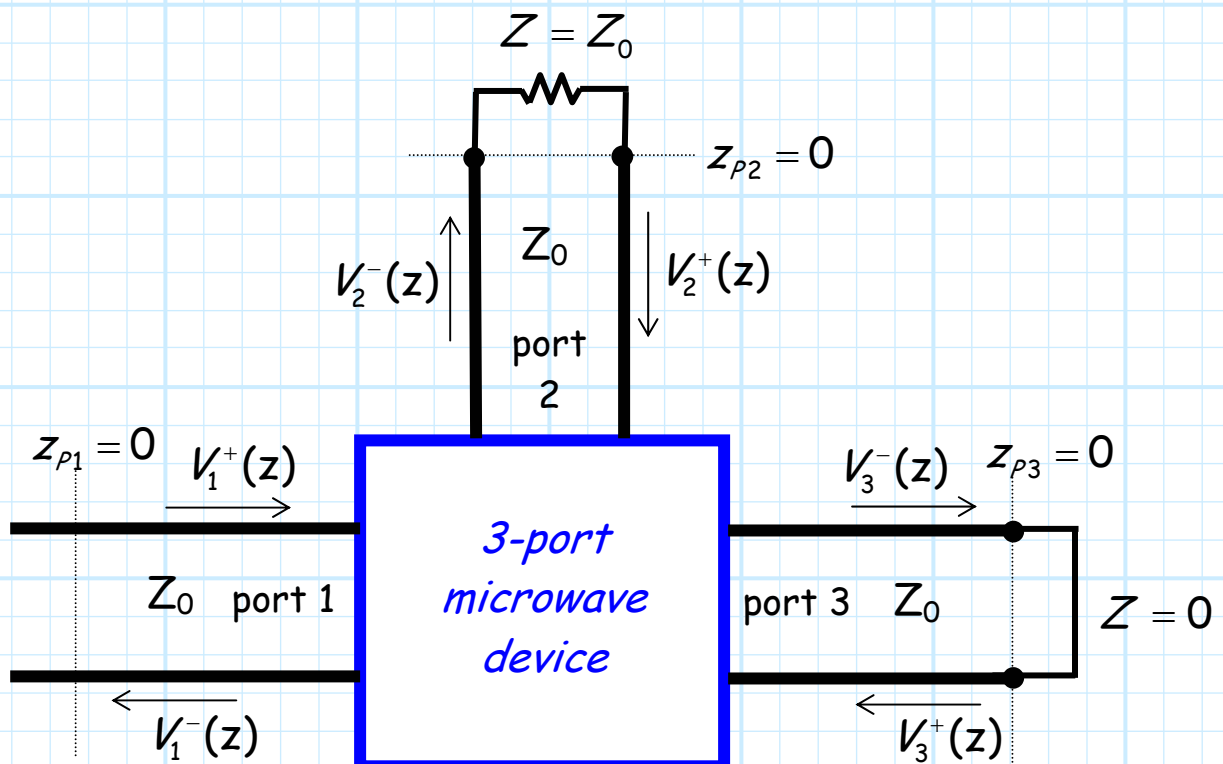A **matched load** is attached to port 2, while a **short circuit** has been placed at port 3:



Because of the **matched** load at port 2 (i.e., $\Gamma_L = 0$), we know that:

$$\frac{V_2^+(z_2 = 0)}{V_2^-(z_2 = 0)} = \frac{V_{02}^+}{V_{02}^-} = 0$$

and therefore:

$$V_{02}^+ = 0$$



You've made a terrible mistake! Fortunately, I was here to correct it for you—since $\Gamma_L = 0$, the constant V_{02}^- (not V_{02}^+) is equal to zero.

NO!! Remember, the signal $V_2^-(z)$ is **incident** on the matched load, and $V_2^+(z)$ is the **reflected** wave from the load (i.e., $V_2^+(z)$ is incident on port 2). Therefore, $V_{02}^+ = 0$ is **correct!**

Likewise, because of the **short** circuit at port 3 ($\Gamma_L = -1$):

$$\frac{V_3^+(z_3 = 0)}{V_3^-(z_3 = 0)} = \frac{V_{03}^+}{V_{03}^-} = -1$$

and therefore:

$$V_{03}^+ = -V_{03}^-$$

Problem:

a) Find the **reflection** coefficient at port 1, i.e.:

$$\Gamma_1 \doteq \frac{V_{01}^-}{V_{01}^+}$$

b) Find the **transmission** coefficient from port 1 to port 2, i.e.,

$$T_{21} \doteq \frac{V_{02}^-}{V_{01}^+}$$

*I am amused by the trivial problems that **you** apparently find so difficult. I know that:*

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = S_{11} = 0.0$$

and

$$T_{21} = \frac{V_{02}^-}{V_{01}^+} = S_{21} = 0.5$$



NO!!! The above statement is **not correct!**



Remember, $V_{01}^-/V_{01}^+ = S_{11}$ **only** if ports 2 and 3 are terminated in **matched** loads! In this problem port 3 is terminated with a **short circuit**.

Therefore:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} \neq S_{11}$$

and similarly:

$$T_{21} = \frac{V_{02}^-}{V_{01}^+} \neq S_{21}$$

To determine the values T_{21} and Γ_1 , we must start with the **three** equations provided by the **scattering matrix**:

$$V_{01}^- = 0.2 V_{02}^+ + 0.5 V_{03}^+$$

$$V_{02}^- = 0.5 V_{01}^+ + 0.2 V_{03}^+$$

$$V_{03}^- = 0.5 V_{01}^+ + 0.5 V_{02}^+$$

and the **two** equations provided by the **attached loads**:

$$V_{02}^+ = 0$$

$$V_{03}^+ = -V_{03}^-$$

We can divide all of these equations by V_{01}^+ , resulting in:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = 0.2 \frac{V_{02}^+}{V_{01}^+} + 0.5 \frac{V_{03}^+}{V_{01}^+}$$

$$\mathcal{T}_{21} = \frac{V_{02}^-}{V_{01}^+} = 0.5 + 0.2 \frac{V_{03}^+}{V_{01}^+}$$

$$\frac{V_{03}^-}{V_{01}^+} = 0.5 + 0.5 \frac{V_{02}^+}{V_{01}^+}$$

$$\frac{V_{02}^+}{V_{01}^+} = 0$$

$$\frac{V_{03}^+}{V_{01}^+} = -\frac{V_{03}^-}{V_{01}^+}$$

Look what we have—**5** equations and **5** unknowns! Inserting equations 4 and 5 into equations 1 through 3, we get:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = -0.5 \frac{V_{03}^+}{V_{01}^+}$$

$$\mathcal{T}_{21} = \frac{V_{02}^-}{V_{01}^+} = 0.5 - 0.2 \frac{V_{03}^+}{V_{01}^+}$$

$$\frac{V_{03}^-}{V_{01}^+} = 0.5$$

Solving, we find:

$$\Gamma_1 = -0.5(0.5) = -0.25$$

$$T_{21} = 0.5 - 0.2(0.5) = 0.4$$

Example: Scattering Parameters

Consider a **two-port device** with a scattering matrix (at some specific frequency ω_0):

$$\bar{\mathbf{S}}(\omega = \omega_0) = \begin{bmatrix} 0.1 & j0.7 \\ j0.7 & -0.2 \end{bmatrix}$$

and $Z_0 = 50\Omega$.

Say that the transmission line connected to **port 2** of this device is terminated in a **matched load**, and that the wave **incident on port 1** is:

$$V_1^+(z_1) = -j2 e^{-j\beta z_1}$$

where $z_{1p} = z_{2p} = 0$.

Determine:

1. the port voltages $V_1(z_1 = z_{1p})$ and $V_2(z_2 = z_{2p})$.
2. the port currents $I_1(z_1 = z_{1p})$ and $I_2(z_2 = z_{2p})$.
3. the net power flowing into port 1

1. Since the **incident** wave on port 1 is:

$$V_1^+(z_1) = -j2 e^{-j\beta z_1}$$

we can conclude (since $z_{1\rho} = 0$):

$$\begin{aligned} V_1^+(z_1 = z_{1\rho}) &= -j2 e^{-j\beta z_{1\rho}} \\ &= -j2 e^{-j\beta(0)} \\ &= -j2 \end{aligned}$$

and since port 2 is **matched** (and **only** because its matched!), we find:

$$\begin{aligned} V_1^-(z_1 = z_{1\rho}) &= S_{11} V_1^+(z_1 = z_{1\rho}) \\ &= 0.1(-j2) \\ &= -j0.2 \end{aligned}$$

The voltage at port 1 is thus:

$$\begin{aligned} V_1(z_1 = z_{1\rho}) &= V_1^+(z_1 = z_{1\rho}) + V_1^-(z_1 = z_{1\rho}) \\ &= -j2.0 - j0.2 \\ &= -j2.2 \\ &= 2.2 e^{-j\pi/2} \end{aligned}$$

Likewise, since port 2 is **matched**:

$$V_2^+(z_2 = z_{2\rho}) = 0$$

And also:

$$\begin{aligned} V_2^-(z_2 = z_{2P}) &= S_{21} V_1^+(z_1 = z_{1P}) \\ &= j0.7(-j2) \\ &= 1.4 \end{aligned}$$

Therefore:

$$\begin{aligned} V_2(z_2 = z_{2P}) &= V_2^+(z_2 = z_{2P}) + V_2^-(z_2 = z_{2P}) \\ &= 0 + 1.4 \\ &= 1.4 \\ &= 1.4 e^{-j0} \end{aligned}$$

2. The port **currents** can be easily determined from the results of the previous section.

$$\begin{aligned} I_1(z_1 = z_{1P}) &= I_1^+(z_1 = z_{1P}) - I_1^-(z_1 = z_{1P}) \\ &= \frac{V_1^+(z_1 = z_{1P})}{Z_0} - \frac{V_1^-(z_1 = z_{1P})}{Z_0} \\ &= -j \frac{2.0}{50} + j \frac{0.2}{50} \\ &= -j \frac{1.8}{50} \\ &= -j0.036 \\ &= 0.036 e^{-j\pi/2} \end{aligned}$$

and:

$$\begin{aligned} I_2(z_2 = z_{2P}) &= I_2^+(z_2 = z_{2P}) - I_2^-(z_2 = z_{2P}) \\ &= \frac{V_2^+(z_2 = z_{2P})}{Z_0} - \frac{V_2^-(z_2 = z_{2P})}{Z_0} \\ &= \frac{0}{50} - \frac{1.4}{50} \\ &= -0.028 \\ &= 0.028 e^{+j\pi} \end{aligned}$$

3. The net power flowing into port 1 is:

$$\begin{aligned} \Delta P_1 &= P_1^+ - P_1^- \\ &= \frac{|V_{01}^+|^2}{2Z_0} - \frac{|V_{01}^-|^2}{2Z_0} \\ &= \frac{(2)^2 - (0.2)^2}{2(50)} \\ &= 0.0396 \text{ Watts} \end{aligned}$$

Matched, Lossless, Reciprocal Devices

Often, we describe a device or network as **matched**, **lossless**, or **reciprocal**.

Q: *What do these three terms mean??*

A: Let's explain each of them **one at a time!**

Matched

A matched device is another way of saying that the **input impedance** at each port is numerically **equal to Z_0** when all other ports are terminated in **matched loads**. As a result, the input **reflection coefficient** of each port is **zero**—no signal will come out of a port when a signal is incident on **that port** (and **only that port**!).

In other words, we want:

$$V_{0m}^- = S_{mm} V_{0m}^+ = 0 \quad \text{for all } m$$

a result that occurs when:

$$S_{mm} = 0 \quad \text{for all } m \text{ if matched.}$$

We find therefore that a matched device will exhibit a scattering matrix where all **diagonal elements are zero**.

Therefore:

$$\bar{\mathbf{S}} = \begin{bmatrix} 0 & 0.1 & j0.2 \\ 0.1 & 0 & 0.3 \\ j0.2 & 0.3 & 0 \end{bmatrix}$$

is an example of a scattering matrix for a **matched**, three port device.

Lossless

For a lossless device, all of the power that delivered to each device port must eventually find its way **out!**

In other words, power is not **absorbed** by the network—no power to be **converted to heat!**

Recall the **power incident** on some port m is related to the amplitude of the **incident wave** (V_{0m}^+) as:

$$P_m^+ = \frac{|V_{0m}^+|^2}{2Z_0}$$

While power of the **wave exiting** the port is:

$$P_m^- = \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the power **delivered** to that port is the **difference** of the two:

$$\Delta P_m = P_m^+ - P_m^- = \frac{|V_{0m}^+|^2}{2Z_0} - \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the **total power incident** on an N -port device is:

$$P^+ = \sum_{m=1}^N P_m^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2$$

Note that:

$$\sum_{m=1}^N |V_{0m}^+|^2 = \overline{\mathbf{V}^+}^H \mathbf{V}^+$$

where operator H indicates the **conjugate transpose** (i.e., Hermetian transpose) operation, so that $\overline{\mathbf{V}^+}^H \mathbf{V}^+$ is the **inner product** (i.e., dot product, or scalar product) of complex vector \mathbf{V}^+ with itself.

Thus, we can write the **total power incident** on the device as:

$$P^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2 = \frac{\overline{\mathbf{V}^+}^H \mathbf{V}^+}{2Z_0}$$

Similarly, we can express the **total power** of the waves **exiting** our M -port network to be:

$$P^- = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^-|^2 = \frac{\overline{\mathbf{V}^-}^H \mathbf{V}^-}{2Z_0}$$

Now, recalling that the incident and exiting wave amplitudes are **related** by the **scattering matrix** of the device:

$$\bar{\mathbf{V}}^- = \bar{\mathbf{S}} \bar{\mathbf{V}}^+$$

Thus we find:

$$P^- = \frac{\overline{\mathbf{V}^-^H \mathbf{V}^-}}{2Z_0} = \frac{\overline{\mathbf{V}^+^H \bar{\mathbf{S}} \bar{\mathbf{S}} \mathbf{V}^+}}{2Z_0}$$

Now, the **total power delivered** to the network is:

$$\Delta P = \sum_{m=1}^M \Delta P = P^+ - P^-$$

Or explicitly:

$$\begin{aligned} \Delta P &= P^+ - P^- \\ &= \frac{\overline{\mathbf{V}^+^H \mathbf{V}^+}}{2Z_0} - \frac{\overline{\mathbf{V}^+^H \bar{\mathbf{S}} \bar{\mathbf{S}} \mathbf{V}^+}}{2Z_0} \\ &= \frac{1}{2Z_0} \overline{\mathbf{V}^+^H \left(\bar{\mathbf{I}} - \bar{\mathbf{S}} \bar{\mathbf{S}} \right) \mathbf{V}^+} \end{aligned}$$

where $\bar{\mathbf{I}}$ is the **identity matrix**.

Q: *Is there actually some **point** to this long, rambling, complex presentation?*

A: Absolutely! If our M-port device is lossless then the total power exiting the device must **always** be equal to the total power incident on it.

If network is **lossless**, then $P^+ = P^-$.

Or stated another way, the total **power delivered** to the device (i.e., the power absorbed by the device) must always be **zero** if the device is lossless!

If network is **lossless**, then $\Delta P = 0$

Thus, we can conclude from our math that for a **lossless device**:

$$\Delta P = \frac{1}{2Z_0} \overline{\mathbf{V}^+}^H \left(\overline{\mathbf{I}} - \overline{\mathbf{S}}^H \overline{\mathbf{S}} \right) \overline{\mathbf{V}^+} = 0 \quad \text{for all } \overline{\mathbf{V}^+}$$

This is true **only** if:

$$\overline{\mathbf{I}} - \overline{\mathbf{S}}^H \overline{\mathbf{S}} = 0 \quad \Rightarrow \quad \overline{\mathbf{S}}^H \overline{\mathbf{S}} = \overline{\mathbf{I}}$$

Thus, we can conclude that the **scattering matrix** of a **lossless** device has the **characteristic**:

If a network is **lossless**, then $\overline{\mathbf{S}}^H \overline{\mathbf{S}} = \overline{\mathbf{I}}$

Q: *Huh? What exactly is this supposed to tell us?*

A: A matrix that satisfies $\overline{\mathbf{S}}^H \overline{\mathbf{S}} = \overline{\mathbf{I}}$ is a special kind of matrix known as a **unitary matrix**.

If a network is **lossless**, then its scattering matrix $\bar{\mathbf{S}}$ is **unitary**.

Q: *How do I recognize a unitary matrix if I see one?*

A: The **columns** of a unitary matrix form an **orthonormal set!**

$$\bar{\mathbf{S}} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

matrix columns

In other words, each **column** of the scattering matrix will have a **magnitude equal to one**:

$$\sum_{m=1}^N |S_{mn}|^2 = 1 \quad \text{for all } n$$

while the inner product (i.e., dot product) of **dissimilar columns** must be **zero**.

$$\sum_{n=1}^N S_{ni} S_{nj}^* = S_{1i} S_{1j}^* + S_{2i} S_{2j}^* + \cdots + S_{Ni} S_{Nj}^* = 0 \quad \text{for all } i \neq j$$

In other words, dissimilar columns are **orthogonal**.

Consider, for example, a lossless **three-port** device. Say a signal is incident on port 1, and that **all other ports are terminated**. The power **incident** on port 1 is therefore:

$$P_1^+ = \frac{|V_{01}^+|^2}{2Z_0}$$

while the power **exiting** the device at each port is:

$$P_m^- = \frac{|V_{0m}^-|^2}{2Z_0} = \frac{|S_{m1}V_{01}^-|^2}{2Z_0} = |S_{m1}|^2 P_1^+$$

The **total** power exiting the device is therefore:

$$\begin{aligned} P^- &= P_1^- + P_2^- + P_3^- \\ &= |S_{11}|^2 P_1^+ + |S_{21}|^2 P_1^+ + |S_{31}|^2 P_1^+ \\ &= (|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2) P_1^+ \end{aligned}$$

Since this device is **lossless**, then the incident power (**only** on port 1) is **equal** to exiting power (i.e, $P^- = P_1^+$). This is true **only** if:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$$

Of course, this will likewise be true if the incident wave is placed on **any** of the **other** ports of this lossless device:

$$\begin{aligned} |S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 + |S_{42}|^2 &= 1 \\ |S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 + |S_{43}|^2 &= 1 \\ |S_{14}|^2 + |S_{24}|^2 + |S_{34}|^2 + |S_{44}|^2 &= 1 \end{aligned}$$

We can state in general then that:

$$\sum_{m=1}^3 |S_{mn}|^2 = 1 \quad \text{for all } n$$

In other words, the columns of the scattering matrix must have **unit magnitude** (a requirement of all **unitary** matrices). It is apparent that this must be true for energy to be conserved.

An **example** of a (unitary) scattering matrix for a **lossless** device is:

$$\underline{\underline{S}} = \begin{bmatrix} 0 & 1/2 & j\sqrt{3}/2 & 0 \\ 1/2 & 0 & 0 & j\sqrt{3}/2 \\ j\sqrt{3}/2 & 0 & 0 & 1/2 \\ 0 & j\sqrt{3}/2 & 1/2 & 0 \end{bmatrix}$$

Reciprocal

Reciprocity results when we build a **passive** (i.e., unpowered) device with **simple** materials.

For a reciprocal network, we find that the elements of the scattering matrix are **related** as:

$$S_{mn} = S_{nm}$$

For example, a reciprocal device will have $S_{21} = S_{12}$ or $S_{32} = S_{23}$. We can write reciprocity in matrix form as:

$$\bar{\bar{S}}^T = \bar{\bar{S}} \quad \text{if reciprocal}$$


where T indicates (non-conjugate) transpose.

An **example** of a scattering matrix describing a **reciprocal**, but **lossy** and **non-matched** device is:

$$\bar{\bar{S}} = \begin{bmatrix} 0.10 & -0.40 & -j0.20 & 0.05 \\ -0.40 & j0.20 & 0 & j0.10 \\ -j0.20 & 0 & 0.10 - j0.30 & -0.12 \\ 0.05 & j0.10 & -0.12 & 0 \end{bmatrix}$$

Coaxial Transmission Lines

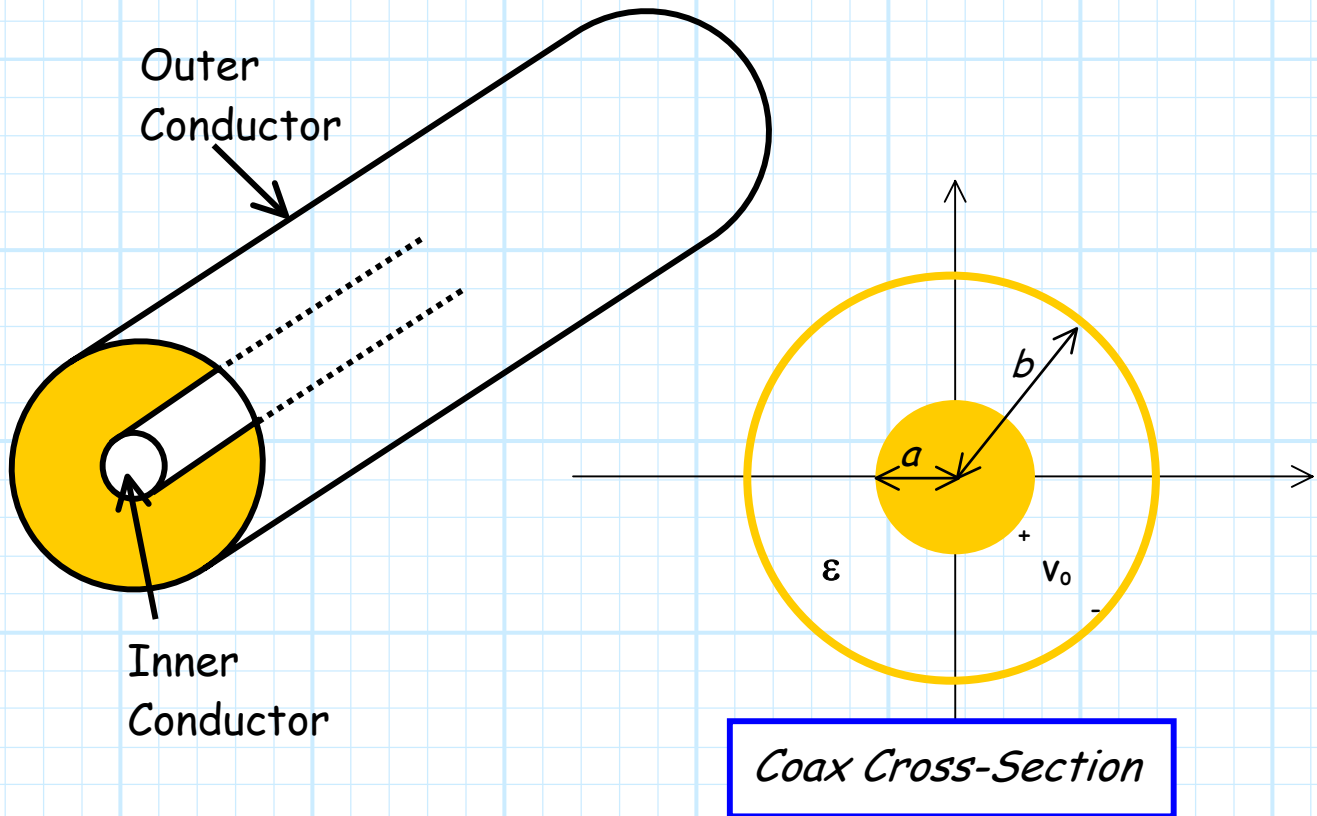
The most common type of transmission line!



The **electric** field (—→) points in the direction \hat{a}_ρ .

The **magnetic** field (----) points in the direction \hat{a}_ϕ .

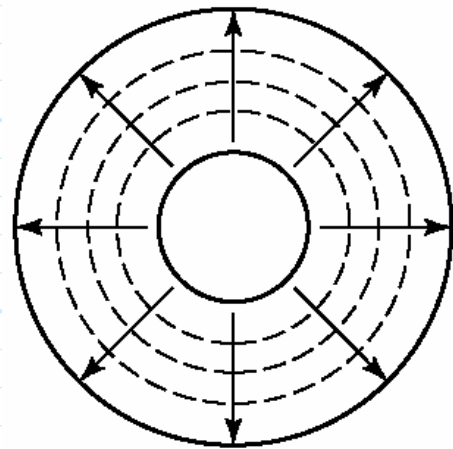E. M. Power flows in the direction \hat{a}_z .



→ A TEM wave!

Recall from EECS 220 that the **capacitance** per/unit length of a coaxial transmission line is:

$$C = \frac{2\pi\epsilon}{\ln[b/a]} \quad \left[\frac{\text{farads}}{\text{meter}} \right]$$

And that the **inductance** per unit length is :

$$L = \frac{\mu_0}{2\pi} \ln \left[\frac{b}{a} \right] \quad \left[\frac{\text{Henries}}{\text{m}} \right]$$

Where of course the **characteristic impedance** is:

$$\begin{aligned} Z_o &= \sqrt{\frac{L}{C}} \\ &= \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon}} \ln \left[\frac{b}{a} \right] \end{aligned}$$

and:

$$\beta = \omega\sqrt{LC} = \omega\sqrt{\mu_0\epsilon}$$

Therefore the **propagation velocity** of each TEM wave within a coaxial transmission line is:

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{\mu_0\epsilon}} = \frac{1}{\sqrt{\mu_0\epsilon_0}} \frac{1}{\sqrt{\epsilon_r}} = c \frac{1}{\sqrt{\epsilon_r}}$$

where $\epsilon_r = \epsilon/\epsilon_0$ is the relative dielectric constant, and c is the "speed of light" ($c = 3 \times 10^8 \text{ m/s}$).

Note then that we can likewise express β in terms ϵ_r :

$$\beta = \omega \sqrt{\mu_0 \epsilon} = \omega \sqrt{\mu_0 \epsilon_0} \sqrt{\epsilon_r} = \frac{\omega}{c} \sqrt{\epsilon_r}$$

Now, the **size** of the coaxial line (a and b) determines **more** than simply Z_0 and β (L and C) of the transmission line. Additionally, the line radius determines the **weight** and bulk of the line, as well as its **power handling** capabilities.

Unfortunately, these two characteristics **conflict** with each other!

1. Obviously, to **minimize** the weight and bulk of a coaxial transmission line, we should make a and b as **small** as possible.
2. However, for a given line voltage, reducing a and b causes the **electric field** within the coaxial line to **increase** (recall the units of electric field are V/m).

A higher electric field causes **two** problems: first, it results in greater **line attenuation** (larger α); second, it can result in **dielectric breakdown**.

Dielectric breakdown results when the electric field within the transmission line becomes so large that the dielectric material is **ionized**. Suddenly, the dielectric becomes a **conductor**, and the value G gets **very** large!


This generally results in the **destruction** of the coax line, and thus must be **avoided**. Thus, **large** coaxial lines are required when extremely **low-loss** is required (i.e., line length l is large), or the delivered **power** is large.

Otherwise, we try to keep our coax lines as **small** as possible!




Coaxial Connectors

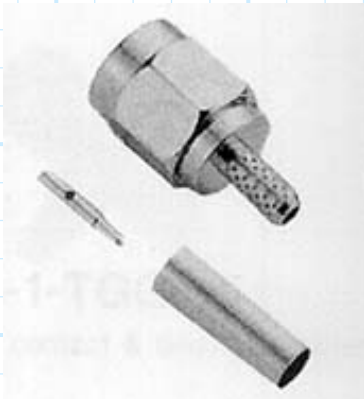There are many types of **connectors** that are used to connect coaxial lines to RF/microwave devices. They include:




SMA

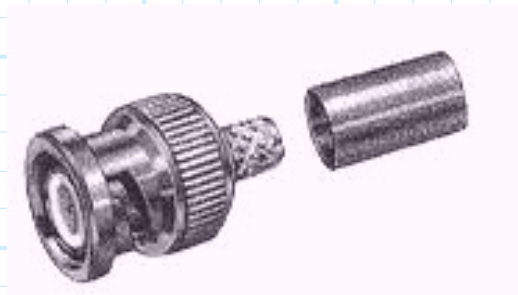The workhorse **microwave** connector. Small size, but works well to > 20 GHz. By microwave standards, moderately priced.



BNC

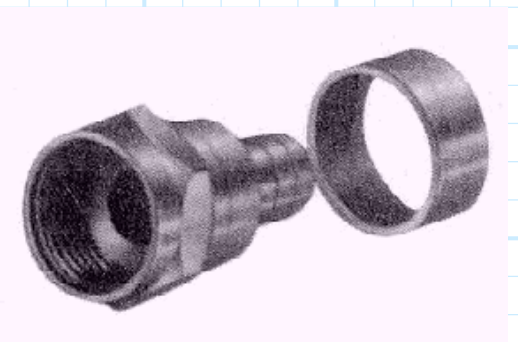The workhorse **RF** connector. Relatively small and cheap, and easy to connect. Don't use this connector past 2 GHz!



F

A poorman's BNC. The RF connector used on most consumer products such as TVs. Cheap, but difficult to connect and not reliable.




N

The **original** microwave connector. Good performance (up to 18GHz), and moderate cost, but large (about 2 cm in diameter)! However, can handle greater **power** than SMA.



UHF

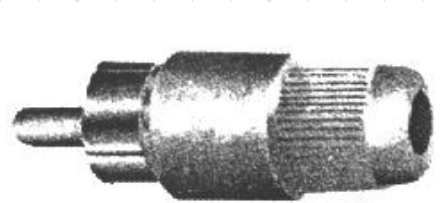The **poorman's N**. About the same size, although **reduced** reliability and performance.



RCA


Not really an RF connector. Used primarily in consumer application for video and audio signals (i.e., <20 MHz). Cheap and easy to connect.



APC-7 and APC-3.5


The **top of the line** connector. Best performance, but cost **big \$\$\$**. Used primarily in test equipment (e.g., network analyzers). 3.5 can work to nearly 40 GHz.

Printed Circuit Board Transmission Lines

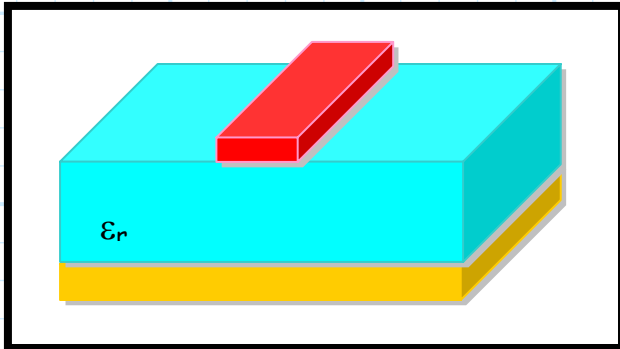


Microstrip

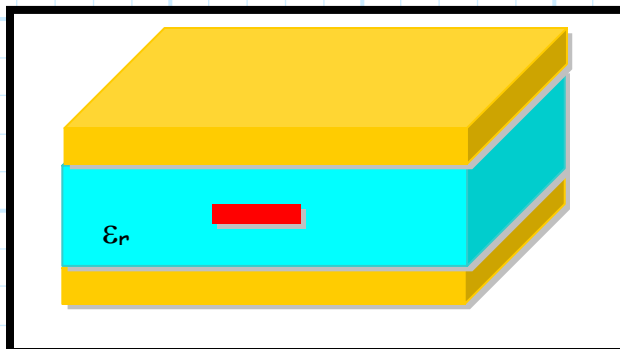Probably most popular PCB transmission line. Easy fabrication and connection, yet is **slightly** dispersive, lossy, and difficult to analyze.




Stripline

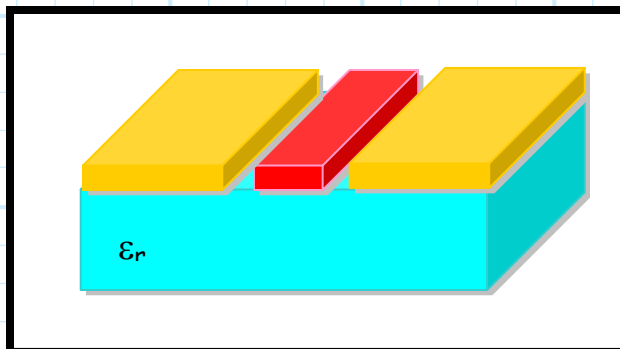Better than microstrip in that it is **not** dispersive, and is more easily analyzed. However, fabrication and connection is more difficult.




Coplanar Waveguide

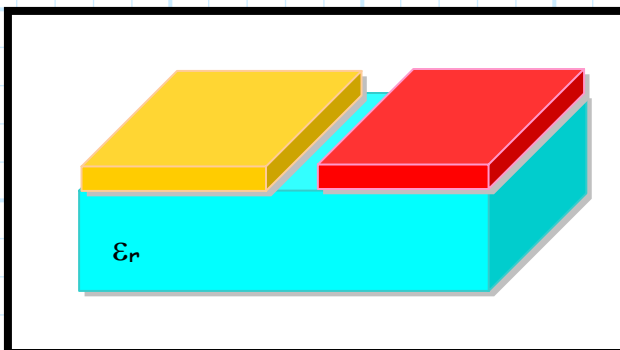The **newest** technology. Perhaps easiest to fabricate and connect components, as **both** ground and conductor are on one side of the board.




Slotline

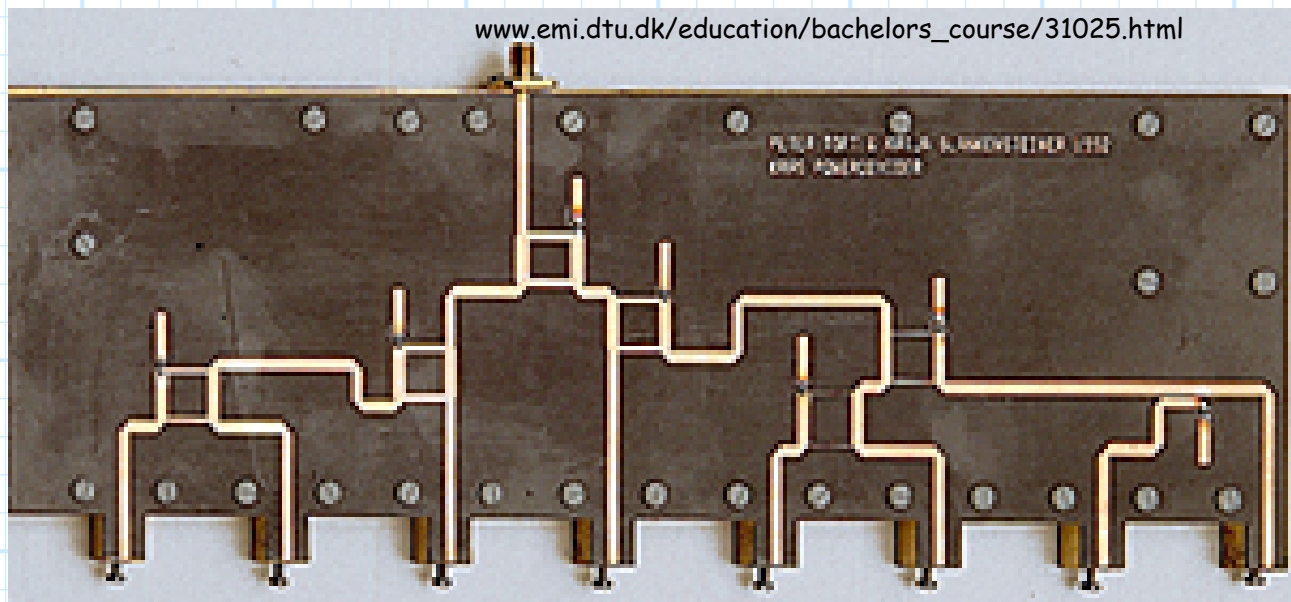Essentially, a dual wire transmission line. Best for **"balanced"** applications. Not used much.



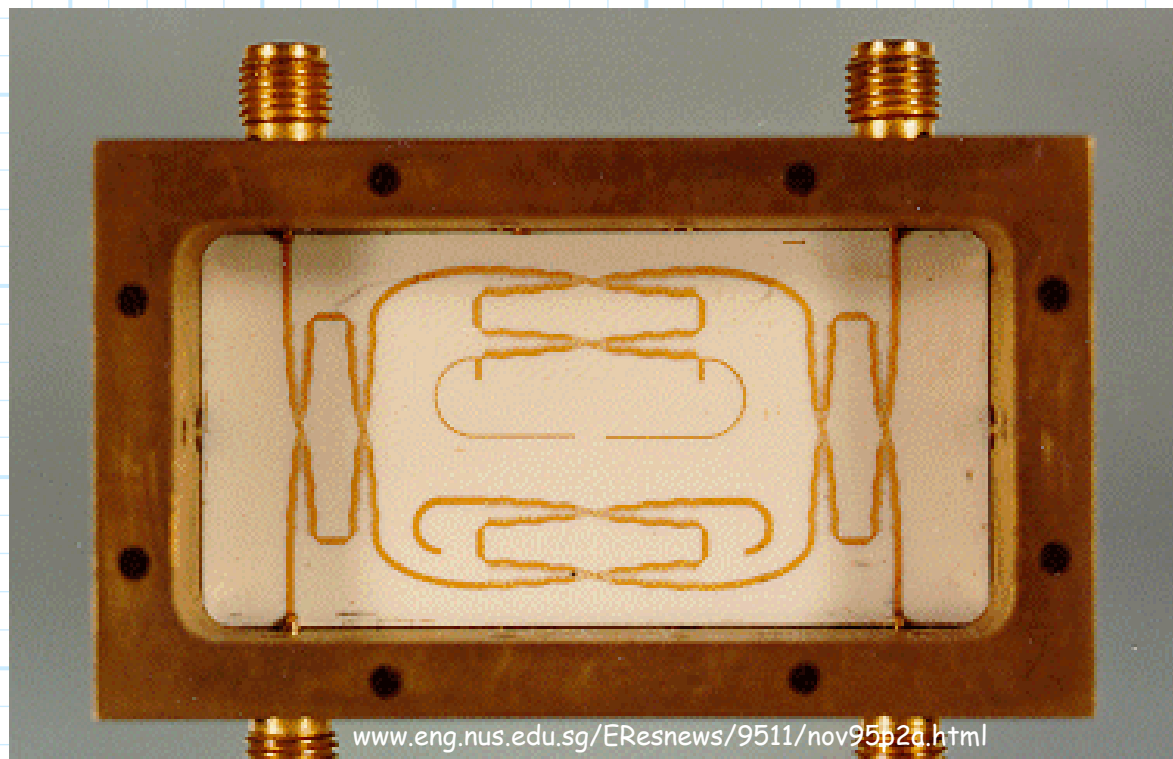An antenna array feed, constructed using **microstrip** transmission lines and circuits.



A wideband **microstrip** coupler.