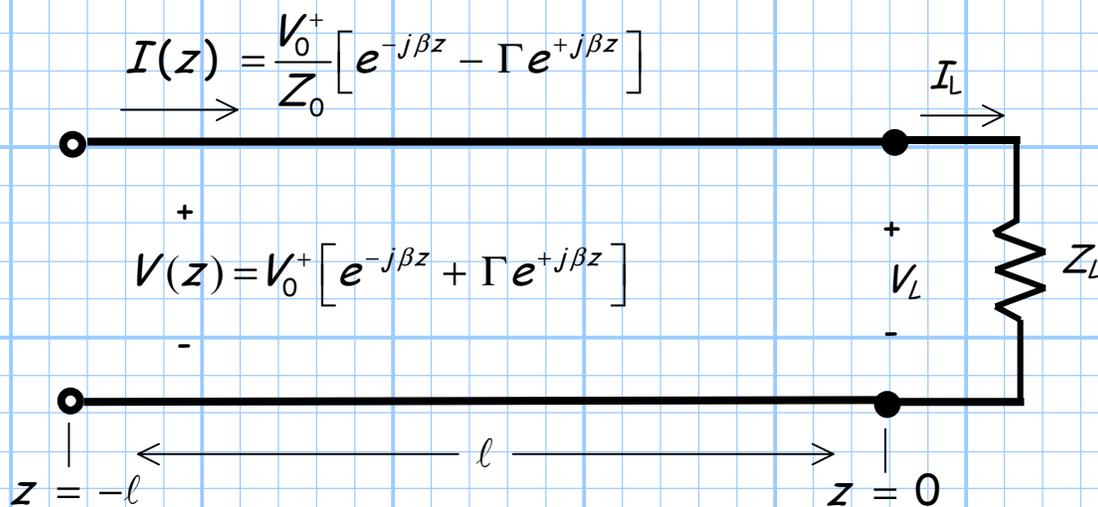


Power Flow and Return Loss

We have discovered that two waves propagate along a transmission line, one in each direction ($V_0^+ e^{-j\beta z}$ and $V_0^- e^{+j\beta z}$).



The result is that electromagnetic energy flows along the transmission line at a given rate (i.e., power).

Q: *How much power flows along a transmission line, and where does that power go?*

A: We can answer that question by determining the power **absorbed** by the load!

The time average power absorbed by an impedance Z_L is:

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} \\
 &= \frac{1}{2} \operatorname{Re}\{V(z=0) I(z=0)^*\} \\
 &= \frac{1}{2 Z_0} \operatorname{Re}\left\{ \left(V_0^+ \left[e^{-j\beta 0} + \Gamma e^{+j\beta 0} \right] \right) \left(V_0^+ \left[e^{-j\beta 0} - \Gamma e^{+j\beta 0} \right] \right)^* \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} \operatorname{Re}\left\{ 1 - (\Gamma^* - \Gamma) - |\Gamma|^2 \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma|^2)
 \end{aligned}$$

The significance of this result can be seen by **rewriting** the expression as:

$$\begin{aligned}
 P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma|^2) \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^+ \Gamma|^2}{2 Z_0} \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^-|^2}{2 Z_0}
 \end{aligned}$$

The two terms in above expression have a very definite **physical meaning**. The first term is the time-averaged **power of the wave** propagating along the transmission line **toward the load**.

We say that this wave is **incident** on the load:

$$P_{inc} = P_+ = \frac{|V_0^+|^2}{Z_0}$$

Likewise, the second term of the P_{abs} equation describes the **power of the wave** moving in the other direction (**away from the load**). We refer to this as the wave **reflected** from the load:

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma|^2 |V_0^+|^2}{2Z_0} = |\Gamma|^2 P_{inc}$$

Thus, the power absorbed by the load is simply:


$$P_{abs} = P_{inc} - P_{ref}$$

or, rearranging, we find:

$$P_{inc} = P_{abs} + P_{ref}$$

This equation is simply an expression of the **conservation of energy** !

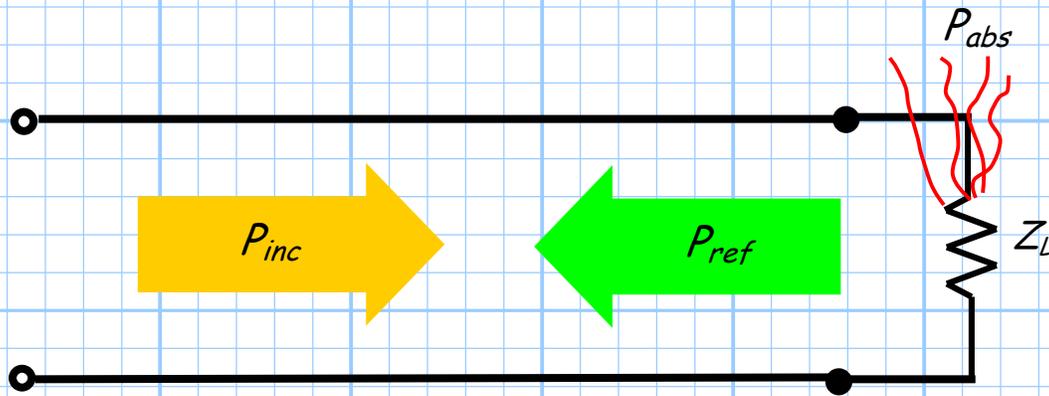It says that power flowing **toward** the load (P_{inc}) is either **absorbed** by the load (P_{abs}) or **reflected** back from the load (P_{ref}).



Note that if $|\Gamma|^2 = 1$, then $P_{inc} = P_{ref}$, and therefore **no power** is absorbed by the **load**.

This of course makes sense !

The magnitude of the reflection coefficient ($|\Gamma|$) is equal to one **only** when the load impedance is **purely reactive** (i.e., purely imaginary).

Of course, a purely reactive element (e.g., capacitor or inductor) **cannot** absorb any power—**all** the power **must** be reflected!

Return Loss

The **ratio** of the reflected power to the incident power is known as **return loss**. Typically, return loss is expressed in **dB**:

$$R.L. = -10 \log_{10} \left[\frac{P_{ref}}{P_{inc}} \right] = -10 \log_{10} |\Gamma|^2$$

For **example**, if the return loss is **10dB**, then **10%** of the incident power is **reflected** at the load, with the remaining **90%** being **absorbed** by the load—we “lose” 10% of the incident power

Likewise, if the return loss is **30dB**, then **0.1 %** of the incident power is **reflected** at the load, with the remaining **99.9%** being **absorbed** by the load—we “lose” 0.1% of the incident power.

Thus, a **larger** numeric value for return loss actually indicates **less** lost power. An **ideal** return loss would be ∞ dB, whereas a return loss of 0 dB indicates that $|\Gamma|=1$ --the load is **reactive!**