

## C. Microwave Sources

**Q:** A passive load  $Z_L$  specifies  $Z(z)$  and  $\Gamma(z)$ , but we still don't explicitly know  $V(z)$ ,  $I(z)$  or  $V^+(z)$ ,  $V^-(z)$ . How are these functions determined?

**A:** All of these quantities are zero, unless a source (generator) is applied to trans. line. The **boundary condition** enforced by the generator will then **explicitly** determine these functions!

### HO: A Transmission Line Connecting Source and Load

**Q:** OK, we can **finally** ask the question that we have been concerned with since the very beginning: How much **power** is delivered to the load by the source?

**A:** HO: Delivered Power


**Q:** So the power transferred depends on the **source**, the **transmission line**, and the **load**. What combination of these devices will result in **maximum** power transfer?

**A:** HO: Special Cases of Source and Input Impedances

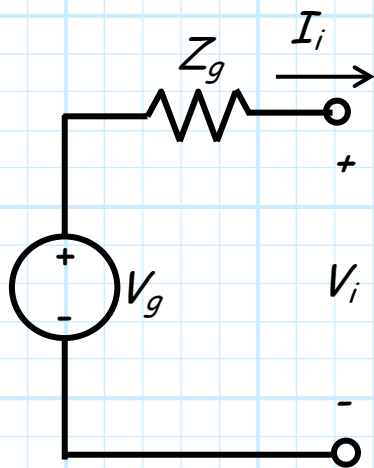
# A Transmission Line Connecting Source & Load

We can think of a transmission line as a conduit that allows **power** to flow from an **output** of one device/network to an **input** of another.

To simplify our analysis, we can model the **input** of the device **receiving** the power with its input impedance (e.g.,  $Z_L$ ), while we can model the device **output delivering** the power with its Thevenin's or Norton's equivalent circuit.




$$V_g = V_i + Z_g I_i$$

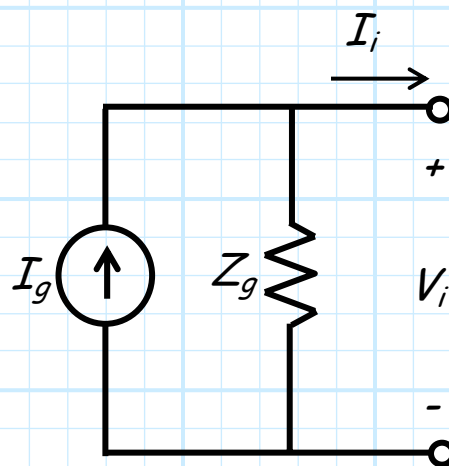

$$I_g = \frac{V_i}{Z_g} + I_i$$

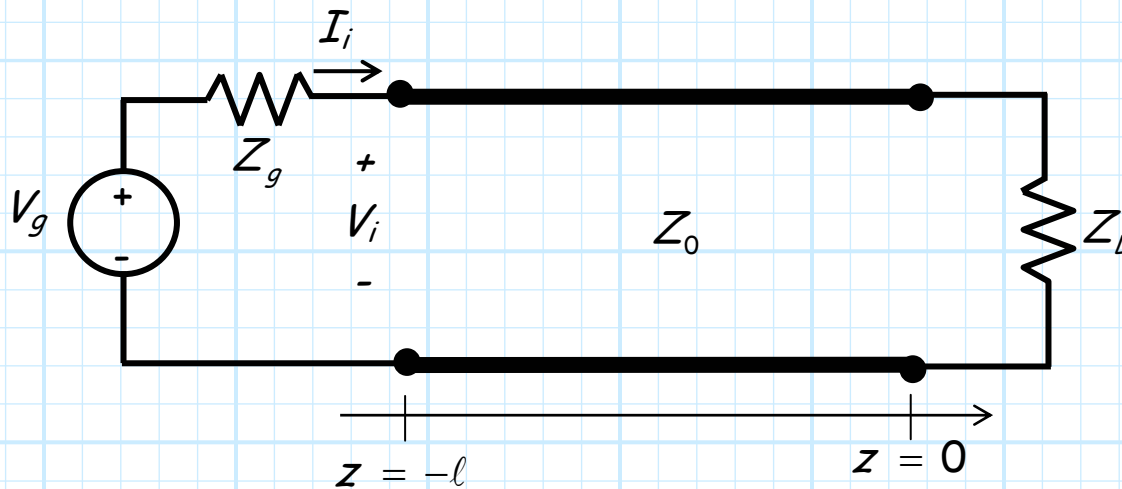Typically, the power source is modeled with its **Thevenin's** equivalent; however, we will find that the **Norton's** equivalent circuit is useful if we express the remainder of the circuit in terms of its **admittance** values (e.g.,  $Y_0, Y_L, Y(z)$ ).



**Recall** from the telegrapher's equations that the current and voltage along the transmission line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

At  $z = 0$ , we enforced the **boundary condition** resulting from Ohm's Law:

$$Z_L = \frac{V_L}{I_L} = \frac{V(z=0)}{I(z=0)} = \frac{(V_0^+ + V_0^-)}{\left(\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}\right)}$$

Which resulted in:

$$\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \doteq \Gamma_L$$

So therefore:

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_L e^{+j\beta z}]$$

We are left with the **question**: just what is the **value** of complex constant  $V_0^+$ ?!?

**This** constant depends on the signal **source**! To determine its exact **value**, we must now apply **boundary conditions** at  $z = -\ell$ .

We know that at the **beginning** of the transmission line:


$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Likewise, we know that the **source** must satisfy:

$$V_g = V_i + Z_g I_i$$

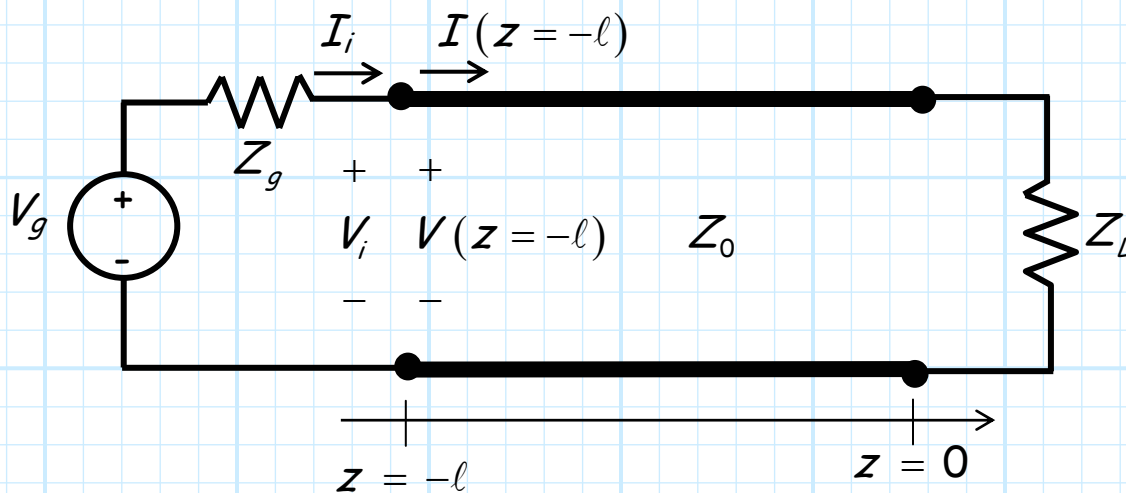To relate these **three** expressions, we need to apply **boundary conditions** at  $z = -\ell$ :



From KVL we find:

$$V_i = V(z = -\ell)$$

And from KCL:

$$I_i = I(z = -\ell)$$


Combining these equations, we find:

$$V_g = V_i + Z_g I_i$$

$$V_g = V_0^+ \left[ e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right] + Z_g \frac{V_0^+}{Z_0} \left[ e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right]$$

One equation  $\rightarrow$  one unknown ( $V_0^+$ )!!

Solving, we find the value of  $V_0^+$ :

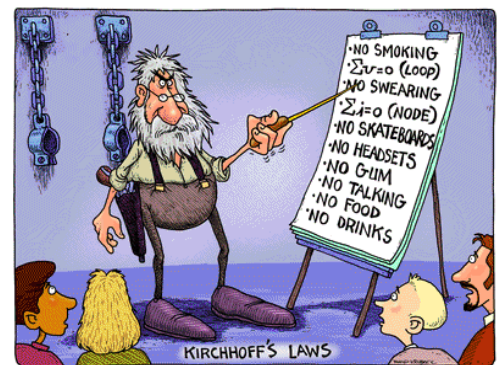

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

where:

$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$

There is one **very important** point that must be made about the result:

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

And that is—the wave  $V_0^+(z)$  **incident** on the load  $Z_L$  is actually dependent on the value of load  $Z_L$  !!!!!

Remember:


$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$

We tend to think of the incident wave  $V_0^+(z)$  being “**caused**” by the source, and it is certainly true that  $V_0^+(z)$  **depends** on the source—after all,  $V_0^+(z) = 0$  if  $V_g = 0$ . However, we find from the equation above that it **likewise** depends on the value of the load!

Thus we **cannot**—in general—consider the incident wave to be the “**cause**” and the reflected wave the “**effect**”. Instead, each wave must obtain the proper **amplitude** (e.g.,  $V_0^+, V_0^-$ ) so that the boundary conditions are satisfied at **both** the beginning and end of the transmission line.
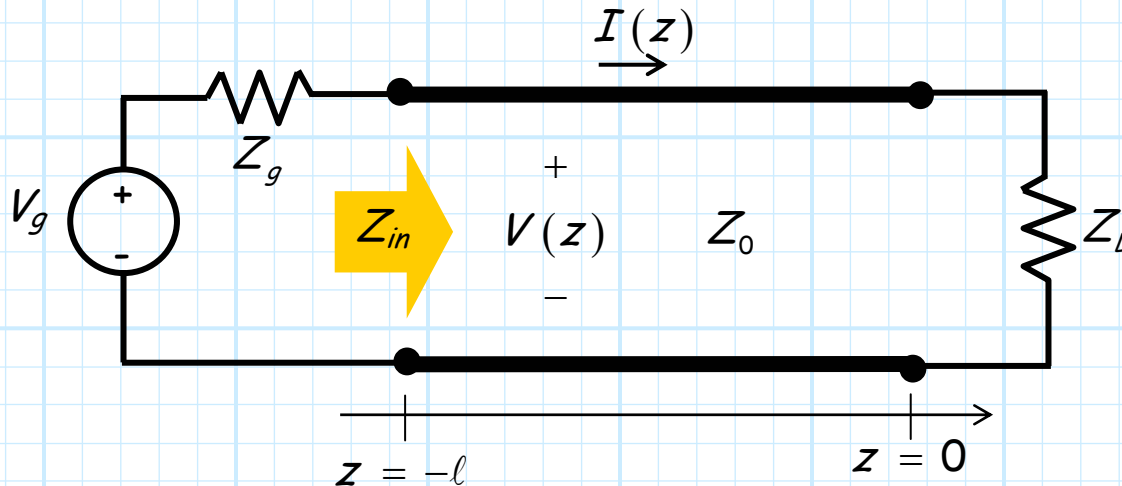
# Delivered Power

**Q:** If the purpose of a transmission line is to transfer **power** from a source to a load, then exactly how much power is **delivered** to  $Z_L$  for the circuit shown below ??



**A:** We of course **could** determine  $V_0^+$  and  $V_0^-$ , and then determine the power absorbed by the load ( $P_{abs}$ ) as:


$$P_{abs} = \frac{1}{2} \operatorname{Re} \{ V(z=0) I^*(z=0) \}$$

However, if the transmission line is **lossless**, then we know that the power delivered to the load must be **equal** to the power "delivered" to the **input** ( $P_{in}$ ) of the transmission line:

$$P_{abs} = P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z=-l) I^*(z=-l) \}$$

However, we can determine this power **without** having to solve for  $V_0^+$  and  $V_0^-$  (i.e.,  $V(z)$  and  $I(z)$ ). We can simply use our knowledge of **circuit theory!**

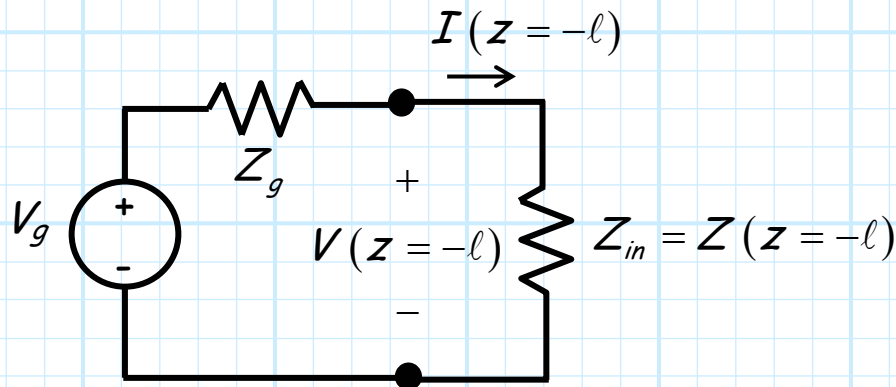We can **transform** load  $Z_L$  to the beginning of the transmission line, so that we can replace the transmission line with its **input impedance**  $Z_{in}$ :



Note by **voltage division** we can determine:

$$V(z = -l) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from **Ohm's Law** we conclude:

$$I(z = -l) = \frac{V_g}{Z_g + Z_{in}}$$

And thus, the **power**  $P_{in}$  delivered to  $Z_{in}$  (and thus the **power**  $P_{abs}$  delivered to the load  $Z_L$ ) is:



$$\begin{aligned}
 P_{abs} &= P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{V_g^*}{(Z_g + Z_{in})^*} \right\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \} \\
 &= \frac{1}{2} |V_g|^2 \frac{|Z_{in}|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ y_{in} \}
 \end{aligned}$$

Note that we could **also** determine  $P_{abs}$  from our **earlier** expression:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

But we would of course have to **first** determine  $V_0^+$  (!):

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

# Special Cases of Source and Load Impedance

Let's look at **specific cases** of  $Z_g$  and  $Z_L$ , and determine how they affect  $V_0^+$  and  $P_{abs}$ .

$$Z_g = Z_0$$

For this case, we find that  $V_0^+$  **simplifies** greatly:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_0(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{1}{1 + \Gamma_{in} + 1 - \Gamma_{in}} \\ &= \frac{1}{2} V_g e^{-j\beta\ell} \end{aligned}$$

Look at what **this** says!

It says that the incident wave in this case is **independent** of the load attached at the other end!

Thus, for the **one** case  $Z_g = Z_0$ , we in fact can consider  $V^+(z)$  as being the source wave, and then the reflected wave  $V^-(z)$  as being the result of this stimulus.

Remember, the complex value  $V_0^+$  is the value of the incident wave evaluated at the end of the transmission line ( $V_0^+ = V^+(z=0)$ ). We can likewise determine the value of the incident wave at the **beginning** of the transmission line (i.e.,  $V^+(z=-\ell)$ ). For this case, where  $Z_g = Z_0$ , we find that this value can be very simply stated (!):

$$\begin{aligned} V^+(z=-\ell) &= V_0^+ e^{-j\beta(z=-\ell)} \\ &= \left( \frac{1}{2} V_g e^{-j\beta\ell} \right) e^{+j\beta\ell} \\ &= \frac{V_g}{2} \end{aligned}$$

Likewise, we find that the delivered power for this case can be simply stated as:

$$\begin{aligned} P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\ &= \frac{|V_g|^2}{8 Z_0} (1 - |\Gamma_L|^2) \end{aligned}$$

$$Z_L = Z_0$$

In this case, we find that  $\Gamma_L = 0$ , and thus  $\Gamma_{in} = 0$ . As a result:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0 + Z_g} \end{aligned}$$

Likewise, we find that:

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2) = \frac{|V_0^+|^2}{2Z_0}$$

Here the delivered power  $P_{abs}$  is simply that of the incident wave ( $P^+$ ), as the matched condition causes the reflected power to be zero ( $P^- = 0$ )!

Inserting the value of  $V_0^+$ , we find:

$$\begin{aligned}
 P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} \\
 &= \frac{|V_g|^2}{2 Z_0} \frac{(Z_0)^2}{|Z_0 + Z_g|^2} \\
 &= \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2}
 \end{aligned}$$

Note that this result can likewise be found by recognizing that  $Z_{in} = Z_0$  when  $Z_L = Z_0$ :

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_0|^2} Z_0 \\
 &= \frac{|V_g|^2}{2} \frac{Z_0}{|Z_g + Z_0|^2}
 \end{aligned}$$

$$Z_{in} = Z_g^*$$

For this case, we find  $Z_L$  takes on whatever value required to make  $Z_{in} = Z_g^*$ . This is a **very** important case!

First, using the fact that:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_g^* - Z_0}{Z_g^* + Z_0}$$

We can show that (trust me!):

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_g^* + Z_0}{4\text{Re}\{Z_g\}}$$

Not a particularly interesting result, but let's look at the absorbed power.

$$\begin{aligned} P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \text{Re}\{Z_{in}\} \\ &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_g^*|^2} \text{Re}\{Z_g^*\} \\ &= \frac{1}{2} \frac{|V_g|^2}{|2\text{Re}\{Z_g^*\}|^2} \text{Re}\{Z_g^*\} \\ &= \frac{1}{2} |V_g|^2 \frac{1}{4\text{Re}\{Z_g^*\}} \doteq P_{avl} \end{aligned}$$

Although this result does not look particularly interesting **either**, we find the result is **very** important!

It can be shown that—for a **given**  $V_g$  and  $Z_g$ —the value of input impedance  $Z_{in}$  that will absorb the **largest possible** amount of power is the value  $Z_{in} = Z_g^*$ .

This case is known as the **conjugate match**, and is essentially the goal of every transmission line problem—to deliver the largest possible power to  $Z_{in}$ , and thus to  $Z_L$  as well!


This maximum delivered power is known as the **available power** ( $P_{avl}$ ) of the source.

There are **two** very important things to understand about this result!


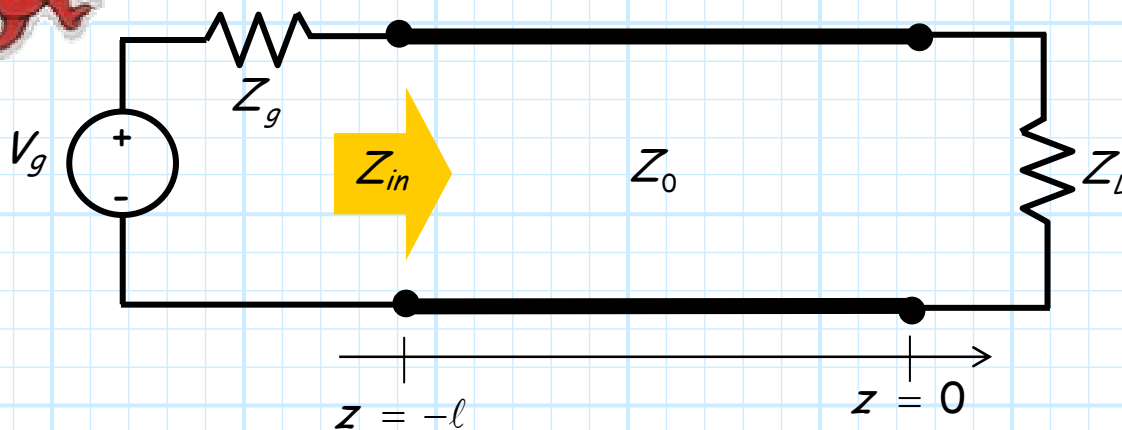
### Very Important Thing #1

Consider again the terminated transmission line:



Recall that if  $Z_L = Z_0$ , the **reflected** wave will be **zero**, and the absorbed power will be:

$$P_{abs} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2} \leq P_{avl}$$

But note if  $Z_L = Z_0$ , the input impedance  $Z_{in} = Z_0$ —but then  $Z_{in} \neq Z_g^*$  (generally)! In other words,  $Z_L = Z_0$  does **not** (generally) result in a **conjugate match**, and thus setting  $Z_L = Z_0$  does **not** result in maximum power absorption!

**Q:** *Huh!? This makes **no sense!** A load value of  $Z_L = Z_0$  will **minimize** the reflected wave ( $P^- = 0$ )—**all** of the incident power will be absorbed.*

*Any other value of  $Z_L = Z_0$  will result in **some** of the incident wave being reflected—how in the world could this **increase** absorbed power?*

*After all, just **look** at the expression for absorbed power:*

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

***Clearly**, this value is maximized when  $\Gamma_L = 0$  (i.e., when  $Z_L = Z_0$ )!!!*



**A:** You are forgetting one very important fact! Although it is true that the load impedance  $Z_L$  affects the **reflected** wave power  $P^-$ , the value of  $Z_L$ —as we have shown in this handout—**likewise** helps determine the value of the **incident** wave (i.e., the value of  $P^+$ ) as well.

- \* Thus, the value of  $Z_L$  that minimizes  $P^-$  will **not** generally maximize  $P^+$ !
- \* **Likewise** the value of  $Z_L$  that maximizes  $P^+$  will not generally minimize  $P^-$ .
- \* Instead, the value of  $Z_L$  that maximizes the **absorbed** power  $P_{abs}$  is, by definition, the value that maximizes the **difference**  $P^+ - P^-$ .

We find that this impedance  $Z_L$  is the value that results in the **ideal** case of  $Z_{in} = Z_g^*$ .

**Q:** *Yes, but what about the case where  $Z_g = Z_0$ ? For that case, we determined that the incident wave is independent of  $Z_L$ . Thus, it would seem that at least for that case, the **delivered** power would be maximized when the **reflected** power was minimized (i.e.,  $Z_L = Z_0$ ).*

**A:** **True!** But think about what the **input** impedance would be in that case— $Z_{in} = Z_0$ . Oh by the way, that provides a **conjugate match** ( $Z_{in} = Z_0 = Z_g^*$ )!

Thus, in some ways, the case  $Z_g = Z_0 = Z_L$  (i.e., both source and load impedances are numerically equal to  $Z_0$ ) is **ideal**. A **conjugate match** occurs, the incident wave is **independent** of  $Z_L$ , there is **no** reflected wave, and all the math **simplifies** quite nicely:

$$V_0^+ = \frac{1}{2} V_g e^{-j\beta l} \qquad P_{abs} = P_{avl} = \frac{|V_g|^2}{8 Z_0}$$



### Very Important Thing #2

Note the conjugate match criteria **says**:

*Given source impedance  $Z_g$ , maximum power transfer occurs when the input impedance is set at value  $Z_{in} = Z_g^*$ .*

It does **NOT** say:

*Given input impedance  $Z_{in}$ , maximum power transfer occurs when the source impedance is set at value  $Z_g = Z_{in}^*$ .*

This last statement is in fact **false!**

A **factual** statement is this:

*Given input impedance  $Z_{in}$ , maximum power transfer occurs when the source impedance is set at value  $Z_g = 0 - jX_{in}$  (i.e.,  $R_g = 0$ ).*

**Q:** Huh??

**A:** Remember, the value of source impedance  $Z_g$  affects the available power  $P_{avl}$  of the source. To maximize  $P_{avl}$ , the real (resistive) component of the source impedance should be as small as possible (regardless of  $Z_{in}$ !), a fact that is **evident** when observing the expression for **available power**:

$$P_{avl} = \frac{1}{2} |V_g|^2 \frac{1}{4 \operatorname{Re}\{Z_g^*\}} = \frac{|V_g|^2}{8R_g}$$

Thus, **maximizing** the power delivered to a load ( $P_{abs}$ ), from a source, has **two** components:

1. Maximize the **power available** ( $P_{avl}$ ) from a source (e.g., minimize  $R_g$ ).
2. **Extract** all of this available power by setting the input impedance  $Z_{in}$  to a value  $Z_{in} = Z_g^*$  (thus  $P_{abs} = P_{avl}$ ).