

## D. Matching Networks

**Q:** *Yikes! The signal source is generally a Thevenin's equivalent of the **output** of some **useful device**, while the load impedance is generally the **input** impedance of some other **useful device**. I do **not** want to—nor typically can I—**change** these devices or **alter** their characteristics.*

*Must I then just **accept** the fact that I will achieve **suboptimum** power transfer?*

**A:** NOPE! All of the available power of the source can be delivered to the load—if we properly construct a **matching network**.

### HO: Matching Networks

**Q:** *But in microwave circuits, a source and load are connected by a transmission line. Can we implement matching networks in transmission line circuits?*

**A:** HO: Matching Networks and Transmission Lines

**Q:** *Matching networks seem almost too good to be true; can we really design and construct them to provide a perfect match?*

**A:** It is relatively easy to provide a near perfect match at precisely **one frequency!**


**But**, since lossless matching networks are made entirely of **reactive** elements (not to mention the reactive components of the source and load impedance), we find that changing the signal frequency will typically **"mismatch"** our circuit!

Thus a difficult challenge for any microwave component designer is to provide a **wideband** match to a transmission line with characteristic impedance  $Z_0$ .

→ **All** microwave components thus have a **finite** operating **bandwidth!**
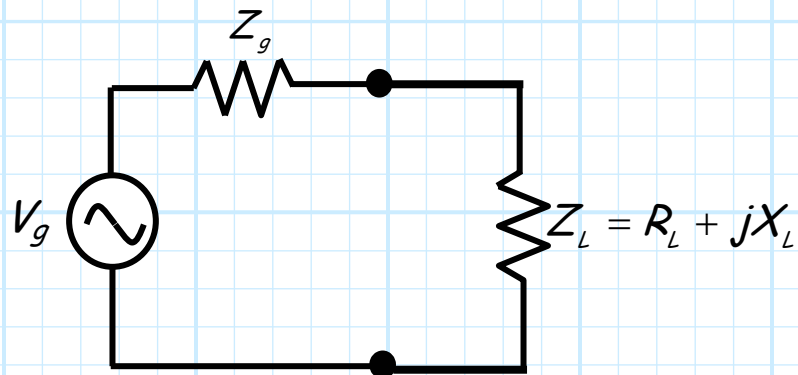
# Matching Networks

Consider again the problem where a **passive load** is attached to an **active source**:



The load will **absorb power**—power that is **delivered** to it by the **source**.

$$\begin{aligned}
 P_L &= \frac{1}{2} \operatorname{Re} \{ V_L I_L^* \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ \left( V_g \frac{Z_L}{Z_g + Z_L} \right) \left( \frac{V_g}{Z_g + Z_L} \right)^* \right\} \\
 &= \frac{1}{2} |V_g|^2 \frac{\operatorname{Re} \{ Z_L \}}{|Z_g + Z_L|^2} \\
 &= \frac{1}{2} |V_g|^2 \frac{R_L}{|Z_g + Z_L|^2}
 \end{aligned}$$

Recall that the power delivered to the load will be **maximized** (for a given  $V_g$  and  $Z_g$ ) if the load impedance is equal to the **complex conjugate** of the source impedance ( $Z_L = Z_g^*$ ).

We call this maximum power the **available power**  $P_{avl}$  of the **source**—it is, after all, the **largest** amount of power that the source can **ever** deliver!

$$\begin{aligned}
 P_L^{max} &\doteq P_{avl} \\
 &= \frac{1}{2} |V_g|^2 \frac{R_g}{|Z_g + Z_g^*|^2} \\
 &= \frac{1}{2} |V_g|^2 \frac{R_g}{|2R_g|^2} \\
 &= \frac{|V_g|^2}{8 R_g}
 \end{aligned}$$

- \* Note the available power of the **source** is dependent on **source** parameters **only** (i.e.,  $V_g$  and  $R_g$ ). This makes sense! Do you see why?
- \* Thus, we can say that to “take full advantage” of all the available power of the source, we must to make the load impedance the complex conjugate of the source impedance.
- \* Otherwise, the power delivered to the load will be less than power made available by the source! In other “words”:


$$P_L \leq P_{avl}$$

**Q:** *But, you said that the load impedance typically models the input impedance of some useful device. We **don't** typically get to "select" or adjust this impedance—it is what it is. Must we then simply **accept** the fact that the delivered power will be less than the available power?*




**A:** NO! We can in fact modify our circuit such that all available source power is delivered to the load—**without** in any way **altering** the impedance value of that load!

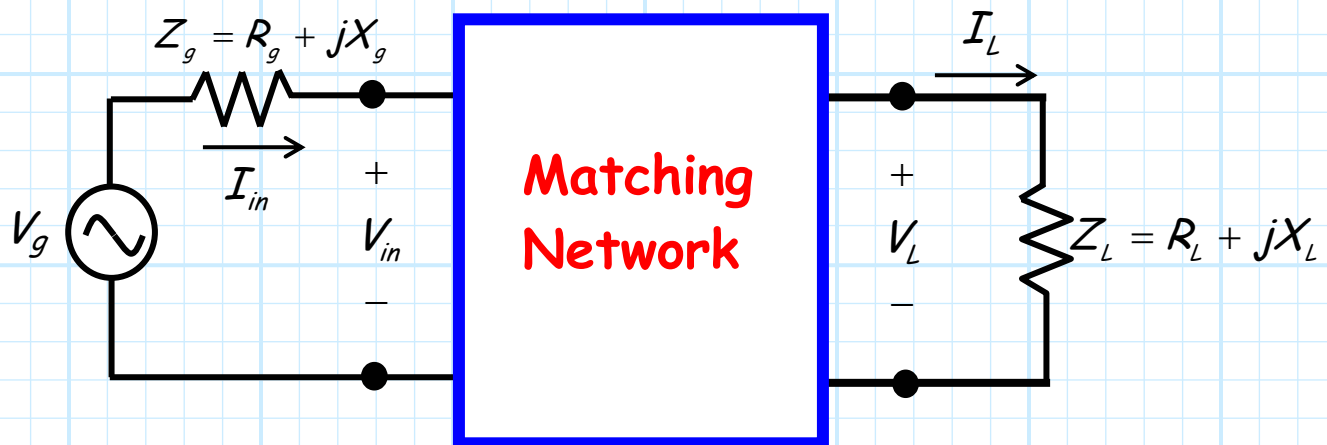To accomplish this, we must insert a **matching network** between the source and the load:



The sole purpose of this matching network is to "transform" the load impedance into an input impedance that is **conjugate matched** to the source! I.E.:
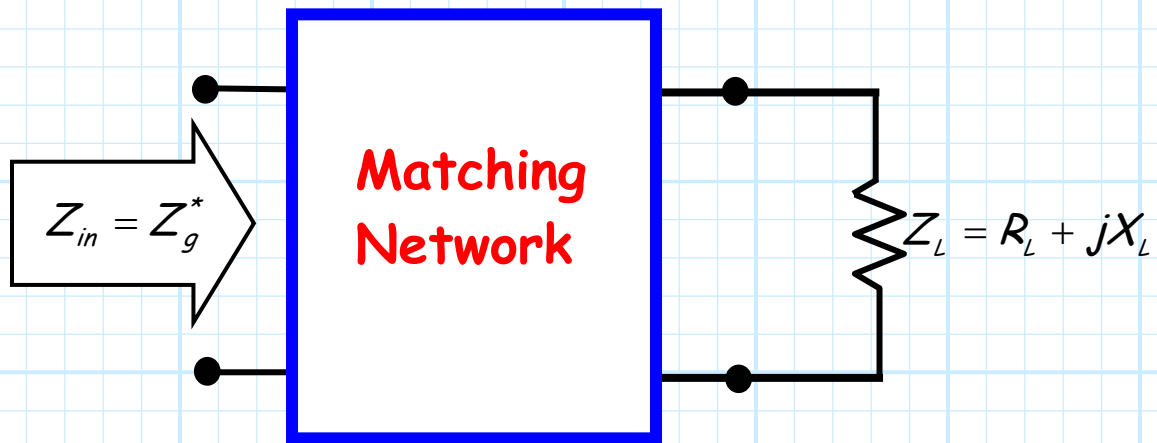
$$Z_{in} = \frac{V_{in}}{I_{in}} = Z_g^*$$




Because of this, **all** available source power is delivered to the input of the matching network (i.e., delivered to  $Z_{in}$ ):

$$P_{in} = P_{avl}$$



**Q:** *Wait just one second! The matching network ensures that **all** available power is delivered to the **input** of the matching network, but that does **not** mean (necessarily) that this power will be delivered to the **load**  $Z_L$ . The power delivered to the load **could** still be **much less** than the available power!*

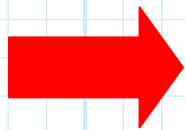**A:** True! To ensure that the **available power** delivered to the input of the matching network is **entirely** delivered to the **load**, we must construct our matching network such that it **cannot absorb any power**—the matching network must be **lossless!**



We must construct our matching network entirely with **reactive elements!**


Examples of reactive elements include inductors, capacitors, transformers, as well as lengths of **lossless transmission lines**.

Thus, constructing a proper lossless matching network will lead to the **happy** condition where:


$$P_L = P_{in} = P_{avl}$$

- \* Note that the design and construction of this lossless network will depend on **both** the value of source impedance  $Z_g$  and load impedance  $Z_L$ .
- \* However, the matching network does **not physically alter** the values of either of these two quantities—the source and load are left physically unchanged!

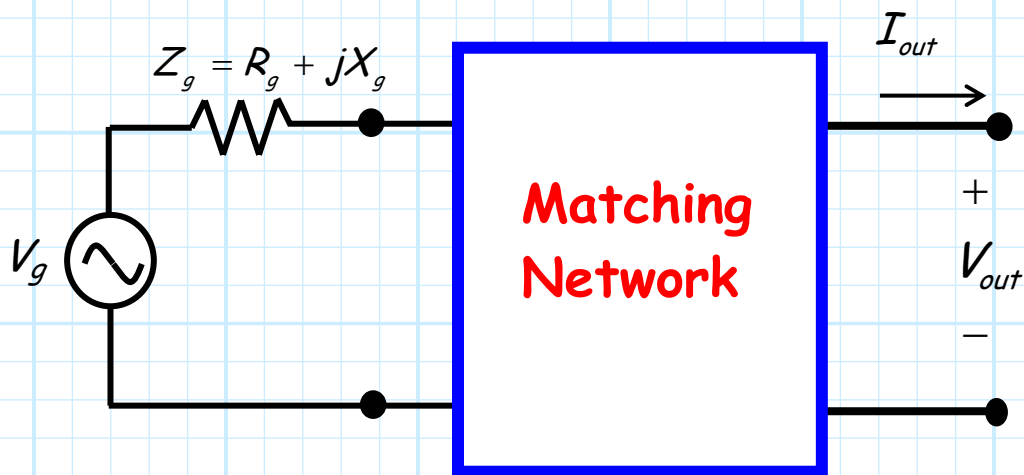
Now, let's consider the matching network from a **different perspective**. Instead of defining it in terms of its **input impedance** when attached the **load**, let's describe it in terms of its **output impedance** when attached to the **source**:



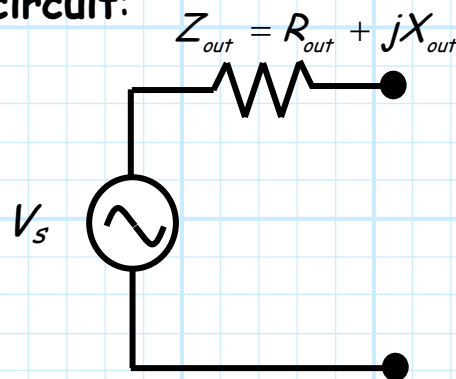This "new" source (i.e., the original source with the matching network attached) can be expressed in terms of its **Thevenin's equivalent circuit**:




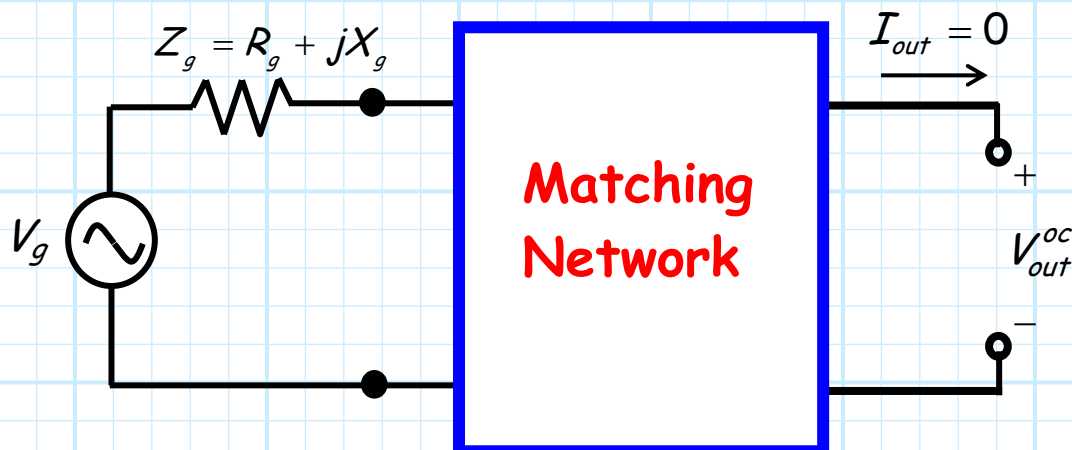This equivalent circuit can be determined by first evaluating (or measuring) the **open-circuit output voltage**  $V_{out}^{oc}$ :





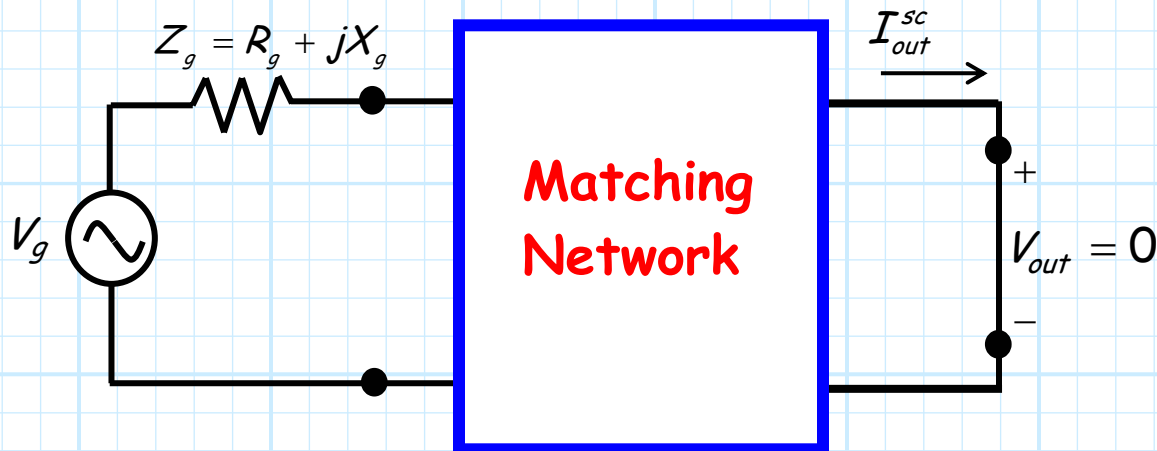And likewise evaluating (or measuring) the **short-circuit output current**  $I_{out}^{sc}$ :



From these two values ( $V_{out}^{oc}$  and  $I_{out}^{sc}$ ) we can determine the **Thevenin's equivalent source**:

$$V_s = V_{out}^{oc} \quad Z_{out} = \frac{V_{out}^{oc}}{I_{out}^{sc}}$$

Note that in general that  $V_s \neq V_g$  and  $Z_{out} \neq Z_g$ —the matching network “transforms” both the values of both the impedance and the voltage source.




**Q:** Arrrrgg! Doesn't that mean that the **available power** of this “transformed” source will be **different** from the original?


**A:** Nope. **If** the matching network is **lossless**, the available power of this equivalent source is **identical** to the available power of the original source—the lossless matching network does **not** alter the available power!

Now, for a **properly** designed, **lossless** matching network, it turns out that (as **you** might have expected!) the output impedance  $Z_{out}$  is equal to the **complex conjugate** of the load impedance. I.E.:


$$Z_{out} = Z_L^*$$

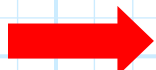 The source and load are again matched!

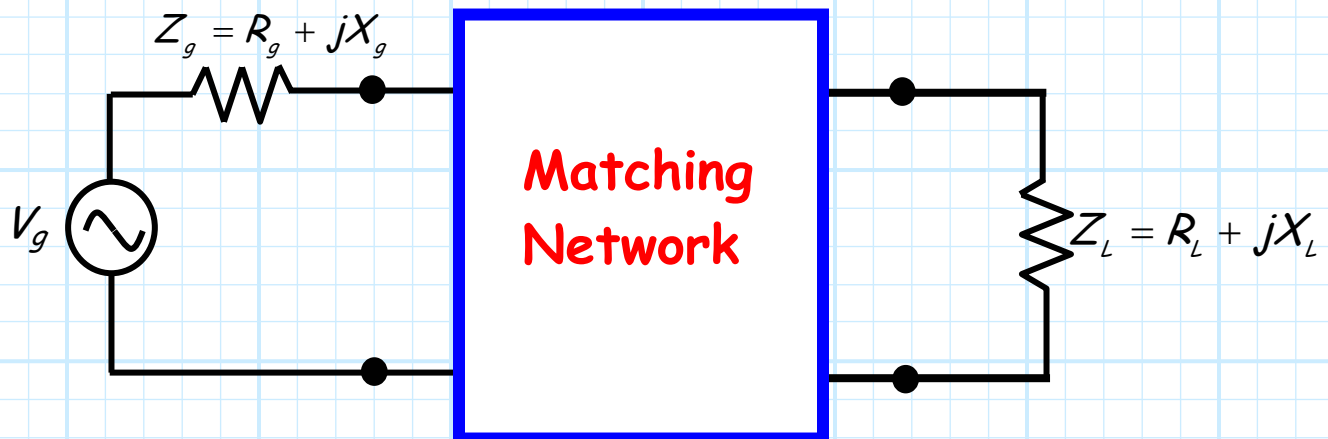
Thus, we can look at the matching network in two equivalent ways:



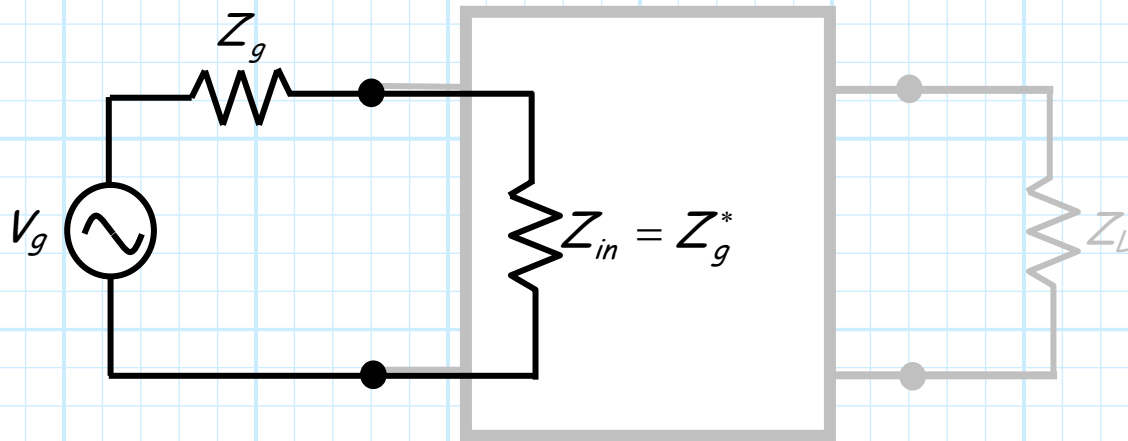**1.** As a network attached to a load, one that "transforms" its impedance to  $Z_{in}$ —a value matched to the source impedance  $Z_g$ :



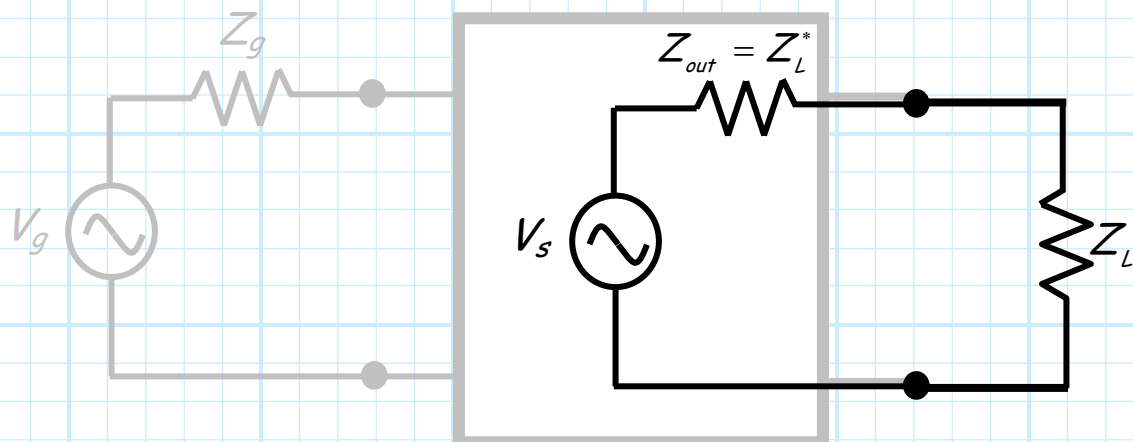
2. Or, as network attached to a source, one that “transforms” its impedance to  $Z_{out}$ —a value matched to the load impedance  $Z_L$ :



Either way, the source and load impedance are conjugate matched—all the available power is delivered to the load!
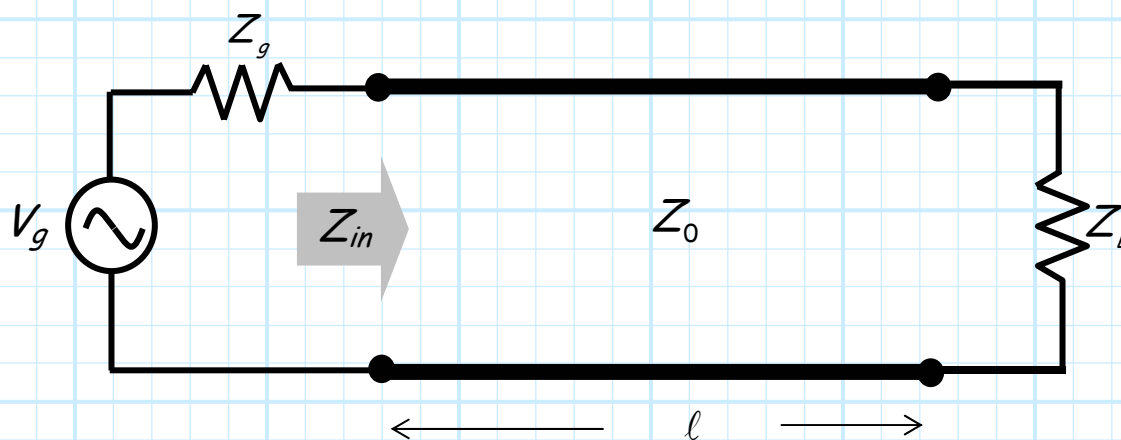
# Matching Networks and Transmission Lines

Recall that a primary purpose of a transmission line is to allow the transfer of **power** from a source to a load.



**Q:** So, say we directly connect an **arbitrary** source to an **arbitrary** load via a length of transmission line. Will the power delivered to the load be equal to the **available power** of the source?

**A:** Not likely! Remember we determined earlier that the efficacy of power transfer depends on:

1. the source impedance  $Z_g$ .
2. load impedance  $Z_L$ .
3. the transmission line characteristic impedance  $Z_0$ .

#### 4. the transmission line length $\ell$ .


Recall that **maximum** power transfer occurred only when these four parameters resulted in the **input impedance** of the transmission line being equal to the **complex conjugate** of the **source impedance** (i.e.,  $Z_{in}^* = Z_g$ ).

It is of course **unlikely** that the very **specific** conditions of a **conjugate match** will occur if we simply connect a length of transmission line between an **arbitrary** source and load, and thus the power delivered to the load will generally be **less** than the **available power** of the source.

**Q:** *Is there any way to use a **matching network** to fix this problem? Can the power delivered to the load be increased to **equal** the available power of the source if there is a transmission line connecting them?*


**A:** There sure is! We can likewise construct a matching network for the case where the source and load are connected by a **transmission line**.

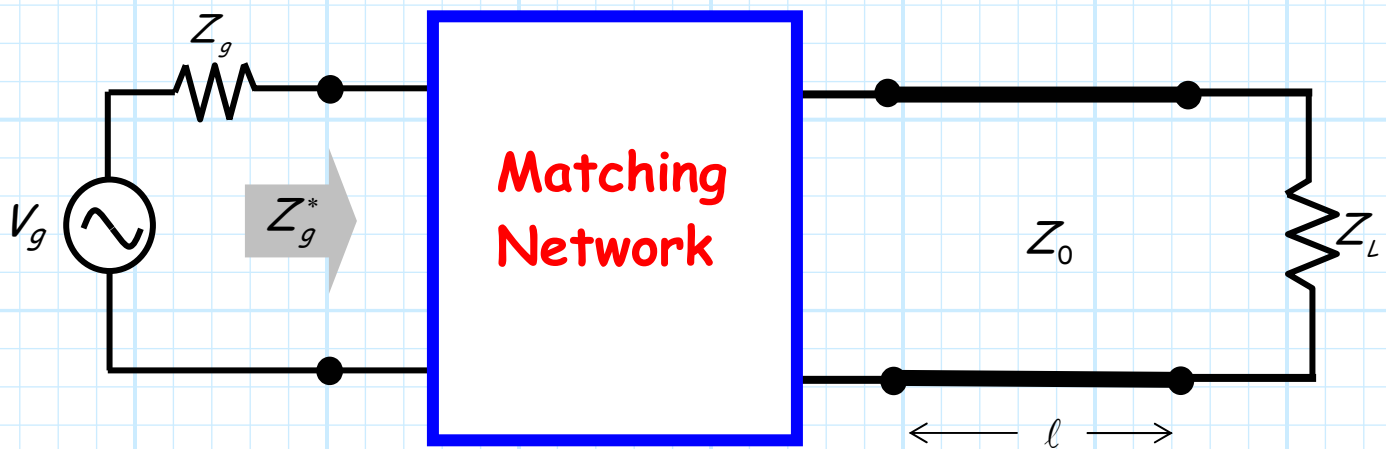For example, we can construct a network to transform the **input impedance** of the transmission line into the complex conjugate of the **source impedance**:




**Q:** *But, do we have to place the matching network between the source and the transmission line?*

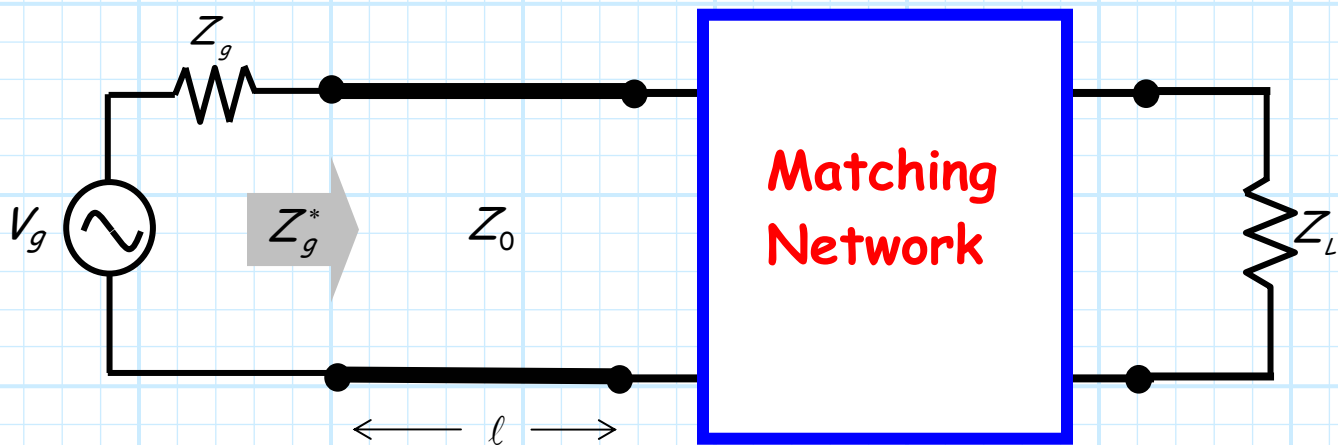**A:** Nope! We could also place a (different) matching network between the transmission line and the load.



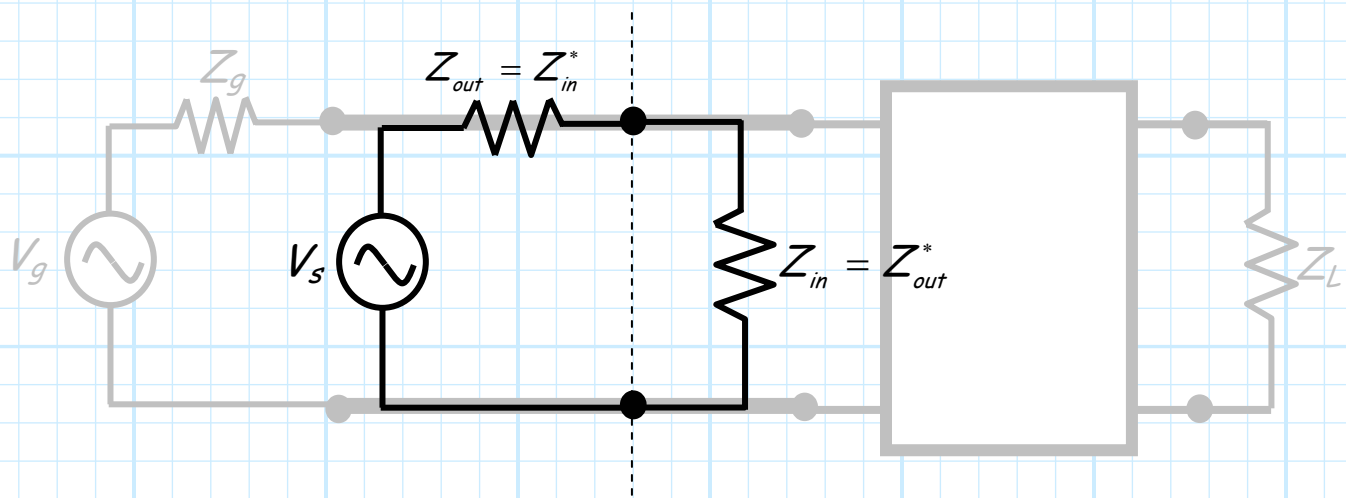
In either case, we find that at **any** and **all** points along this matched circuit, the output impedance of the equivalent **source** (i.e., looking left) will be equal to the **complex conjugate** of the **input impedance** (i.e., looking right).




**Q:** So which method should we choose? Do engineers typically place the matching network between the source and the transmission line, or place it between the transmission line and the load?

**A:** Actually, the typical solution is to do **both**!

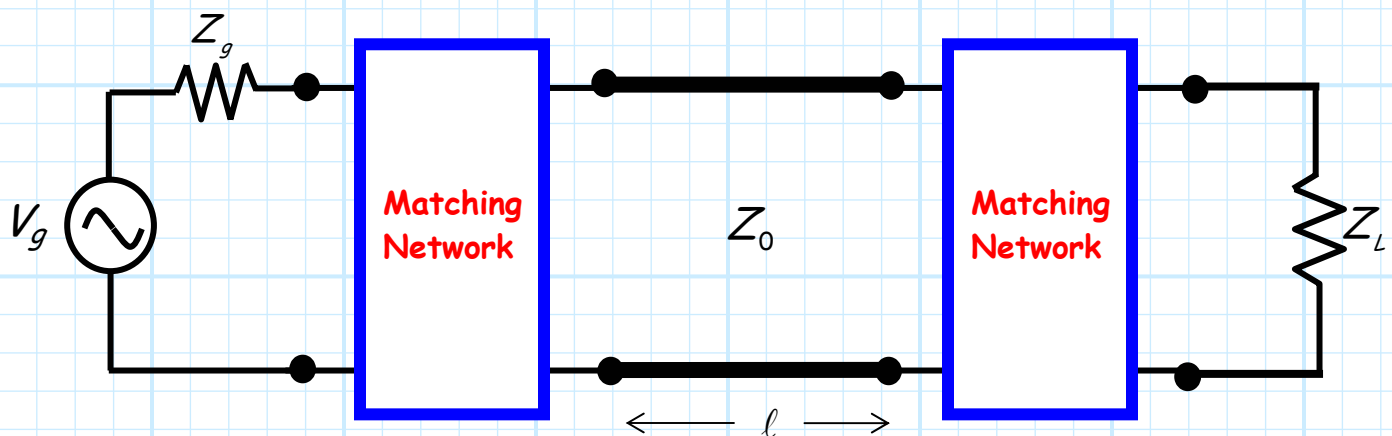
We find that often there is a matching network between the a source and the transmission line, **and** between the line and the load.



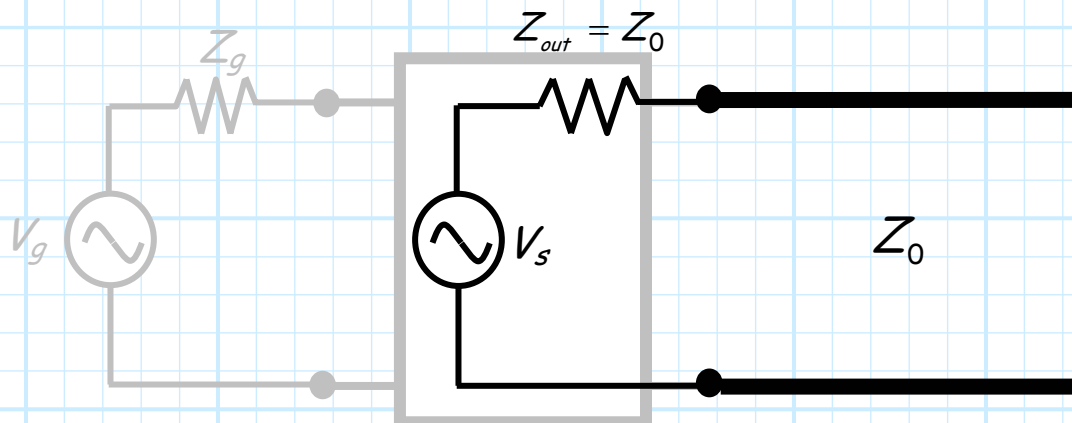The first network matches the **source** to the **transmission line**—in other words, it transforms the **output impedance** of the equivalent source to a value numerically equal to **characteristic impedance  $Z_0$** :



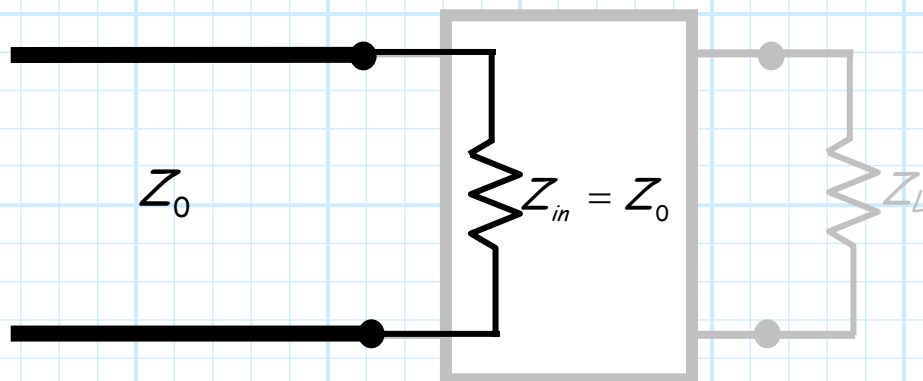The second network matches the **load** to the **transmission line**—in other words it transforms the **load impedance** to a value numerically equal to **characteristic impedance  $Z_0$** :



**Q:** *Yikes! Why would we want to build **two** separate matching networks, instead of just **one**?*



**A:** By using two separate matching networks, we can **decouple** the design problem. Recall again that the design of a **single** matching network solution would depend on four separate parameters:

1. the source impedance  $Z_g$ .
2. load impedance  $Z_L$ .
3. the transmission line characteristic impedance  $Z_0$ .
4. the transmission line length  $\ell$ .

Alternatively, the design of the network matching the **source** and **transmission line** depends on **only**:

1. the load impedance  $Z_g$ .
2. the transmission line characteristic impedance  $Z_0$ .

Whereas, the design of the network matching the **load** and **transmission line** depends on **only**:

1. the source impedance  $Z_L$ .
2. the transmission line characteristic impedance  $Z_0$ .

Note that **neither** design depends on the transmission line **length**  $\ell$ !

**Q:** *How is that possible?*

**A:** Remember the case where  $Z_g = Z_0 = Z_L$ . For that **special** case, we found that a conjugate match was the result—**regardless** of the transmission line length.

Thus, by matching the source to line impedance  $Z_0$  **and** likewise matching the load to the line impedance, a conjugate match is **assured**—but the **length** of the transmission line does **not** matter!

In fact, the typically problem for microwave engineers is to match a load (e.g., device input impedance) to a **standard** transmission line impedance (typically  $Z_0 = 50\Omega$ ); **or** to independently match a source (e.g., device output impedance) to a **standard** line impedance.

A **conjugate match** is thus obtained by connecting the two with a transmission line of **any length**!

