

Special Problem 3.B-4

For a specific frequency, an **amplifier** has a scattering matrix of the form:

$$\mathbf{S} = \begin{pmatrix} 0.01 & 0.001 \\ 15.0 & 0.01 \end{pmatrix}$$

What is this amplifier's **gain** and **reverse isolation**??