## Special Problem 3.G-4

Incident on one port of a directional coupler is a signal with power 10.0 mW. No power is exiting (i.e., reflected from) this port.

No other signals are incident on this device.

Exiting the three other ports of the coupler are signals of 7.0 mW, 2.5 mW, and 0.01 mW.

Determine the Coupling, Insertion Loss, and Directivity of this coupler.

Jim Stiles The Univ. of Kansas Dept. of EECS