

Special Problem 4.D-2

For the design below, determine the **largest possible** value of P_{in} such that **none** of the three devices are in saturation.

