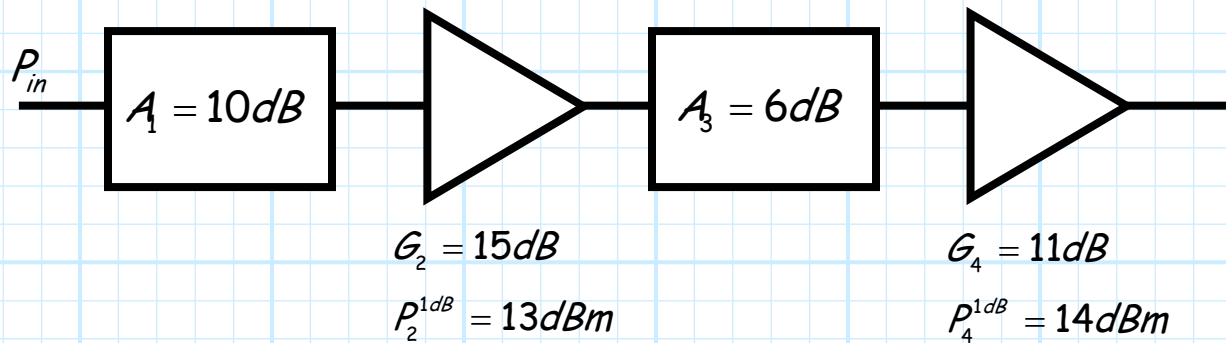


Special Problem 4.D-7

The following microwave network consists of **two amplifiers** and **two attenuators**.



Determine the value of **input** power P_{in} that will cause this network to **saturate**.