

Special Problem II.A-26

Say you require a filter with a **center frequency** $f_o = 1.0 \text{ GHz}$, and **bandwidth** $\Delta f = 100 \text{ MHz}$.

You need the attenuation of the filter to be **40 dB** at $f = 1.1 \text{ GHz}$

1. Determine the filter **order** required for a:

- a) Butterworth Filter
- b) Chebychev with 0.5 dB passband ripple.
- c) Chebychev with 3.0 dB passband ripple.

2. Using the results in part 1, determine the filter **attenuation** at $f = 930 \text{ MHz}$ for **each** of the three filter designs.