### 2.1 - The Lumped Element Circuit Model for Transmission Lines

Reading Assignment: pp. 1-5, 49-52

Q: So just what is a transmission line?

Q: Oh, so it's simply a conducting wire, right?

**A**:

**A**:

 $\rightarrow$ 

### HO: The Telegraphers Equations

**Q:** So, what complex functions I(z) and V(z) **do** satisfy both telegrapher equations?

**A**:

HO: The Transmission Line Wave Equations

**Q:** Are the solutions for I(z) and V(z) completely independent, or are they related in any way ?

**A**:

#### HO: The Transmission Line Characteristic Impedance

**Q:** So what is the significance of the complex constant  $\gamma$ ? What does it tell us?

**A**:

### HO: The Complex Propagation Constant

**Q:** Is characteristic impedance  $Z_0$  the same as the concept of impedance I learned about in circuits class?

**A**:

### HO: Line Impedance

**Q:** These wave functions  $V^+(z)$  and  $V^-(z)$  seem to be important. How are they related?

**A**:

### HO: The Reflection Coefficient

Jim Stiles

**Q:** Now, you said earlier that characteristic impedance  $Z_0$  is a complex value. But I recall engineers referring to a transmission line as simply a "50 Ohm line", or a "300 Ohm line". But these are real values; are they not referring to characteristic impedance  $Z_0$ ??

**A**:

#### HO: The Lossless Transmission Line

## The Telegrapher Equations

Consider a section of "wire":



**Q**: Huh ?! Current *i* and voltage *v* are a function of **position** *z* ?? Shouldn't  $i(z,t) = i(z + \Delta z,t)$  and  $v(z,t) = v(z + \Delta z,t)$  ?

A: NO ! Because a wire is never a **perfect** conductor.

A "wire" will have:

- 1) Inductance
- 2) Resistance
- 3) Capacitance
- 4) Conductance



Dividing the first equation by  $\Delta z$ , and then taking the limit as  $\Delta z \rightarrow 0$ :

$$\lim_{\Delta z \to 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial \mathbf{v}(\mathbf{z},t)}{\partial \mathbf{z}} = -\mathbf{R}\,\mathbf{i}(\mathbf{z},t) - L\frac{\partial \mathbf{i}(\mathbf{z},t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z,t)}{\partial z} = -\mathcal{G}v(z,t) - \mathcal{C}\frac{\partial v(z,t)}{\partial t}$$

If v(z,t) and i(z,t) have the form:

$$V(z,t) = \operatorname{Re}\left\{V(z)e^{j\omega t}\right\}$$
 and  $i(z,t) = \operatorname{Re}\left\{I(z)e^{j\omega t}\right\}$ 

then these equations become:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(\mathcal{G} + j\omega \mathcal{C}) V(z)$$

These equations are known as the telegrapher's equations !

\* The functions I(z) and V(z) are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function  $e^{j\omega t}$ .

\* Thus, I(z) and V(z) describe the current and voltage along the transmission line, as a function as position z.

 Remember, not just any function I(z) and V(z) can exist on a transmission line, but rather only those functions that satisfy the telegraphers equations.

> Our task, therefore, is to solve the telegrapher equations and find **all** solutions I(z) and V(z)!

## <u>The Transmission Line</u> <u>Wave Equation</u>

**Q:** So, what functions I (z) and V (z) **do** satisfy both telegrapher's equations??

A: To make this easier, we will combine the telegrapher equations to form one differential equation for V(z) and another for I(z).

First, take the **derivative** with respect to z of the **first** telegrapher equation:

$$\frac{\partial}{\partial z} \left\{ \frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z) \right\}$$
$$= \frac{\partial^2 V(z)}{\partial z^2} = -(R + j\omega L) \frac{\partial I(z)}{\partial z}$$

Note that the **second** telegrapher equation expresses the derivative of I(z) in terms of V(z):

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$

Combining these two equations, we get an equation involving V(z) only:



where it is apparent that:

$$\gamma^2 \doteq (R + j\omega L)(G + j\omega C)$$

In a **similar** manner (i.e., begin by taking the derivative of the **second** telegrapher equation), we can derive the differential equation:

$$\frac{\partial^2 I(z)}{\partial z} = \gamma^2 I(z)$$

We have **decoupled** the telegrapher's equations, such that we now have **two** equations involving **one** function only:

$$\frac{\partial^2 V(z)}{\partial z} = \gamma^2 V(z)$$

$$\frac{\partial^2 I(z)}{\partial z} = \gamma^2 I(z)$$

Note only **special** functions satisfy these equations: if we take the double derivative of the function, the result is the **original function** (to within a constant)!

Jim Stiles

**Q:** Yeah right! Every function that **I** know is **changed** after a double differentiation. What kind of "magical" function could possibly satisfy this differential equation?

A: Such functions do exist!

For example, the functions  $V(z) = e^{-\gamma z}$  and  $V(z) = e^{+\gamma z}$  each satisfy this transmission line wave equation (insert these into the differential equation and see for yourself!).

Likewise, since the transmission line wave equation is a linear differential equation, a weighted superposition of the two solutions is also a solution (again, insert this solution to and see for yourself!):

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

In fact, it turns out that **any** and **all** possible solutions to the differential equations can be expressed in **this** simple form!

Therefore, the **general** solution to these wave equations (and thus the telegrapher equations) are:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

where  $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ ,  $I_0^-$ , and  $\gamma$  are complex constants.

 $\rightarrow$  It is unfathomably important that you understand what this result means!

It means that the functions V(z) and I(z), describing the current and voltage at **all** points z along a transmission line, can **always** be **completely** specified with just **four complex constants**  $(V_0^+, V_0^-, I_0^+, I_0^-)!!$ 

We can alternatively write these solutions as:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = I^+(z) + I^-(z)$$

where:

$$V^{+}(z) \doteq V_{0}^{+} e^{-\gamma z}$$
  $V^{-}(z) \doteq V_{0}^{-} e^{+\gamma z}$ 

 $I^+(z) \doteq I_0^+ e^{-\gamma z}$ 

 $I^{-}(z) \doteq I_{0}^{-} e^{+\gamma z}$ 

The two terms in each solution describe **two waves** propagating in the transmission line, **one** wave  $(V^+(z) \text{ or } I^+(z))$  propagating in one direction (+z) and the **other** wave  $(V^-(z) \text{ or } I^-(z))$ propagating in the **opposite** direction (-z).

$$V^{-}(z) = V_{0}^{-} e^{+\gamma z}$$
  
 $V^{+}(z) = V_{0}^{+} e^{-\gamma z}$ 

Therefore, we call the differential equations introduced in this handout the **transmission line wave equations**.

### Q: So just what are the complex values $V_0^+$ , $V_0^-$ , $I_0^+$ , $I_0^-$ ?

A: Consider the wave solutions at **one** specific point on the transmission line—the point z = 0. For example, we find that:

$$V^{+}(z = 0) = V_{0}^{+} e^{-\gamma(z=0)}$$
$$= V_{0}^{+} e^{-(0)}$$
$$= V_{0}^{+}(1)$$
$$= V_{0}^{+}$$

In other words,  $V_0^+$  is simply the **complex** value of the wave function  $V^+(z)$  at the point z=0 on the transmission line!

Z

 $V_0^- = V^- (z = 0)$ 

 $I_0^+ = I^+ (z = 0)$ 

Likewise, we find:

 $\mathcal{I}_0^- = \mathcal{I}^- \big( z = 0 \big)$ 

Again, the four complex values  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are **all** that is needed to determine the voltage and current at any and all points on the transmission line.

More specifically, **each** of these four complex constants completely specifies **one** of the four transmission line wave functions  $V^+(z)$ ,  $I^+(z)$ ,  $V^-(z)$ ,  $I^-(z)$ .

**Q:** But what **determines** these wave functions? How do we **find** the values of constants  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$ ?

A: As you might expect, the voltage and current on a transmission line is determined by the devices **attached** to it on either end (e.g., active sources and/or passive loads)!

The precise values of  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are therefore determined by satisfying the **boundary conditions** applied at **each end** of the transmission line—much more on this **later**!

#### 1/4

# <u>The Characteristic</u> <u>Impedance of a</u> <u>Transmission Line</u>

So, from the telegrapher's differential equations, we know that the complex current I(z) and voltage V(z) must have the form:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$

Let's insert the expression for V(z) into the first telegrapher's equation, and see what happens !

$$\frac{dV(z)}{dz} = -\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{+\gamma z} = -(R + j\omega L)I(z)$$

Therefore, rearranging, I(z) must be:

$$I(z) = \frac{\gamma}{R+j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{+\gamma z})$$

Jim Stiles







Thus, we come to the **startling** conclusion that:

$$\frac{\mathcal{V}^{+}(z)}{\mathcal{I}^{+}(z)} = \sqrt{\frac{\mathcal{R} + j\omega\mathcal{L}}{\mathcal{G} + j\omega\mathcal{C}}} \quad \text{and} \quad \frac{-\mathcal{V}^{-}(z)}{\mathcal{I}^{-}(z)} = \sqrt{\frac{\mathcal{R} + j\omega\mathcal{L}}{\mathcal{G} + j\omega\mathcal{C}}}$$

### Q: What's so startling about this conclusion?

A: Note that although the magnitude and phase of each propagating wave is a function of transmission line position z (e.g.,  $V^+(z)$  and  $I^+(z)$ ), the ratio of the voltage and current of each wave is independent of position—a constant with respect to position z!

Although  $V_0^{\pm}$  and  $I_0^{\pm}$  are determined by **boundary conditions** (i.e., what's connected to either end of the transmission line), the **ratio**  $V_0^{\pm}/I_0^{\pm}$  is determined by the parameters of the transmission line **only** (*R*, *L*, *G*, *C*).

 $\rightarrow$  This ratio is an important characteristic of a transmission line, called its Characteristic Impedance Z<sub>0</sub>.

$$Z_{0} \doteq \frac{V_{0}}{I_{0}} = \frac{-V_{0}}{I_{0}} = \sqrt{\frac{R + j\omega L}{\mathcal{G} + j\omega \mathcal{C}}}$$
We can therefore describe the current and voltage along a transmission line as:  

$$V(z) = V_{0}^{+} e^{-\gamma z} + V_{0}^{-} e^{+\gamma z}$$

$$I(z) = \frac{V_{0}^{+}}{Z_{0}} e^{-\gamma z} - \frac{V_{0}^{-}}{Z_{0}} e^{+\gamma z}$$
or equivalently:  

$$V(z) = Z_{0} I_{0}^{+} e^{-\gamma z} - Z_{0} I_{0}^{-} e^{+\gamma z}$$

$$I(z) = I_{0}^{+} e^{-\gamma z} + I_{0}^{-} e^{+\gamma z}$$
Note that instead of characterizing a transmission line with real parameters *R*, *G*, *L*, and *C*, we can (and typically do!) describe a transmission line using complex parameters Z\_{0} and  $\gamma$ .

## The Complex Propagation

### <u>Constant $\gamma$ </u>

Recall that the current and voltage along a transmission line have the form:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z}$$

where  $Z_0$  and  $\gamma$  are **complex constants** that describe the properties of a transmission line. Since  $\gamma$  is complex, we can consider both its **real** and **imaginary** components.

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$
$$\doteq \alpha + j\beta$$

where  $\alpha = Re\{\gamma\}$  and  $\beta = Im\{\gamma\}$ . Therefore, we can write:

$$e^{-\gamma z} = e^{-(\alpha + j\beta) z} = e^{-\alpha z} e^{-j\beta z}$$

Since  $|e^{-j\beta z}|=1$ , then  $e^{-\alpha z}$  alone determines the magnitude of  $e^{-\gamma z}$ .



Therefore,  $\alpha$  expresses the **attenuation** of the signal due to the loss in the transmission line.

Since  $e^{-\alpha z}$  is a real function, it expresses the **magnitude** of  $e^{-\gamma z}$  only. The **relative phase**  $\phi(z)$  of  $e^{-\gamma z}$  is therefore determined by  $e^{-j\beta z} = e^{-j\phi(z)}$  only (recall  $|e^{-j\beta z}| = 1$ ).

From Euler's equation:

$$e^{j\phi(z)} = e^{j\beta z} = cos(\beta z) + j sin(\beta z)$$

Therefore,  $\beta z$  represents the **relative phase**  $\phi(z)$  of the oscillating signal, as a function of transmission line position z. Since phase  $\phi(z)$  is expressed in radians, and z is distance (in meters), the value  $\beta$  must have units of :

$$\beta = \frac{\phi}{z}$$
  $\frac{radians}{meter}$ 

ł

The wavelength  $\lambda$  of the signal is the distance  $\Delta z_{2\pi}$  over which the relative phase changes by  $2\pi$  radians. So:

$$2\pi = \phi(z + \Delta z_{2\pi}) - \phi(z) = \beta \Delta z_{2\pi} = \beta \lambda$$

or, rearranging:

$$\beta = \frac{2\pi}{\lambda}$$

Since the signal is oscillating in time at rate  $\omega$  rad/sec, the propagation velocity of the wave is:

$$v_p = \frac{\omega}{\beta} = \frac{\omega\lambda}{2\pi} = f\lambda$$
  $\left(\frac{m}{\sec} = \frac{rad}{\sec}\frac{m}{rad}\right)$ 

where f is frequency in cycles/sec.

Recall we originally considered the transmission line current and voltage as a function of time and position (i.e., v(z,t) and i(z,t)). We assumed the time function was sinusoidal, oscillating with frequency  $\omega$ :

$$V(z,t) = Re\{V(z)e^{j\omega t}\}$$

$$i(z,t) = Re \{I(z)e^{j\omega t}\}$$

Jim Stiles

Now that we **know** V(z) and I(z), we can write the original functions as:

$$v(z,t) = Re\left\{V_0^+ e^{-\alpha z} e^{-j(\beta z - \omega t)} + V_0^- e^{\alpha z} e^{j(\beta z + \omega t)}\right\}$$

$$i(z,t) = \mathbf{Re} \left\{ \frac{V_0^+}{Z_0} e^{-\alpha z} e^{-j(\beta z - \omega t)} - \frac{V_0^+}{Z_0} e^{\alpha z} e^{j(\beta z + \omega t)} \right\}$$

The first term in each equation describes a wave **propagating** in the +z direction, while the second describes a wave propagating in the **opposite** (-z) direction.

### <u>Line Impedance</u>

Now let's define line impedance Z(z), which is simply the ratio of the complex line voltage and complex line current:

$$Z(z) = \frac{V(z)}{I(z)}$$

**Q:** Hey! I know what this is! The ratio of the voltage to current is simply the characteristic impedance  $Z_0$ , right ???

A: NO! The line impedance Z(z) is (generally speaking) NOT the transmission line characteristic impedance  $Z_0 \parallel \parallel$ 

It is unfathomably important that you understand this!!!!

To see why, recall that:

$$V(z) = V^+(z) + V^-(z)$$



This is actually confirmed by the equation above. Say that  $V^{-}(z) = 0$ , so that only **one** wave  $(V^{+}(z))$  is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance**  $Z_0$ !

 $Z(z) = \frac{V(z)}{I(z)} = Z_0\left(\frac{V^+(z)}{V^+(z)}\right) = \frac{V^+(z)}{I^+(z)} = Z_0 \quad \text{(when } V^+(z)\text{)}$ 

**Q:** So, it appears to me that characteristic impedance  $Z_0$  is a **transmission line parameter**, depending **only** on the transmission line values R, G, L, and C.

Whereas line impedance is Z(z) depends the magnitude and phase of the two propagating waves  $V^+(z)$  and  $V^-(z)$ --values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!

Right !?

A: Exactly! Moreover, note that characteristic impedance  $Z_0$  is simply a number, whereas line impedance Z(z) is a function of position (z) on the transmission line.

## The Reflection Coefficient

So, we know that the transmission line voltage V(z) and the transmission line current I(z) can be related by the line impedance Z(z):

$$V(z) = Z(z) I(z)$$

or equivalently:

 $I(z) = \frac{V(z)}{Z(z)}$ 

Expressing the "activity" on a transmission line in terms of voltage, current and impedance is of course **perfectly** valid. However, let us look **closer** at the expression for each of these quantities:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = \frac{V^{+}(z) - V^{-}(z)}{Z_{0}}$$

$$Z(z) = Z_0 \left( \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right)$$

It is evident that we can **alternatively** express all "activity" on the transmission line in terms of the two transmission line **waves**  $V^+(z)$  and  $V^-(z)$ .

In other words, we can describe transmission line activity in terms of:

$$V^{\scriptscriptstyle +}(z)$$
 and  $V^{\scriptscriptstyle -}(z)$ 

instead of:

$$V(z)$$
 and  $I(z)$ 

**Q:** But V(z) and I(z) are related by line impedance Z(z):

$$Z(z) = \frac{V(z)}{I(z)}$$

How are  $V^{+}(z)$  and  $V^{-}(z)$  related?

A: Similar to line impedance, we can define a new parameter the **reflection coefficient**  $\Gamma(z)$ --as the **ratio** of the two quantities:

$$\Gamma(\boldsymbol{z}) \doteq \frac{\boldsymbol{V}^{-}(\boldsymbol{z})}{\boldsymbol{V}^{+}(\boldsymbol{z})}$$

More specifically, we can express  $\Gamma(z)$  as:

$$\Gamma(z) = \frac{V_0^- e^{+\gamma z}}{V_0^+ e^{-\gamma z}} = \frac{V_0^-}{V_0^+} e^{+2\gamma z}$$

Note then, the value of the reflection coefficient at z=0 is:

$$\Gamma(z = 0) = \frac{V_0^{-}}{V_0^{+}} e^{+2\gamma(0)}$$
$$= \frac{V_0^{-}}{V_0^{+}}$$

We define this value as  $\Gamma_0$ , where:

$$\Gamma_{0} \doteq \Gamma(z=0) = \frac{V_{0}^{-}}{V_{0}^{+}}$$

Note then that we can alternatively write  $\Gamma(z)$  as:

$$\Gamma(\boldsymbol{Z}) = \Gamma_0 \boldsymbol{e}^{+2\gamma \boldsymbol{Z}}$$



Look what happened—the line impedance can be completely and explicitly expressed in terms of reflection coefficient $\Gamma(z)$ !

Or, rearranging, we find that the reflection coefficient  $\Gamma(z)$  can likewise be written in terms of line impedance:

$$\Gamma(\boldsymbol{z}) = \frac{Z(\boldsymbol{z}) - Z_0}{Z(\boldsymbol{z}) + Z_0}$$

Thus, the values  $\Gamma(z)$  and Z(z) are **equivalent** parameters if we know **one**, then we can determine the **other**!

Likewise, the relationships:

$$V(z) = Z(z) I(z)$$

and:

$$\mathcal{V}^{-}(\boldsymbol{z}) = \Gamma(\boldsymbol{z}) \mathcal{V}^{+}(\boldsymbol{z})$$

are equivalent relationships—we can use either when describing an transmission line.

> Based on circuits experience, you might be **tempted** to always use the **first** relationship. However, we will find that it is also **very** useful (as well as simple) to describe activity on a transmission line in terms of the **second** relationship—in terms of the **two** propagating transmission line **waves**!

### <u>The Lossless</u> Transmission Line

Say a transmission line is **lossless** (i.e., *R=G*=0); the transmission line equations are then **significantly** simplified!

Characteristic Impedance

$$Z_{0} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$
$$= \sqrt{\frac{j\omega L}{j\omega C}}$$
$$= \sqrt{\frac{L}{C}}$$

Note the characteristic impedance of a lossless transmission line is purely real (i.e.,  $Im\{Z_0\}=0$ )!

Propagation Constant

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$
$$= \sqrt{(j\omega L)(j\omega C)}$$
$$= \sqrt{-\omega^2 LC}$$
$$= j\omega \sqrt{LC}$$

The wave propagation constant is purely **imaginary**!

In other words, for a lossless transmission line:

 $\alpha = 0$  and  $\beta = \omega \sqrt{LC}$ 

#### Voltage and Current

The **complex functions** describing the magnitude and phase of the voltage/current at every location *z* along a transmission line are for a **lossless** line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

### Line Impedance

The complex function describing the impedance at every point along a lossless transmission line is:

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

Reflection Coefficient

The **complex function** describing the reflection at every point along a **lossless** transmission line is:

$$\Gamma(z) = \frac{V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

### Wavelength and Phase Velocity

We can now **explicitly** write the wavelength and propagation velocity of the two transmission line waves in terms of transmission line parameters *L* and *C*:

 $\lambda = \frac{2\pi}{\beta} = \frac{1}{f\sqrt{LC}}$ 

 $v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{IC}}$ 



**Q:** Oh **please**, continue wasting my valuable time. We both know that a **perfectly** lossless transmission line is a physical **impossibility**.

A: True! However, a low-loss line is possible—in fact, it is typical! If  $R \ll \omega L$  and  $G \ll \omega C$ , we find that the lossless transmission line equations are excellent approximations!

Unless otherwise indicated, we will use the lossless equations to **approximate** the behavior of a **low-loss** transmission line.

The lone **exception** is when determining the attenuation of a **long** transmission line. For that case we will use the approximation:

where  $Z_0 = \sqrt{L/C}$ .

<u>A summary of lossless transmission line equations</u>

 $\alpha \approx \frac{1}{2} \left( \frac{R}{Z_0} + GZ_0 \right)$ 

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\gamma = j\omega\sqrt{LC}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

$$Z(z) = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

$$V^{+}(z) = V_{0}^{+} e^{-j\beta z}$$
  $V^{-}(z) = V_{0}^{-} e^{+j\beta z}$ 

$$\Gamma(\boldsymbol{z}) = \frac{\boldsymbol{V}_0^-}{\boldsymbol{V}_0^+} \boldsymbol{e}^{+j^2\beta \boldsymbol{z}}$$

$$\beta = \omega \sqrt{LC} \qquad \qquad \lambda = \frac{1}{f \sqrt{LC}}$$

$$v_{p} = \frac{1}{\sqrt{LC}}$$

The Univ. of Kansas