

2.3 - The Terminated, Lossless Transmission Line

Reading Assignment: pp. 56-63

We now know that a **lossless** transmission line is **completely** characterized by **real** constants Z_0 and β .

Likewise, the **2 waves** propagating on a transmission line are **completely** characterized by **complex** constants V_0^+ and V_0^- .

Q: Z_0 and β are determined from L , C , and ω . How do we find V_0^+ and V_0^- ?

A: Apply **Boundary Conditions!**

Every transmission line has **2 "boundaries"**

- 1) At one end of the transmission line.
- 2) At the **other** end of the trans line!

Typically, there is a **source** at one end of the line, and a **load** at the other.

→ The purpose of the transmission line is to get power **from** the source, **to** the load!

Let's apply the **load** boundary condition!

HO: THE TERMINATED, LOSSLESS TRANSMISSION LINE

Q: *So, the purpose of the transmission line is to transfer E.M. energy from the source to the load. Exactly how much power is flowing in the transmission line, and how much is delivered to the load?*

A: HO: INCIDENT, REFLECTED, AND ABSORBED POWER

Let's look at several "special" values of **load impedance**, as well as the interesting transmission line behavior they create.

HO: SPECIAL VALUES OF LOAD IMPEDANCE

Q: *So the line impedance at the **end** of a line must be load impedance Z_L (i.e., $Z(z = z_L) = Z_L$); what is the line impedance at the **beginning** of the line (i.e., $Z(z = z_L - \ell) = ?$)?*

A: The input impedance !

HO: TRANSMISSION LINE INPUT IMPEDANCE

EXAMPLE: INPUT IMPEDANCE

Q: *For a given Z_L we can determine an equivalent Γ_L . Is there an equivalent Γ_{in} for each Z_{in} ?*

A: HO: THE REFLECTION COEFFICIENT TRANSFORMATION

Note that we can **specify** a load with its impedance Z_L or equivalently, its reflection coefficient Γ_L .

Q: *But these are both complex values. Isn't there a way of specifying a load with a real value?*

A: Yes (sort of)! The two most common methods are Return Loss and **VSWR**.

HO: RETURN LOSS AND VSWR

Q: *What happens if our transmission line is terminated by something **other** than a load? Is our transmission line theory **still** valid?*

A: As long as a transmission line is connected to linear devices our theory is valid. However, we must be careful to properly apply the **boundary conditions** associated with each linear device!

EXAMPLE: THE TRANSMISSION COEFFICIENT

EXAMPLE: APPLYING BOUNDARY CONDITIONS

EXAMPLE: ANOTHER BOUNDARY CONDITION PROBLEM