

## 2.3 - The Terminated, Lossless Transmission Line

**Reading Assignment:** pp. 57-64

We now know that a **lossless** transmission line is **completely** characterized by **real** constants  $Z_0$  and  $\beta$ .

Likewise, the **2 waves** propagating on a transmission line are **completely** characterized by **complex** constants  $V_0^+$  and  $V_0^-$ .

**Q:**  $Z_0$  and  $\beta$  are determined from  $L$ ,  $C$ , and  $\omega$ . How do we find  $V_0^+$  and  $V_0^-$ ?

**A:**

Every transmission line has 2 "boundaries"

- 1)
- 2)

Typically, there is a **source** at one end of the line, and a **load** at the other.

→

Let's apply the **load** boundary condition!

## HO: The Terminated, Lossless Transmission Line

### HO: Special Values of Load Impedance

**Q:** *So the line impedance at the **end** of a line must be load impedance  $Z_L$  (i.e.,  $Z(z = z_L) = Z_L$ ); what is the line impedance at the **beginning** of the line (i.e.,  $Z(z = z_L - \ell) = ?$ )?*

**A:**

### HO: Transmission Line Input Impedance

#### Example: Input Impedance

**Q:** *For a given  $Z_L$  we can determine an equivalent  $\Gamma_L$ . Is there an equivalent  $\Gamma_{in}$  for each  $Z_{in}$ ?*

**A:** HO: The Reflection Coefficient Transformation

**Q:** *So, the purpose of the transmission line is to transfer **E.M. energy** from the source to the load. Exactly how much **power** is flowing in the transmission line, and how much is **delivered** to the load?*

**A:** HO: Power Flow and Return Loss

Note that we can **specify** a load with:

- 1)
- 2)
- 3)

### HO: VSWR

**Q:** *What happens if our transmission line is terminated by something **other** than a load? Is our transmission line theory **still** valid?*


**A:** As long as a transmission line is connected to linear devices our theory is valid. However, we must be careful to properly apply the **boundary conditions** associated with each linear device!

### Example: The Transmission Coefficient

### Example: Applying Boundary Conditions
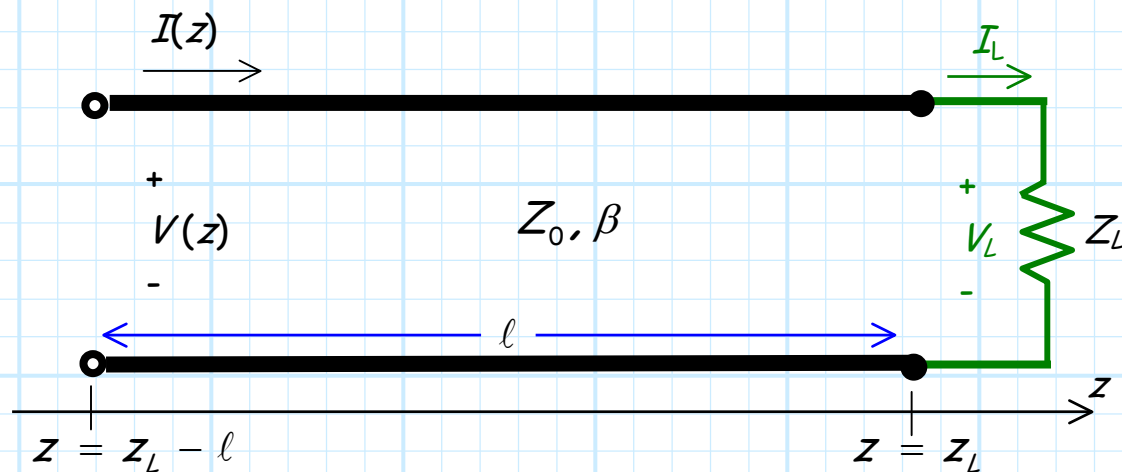
# The Terminated, Lossless Transmission Line

Now let's **attach** something to our transmission line. Consider a **lossless** line, length  $\ell$ , terminated with a load  $Z_L$ .



**Q:** What is the **current** and **voltage** at each and **every** point on the transmission line (i.e., what is  $I(z)$  and  $V(z)$  for **all** points  $z$  where  $z_L - \ell \leq z \leq z_L$  )?

**A:** To find out, we must apply **boundary conditions**!

In other words, at the **end** of the transmission line ( $z = z_L$ )—where the load is **attached**—we have **many** requirements that **all** must be satisfied!

1. To begin with, the voltage and current ( $I(z = z_L)$  and  $V(z = z_L)$ ) must be consistent with a valid **transmission line solution**:


$$\begin{aligned} V(z = z_L) &= V^+(z = z_L) + V^-(z = z_L) \\ &= V_0^+ e^{-j\beta z_L} + V_0^- e^{+j\beta z_L} \end{aligned}$$

$$\begin{aligned} I(z = z_L) &= \frac{V_0^+(z = z_L)}{Z_0} - \frac{V_0^-(z = z_L)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta z_L} - \frac{V_0^-}{Z_0} e^{+j\beta z_L} \end{aligned}$$

2. Likewise, the load voltage and current must be related by **Ohm's law**:

$$V_L = Z_L I_L$$

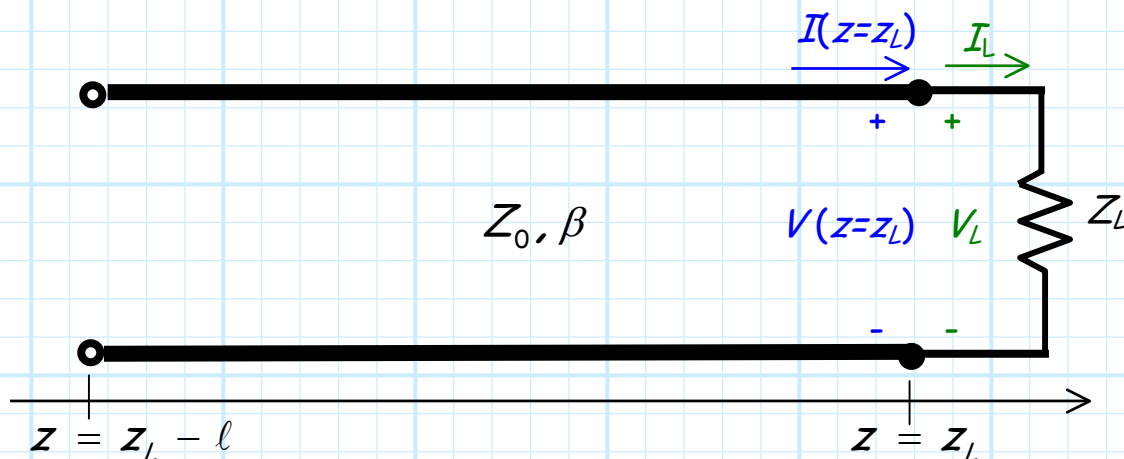3. Most importantly, we recognize that the values  $I(z = z_L)$ ,  $V(z = z_L)$  and  $I_L$ ,  $V_L$  are **not** independent, but in fact are strictly related by **Kirchoff's Laws**!




From KVL and KCL we find these requirements:

$$V(z = z_L) = V_L$$

$$I(z = z_L) = I_L$$

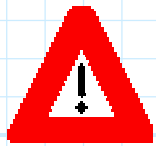These are the **boundary conditions** for **this** particular problem.



→ **Careful!** Different transmission line problems lead to **different** boundary conditions—you must access each problem **individually** and **independently**!

**Combining** these equations and boundary conditions, we find that:

$$V_L = Z_L I_L$$

$$V(z = z_L) = Z_L I(z = z_L)$$

$$V^+(z = z_L) + V^-(z = z_L) = \frac{Z_L}{Z_0} (V^+(z = z_L) - V^-(z = z_L))$$

Rearranging, we can conclude:

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

**Q:** Hey wait as second! We earlier defined  $V^-(z)/V^+(z)$  as **reflection coefficient**  $\Gamma(z)$ . How does this relate to the expression above?

**A:** Recall that  $\Gamma(z)$  is a **function** of transmission line position  $z$ . The value  $V^-(z = z_L)/V^+(z = z_L)$  is simply the value of function  $\Gamma(z)$  **evaluated** at  $z = z_L$  (i.e., evaluated at the **end** of the line):

$$\frac{V^-(z = z_L)}{V^+(z = z_L)} = \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

This value is of **fundamental** importance for the terminated transmission line problem, so we provide it with its **own** special symbol ( $\Gamma_L$ )!

$$\Gamma_L \doteq \Gamma(z = z_L) = \frac{Z_L - Z_0}{Z_L + Z_0}$$

**Q:** Wait! We **earlier** determined that:

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$

so it would seem that:

$$\Gamma_L = \Gamma(z = z_L) = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

**Which expression is correct??**

**A:** They **both** are! It is evident that the two expressions:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and} \quad \Gamma_L = \frac{Z(z = z_L) - Z_0}{Z(z = z_L) + Z_0}$$

are **equal** if:

$$Z(z = z_L) = Z_L$$

And since we know that from **Ohm's Law**:

$$Z_L = \frac{V_L}{I_L}$$

and from **Kirchoff's Laws**:

$$\frac{V_L}{I_L} = \frac{V(z = z_L)}{I(z = z_L)}$$

and that **line impedance** is:

$$\frac{V(z = z_L)}{I(z = z_L)} = Z(z = z_L)$$


we find it apparent that the **line impedance** at the **end** of the transmission line is **equal** to the **load impedance**:

$$Z(z = z_L) = Z_L$$

The above expression is essentially **another** expression of the **boundary condition** applied at the **end** of the transmission line.



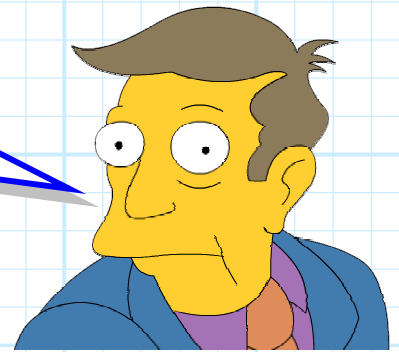**Q:** *I'm confused! Just what are we trying to accomplish in this handout?*



**A:** We are trying to find  $V(z)$  and  $I(z)$  when a lossless transmission line is terminated by a load  $Z_L$ !

We can now determine the value of  $V_0^-$  in terms of  $V_0^+$ . Since:

$$\Gamma_L = \frac{V^-(z=z_L)}{V^+(z=z_L)} = \frac{V_0^- e^{+j\beta z_L}}{V_0^+ e^{-j\beta z_L}}$$

We find:

$$V_0^- = e^{-2j\beta z_L} \Gamma_L V_0^+$$

And therefore we find:

$$V^-(z) = (e^{-2j\beta z_L} \Gamma_L V_0^+) e^{+j\beta z}$$

$$V(z) = V_0^+ \left[ e^{-j\beta z} + (e^{-2j\beta z_L} \Gamma_L) e^{+j\beta z} \right]$$


$$I(z) = \frac{V_0^+}{Z_0} \left[ e^{-j\beta z} - (e^{-2j\beta z_L} \Gamma_L) e^{+j\beta z} \right]$$

where:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\underline{z_L = 0}$$

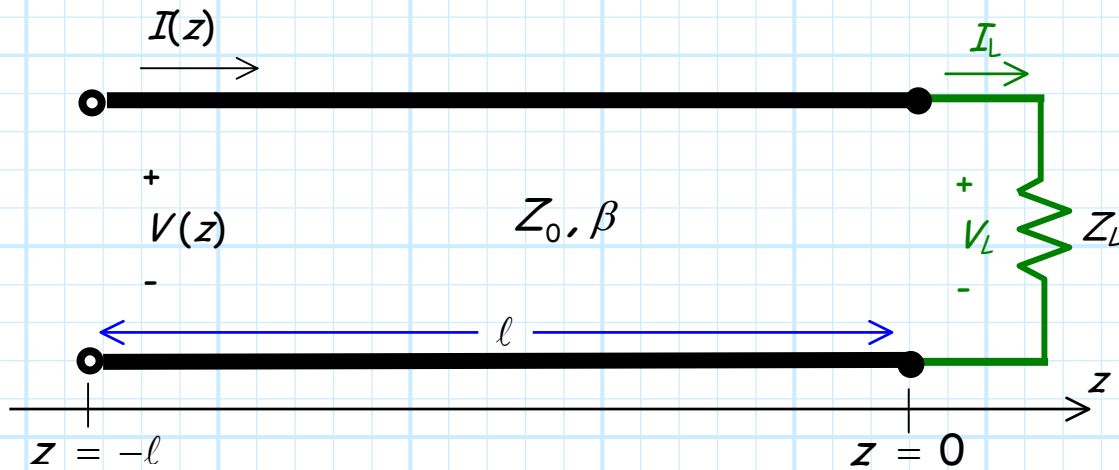Now, we can further **simplify** our analysis by **arbitrarily** assigning the end point  $z_L$  a **zero** value (i.e.,  $z_L = 0$ ):



If the load is located at  $z=0$  (i.e., if  $z_L = 0$ ), we find that:

$$\begin{aligned} V(z=0) &= V^+(z=0) + V^-(z=0) \\ &= V_0^+ e^{-j\beta(0)} + V_0^- e^{+j\beta(0)} \\ &= V_0^+ + V_0^- \end{aligned}$$

$$\begin{aligned} I(z=0) &= \frac{V_0^+(z=0)}{Z_0} - \frac{V_0^-(z=0)}{Z_0} \\ &= \frac{V_0^+}{Z_0} e^{-j\beta(0)} - \frac{V_0^-}{Z_0} e^{+j\beta(0)} \\ &= \frac{V_0^+ - V_0^-}{Z_0} \end{aligned}$$

$$Z(z=0) = Z_0 \left( \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right)$$

Likewise, it is apparent that if  $z_L = 0$ ,  $\Gamma_L$  and  $\Gamma_0$  are the same:

$$\Gamma_L = \Gamma(z = z_L) = \frac{V^-(z = 0)}{V^+(z = 0)} = \frac{V_0^-}{V_0^+} = \Gamma_0$$

Therefore:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_0$$

Thus, we can write the line current and voltage simply as:

$$\begin{aligned} V(z) &= V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}] \\ I(z) &= \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_L e^{+j\beta z}] \end{aligned} \quad [\text{for } z_L = 0]$$

**Q:** But, how do we determine  $V_0^+$  ??

**A:** We require a **second** boundary condition to determine  $V_0^+$ . The only boundary left is at the **other end** of the transmission line. Typically, a **source** of some sort is located there. This makes physical sense, as something must generate the **incident** wave !

# Special Values of Load Impedance

Let's look at some **specific** values of load impedance

$Z_L = R_L + jX_L$  and see what happens on our transmission line!

**1.**  $Z_L = Z_0$

In this case, the **load** impedance is **numerically** equal to the **characteristic** impedance of the transmission line. Assuming the line is **lossless**, then  $Z_0$  is **real**, and thus:

$$R_L = Z_0 \quad \text{and} \quad X_L = 0$$

It is evident that the resulting load reflection coefficient is **zero**:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

This result is very interesting, as it means that there is **no reflected wave**  $V^-(z)$ !

$$\begin{aligned} V^-(z) &= (e^{-2j\beta z_L} \Gamma_L V_0^+) e^{+j\beta z} \\ &= (e^{-2j\beta z_L} (0) V_0^+) e^{+j\beta z} \\ &= 0 \end{aligned}$$

Thus, the **total** voltage and current along the transmission line is simply voltage and current of the **incident** wave:

$$V(z) = V^+(z) = V_0^+ e^{-j\beta z}$$

$$I(z) = I^+(z) = \frac{V_0^+}{Z_0} e^{-j\beta z}$$

Meaning that the **line** impedance is likewise **numerically** equal to the **characteristic** impedance of the transmission line for **all** line position  $z$ :

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_0^+ e^{-j\beta z}}{V_0^+ e^{-j\beta z}} = Z_0$$

And likewise, the reflection coefficient is **zero** at **all** points along the line:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{0}{V^+(z)} = 0$$

We call this condition (when  $Z_L = Z_0$ ) the **matched** condition, and the load  $Z_L = Z_0$  a **matched load**.

## 2. $Z_L = 0$

A device with **no** impedance is called a **short** circuit! I.E.:

$$R_L = 0 \quad \text{and} \quad X_L = 0$$

In this case, the **voltage** across the load—and thus the voltage at the end of the transmission line—is **zero**:

$$V_L = Z_L I_L = 0 \quad \text{and} \quad V(z = z_L) = 0$$

Note that this does **not** mean that the **current** is zero!

$$I_L = I(z = z_L) \neq 0$$

For a **short**, the resulting load reflection coefficient is therefore:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1$$

Meaning (assuming  $z_L = 0$ ):

$$V_0^- = -V_0^+$$

As a result, the total **voltage** and **current** along the transmission line is simply:

$$V(z) = V_0^+ (e^{-j\beta z} - e^{+j\beta z}) = -j2V_0^+ \sin(\beta z)$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} + e^{+j\beta z}) = \frac{2V_0^+}{Z_0} \cos(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of a **trigonometric** function:

$$Z(z) = \frac{V(z)}{I(z)} = -jZ_0 \tan(\beta z)$$

Note that this impedance is **purely reactive**. This means that the current and voltage on the transmission line will be everywhere  $90^\circ$  **out of phase**.

Hopefully, this was likewise apparent to **you** when you **observed** the expressions for  $V(z)$  and  $I(z)$ !

Note at the **end** of the line (i.e.,  $z = z_L = 0$ ), we find that

$$V(z = 0) = -j2V_0^+ \sin(0) = 0$$

$$I(z = 0) = \frac{2V_0^+}{Z_0} \cos(0) = \frac{2V_0^+}{Z_0}$$

As expected, the voltage is **zero** at the end of the transmission line (i.e. the voltage across the **short**). Likewise, the **current** at the end of the line (i.e., the current through the short) is at a **maximum**!

Finally, we note that the **line** impedance at the **end** of the transmission line is:

$$Z(z = 0) = -jZ_0 \tan(0) = 0$$

Just as we expected—a **short** circuit!

Finally, the reflection coefficient **function** is (assuming  $z_L = 0$ ):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{-V_0^+ e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = -e^{j\beta z}$$

Note that for **this** case  $|\Gamma(z)| = 1$ , meaning that:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

### 3. $Z_L = \infty$

A device with **infinite** impedance is called an **open** circuit!  
I.E.:

$$R_L = \infty \quad \text{and/or} \quad X_L = \pm\infty$$

In this case, the **current** through the load—and thus the current at the end of the transmission line—is **zero**:

$$I_L = \frac{V_L}{Z_L} = 0 \quad \text{and} \quad I(z = z_L) = 0$$

Note that this does **not** mean that the **voltage** is zero!

$$V_L = V(z = z_L) \neq 0$$



For an **open**, the resulting load reflection coefficient is:

$$\Gamma_L = \lim_{Z_L \rightarrow \infty} \frac{Z_L - Z_0}{Z_L + Z_0} = \lim_{Z_L \rightarrow \infty} \frac{Z_L}{Z_L} = 1$$

Meaning (assuming  $z_L = 0$ ):

$$V_0^- = V_0^+$$

As a result, the **total** voltage and current along the transmission line is simply (assuming  $z_L = 0$ ):

$$V(z) = V_0^+ (e^{-j\beta z} + e^{+j\beta z}) = 2V_0^+ \cos(\beta z)$$

$$I(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{+j\beta z}) = -j \frac{2V_0^+}{Z_0} \sin(\beta z)$$

Meaning that the **line impedance** can likewise be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = jZ_0 \cot(\beta z)$$

Again note that this impedance is **purely reactive**—  $V(z)$  and  $I(z)$  are again  $90^\circ$  **out of phase**!

Note at the **end** of the line (i.e.,  $z = z_L = 0$ ), we find that

$$V(z=0) = 2V_0^+ \cos(0) = \frac{2V_0^+}{Z_0}$$

$$I(z=0) = -j \frac{2V_0^+}{Z_0} \sin(0) = 0$$

As expected, the **current is zero** at the end of the transmission line (i.e. the current through the **open**). Likewise, the **voltage** at the end of the line (i.e., the voltage across the open) is at a **maximum**!

Finally, we note that the **line impedance** at the **end** of the transmission line is:

$$Z(z=0) = jZ_0 \cot(0) = \infty$$

Just as we expected—an **open** circuit!

Finally, the reflection coefficient is (assuming  $z_L = 0$ ):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V_0^+ e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = e^{+j2\beta z}$$

Note that likewise for **this** case  $|\Gamma(z)| = 1$ , meaning **again** that:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

#### 4. $R_L = 0$

For this case, the load impedance is **purely reactive** (e.g. a capacitor or inductor):

$$Z_L = jX_L$$

Thus, **both** the current through the load, and voltage across the load, are **non-zero**:

$$I_L = I(z = z_L) \neq 0$$

$$V_L = V(z = z_L) \neq 0$$

The resulting load reflection coefficient is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX_L - Z_0}{jX_L + Z_0}$$

Given that  $Z_0$  is real (i.e., the line is **lossless**), we find that this load reflection coefficient is generally some **complex** number.

We can rewrite this value explicitly in terms of its **real** and **imaginary** part as:

$$\Gamma_L = \frac{jX_L - Z_0}{jX_L + Z_0} = \left( \frac{X_L^2 - Z_0^2}{X_L^2 + Z_0^2} \right) + j \left( \frac{2Z_0 X_L}{X_L^2 + Z_0^2} \right)$$

*Yuck! This **isn't** much help!*

Let's instead write this complex value  $\Gamma_L$  in terms of its **magnitude** and **phase**. For **magnitude** we find a much more straightforward result!

$$|\Gamma_L|^2 = \frac{|jX_L - Z_0|^2}{|jX_L + Z_0|^2} = \frac{X_L^2 + Z_0^2}{X_L^2 + Z_0^2} = 1$$

Its magnitude is **one**! Thus, we find that for reactive loads, the reflection coefficient can be simply expressed as:

$$\Gamma_L = e^{j\theta_\Gamma}$$

where

$$\theta_\Gamma = \tan^{-1} \left[ \frac{2Z_0 X_L}{X_L^2 - Z_0^2} \right]$$

We can therefore conclude that for a **reactive load**:

$$V_0^- = e^{j\theta_\Gamma} V_0^+$$

As a result, the **total** voltage and current along the transmission line is simply (assuming  $z_L = 0$ ):

$$\begin{aligned} V(z) &= V_0^+ (e^{-j\beta z} + e^{+j\theta_\Gamma} e^{+j\beta z}) \\ &= V_0^+ e^{+j\theta_\Gamma/2} (e^{-j(\beta z + \theta_\Gamma/2)} + e^{+j(\beta z + \theta_\Gamma/2)}) \\ &= 2V_0^+ e^{+j\theta_\Gamma/2} \cos(\beta z + \theta_\Gamma/2) \end{aligned}$$

$$\begin{aligned}
 I(z) &= \frac{V_0^+}{Z_0} (e^{-j\beta z} - e^{+j\beta z}) \\
 &= \frac{V_0^+}{Z_0} e^{+j\theta_L/2} (e^{-j(\beta z + \theta_L/2)} - e^{+j(\beta z + \theta_L/2)}) \\
 &= -j \frac{2V_0^+}{Z_0} e^{+j\theta_L/2} \sin(\beta z + \theta_L/2)
 \end{aligned}$$

Meaning that the **line impedance** can again be written in terms of trigonometric function:

$$Z(z) = \frac{V(z)}{I(z)} = jZ_0 \cot(\beta z + \theta_L/2)$$

Again note that this impedance is **purely reactive**—  $V(z)$  and  $I(z)$  are once again  $90^\circ$  out of phase!

Note at the **end** of the line (i.e.,  $z = z_L = 0$ ), we find that

$$V(z=0) = 2V_0^+ \cos(\theta_L/2)$$

$$I(z=0) = -j \frac{2V_0^+}{Z_0} \sin(\theta_L/2)$$

As expected, **neither** the current **nor** voltage at the end of the line are zero.

We also note that the line impedance at the end of the transmission line is:

$$Z(z=0) = jZ_0 \cot(\theta_r/2)$$

With a little trigonometry, we can show (trust me!) that:

$$\cot(\theta_r/2) = \frac{X_L}{Z_0}$$

and therefore:

$$Z(z=0) = jZ_0 \cot(\theta_r/2) = jX_L = Z_L$$

Just as we **expected!**

Finally, the reflection coefficient **function** is (assuming  $Z_L = 0$ ):

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} = \frac{V_0^+ e^{+j\theta_r} e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = e^{+j2(\beta z + \theta_r/2)}$$

Note that likewise for **this** case  $|\Gamma(z)| = 1$ , meaning **once again**:

$$|V^-(z)| = |V^+(z)|$$

In other words, the **magnitude** of each **wave** on the transmission line is the **same**—the reflected wave is **just** as big as the incident wave!

**Q:** *Gee, a **reactive** load leads to results very **similar** to that of an **open** or **short** circuit. Is this just **coincidence**?*

**A:** Hardly! An open and short **are** in fact reactive loads—they **cannot absorb power** (think about this!).

Specifically, for an **open**, we find  $\theta_\Gamma = 0$ , so that:

$$\Gamma_L = e^{j\theta_\Gamma} = 1$$

Likewise, for a **short**, we find that  $\theta_\Gamma = \pi$ , so that:

$$\Gamma_L = e^{j\theta_\Gamma} = -1$$

### 5. $X_L = 0$

For this case, the load impedance is **purely real** (e.g. a **resistor**):

$$Z_L = R_L$$

Thus, **both** the current through the load, and voltage across the load, are **non-zero**:

$$I_L = I(z = z_L) \neq 0$$

$$V_L = V(z = z_L) \neq 0$$

The resulting **load reflection coefficient** is:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R - Z_0}{R + Z_0}$$

Given that  $Z_0$  is real (i.e., the line is **lossless**), we find that this load reflection coefficient must be a purely **real** value!

In other words:

$$\operatorname{Re}\{\Gamma_L\} = \frac{R - Z_0}{R + Z_0} \quad \operatorname{Im}\{\Gamma_L\} = 0$$

The magnitude is thus:

$$|\Gamma_L| = \left| \frac{R - Z_0}{R + Z_0} \right|$$

whereas the phase  $\theta_r$  can take on one of two values:

$$\theta_r = \begin{cases} 0 & \text{if } \operatorname{Re}\{\Gamma_L\} > 0 \text{ (i.e., if } R_L > Z_0) \\ \pi & \text{if } \operatorname{Re}\{\Gamma_L\} < 0 \text{ (i.e., if } R_L < Z_0) \end{cases}$$

For this case, the impedance at the **end** of the line must be **real** ( $Z(z = z_L) = R_L$ ). Thus, the current and the voltage at this point are precisely **in phase**.

**However**, even though the **load** impedance is real, the **line** impedance at all other points on the line is generally **complex**!

Moreover, the **general** current and voltage expressions, as well as reflection coefficient function, **cannot** be further simplified for the case where  $Z_L = R_L$ .



**Q:** *Why is that? When the load was purely **imaginary** (reactive), we were able to **simply** our general expressions, and likewise deduce all sorts of interesting results!*

**A:** True! And here's **why**. Remember, a **lossless** transmission line has series inductance and shunt capacitance **only**. In other words, a length of lossless transmission line is a **purely reactive** device (it absorbs **no** energy!).

\* If we attach a **purely reactive** load at the end of the transmission line, we still have a **completely** reactive system (load and transmission line). Because this system has **no** resistive (i.e., real) component, the general expressions for line impedance, line voltage, etc. can be significantly **simplified**.

\* However, if we attach a **purely real** load to our reactive transmission line, we now have a **complex** system, with **both** real and imaginary (i.e., resistive and reactive) components. This **complex** case is exactly what our general expressions **already** describes—**no** further simplification is possible!

$$5. Z_L = R_L + jX_L$$

Now, let's look at the **general** case, where the **load** has both a **real** (resistive) and **imaginary** (reactive) component.

**Q:** *Haven't we **already** determined all the **general** expressions (e.g.,  $\Gamma_L, V(z), I(z), Z(z), \Gamma(z)$ ) for this general case? Is there **anything** else left to be determined?*

**A:** There is **one** last thing we need to discuss. It seems trivial, but its ramifications are **very** important!

For you see, the “general” case is **not**, in reality, quite so general. Although the reactive component of the load can be **either** positive or negative ( $-\infty < X_L < \infty$ ), the resistive component of a passive load **must** be positive ( $R_L > 0$ )—there’s **no** such thing as **negative** resistor!

This leads to one **very** important and useful result. Consider the **load reflection coefficient**:

$$\begin{aligned}\Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{(R_L + jX_L) - Z_0}{(R_L + jX_L) + Z_0} \\ &= \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L}\end{aligned}$$

Now let’s look at the **magnitude** of this value:

$$\begin{aligned}
 |\Gamma_L|^2 &= \left| \frac{(R_L - Z_0) + jX_L}{(R_L + Z_0) + jX_L} \right|^2 \\
 &= \frac{(R_L - Z_0)^2 + X_L^2}{(R_L + Z_0)^2 + X_L^2} \\
 &= \frac{(R_L^2 - 2R_L Z_0 + Z_0^2) + X_L^2}{(R_L^2 + 2R_L Z_0 + Z_0^2) + X_L^2} \\
 &= \frac{(R_L^2 + Z_0^2 + X_L^2) - 2R_L Z_0}{(R_L^2 + Z_0^2 + X_L^2) + 2R_L Z_0}
 \end{aligned}$$

It is apparent that since both  $R_L$  and  $Z_0$  are **positive**, the **numerator** of the above expression must be **less** than (or equal to) the **denominator** of the above expression.

→ In other words, the magnitude of the load reflection coefficient is always **less** than or equal to one!

$$|\Gamma_L| \leq 1 \quad (\text{for } R_L \geq 0)$$

Moreover, we find that this means the reflection coefficient **function** likewise always has a magnitude **less** than or equal to one, for **all** values of position  $z$ .

$$|\Gamma(z)| \leq 1 \quad (\text{for all } z)$$


Which means, of course, that the **reflected** wave will always have a magnitude **less** than that of the **incident** wave magnitude:

$$|V^-(z)| \leq |V^+(z)| \quad (\text{for all } z)$$

We will find out later that this result is consistent with **conservation of energy**—the reflected wave from a passive load **cannot** be larger than the wave incident on it.
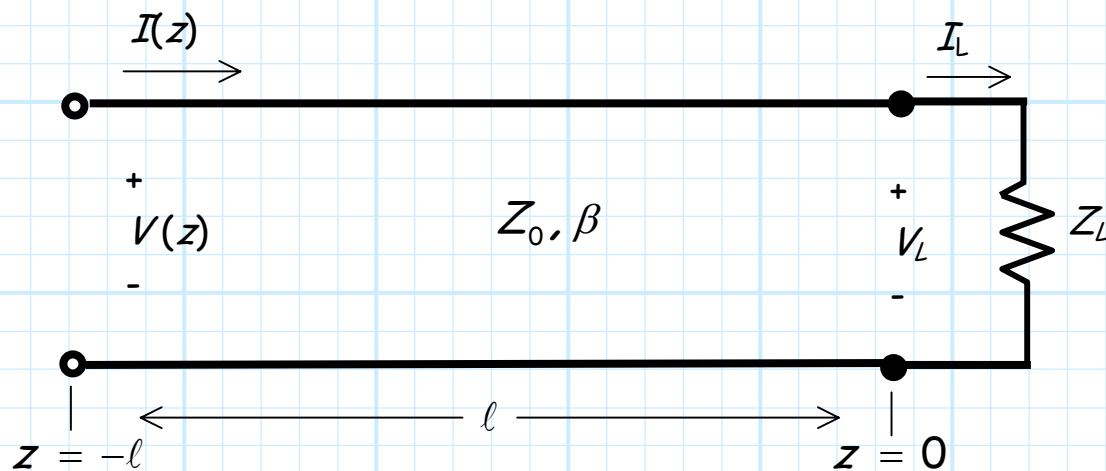
# Transmission Line Input Impedance

Consider a **lossless** line, length  $\ell$ , terminated with a load  $Z_L$ .



Let's determine the **input impedance** of this line!

**Q:** *Just what do you mean by **input impedance**?*

**A:** The input impedance is simply the line impedance seen at the **beginning** ( $z = -\ell$ ) of the transmission line, i.e.:

$$Z_{in} = Z(z = -\ell) = \frac{V(z = -\ell)}{I(z = -\ell)}$$

Note  $Z_{in}$  equal to **neither** the load impedance  $Z_L$  **nor** the characteristic impedance  $Z_0$ !

$$Z_{in} \neq Z_L \quad \text{and} \quad Z_{in} \neq Z_0$$

To determine exactly what  $Z_{in}$  is, we first must determine the voltage and current at the **beginning** of the transmission line ( $z = -\ell$ ).

$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Therefore:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left( \frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right)$$

We can explicitly write  $Z_{in}$  in terms of load  $Z_L$  using the previously determined relationship:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Combining these two expressions, we get:

$$\begin{aligned} Z_{in} &= Z_0 \frac{(Z_L + Z_0)e^{+j\beta\ell} + (Z_L - Z_0)e^{-j\beta\ell}}{(Z_L + Z_0)e^{+j\beta\ell} - (Z_L - Z_0)e^{-j\beta\ell}} \\ &= Z_0 \left( \frac{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) + Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})}{Z_L(e^{+j\beta\ell} + e^{-j\beta\ell}) - Z_0(e^{+j\beta\ell} - e^{-j\beta\ell})} \right) \end{aligned}$$

Now, recall **Euler's equations**:

$$e^{+j\beta\ell} = \cos \beta\ell + j \sin \beta\ell$$

$$e^{-j\beta\ell} = \cos \beta\ell - j \sin \beta\ell$$

Using Euler's relationships, we can likewise write the input impedance without the **complex** exponentials:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right) \\ &= Z_0 \left( \frac{Z_L + j Z_0 \tan \beta \ell}{Z_0 + j Z_L \tan \beta \ell} \right) \end{aligned}$$

Note that depending on the values of  $\beta$ ,  $Z_0$  and  $\ell$ , the input impedance can be **radically** different from the load impedance  $Z_L$ !

### Special Cases

Now let's look at the  $Z_{in}$  for some important **load** impedances and **line lengths**.

→ You should commit these results to **memory**!

1.  $\ell = \lambda/2$

If the length of the transmission line is exactly **one-half** wavelength ( $\ell = \lambda/2$ ), we find that:

$$\beta \ell = \frac{2\pi}{\lambda} \frac{\lambda}{2} = \pi$$


meaning that:

$$\cos \beta \ell = \cos \pi = -1 \quad \text{and} \quad \sin \beta \ell = \sin \pi = 0$$

and therefore:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right) \\ &= Z_0 \left( \frac{Z_L (-1) + j Z_L (0)}{Z_0 (-1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

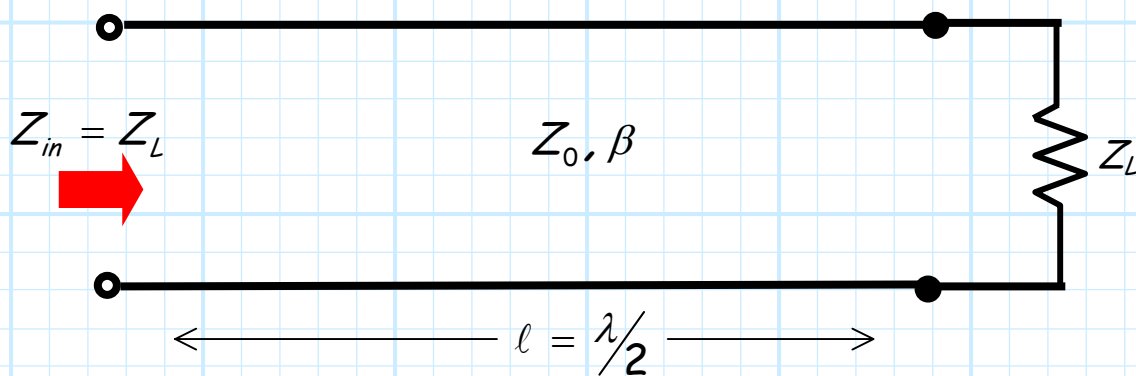In other words, if the transmission line is precisely **one-half wavelength** long, the **input** impedance is equal to the **load** impedance, **regardless** of  $Z_0$  or  $\beta$ .



2.  $\ell = \lambda/4$

If the length of the transmission line is exactly **one-quarter wavelength** ( $\ell = \lambda/4$ ), we find that:

$$\beta \ell = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

meaning that:

$$\cos \beta \ell = \cos \pi/2 = 0 \quad \text{and} \quad \sin \beta \ell = \sin \pi/2 = 1$$



and therefore:


$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right) \\ &= Z_0 \left( \frac{Z_L (0) + j Z_0 (1)}{Z_0 (0) + j Z_L (1)} \right) \\ &= \frac{(Z_0)^2}{Z_L} \end{aligned}$$

In other words, if the transmission line is precisely **one-quarter wavelength** long, the **input** impedance is **inversely** proportional to the **load** impedance.

Think about what this means! Say the load impedance is a **short** circuit, such that  $Z_L = 0$ . The **input impedance** at beginning of the  $\lambda/4$  transmission line is therefore:

$$Z_{in} = \frac{(Z_0)^2}{Z_L} = \frac{(Z_0)^2}{0} = \infty$$

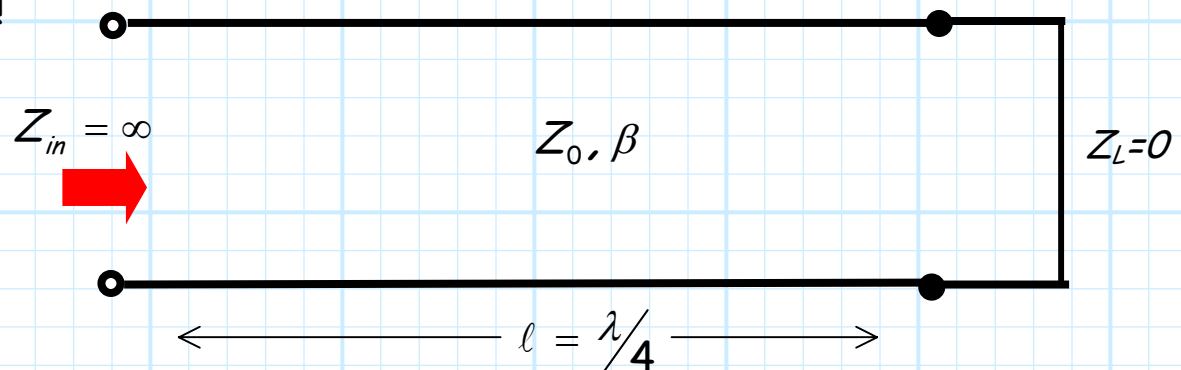$Z_{in} = \infty$  ! This is an **open** circuit! The quarter-wave transmission line **transforms** a short-circuit into an open-circuit—and vice versa!




### 3. $Z_L = Z_0$

If the load is **numerically equal** to the characteristic impedance of the transmission line (a real value), we find that the input impedance becomes:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right) \\ &= Z_0 \left( \frac{Z_0 \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_0 \sin \beta \ell} \right) \\ &= Z_0 \end{aligned}$$

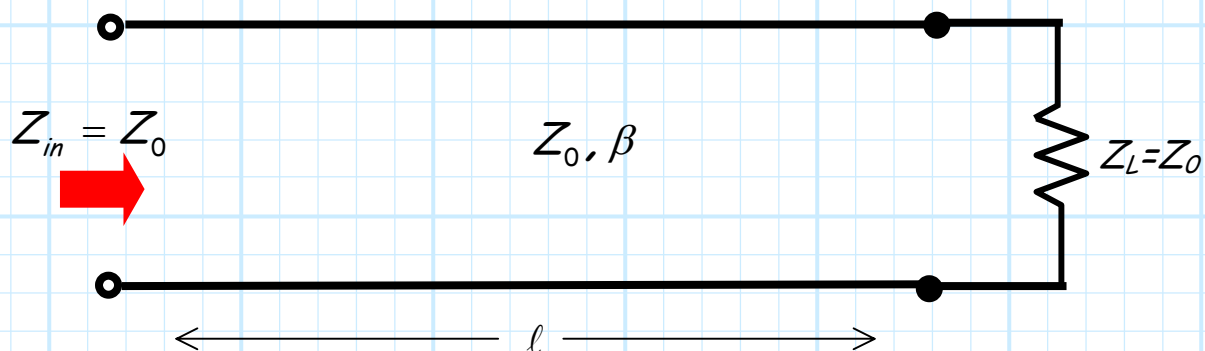In other words, if the **load** impedance is equal to the transmission line **characteristic** impedance, the **input** impedance will be likewise be equal to  $Z_0$  regardless of the transmission line length  $\ell$ .




### 4. $Z_L = j X_L$

If the load is **purely reactive** (i.e., the resistive component is zero), the input impedance is:

$$\begin{aligned}
 Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right) \\
 &= Z_0 \left( \frac{j X_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j^2 X_L \sin \beta \ell} \right) \\
 &= j Z_0 \left( \frac{X_L \cos \beta \ell + Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell - X_L \sin \beta \ell} \right)
 \end{aligned}$$

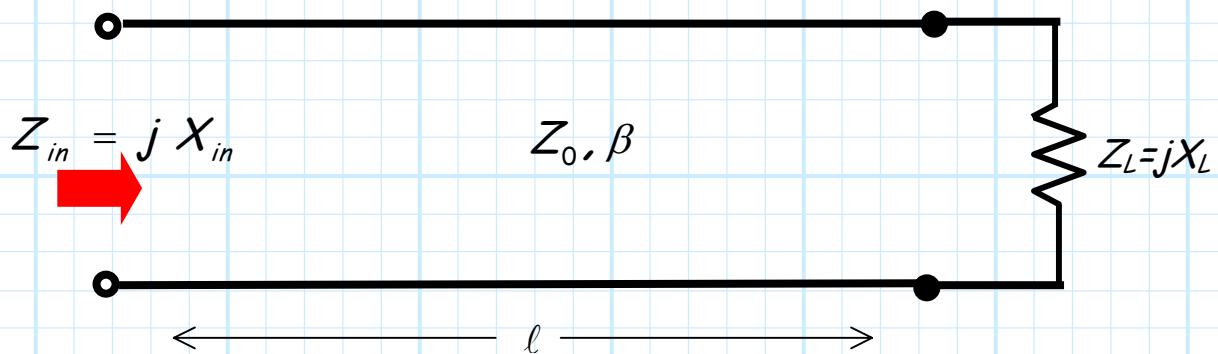In other words, if the load is purely reactive, then the input impedance will **likewise** be purely reactive, **regardless** of the line length  $\ell$ .



Note that the **opposite** is **not** true: even if the load is **purely resistive** ( $Z_L = R$ ), the input impedance will be **complex** (both resistive and reactive components).

**Q:** *Why is this?*

**A:**

## 5. $\ell \ll \lambda$

If the transmission line is **electrically small**—its length  $\ell$  is small with respect to signal wavelength  $\lambda$ --we find that:

$$\beta\ell = \frac{2\pi}{\lambda} \ell = 2\pi \frac{\ell}{\lambda} \approx 0$$

and thus:

$$\cos \beta\ell = \cos 0 = 1 \quad \text{and} \quad \sin \beta\ell = \sin 0 = 0$$

so that the input impedance is:

$$\begin{aligned} Z_{in} &= Z_0 \left( \frac{Z_L \cos \beta\ell + j Z_0 \sin \beta\ell}{Z_0 \cos \beta\ell + j Z_L \sin \beta\ell} \right) \\ &= Z_0 \left( \frac{Z_L (1) + j Z_L (0)}{Z_0 (1) + j Z_L (0)} \right) \\ &= Z_L \end{aligned}$$

In other words, if the transmission line length is much smaller than a wavelength, the **input** impedance  $Z_{in}$  will **always** be equal to the **load** impedance  $Z_L$ .

**This** is the assumption we used in all previous circuits courses (e.g., EECS 211, 212, 312, 412)! In those courses, we assumed that the signal frequency  $\omega$  is relatively **low**, such that the signal wavelength  $\lambda$  is **very large** ( $\lambda \gg \ell$ ).


Note also for this case ( the electrically short transmission line), the voltage and current at each end of the transmission line are approximately the **same**!

$$V(z = -\ell) \approx V(z = 0) \quad \text{and} \quad I(z = -\ell) \approx I(z = 0) \quad \text{if} \quad \ell \ll \lambda$$


If  $\ell \ll \lambda$ , our "wire" behaves **exactly** as it did in EECS 211 !

# Example: Input Impedance

Consider the following circuit:

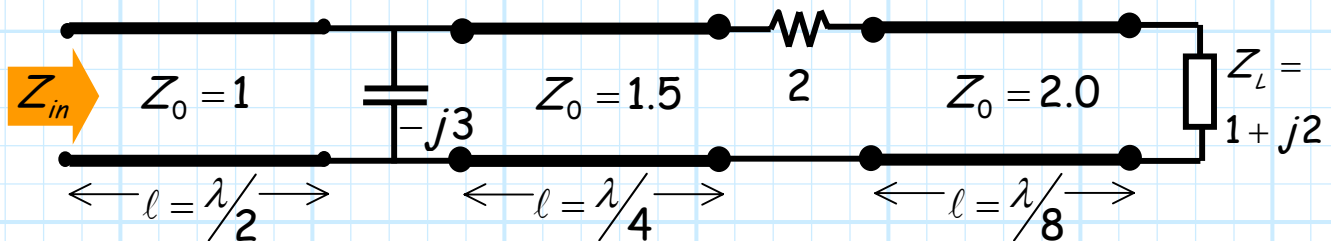

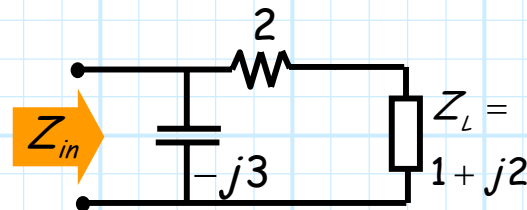If we **ignored** our new  $\mu$ -wave knowledge, we might **erroneously** conclude that the input impedance of this circuit is:




Therefore:

$$Z_{in} = \frac{-j3(2+1+j2)}{-j3+2+1+j2} = \frac{6-j9}{3-j} = 2.7 - j2.1$$

Of course, this is **not** the correct answer!

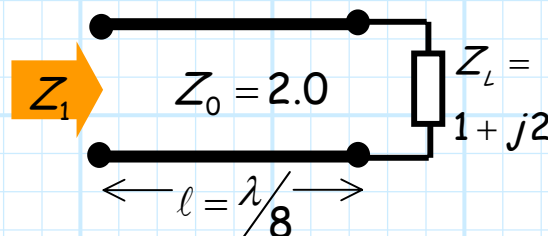
We must use our **transmission line theory** to determine an accurate value. Define  $Z_1$  as the input impedance of the last section:



we find that  $Z_1$  is :


$$\begin{aligned}
 Z_1 &= Z_0 \left( \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right) \\
 &= 2 \left( \frac{(1 + j2) \cos(\pi/4) + j 2 \sin(\pi/4)}{2 \cos(\pi/4) + j(1 + j2) \sin(\pi/4)} \right) \\
 &= 2 \left( \frac{1 + j4}{j} \right) \\
 &= 8 - j2
 \end{aligned}$$

Therefore, our circuit now becomes:

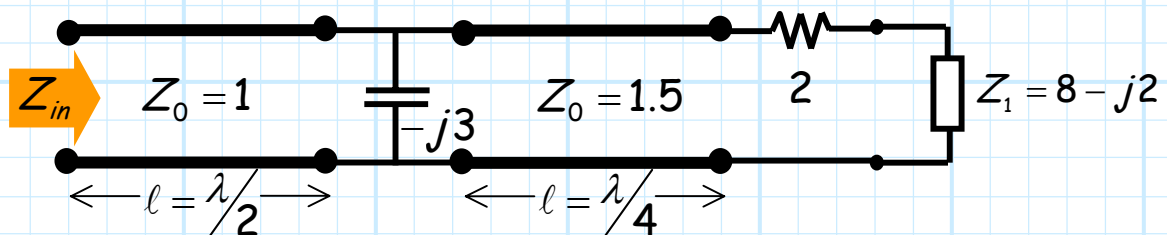


Note the resistor is in **series** with impedance  $Z_1$ . We can **combine** these two into one impedance defined as  $Z_2$ :
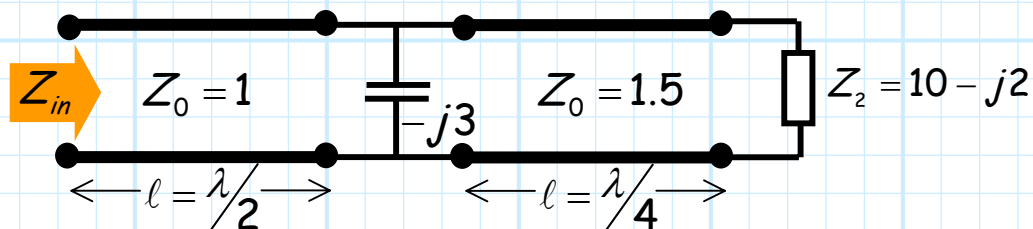
$$Z_2 = 2 + Z_1 = 2 + (8 - j2) = 10 - j2$$



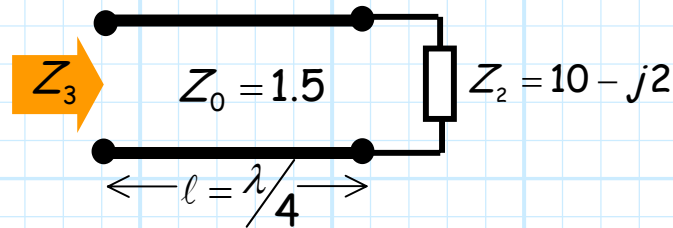
Now let's define the input impedance of the **middle** transmission line section as  $Z_3$ :



Note that this transmission line is a **quarter wavelength** ( $\ell = \lambda/4$ ). This is one of the **special** cases we considered earlier! The input impedance  $Z_3$  is:

$$\begin{aligned} Z_3 &= \frac{Z_0^2}{Z_L} \\ &= \frac{Z_0^2}{Z_2} \\ &= \frac{1.5^2}{10 - j2} \\ &= 0.21 + j0.043 \end{aligned}$$

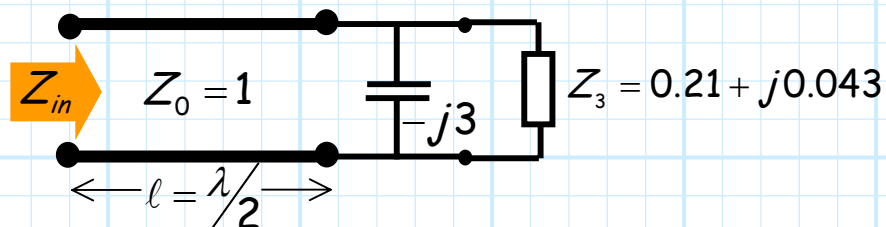Thus, we can further **simplify** the original circuit as:




Now we find that the impedance  $Z_3$  is **parallel** to the capacitor. We can **combine** the two impedances and define the result as impedance  $Z_4$ :



$$\begin{aligned}
 Z_4 &= -j3 \parallel (0.21 + j0.043) \\
 &= \frac{-j3(0.21 + j0.043)}{-j3 + 0.21 + j0.043} \\
 &= 0.22 + j0.028
 \end{aligned}$$

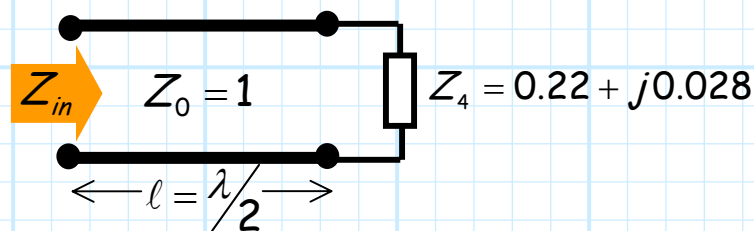
Now we are left with **this** equivalent circuit:




Note that the remaining transmission line section is a **half wavelength**! This is one of the **special** situations we discussed in a previous handout. Recall that the **input** impedance in this case is simply equal to the **load** impedance:

$$Z_{in} = Z_L = Z_4 = 0.22 + j0.028$$

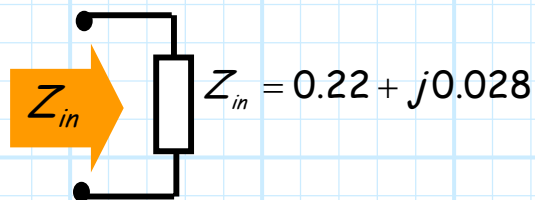
Whew! We are **finally** done. The **input impedance** of the original circuit is:



Note this means that **this** circuit:

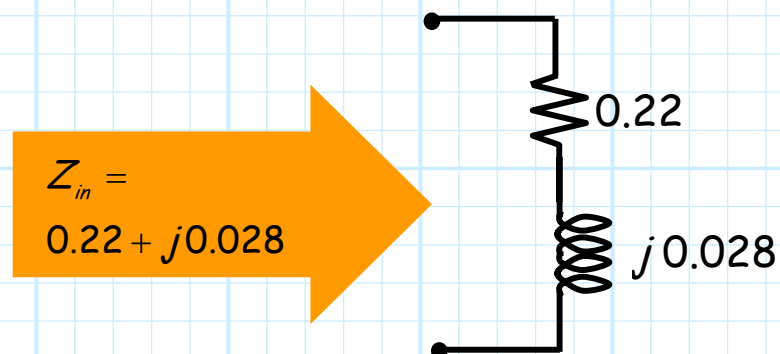

and **this** circuit:

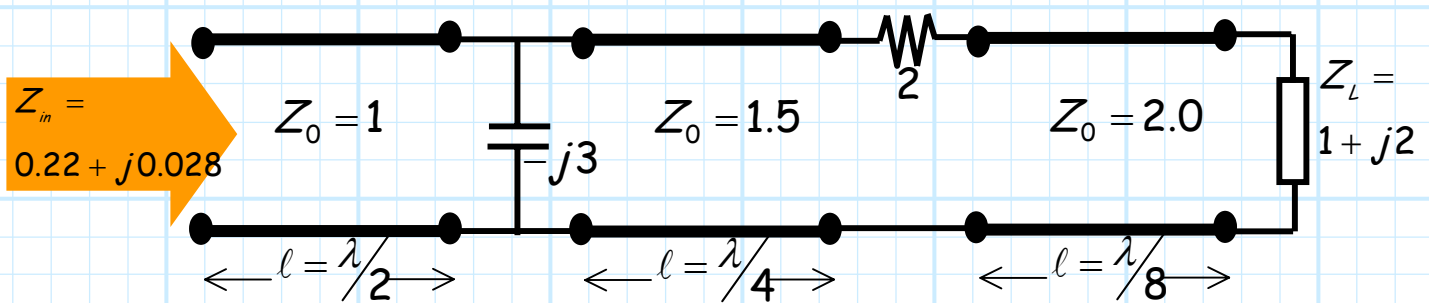

are precisely the **same**! They have **exactly** the same impedance, and thus they "behave" precisely the **same** way in any circuit (but **only** at frequency  $\omega_0$ !).


# The Reflection Coefficient Transformation

The **load** at the end of some length of a transmission line (with characteristic impedance  $Z_0$ ) can be specified in terms of its impedance  $Z_L$  **or** its reflection coefficient  $\Gamma_L$ .

Note **both** values are complex, and **either one** completely specifies the load—if you know **one**, you know the **other**!

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{and} \quad Z_L = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

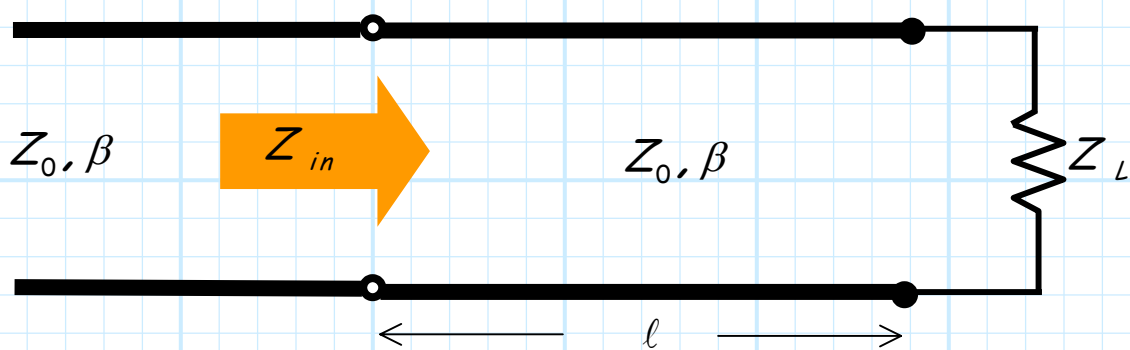Recall that we determined how a length of transmission line **transformed** the load **impedance** into an input **impedance** of a (generally) different value:




where:

$$Z_{in} = Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right)$$

$$= Z_0 \left( \frac{Z_L + j Z_0 \tan \beta \ell}{Z_0 + j Z_L \tan \beta \ell} \right)$$

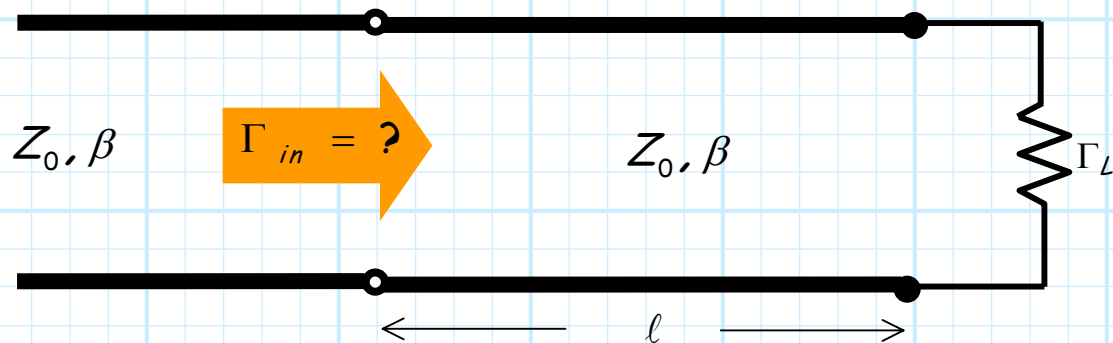**Q:** Say we know the load in terms of its **reflection coefficient**. How can we express the **input impedance** in terms its **reflection coefficient** (call this  $\Gamma_{in}$ )?



**A:** Well, we could execute these **three** steps:

1. Convert  $\Gamma_L$  to  $Z_L$ :

$$Z_L = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

2. Transform  $Z_L$  down the line to  $Z_{in}$ :

$$Z_{in} = Z_0 \left( \frac{Z_L \cos \beta \ell + j Z_0 \sin \beta \ell}{Z_0 \cos \beta \ell + j Z_L \sin \beta \ell} \right)$$

3. Convert  $Z_{in}$  to  $\Gamma_{in}$ :

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

**Q:** *Yikes! This is a **ton** of complex arithmetic—**isn't there an easier way?***

**A:** Actually, there is!

Recall in an **earlier handout** that the input impedance of a transmission line length  $\ell$ , terminated with a load  $\Gamma_L$ , is:

$$Z_{in} = \frac{V(z = -\ell)}{I(z = -\ell)} = Z_0 \left( \frac{e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}}{e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}} \right)$$

Note this **directly** relates  $\Gamma_L$  to  $Z_{in}$  (steps 1 and 2 combined!).

If we directly **insert** this equation into:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

we get an equation **directly** relating  $\Gamma_L$  to  $\Gamma_{in}$ :

$$\begin{aligned}
 \Gamma_{in} &= \frac{Z_0 \left( e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right) - \left( e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right)}{Z_0 \left( e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right) + \left( e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right)} \\
 &= \frac{2\Gamma_L e^{-j\beta\ell}}{2e^{+j\beta\ell}} \\
 &= \Gamma_L e^{-j\beta\ell} e^{-j\beta\ell} \\
 &= \Gamma_L e^{-j2\beta\ell}
 \end{aligned}$$

**Q:** Hey! This result looks **familiar**. Haven't we seen something like this **before**?

**A:** Absolutely! Recall that we found that the reflection coefficient **function**  $\Gamma(z)$  can be expressed as:

$$\Gamma(z) = \Gamma_0 e^{2\gamma z}$$

Now, for a **lossless** line, we know that  $\gamma = j\beta$ , so that:

$$\Gamma(z) = \Gamma_0 e^{j2\beta z}$$

Evaluating this function at the **beginning** of the line (i.e., at  $z = z_L - \ell$ ):

$$\begin{aligned}
 \Gamma(z = z_L - \ell) &= \Gamma_0 e^{j2\beta(z_L - \ell)} \\
 &= \Gamma_0 e^{j2\beta z_L} e^{-j2\beta\ell}
 \end{aligned}$$

But, we recognize that:

$$\Gamma_0 e^{j2\beta z_L} = \Gamma(z = z_L) = \Gamma_L$$

And so:

$$\begin{aligned}\Gamma(z = z_L - \ell) &= \Gamma_0 e^{j2\beta z_L} e^{-j2\beta \ell} \\ &= \Gamma_L e^{-j2\beta \ell}\end{aligned}$$

Thus, we find that  $\Gamma_{in}$  is simply the value of function  $\Gamma(z)$  **evaluated** at the line **input** of  $z = z_L - \ell$  !

$$\Gamma_{in} = \Gamma(z = z_L - \ell) = \Gamma_L e^{-j2\beta \ell}$$

Makes sense! After all, the input impedance is **likewise** simply the line impedance evaluated at the line input of  $z = z_L - \ell$ :

$$Z_{in} = Z(z = z_L - \ell)$$

It is apparent that from the above expression that the reflection coefficient at the input is simply related to  $\Gamma_L$  by a **phase shift** of  $2\beta \ell$ .

In other words, the **magnitude** of  $\Gamma_{in}$  is the **same** as the magnitude of  $\Gamma_L$ !

$$\begin{aligned}|\Gamma_{in}| &= |\Gamma_L| |e^{j(\theta_\Gamma - 2\beta \ell)}| \\ &= |\Gamma_L| (1) \\ &= |\Gamma_L|\end{aligned}$$


If we **think** about this, it makes **perfect sense**!

Recall that the power **absorbed** by the load  $\Gamma_{in}$  would be:

$$P_{abs}^{in} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_{in}|^2)$$

while that absorbed by the **load**  $\Gamma_L$  is:

$$P_{abs}^L = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

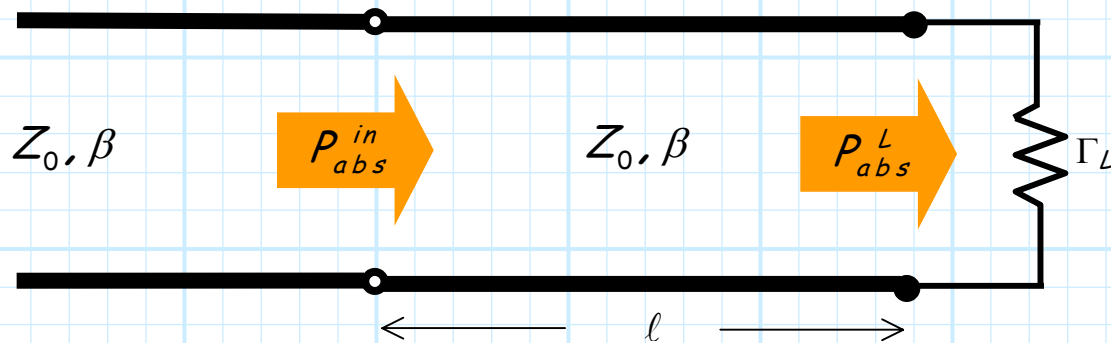

Recall, however, that a lossless transmission line can absorb **no** power! By adding a length of transmission line to load  $\Gamma_L$ , we have added only **reactance**. Therefore, the power absorbed by load  $\Gamma_{in}$  is **equal** to the power absorbed by  $\Gamma_L$ :

$$\begin{aligned} P_{abs}^{in} &= P_{abs}^L \\ \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_{in}|^2) &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\ 1 - |\Gamma_{in}|^2 &= 1 - |\Gamma_L|^2 \end{aligned}$$




Thus, we can conclude from **conservation of energy** that:

$$|\Gamma_{in}| = |\Gamma_L|$$

Which of course is **exactly** the result we just found!

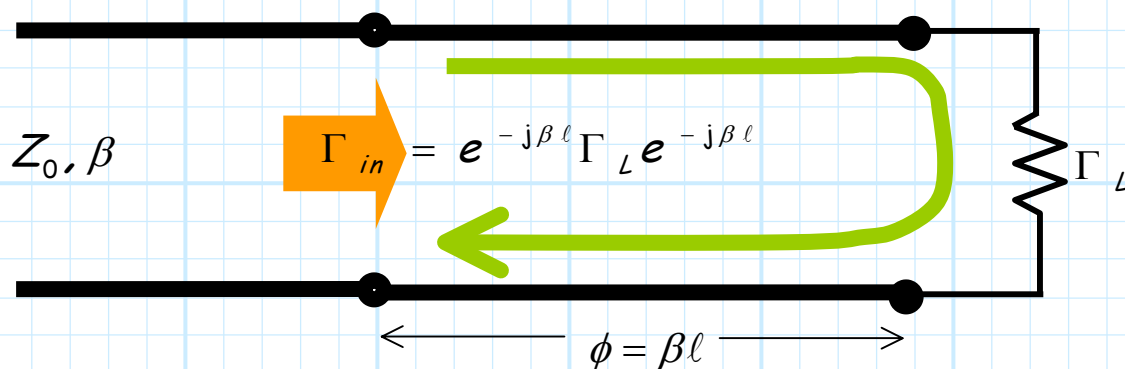Finally, the **phase shift** associated with transforming the load  $\Gamma_L$  down a transmission line can be attributed to the phase shift associated with the wave propagating a length  $\ell$  down the line, reflecting from load  $\Gamma_L$ , and then propagating a length  $\ell$  back up the line:



To **emphasize** this wave interpretation, we recall that by definition, we can write  $\Gamma_{in}$  as:


$$\Gamma_{in} = \Gamma(z = z_L - \ell) = \frac{V^-(z = z_L - \ell)}{V^+(z = z_L - \ell)}$$

Therefore:

$$\begin{aligned} V^-(z = z_L - \ell) &= \Gamma_{in} V^+(z = z_L - \ell) \\ &= e^{-j\beta\ell} \Gamma_L e^{-j\beta\ell} V^+(z = z_L - \ell) \end{aligned}$$
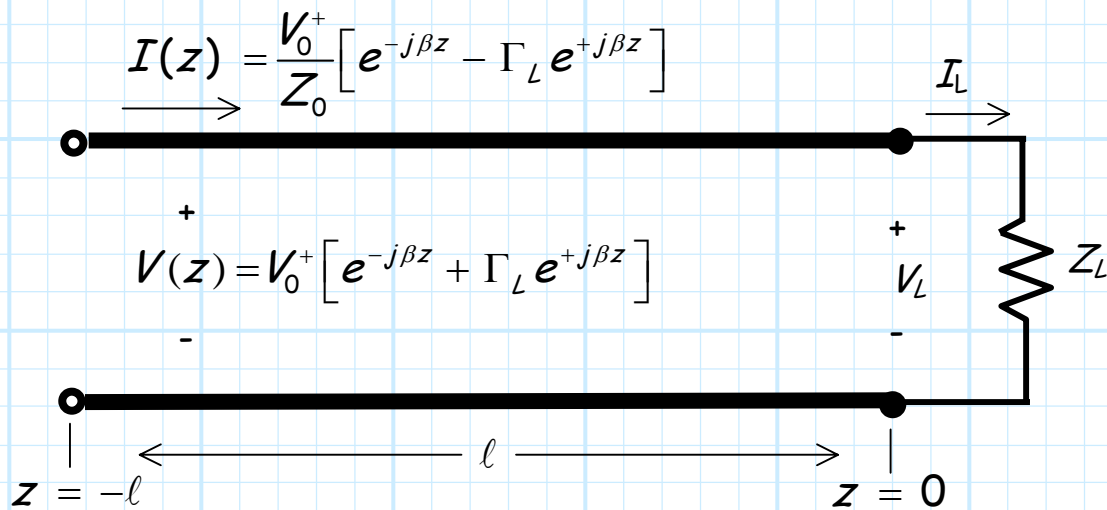
# Power Flow and Return Loss

We have discovered that **two waves propagate** along a transmission line, one in each direction ( $V^+(z)$  and  $V^-(z)$ ).



The result is that electromagnetic energy flows along the transmission line at a given rate (i.e., **power**).

**Q:** *How much power flows along a transmission line, and where does that power go?*

**A:** We can answer that question by determining the power **absorbed** by the load!

The **time average** power absorbed by an impedance  $Z_L$  is:

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \operatorname{Re} \{ V_L I_L^* \} \\
 &= \frac{1}{2} \operatorname{Re} \{ V(z=0) I(z=0)^* \} \\
 &= \frac{1}{2 Z_0} \operatorname{Re} \left\{ \left( V_0^+ \left[ e^{-j\beta 0} + \Gamma_L e^{+j\beta 0} \right] \right) \left( V_0^+ \left[ e^{-j\beta 0} - \Gamma_L e^{+j\beta 0} \right] \right)^* \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} \operatorname{Re} \left\{ 1 - (\Gamma_L^* - \Gamma_L) - |\Gamma_L|^2 \right\} \\
 &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)
 \end{aligned}$$

The significance of this result can be seen by **rewriting** the expression as:

$$\begin{aligned}
 P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^+ \Gamma_L|^2}{2 Z_0} \\
 &= \frac{|V_0^+|^2}{2 Z_0} - \frac{|V_0^-|^2}{2 Z_0}
 \end{aligned}$$

The two terms in above expression have a very definite **physical meaning**. The first term is the time-averaged **power of the wave** propagating along the transmission line **toward the load**.

We say that this wave is **incident** on the load:

$$P_{inc} = P_+ = \frac{|V_0^+|^2}{2Z_0}$$

Likewise, the second term of the  $P_{abs}$  equation describes the **power of the wave** moving in the other direction (**away from the load**). We refer to this as the wave **reflected** from the load:

$$P_{ref} = P_- = \frac{|V_0^-|^2}{2Z_0} = \frac{|\Gamma_L|^2 |V_0^+|^2}{2Z_0} = |\Gamma_L|^2 P_{inc}$$

Thus, the power **absorbed** by the load is simply:


$$P_{abs} = P_{inc} - P_{ref}$$

or, rearranging, we find:

$$P_{inc} = P_{abs} + P_{ref}$$

This equation is simply an expression of the **conservation of energy** !

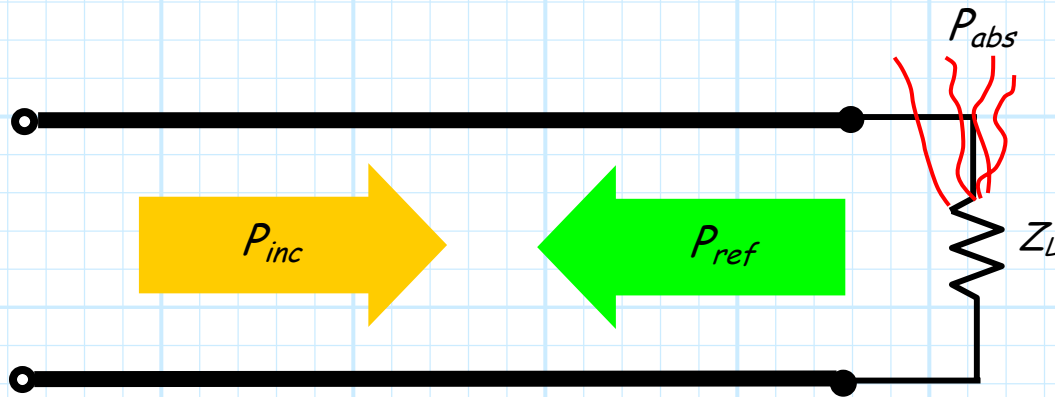It says that power flowing **toward** the load ( $P_{inc}$ ) is either **absorbed** by the load ( $P_{abs}$ ) or **reflected** back from the load ( $P_{ref}$ ).



Note that if  $|\Gamma_L|^2 = 1$ , then  $P_{inc} = P_{ref}$ , and therefore **no power** is absorbed by the **load**.

This of course **makes sense** !

The magnitude of the reflection coefficient ( $|\Gamma_L|$ ) is equal to one **only** when the load impedance is **purely reactive** (i.e., purely imaginary).

Of course, a purely reactive element (e.g., capacitor or inductor) **cannot** absorb any power—**all** the power **must** be reflected!

### Return Loss

The **ratio** of the reflected power to the incident power is known as **return loss**. Typically, return loss is expressed in **dB**:

$$R.L. = -10 \log_{10} \left[ \frac{P_{ref}}{P_{inc}} \right] = -10 \log_{10} |\Gamma_L|^2$$

For **example**, if the return loss is **10dB**, then **10%** of the incident power is **reflected** at the load, with the remaining **90%** being **absorbed** by the load—we “lose” 10% of the incident power

Likewise, if the return loss is **30dB**, then **0.1 %** of the incident power is **reflected** at the load, with the remaining **99.9%** being **absorbed** by the load—we “lose” 0.1% of the incident power.

Thus, a **larger** numeric value for return loss **actually** indicates **less** lost power! An **ideal** return loss would be  $\infty$  dB, whereas a return loss of 0 dB indicates that  $|\Gamma_L| = 1$ --the load is **reactive**!

# VSWR

Consider again the **voltage** along a terminated transmission line, as a function of **position**  $z$ :

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

Recall this is a **complex** function, the magnitude of which expresses the **magnitude** of the **sinusoidal signal** at position  $z$ , while the phase of the complex value represents the relative **phase** of the sinusoidal signal.

Let's look at the **magnitude** only:

$$\begin{aligned} |V(z)| &= |V_0^+| |e^{-j\beta z} + \Gamma_L e^{+j\beta z}| \\ &= |V_0^+| |e^{-j\beta z}| |1 + \Gamma_L e^{+j2\beta z}| \\ &= |V_0^+| |1 + \Gamma_L e^{+j2\beta z}| \end{aligned}$$

**ICBST** the **largest** value of  $|V(z)|$  occurs at the location  $z$  where:

$$\Gamma_L e^{+j2\beta z} = |\Gamma_L| + j0$$

while the **smallest** value of  $|V(z)|$  occurs at the location  $z$  where:

$$\Gamma_L e^{+j2\beta z} = -|\Gamma_L| + j0$$

As a result we can conclude that:

$$|V(z)|_{\max} = |V_0^+| (1 + |\Gamma_L|)$$

$$|V(z)|_{\min} = |V_0^+| (1 - |\Gamma_L|)$$

The ratio of  $|V(z)|_{\max}$  to  $|V(z)|_{\min}$  is known as the **Voltage Standing Wave Ratio (VSWR)**:

$$VSWR \doteq \frac{|V(z)|_{\max}}{|V(z)|_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad \therefore \quad 1 \leq VSWR \leq \infty$$

Note if  $|\Gamma_L| = 0$  (i.e.,  $Z_L = Z_0$ ), then  $VSWR = 1$ . We find for this case:

$$|V(z)|_{\max} = |V(z)|_{\min} = |V_0^+|$$

In other words, the voltage magnitude is a **constant** with respect to position  $z$ .


Conversely, if  $|\Gamma_L| = 1$  (i.e.,  $Z_L = jX$ ), then  $VSWR = \infty$ . We find for **this** case:

$$|V(z)|_{\min} = 0 \quad \text{and} \quad |V(z)|_{\max} = 2|V_0^+|$$

In other words, the voltage magnitude varies **greatly** with respect to position  $z$ .




As with **return loss**, VSWR is dependent on the **magnitude** of  $\Gamma_L$  (i.e.,  $|\Gamma_L|$ ) **only** !

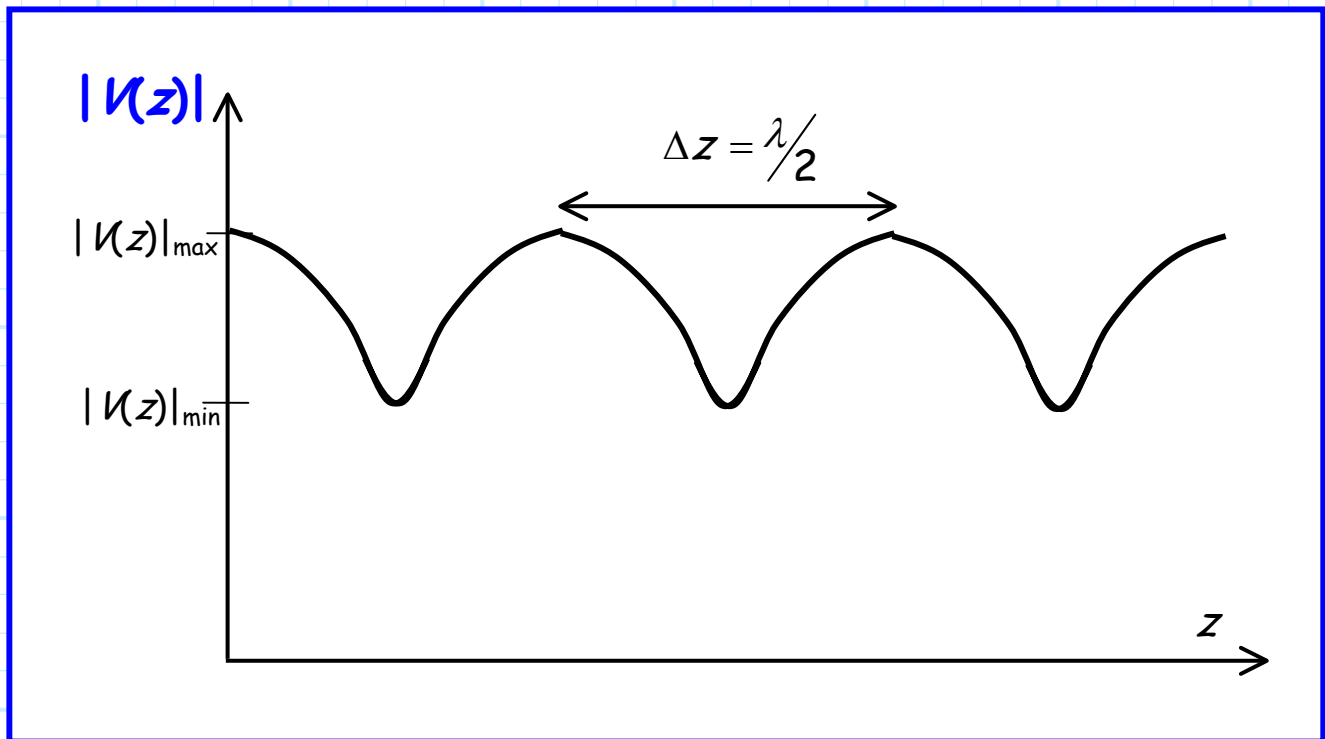

# The Transmission Coefficient T

Consider this circuit:

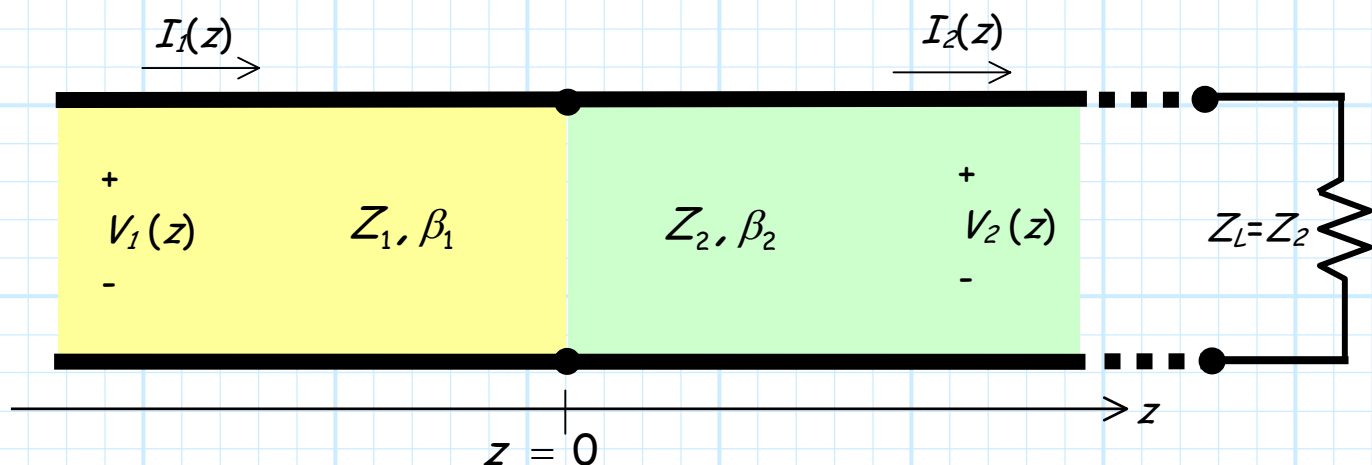

I.E., a transmission line with characteristic impedance  $Z_1$  **transitions** to a **different** transmission line at location  $z=0$ . This second transmission line has different **characteristic impedance**  $Z_2$  ( $Z_1 \neq Z_2$ ). This second line is **terminated** with a load  $Z_L = Z_2$  (i.e., the second line is **matched**).

**Q:** *What is the voltage and current along each of these two transmission lines? More specifically, what are  $V_{01}^+$ ,  $V_{01}^-$ ,  $V_{02}^+$  and  $V_{02}^-$  ??*

**A:** Since a source has not been specified, we can only determine  $V_{01}^-$ ,  $V_{02}^+$  and  $V_{02}^-$  in terms of complex constant  $V_{01}^+$ . To accomplish this, we must apply a **boundary condition** at  $z=0$ !

$$z < 0$$

We know that the voltage along the **first** transmission line is:

$$V_1(z) = V_{01}^+ e^{-j\beta_1 z} + V_{01}^- e^{+j\beta_1 z} \quad [\text{for } z < 0]$$

while the **current** along that same line is described as:

$$I_1(z) = \frac{V_{01}^+}{Z_1} e^{-j\beta_1 z} - \frac{V_{01}^-}{Z_1} e^{+j\beta_1 z} \quad [\text{for } z < 0]$$

$$z > 0$$

We likewise know that the voltage along the **second** transmission line is:

$$V_2(z) = V_{02}^+ e^{-j\beta_2 z} + V_{02}^- e^{+j\beta_2 z} \quad [\text{for } z > 0]$$

while the **current** along that same line is described as:

$$I_2(z) = \frac{V_{02}^+}{Z_2} e^{-j\beta_2 z} - \frac{V_{02}^-}{Z_2} e^{+j\beta_2 z} \quad [\text{for } z > 0]$$

Moreover, since the second line is terminated in a **matched load**, we know that the **reflected** wave from this load must be zero:

$$V_2^-(z) = V_{02}^- e^{-j\beta_2 z} = 0$$


The voltage and current along the **second** transmission line is thus simply:

$$V_2(z) = V_2^+(z) = V_{02}^+ e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

$$I_2(z) = I_2^+(z) = \frac{V_{02}^+}{Z_2} e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

$$z=0$$

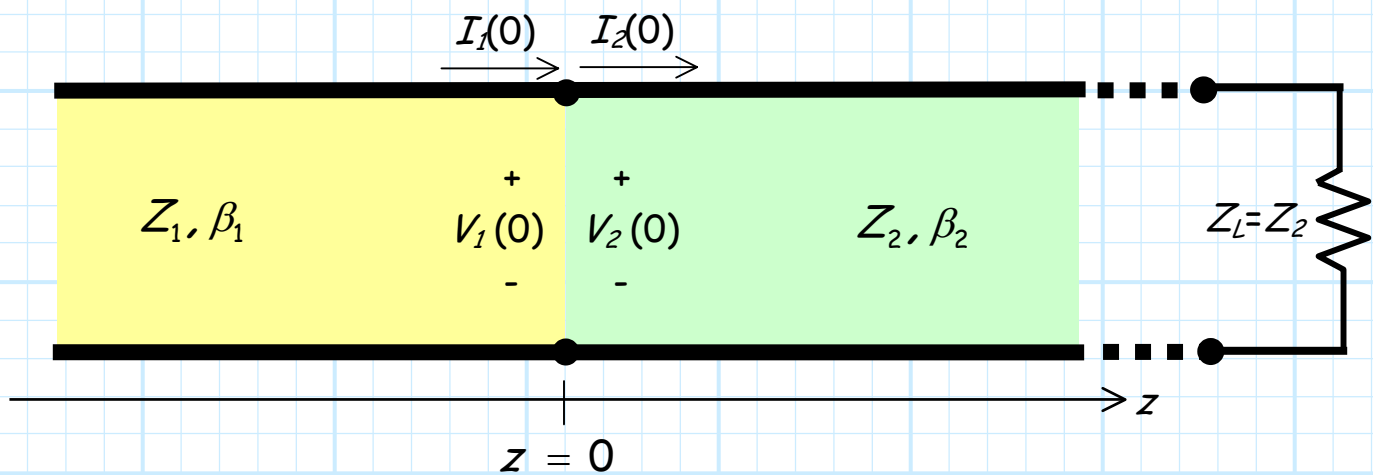At the location where these two transmission lines meet, the current and voltage expressions each **must** satisfy some specific **boundary conditions**:



The **first** boundary condition comes from **KVL**, and states that:

$$V_1(z=0) = V_2(z=0)$$

$$V_{01}^+ e^{-j\beta_1(0)} + V_{01}^- e^{+j\beta_1(0)} = V_{02}^+ e^{-j\beta_2(0)}$$

$$V_{01}^+ + V_{01}^- = V_{02}^+$$

while the **second** boundary condition comes from **KCL**, and states that:

$$I_1(z=0) = I_2(z=0)$$

$$\frac{V_{01}^+}{Z_1} e^{-j\beta_1(0)} - \frac{V_{01}^-}{Z_1} e^{+j\beta_1(0)} = \frac{V_{02}^+}{Z_2} e^{-j\beta_2(0)}$$

$$\frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} = \frac{V_{02}^+}{Z_2}$$

We now have **two** equations and **two** unknowns ( $V_{01}^-$  and  $V_{02}^+$ )! We can **solve** for each in terms of  $V_{01}^+$  (i.e., the **incident** wave).

From the **first** boundary condition we can state:

$$V_{01}^- = V_{02}^+ - V_{01}^+$$

Inserting this into the **second** boundary condition, we find an expression involving **only**  $V_{02}^+$  and  $V_{01}^+$ :

$$\frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} = \frac{V_{02}^+}{Z_2}$$

$$\frac{V_{01}^+}{Z_1} - \frac{V_{02}^+ - V_{01}^+}{Z_1} = \frac{V_{02}^+}{Z_2}$$

$$\frac{2V_{01}^+}{Z_1} = \frac{V_{02}^+}{Z_2} + \frac{V_{02}^+}{Z_1}$$

Solving this expression, we find:

$$V_{02}^+ = \left( \frac{2Z_2}{Z_1 + Z_2} \right) V_{01}^+$$

We can therefore define a **transmission coefficient**, which relates  $V_{02}^+$  to  $V_{01}^+$ :

$$T_0 \doteq \frac{V_{02}^+}{V_{01}^+} = \frac{2Z_2}{Z_1 + Z_2}$$

Meaning that  $V_{02}^+ = T V_{01}^+$ , and thus:

$$V_2(z) = V_2^+(z) = T V_{01}^+ e^{-j\beta_2 z} \quad [\text{for } z > 0]$$

We can **likewise** determine the constant  $V_{01}^-$  in terms of  $V_{01}^+$ . We again start with the **first** boundary condition, from which we concluded:

$$V_{02}^+ = V_{01}^+ + V_{01}^-$$

We can insert this into the **second** boundary condition, and determine an expression involving  $V_{01}^-$  and  $V_{01}^+$  **only**:

$$\begin{aligned} \frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} &= \frac{V_{02}^+}{Z_2} \\ \frac{V_{01}^+}{Z_1} - \frac{V_{01}^-}{Z_1} &= \frac{V_{01}^+ + V_{01}^-}{Z_2} \\ \left( \frac{1}{Z_1} - \frac{1}{Z_2} \right) V_{01}^+ &= \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) V_{01}^- \end{aligned}$$

Solving this expression, we find:


$$V_{01}^- = \left( \frac{Z_2 - Z_1}{Z_2 + Z_1} \right) V_{01}^+$$

We can therefore define a **reflection coefficient**, which relates  $V_{01}^-$  to  $V_{01}^+$ :


$$\Gamma_0 \doteq \frac{V_{01}^-}{V_{01}^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

This result should **not** surprise us!

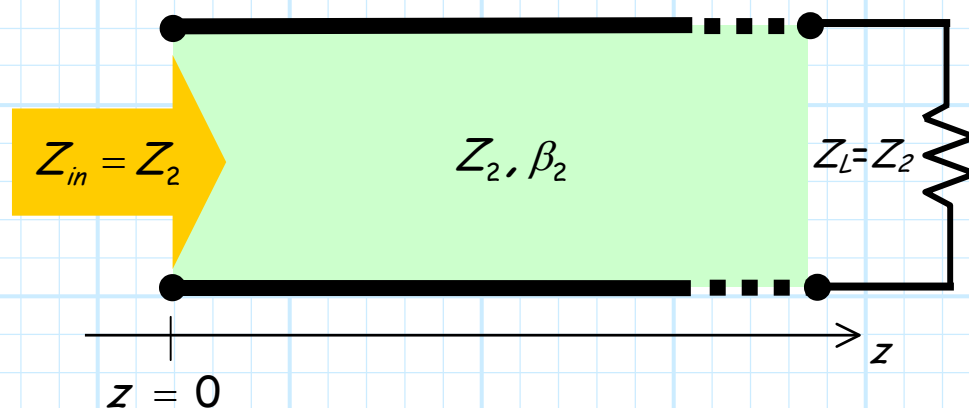Note that because the **second** transmission line is **matched**, its **input** impedance is equal to  $Z_1$ :



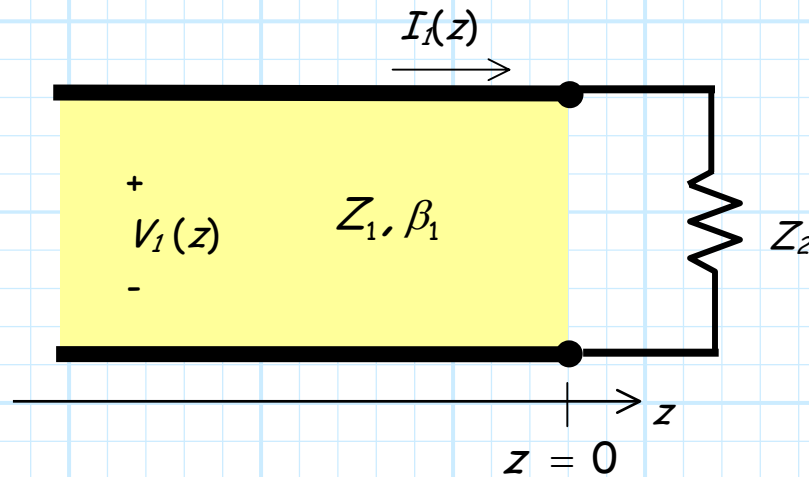and thus we can **equivalently** write the entire circuit as:



We have already analyzed **this** circuit! We know that:

$$\begin{aligned} V_{01}^- &= \Gamma_L V_{01}^+ \\ &= \left( \frac{Z_2 - Z_1}{Z_2 + Z_1} \right) V_{01}^+ \end{aligned}$$

Which is **exactly** the same result as we determined earlier!

The values of the reflection coefficient  $\Gamma_0$  and the transmission coefficient  $T_0$  are **not** independent, but in fact are directly **related**. Recall the **first** boundary expressed was:

$$V_{01}^+ + V_{01}^- = V_{02}^+$$

Dividing this by  $V_{01}^+$ :

$$1 + \frac{V_{01}^-}{V_{01}^+} = \frac{V_{02}^+}{V_{01}^+}$$




Since  $\Gamma_0 = V_{01}^- / V_{01}^+$  and  $\mathcal{T}_0 = V_{02}^+ / V_{01}^+$ :

$$1 + \Gamma_0 = \mathcal{T}_0$$

Note the result  $\mathcal{T}_0 = 1 + \Gamma_0$  is true for **this** particular circuit, and therefore is **not** a universally valid expression for two-port networks!

# Example: Applying Boundary Conditions

Consider this circuit:

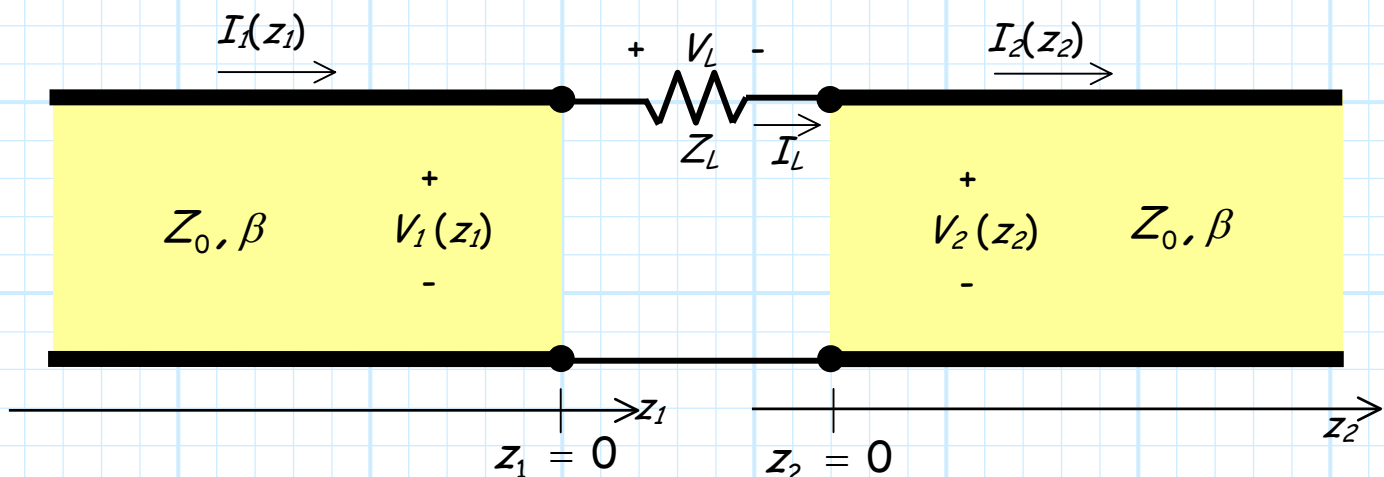

I.E., Two transmissions of **identical** characteristic impedance are connect by a **series** impedance  $Z_L$ . This second line is eventually **terminated** with a load  $Z_L = Z_0$  (i.e., the second line is **matched**).

**Q:** *What is the voltage and current along each of these two transmission lines? More specifically, what are  $V_{01}^+$ ,  $V_{01}^-$ ,  $V_{02}^+$  and  $V_{02}^-$  ??*

**A:** Since a source has not been specified, we can only determine  $V_{01}^-$ ,  $V_{02}^+$  and  $V_{02}^-$  in terms of complex constant  $V_{01}^+$ . To accomplish this, we must apply a **boundary conditions** at the end of each line!

$$z_1 < 0$$

We know that the voltage along the **first** transmission line is:

$$V_1(z_1) = V_{01}^+ e^{-j\beta z_1} + V_{01}^- e^{+j\beta z_1} \quad [\text{for } z_1 < 0]$$

while the **current** along that same line is described as:

$$I_1(z_1) = \frac{V_{01}^+}{Z_0} e^{-j\beta z_1} - \frac{V_{01}^-}{Z_0} e^{+j\beta z_1} \quad [\text{for } z_1 < 0]$$

$$z_2 > 0$$

We likewise know that the voltage along the **second** transmission line is:

$$V_2(z_2) = V_{02}^+ e^{-j\beta z_2} + V_{02}^- e^{+j\beta z_2} \quad [\text{for } z_2 > 0]$$

while the **current** along that same line is described as:

$$I_2(z_2) = \frac{V_{02}^+}{Z_0} e^{-j\beta z_2} - \frac{V_{02}^-}{Z_0} e^{+j\beta z_2} \quad [\text{for } z_2 > 0]$$

Moreover, since the second line is terminated in a **matched load**, we know that the **reflected** wave from this load must be zero:

$$V_2^-(z_2) = V_{02}^- e^{-j\beta z_2} = 0$$


The voltage and current along the **second** transmission line is thus simply:

$$V_2(z_2) = V_2^+(z_2) = V_{02}^+ e^{-j\beta z_2} \quad [\text{for } z_2 > 0]$$

$$I_2(z_2) = I_2^+(z_2) = \frac{V_{02}^+}{Z_2} e^{-j\beta z_2} \quad [\text{for } z_2 > 0]$$

$$z=0$$

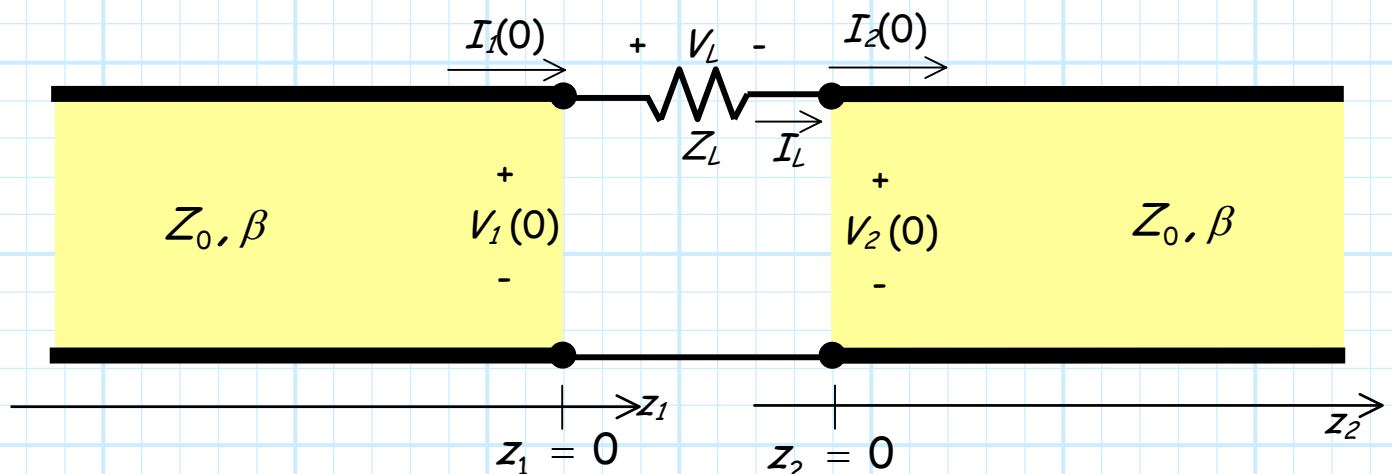At the location where these two transmission lines meet, the current and voltage expressions each **must** satisfy some specific **boundary conditions**:



The **first** boundary condition comes from **KVL**, and states that:

$$V_1(z=0) - I_L Z_L = V_2(z=0)$$

$$V_{01}^+ e^{-j\beta(0)} + V_{01}^- e^{+j\beta(0)} - I_L Z_L = V_{02}^+ e^{-j\beta(0)}$$

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

the **second** boundary condition comes from **KCL**, and states that:

$$I_1(z=0) = I_L$$

$$\frac{V_{01}^+}{Z_0} e^{-j\beta(0)} - \frac{V_{01}^-}{Z_0} e^{+j\beta(0)} = I_L$$

$$V_{01}^+ - V_{01}^- = Z_0 I_L$$

while the **third** boundary condition likewise comes from **KCL**, and states that:

$$I_L = I_2(z=0)$$

$$I_L = \frac{V_{02}^+}{Z_0} e^{-j\beta(0)}$$

$$Z_0 I_L = V_{02}^+$$

Finally, we have Ohm's Law:

$$V_L = Z_L I_L$$

Note that we now have **four** equations and **four** unknowns ( $V_{01}^-$ ,  $V_{02}^+$ ,  $V_L$ ,  $I_L$ )! We can **solve** for each in terms of  $V_{01}^+$  (i.e., the **incident** wave).

For **example**, let's determine  $V_{02}^+$  (in terms of  $V_{01}^+$ ). We combine the **first** and **second** boundary conditions to determine:

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

$$V_{01}^+ + (V_{01}^+ - Z_0 I_L) - I_L Z_L = V_{02}^+$$

$$2V_{01}^+ - I_L (Z_0 + Z_L) = V_{02}^+$$

And then adding in the **third** boundary condition:

$$2V_{01}^+ - I_L (Z_0 + Z_L) = V_{02}^+$$


$$2V_{01}^+ - \frac{V_{02}^+}{Z_0} (Z_0 + Z_L) = V_{02}^+$$

$$2V_{01}^+ = V_{02}^+ \left( \frac{2Z_0 + Z_L}{Z_0} \right)$$

Thus, we find that  $V_{02}^+ = T_0 V_{01}^+$ :

$$T_0 \doteq \frac{V_{02}^+}{V_{01}^+} = \frac{2Z_0}{2Z_0 + Z_L}$$

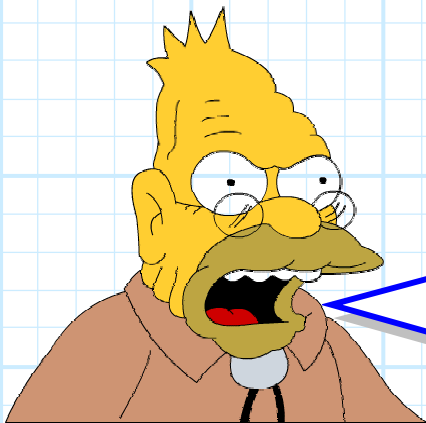Now let's determine  $V_{01}^-$  (in terms of  $V_{01}^+$ ).



**Q:** *Why are you wasting our time? Don't we **already** know that  $V_{01}^- = \Gamma_0 V_{01}^+$ , where:*

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

**A:** Perhaps. Humor me while I **continue** with our **boundary condition** analysis.

We combine the **first** and **third** boundary conditions to determine:

$$V_{01}^+ + V_{01}^- - I_L Z_L = V_{02}^+$$

$$V_{01}^+ + V_{01}^- - I_L Z_L = Z_0 I_L$$

$$V_{01}^+ + V_{01}^- = I_L (Z_0 + Z_L)$$

And then adding the **second** boundary condition:

$$V_{01}^+ + V_{01}^- = I_L (Z_0 + Z_L)$$

$$V_{01}^+ + V_{01}^- = \frac{(V_{01}^+ - V_{01}^-)}{Z_0} (Z_0 + Z_L)$$


$$V_{01}^+ \left( \frac{Z_L}{Z_0} \right) = V_{01}^- \left( \frac{2Z_0 + Z_L}{Z_0} \right)$$

Thus, we find that  $V_{01}^- = \Gamma_0 V_{01}^+$ , where:

$$\Gamma_0 \doteq \frac{V_{01}^-}{V_{01}^+} = \frac{Z_L}{Z_L + 2Z_0}$$


Note this is **not** the expression:
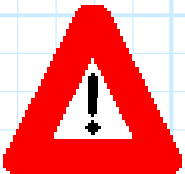
$$\Gamma_0 \neq \frac{Z_L - Z_0}{Z_L + Z_0}$$



This is a completely **different** problem than the transmission line simply terminated by load  $Z_L$ . Thus, the **results** are likewise different. This shows that you must always **carefully** consider the problem you are attempting to solve, and guard against using "shortcuts" with previously derived expressions that may be **inapplicable**.

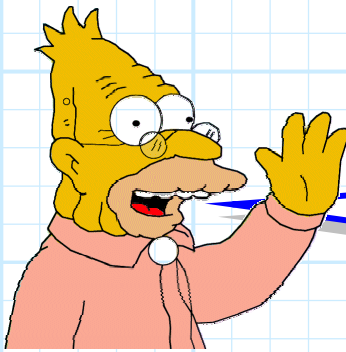
→ This is why you must know **why** a correct answer is correct!




**Q:** But, isn't there **some** way to solve this using our previous work?

**A:** Actually, there is!

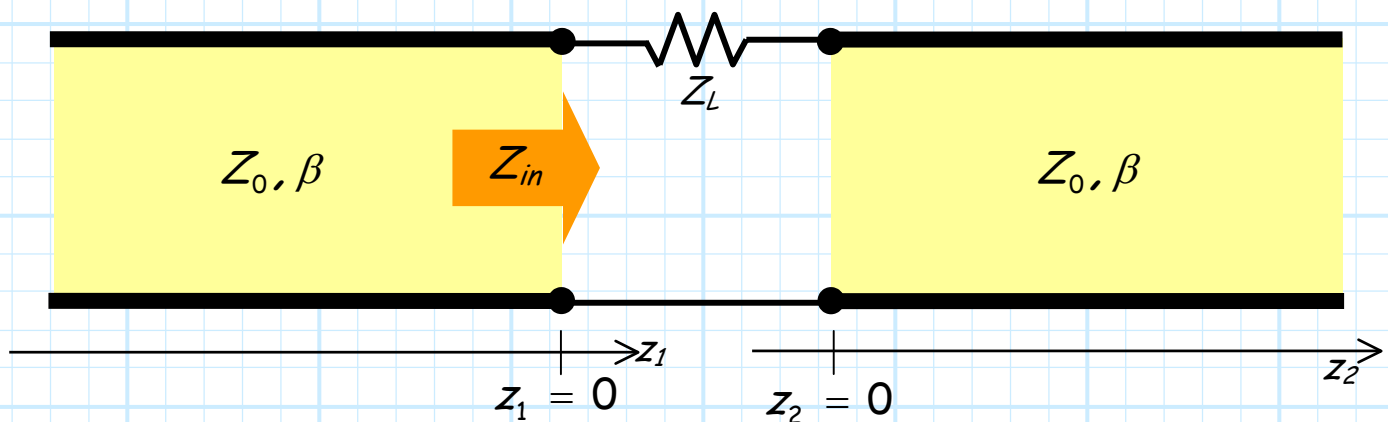An **alternative** way for finding  $\Gamma_0 = V_{01}^- / V_{01}^+$  is to determine the **input impedance at the end of the first transmission line**:




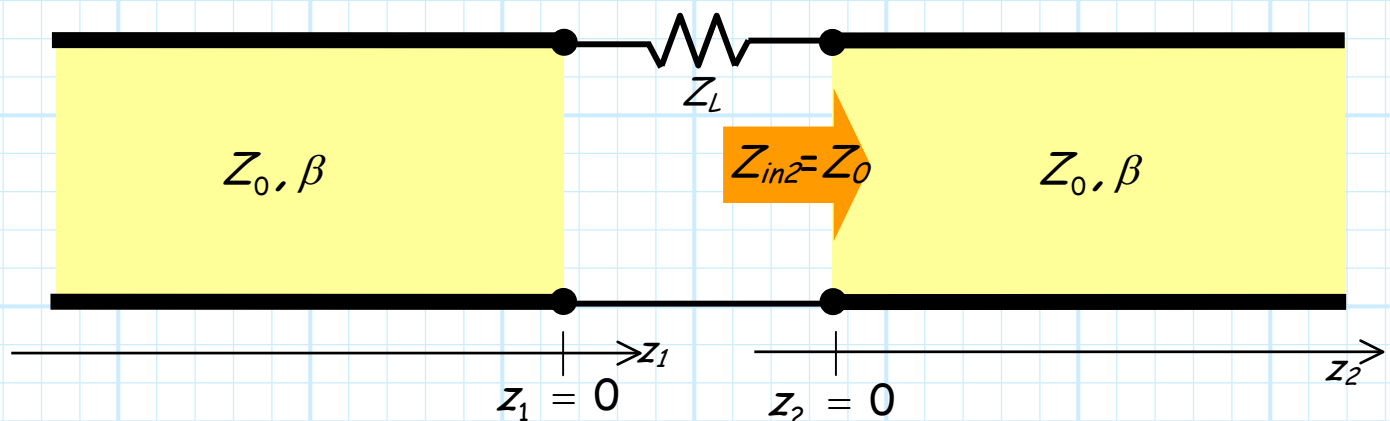Note that since the second line is (eventually) terminated in a matched load, the input impedance at the **beginning** of the **second** line is simply equal to  $Z_0$ .





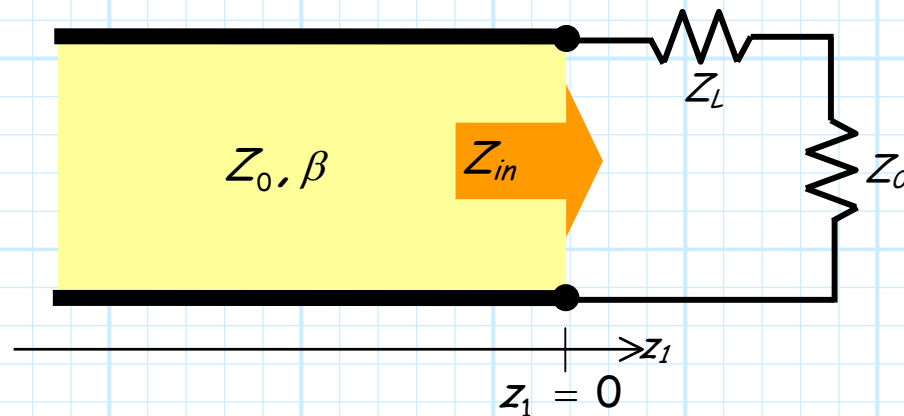
Thus, the **equivalent** circuit becomes:



And it is apparent that:

$$Z_{in} = Z_L + Z_0$$

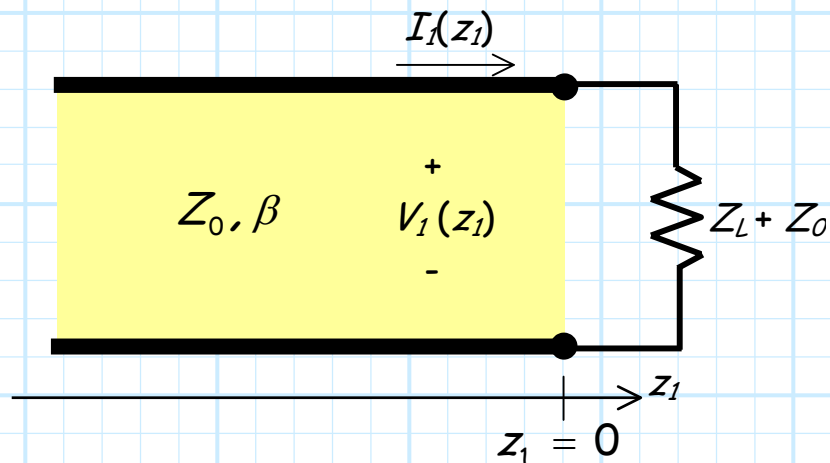As far as the first section of transmission line is concerned, it is **terminated** in a load with impedance  $Z_L + Z_0$ . The current and voltage along this first transmission line is **precisely** the same as if it **actually** were!



Thus, we find that  $\Gamma_0 = V_{01}^- / V_{01}^+$ , where:

$$\begin{aligned}\Gamma_0 &= \frac{Z(z_1=0) - Z_0}{Z(z_1=0) + Z_0} \\ &= \frac{(Z_L + Z_0) - Z_0}{(Z_L + Z_0) + Z_0} \\ &= \frac{Z_L}{Z_L + 2Z_0}\end{aligned}$$


**Precisely** the same result as before!

Now, one **more** point. Recall we found in an **earlier** handout that  $T_0 = 1 + \Gamma_0$ . But for this example we find that this statement is **not valid**:

$$1 + \Gamma_0 = \frac{2(Z_L + Z_0)}{Z_L + 2Z_0} \neq T_0$$

Again, be **careful** when analyzing microwave circuits!

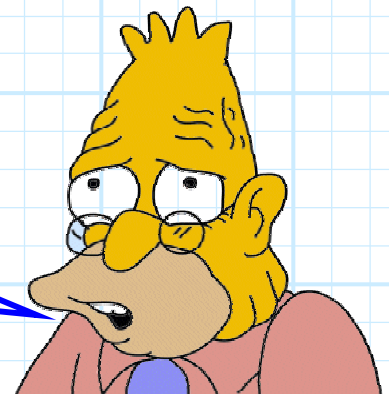**Q:** *But this seems so difficult. How will I know if I have made a mistake?*



**A:** An important engineering tool that **you** must master is commonly referred to as the "**sanity check**".

Simply put, a sanity check is simply **thinking** about your result, and determining whether or not it **makes sense**. A great **strategy** is to set one of the variables to a value so that the **physical** problem becomes **trivial**—so trivial that the correct answer is **obvious** to you. Then make sure your results **likewise** provide this obvious answer!


For example, consider the problem we just finished analyzing. Say that the impedance  $Z_L$  is actually a **short** circuit ( $Z_L=0$ ). We find that:

$$\Gamma_0 = \left. \frac{Z_L}{Z_L + 2Z_0} \right|_{Z_L=0} = 0 \quad T_0 = \left. \frac{2Z_0}{2Z_0 + Z_L} \right|_{Z_L=0} = 1$$


Likewise, consider the case where  $Z_L$  is actually an **open** circuit ( $Z_L=\infty$ ). We find that:

$$\Gamma_0 = \left. \frac{Z_L}{Z_L + 2Z_0} \right|_{Z_L=\infty} = 1 \quad T_0 = \left. \frac{2Z_0}{2Z_0 + Z_L} \right|_{Z_L=\infty} = 0$$

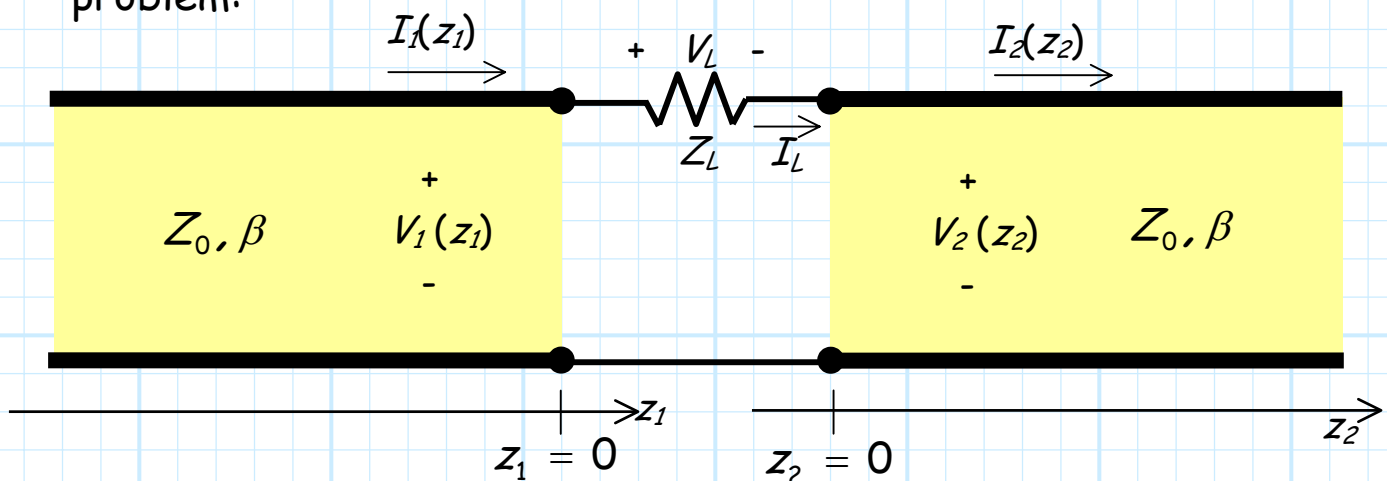**Think** about what these results mean in terms of the **physical** problem:



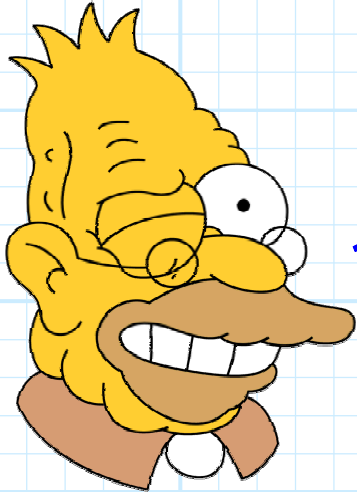**Q:** Do these results **make sense**? Have we **passed** the sanity check?



**A:** *I'll let **you** decide!*  
*What do you **think**?*