

2.6 - Generator and Load Mismatches

Reading Assignment: pp. 77-79

Q: *How is the incident wave $V^+(z)$ generated on a transmission line?*

A:

HO: A Transmission Line Connecting Source and Load

Q: *So, how can we determine the power delivered by a source?*

A: HO: Delivered Power


Q: *So how do we insure that the delivered power is as large as possible?*

A: HO: Special Cases of Source and Load Impedance


A Transmission Line Connecting Source & Load

We can think of a transmission line as a conduit that allows **power to flow from an output of one device/network to an input of another.**

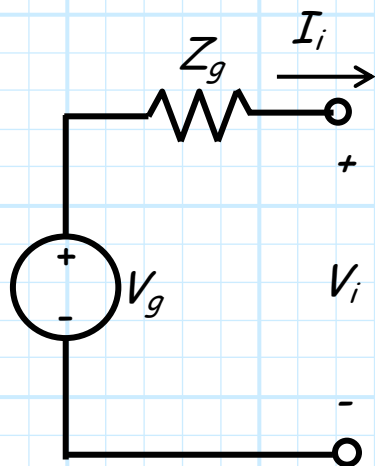To simplify our analysis, we can model the **input** of the device **receiving** the power with its input impedance (e.g., Z_L), while we can model the device **output delivering** the power with its Thevenin's or Norton's equivalent circuit.




$$V_g = V_i + Z_g I_i$$

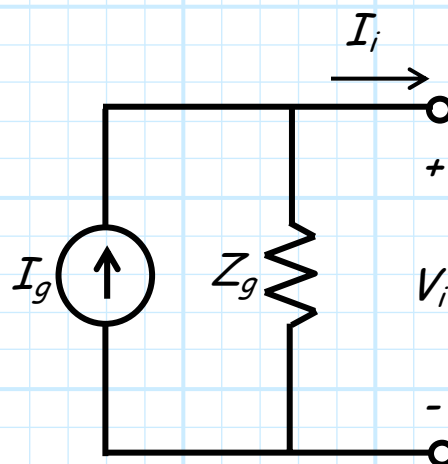

$$I_g = \frac{V_i}{Z_g} + I_i$$

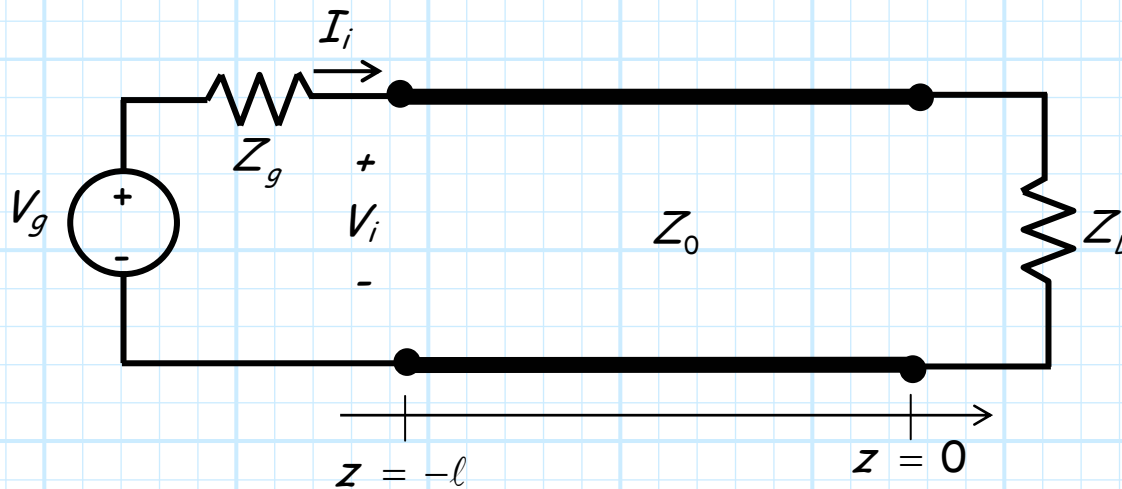Typically, the power source is modeled with its **Thevenin's** equivalent; however, we will find that the **Norton's** equivalent circuit is useful if we express the remainder of the circuit in terms of its **admittance** values (e.g., $Y_0, Y_L, Y(z)$).



Recall from the telegrapher's equations that the current and voltage along the transmission line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

At $z = 0$, we enforced the **boundary condition** resulting from Ohm's Law:

$$Z_L = \frac{V_L}{I_L} = \frac{V(z=0)}{I(z=0)} = \frac{(V_0^+ + V_0^-)}{\left(\frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}\right)}$$

Which resulted in:

$$\frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \doteq \Gamma_L$$

So therefore:

$$V(z) = V_0^+ [e^{-j\beta z} + \Gamma_L e^{+j\beta z}]$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma_L e^{+j\beta z}]$$

We are left with the **question**: just what is the **value** of complex constant V_0^+ ?!?

This constant depends on the signal **source**! To determine its exact **value**, we must now apply **boundary conditions** at $z = -\ell$.

We know that at the **beginning** of the transmission line:


$$V(z = -\ell) = V_0^+ [e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell}]$$

$$I(z = -\ell) = \frac{V_0^+}{Z_0} [e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell}]$$

Likewise, we know that the **source** must satisfy:

$$V_g = V_i + Z_g I_i$$

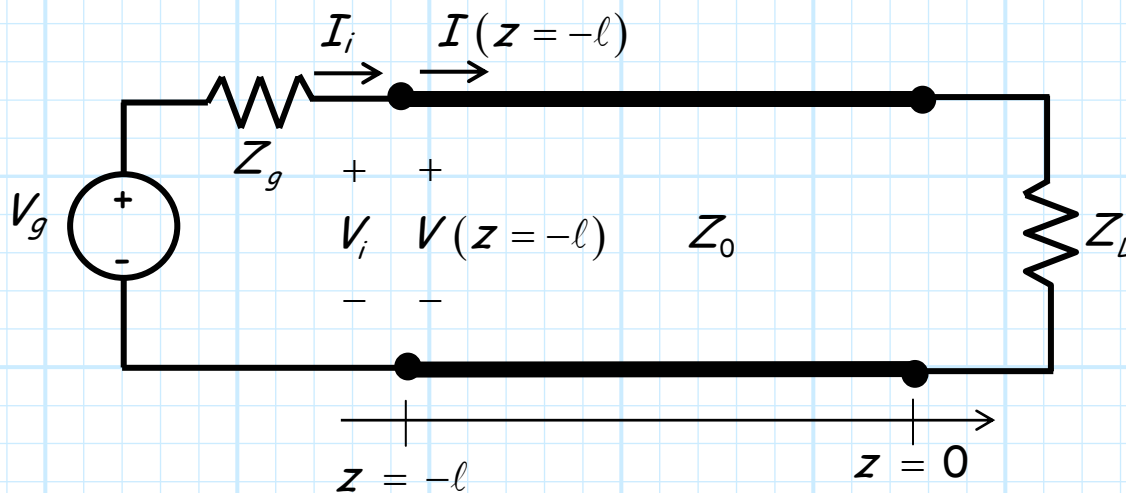To relate these **three** expressions, we need to apply **boundary conditions** at $z = -\ell$:



From **KVL** we find:

$$V_i = V(z = -\ell)$$

And from **KCL**:

$$I_i = I(z = -\ell)$$

Combining these equations, we find:

$$V_g = V_i + Z_g I_i$$

$$V_g = V_0^+ \left[e^{+j\beta\ell} + \Gamma_L e^{-j\beta\ell} \right] + Z_g \frac{V_0^+}{Z_0} \left[e^{+j\beta\ell} - \Gamma_L e^{-j\beta\ell} \right]$$

One equation \rightarrow **one unknown** (V_0^+)!!

Solving, we find the value of V_0^+ :



$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

where:

$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$

Note this result looks different than the equation in your textbook (eq. 2.71):

$$V_0^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta\ell}}{(1 - \Gamma_L \Gamma_g e^{-j2\beta\ell})}$$



where:

$$\Gamma_g \doteq \frac{Z_g - Z_0}{Z_g + Z_0}$$

I like **my** expression better.

Although the two equations are equivalent, **my** expression is explicitly written in terms of $\Gamma_{in} = \Gamma(z = -\ell)$ (a very **useful**, **precise**, and **unambiguous** value), while the book's expression is written in terms of this **so-called** "source reflection coefficient" Γ_g (a **misleading**, **confusing**, **ambiguous**, and mostly **useless** value).

Specifically, we might be **tempted** to equate Γ_g with the value $\Gamma(z = -\ell) = \Gamma_{in}$, but it is **not** ($\Gamma_g \neq \Gamma(z = -\ell)$)!

There is one **very important** point that must be made about the result:

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

And that is—the wave $V_0^+(z)$ **incident** on the load Z_L is actually dependent on the value of load Z_L !!!!!

Remember:

$$\Gamma_{in} = \Gamma(z = -\ell) = \Gamma_L e^{-j2\beta\ell}$$


We tend to think of the incident wave $V_0^+(z)$ being “**caused**” by the source, and it is certainly true that $V_0^+(z)$ **depends** on the source—after all, $V_0^+(z) = 0$ if $V_g = 0$. However, we find from the equation above that it **likewise** depends on the value of the load!

Remember, this solution is a **steady-state** solution. Just like the **multiple reflection** viewpoint for a $\lambda/4$ transformer, we can (sort of) view the waves on this transmission line as “bouncing” back and forth until the boundary conditions are satisfied at **both** ends.

Thus we **cannot**—in general—consider the incident wave to be the “**cause**” and the reflected wave the “**effect**”. Instead, each wave must obtain the proper **amplitude** (e.g., V_0^+, V_0^-) so that the boundary conditions are satisfied at **both** the beginning and end of the transmission line.

Delivered Power

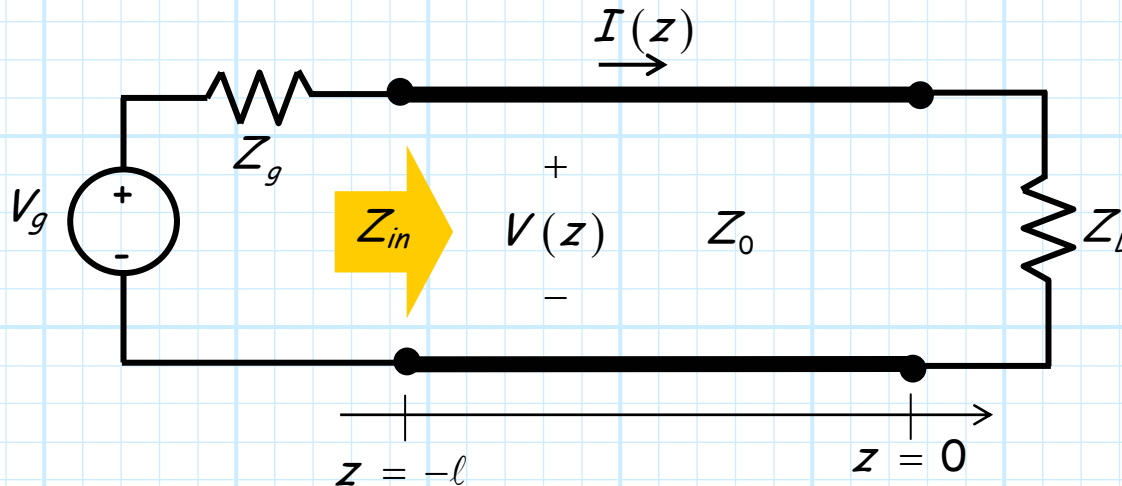Q: If the purpose of a transmission line is to transfer **power** from a source to a load, then exactly how much power is **delivered** to Z_L for the circuit shown below ??



A: We of course **could** determine V_0^+ and V_0^- , and then determine the power absorbed by the load (P_{abs}) as:


$$P_{abs} = \frac{1}{2} \text{Re} \{ V(z=0) I^*(z=0) \}$$

However, if the transmission line is **lossless**, then we know that the power delivered to the load must be **equal** to the power "delivered" to the **input** (P_{in}) of the transmission line:

$$P_{abs} = P_{in} = \frac{1}{2} \text{Re} \{ V(z=-l) I^*(z=-l) \}$$

However, we can determine this power **without** having to solve for V_0^+ and V_0^- (i.e., $V(z)$ and $I(z)$). We can simply use our knowledge of **circuit theory!**

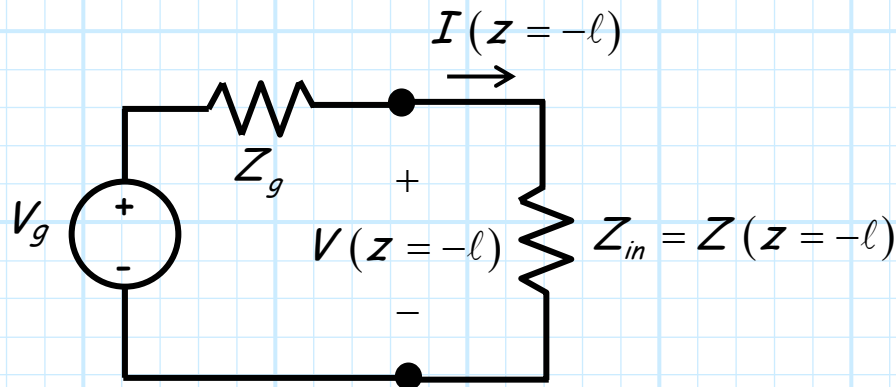We can **transform** load Z_L to the beginning of the transmission line (by direct calculation—or with a Smith Chart!), so that we can replace the transmission line with its **input impedance** Z_{in} :



Note by **voltage division** we can determine:

$$V(z = -l) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from **Ohm's Law** we conclude:

$$I(z = -l) = \frac{V_g}{Z_g + Z_{in}}$$

And thus, the **power** P_{in} delivered to Z_{in} (and thus the **power** P_{abs} delivered to the load Z_L) is:

$$\begin{aligned}
 P_{abs} &= P_{in} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{V_g^*}{(Z_g + Z_{in})^*} \right\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \} \\
 &= \frac{1}{2} |V_g|^2 \frac{|Z_{in}|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ y_{in} \}
 \end{aligned}$$

Note that we could **also** determine P_{abs} from our **earlier** expression:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

But we would of course have to **first** determine V_0^+ (!):

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$

Special Cases of Source and Load Impedance

Let's look at **specific cases** of Z_g and Z_L , and determine how they affect V_0^+ and P_{abs} .

$$Z_g = Z_0$$

For this case, we find that V_0^+ **simplifies** greatly:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_0(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{1}{1 + \Gamma_{in} + 1 - \Gamma_{in}} \\ &= \frac{1}{2} V_g e^{-j\beta\ell} \end{aligned}$$

Look at what **this** says!

It says that the incident wave in this case is **independent** of the load attached at the other end!

Thus, for the **one** case $Z_g = Z_0$, we in fact can consider $V^+(z)$ as being the result of the source alone, and then the reflected wave $V^-(z)$ as being the result of this stimulus.

Remember, the complex value V_0^+ is the value of the incident wave evaluated at the **end** ($z_L=0$) of the transmission line ($V_0^+ = V^+(z=0)$). We can likewise determine the value of the incident wave at the **beginning** of the transmission line (i.e., $V^+(z=-\ell)$). For this case, where $Z_g = Z_0$, we find that this value is very simply stated (!):

$$\begin{aligned} V^+(z=-\ell) &= V_0^+ e^{-j\beta(z=-\ell)} \\ &= \left(\frac{1}{2} V_g e^{-j\beta\ell} \right) e^{+j\beta\ell} \\ &= \frac{V_g}{2} \end{aligned}$$

Likewise, we find that the delivered power for this case can be simply stated as:

$$\begin{aligned} P_{abs} &= \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) \\ &= \frac{|V_g|^2}{8 Z_0} (1 - |\Gamma_L|^2) \end{aligned}$$

$$Z_L = Z_0$$

In this case, we find that $\Gamma_L = 0$, and thus $\Gamma_{in} = 0$. As a result:

$$\begin{aligned} V_0^+ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \\ &= V_g e^{-j\beta\ell} \frac{Z_0}{Z_0 + Z_g} \end{aligned}$$

Likewise, we find that:

$$\begin{aligned} P_{abs} &= \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2) \\ &= \frac{|V_0^+|^2}{2Z_0} \\ &= \frac{|V_g|^2}{2Z_0} \frac{(Z_0)^2}{|Z_0 + Z_g|^2} \\ &= \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2} \end{aligned}$$

Note that this result can likewise be found by recognizing that $Z_{in} = Z_0$ when $Z_L = Z_0$:

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_0|^2} Z_0 \\
 &= \frac{|V_g|^2}{2} \frac{Z_0}{|Z_g + Z_0|^2}
 \end{aligned}$$

$$Z_{in} = Z_g^*$$

For this case, we find Z_L takes on whatever value required to make $Z_{in} = Z_g^*$. This is a **very** important case!

First, using the fact that:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_g^* - Z_0}{Z_g^* + Z_0}$$

We can show that (trust me!):

$$V_0^+ = V_g e^{-j\beta l} \frac{Z_g^* + Z_0}{4 \operatorname{Re}\{Z_g\}}$$


Not a particularly interesting result, but let's look at the absorbed power.

$$\begin{aligned}
 P_{abs} &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re}\{Z_{in}\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_g^*|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|2\operatorname{Re}\{Z_g^*\}|^2} \operatorname{Re}\{Z_g^*\} \\
 &= \frac{1}{2} |V_g|^2 \frac{1}{4\operatorname{Re}\{Z_g^*\}}
 \end{aligned}$$

Although this result does not look particularly interesting **either**, we find the result is **very** important!

It can be shown that—for a **given** V_g and Z_g —the value of input impedance Z_{in} that will absorb the **largest possible** amount of power is the value $Z_{in} = Z_g^*$.

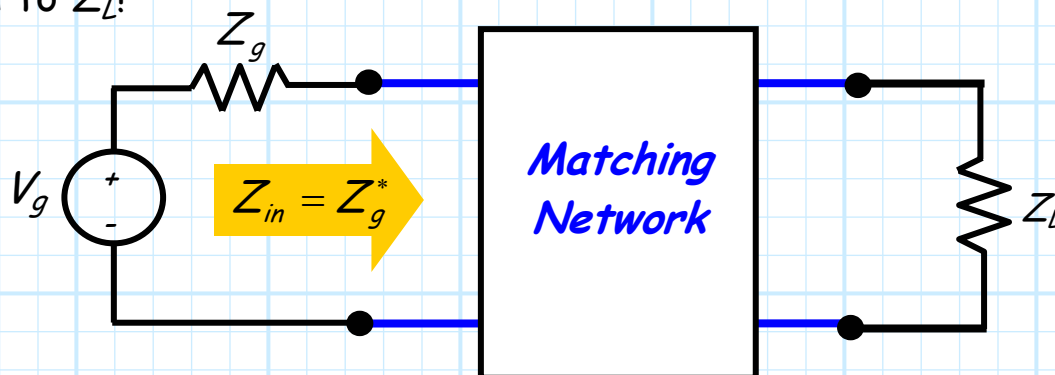
This case is known as the **conjugate match**, and is essentially the goal of every matching network—after all, the largest possible power delivered to Z_{in} is the **largest possible** power delivered to Z_L !



There are **two** very important things to understand about this result!

Very Important Thing #1

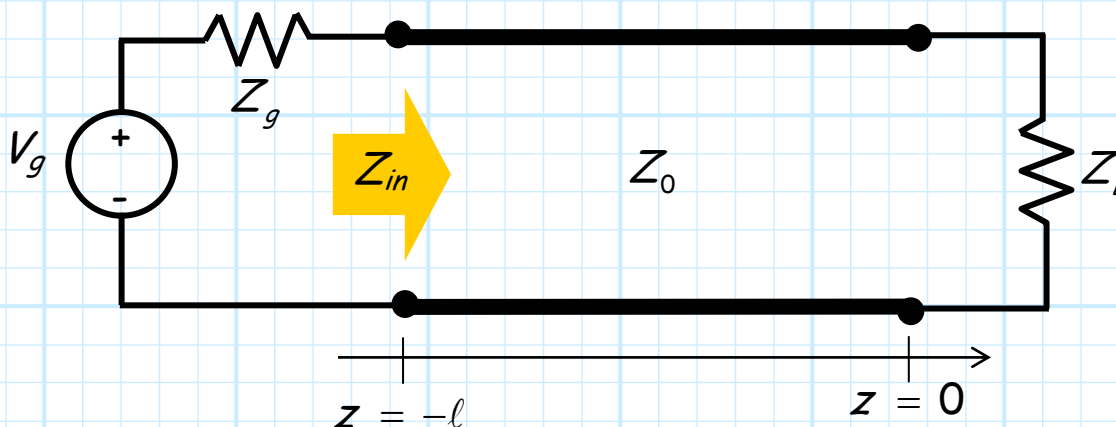Consider again the terminated transmission line:



Recall that if $Z_L = Z_0$, the **reflected** wave will be **zero**, and the absorbed power will be:

$$P_{abs} = \frac{|V_g|^2}{2} \frac{Z_0}{|Z_0 + Z_g|^2}$$

But note if $Z_L = Z_0$, then the input impedance $Z_{in} = Z_0$ but then $Z_{in} \neq Z_g^*$ (generally)! In other words, $Z_L = Z_0$ does **not** (generally) result in a **conjugate match**, and thus setting $Z_L = Z_0$ does **not** result in maximum power absorption!

Q: Wait! This makes **no** sense to me! A load value of $Z_L = Z_0$ will **minimize** the reflected wave ($P^- = 0$)—**all** of the incident power will be absorbed. Any other value of $Z_L \neq Z_0$ will result in **some** of the incident wave being reflected—how in the world could this **increase** absorbed power?

After all, just **look** at the expression for absorbed power:

$$P_{abs} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2)$$

Clearly, this value is maximized when $\Gamma_L = 0$ (i.e., when $Z_L = Z_0$)!!! Isn't it ????




A: You are forgetting one very important fact! Although it is true that the load impedance Z_L affects the **reflected** wave power P^- , the value of Z_L —as we have shown in this handout—**likewise** helps determine the value of the **incident** wave (i.e., the value of P^+) as well.

Thus, the value of Z_L that minimizes P^- will **not** generally maximize P^+ , **nor** will the value of Z_L that maximizes P^+ likewise minimize P^- .

Instead, the value of Z_L that maximizes the **absorbed** power is, by definition, the value that maximizes the **difference** $P^+ - P^-$.

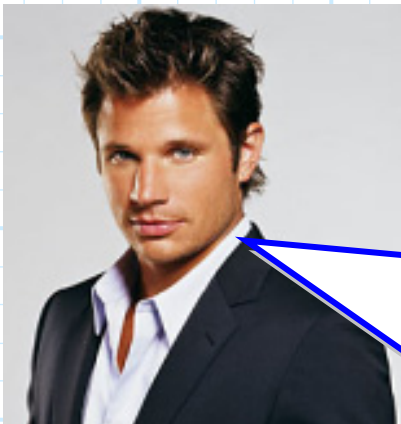We find that this value of Z_L is the value that makes Z_{in} as "close" as possible to the **ideal** case of $Z_{in} = Z_g^*$.



Q: Yes, but what about the case where $Z_g = Z_0$? For that case, we determined that the incident wave is independent of Z_L . Thus, it would seem that at least for that case, the **delivered** power would be maximized when the **reflected** power was minimized (i.e., $Z_L = Z_0$).

A: True! But think about what the **input** impedance would be in that case— $Z_{in} = Z_0$. Oh by the way, that provides a **conjugate match** ($Z_{in} = Z_0 = Z_g^*$)!

Thus, in some ways, the case $Z_g = Z_0 = Z_L$ (i.e., **both** source and load impedances are equal to Z_0) is **ideal**. A **conjugate match** occurs, the incident wave is **independent** of Z_L , there is **no** reflected wave, and all the math **simplifies** quite nicely:

$$V_0^+ = \frac{1}{2} V_g e^{-j\beta\ell}$$

$$P_{abs} = \frac{|V_g|^2}{8 Z_0}$$

Very Important Thing #2

Note the conjugate match criteria **says**:

Given V_g and Z_g , maximum power transfer occurs when

$$Z_{in} = Z_g^*.$$

It does **NOT** say:

Given V_g and Z_{in} , maximum power transfer occurs when

$$Z_g^* = Z_{in}.$$

This last statement is in fact **false!**

A **factual** statement is this:

Given V_g and Z_{in} , maximum power transfer occurs when:

$$\text{Re}\{Z_g\} = 0 \quad \text{and} \quad \text{Im}\{Z_g\} = -\text{Im}\{Z_{in}\}$$

A fact that is **evident** when observing the expression:

$$P_{abs} = \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \text{Re}\{Z_{in}\}$$

In other words, given a choice, use a source with the **smallest** possible **output resistance** (given that V_g remains **constant**).