

## 5.8 - Tapered Lines

**Reading Assignment:** *pp. 255-261*

We can also build matching networks where the characteristic impedance of a transmission line changes **continuously** with position  $z$ .

We call these matching networks **tapered lines**.

**HO: TAPERED LINES**