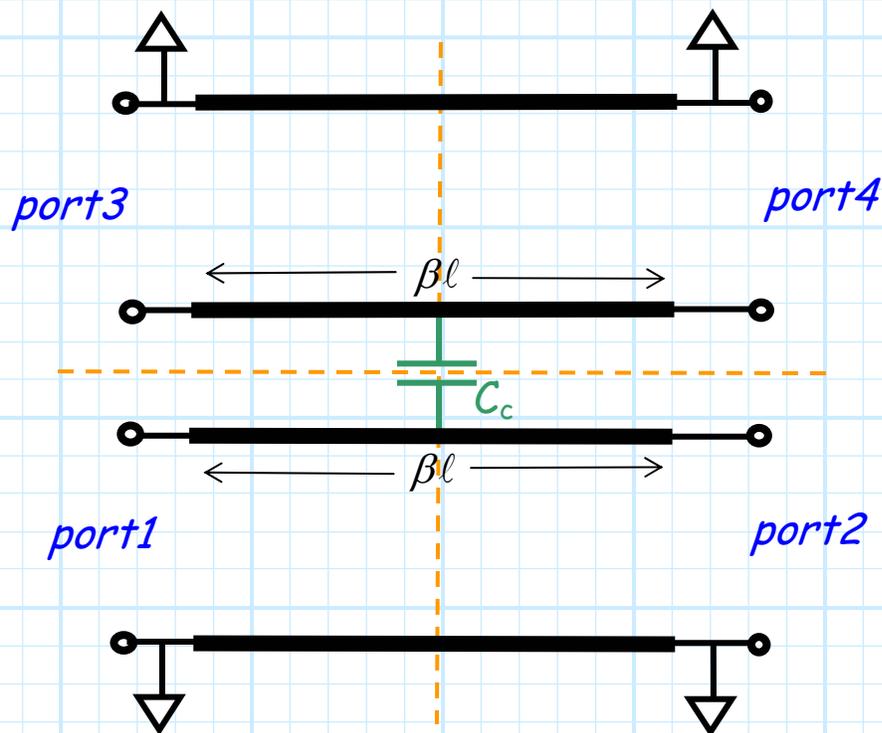


Analysis and Design of Coupled-Line Couplers


A pair of coupled lines forms a **4-port** device with **two** planes of reflection symmetry—it exhibits D_4 symmetry.




As a result, we know that the **scattering matrix** of this four-port device has just **4 independent** elements:

$$S = \begin{bmatrix} S_{11} & S_{21} & S_{31} & S_{41} \\ S_{21} & S_{11} & S_{41} & S_{31} \\ S_{31} & S_{41} & S_{11} & S_{21} \\ S_{41} & S_{31} & S_{21} & S_{11} \end{bmatrix}$$

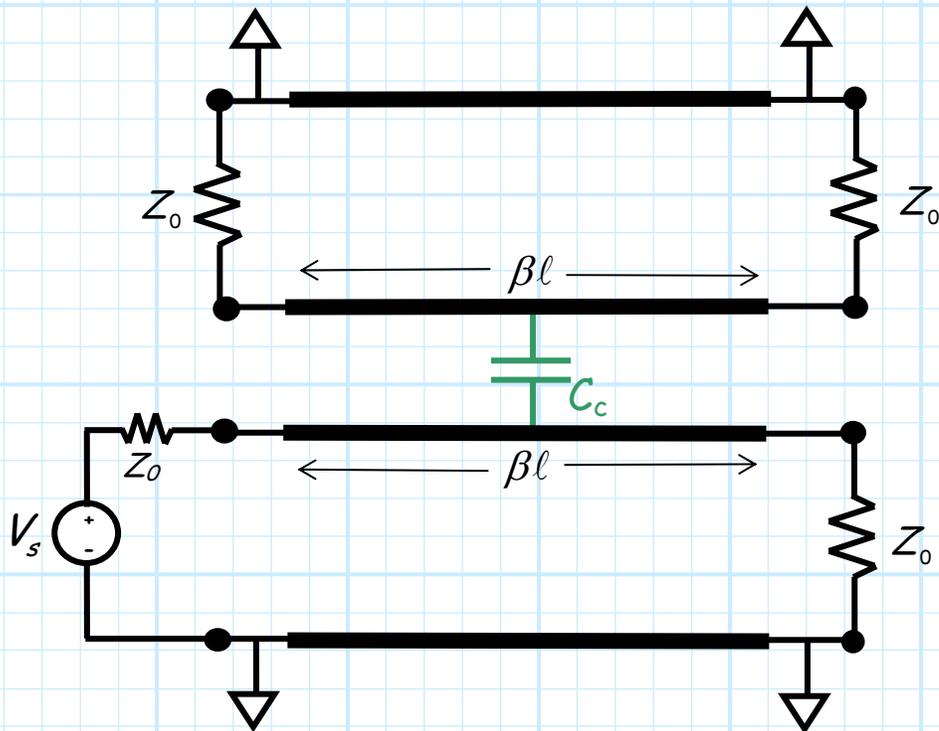
To determine these four elements, we can apply a **source to port 1** and then **terminate all other ports**:



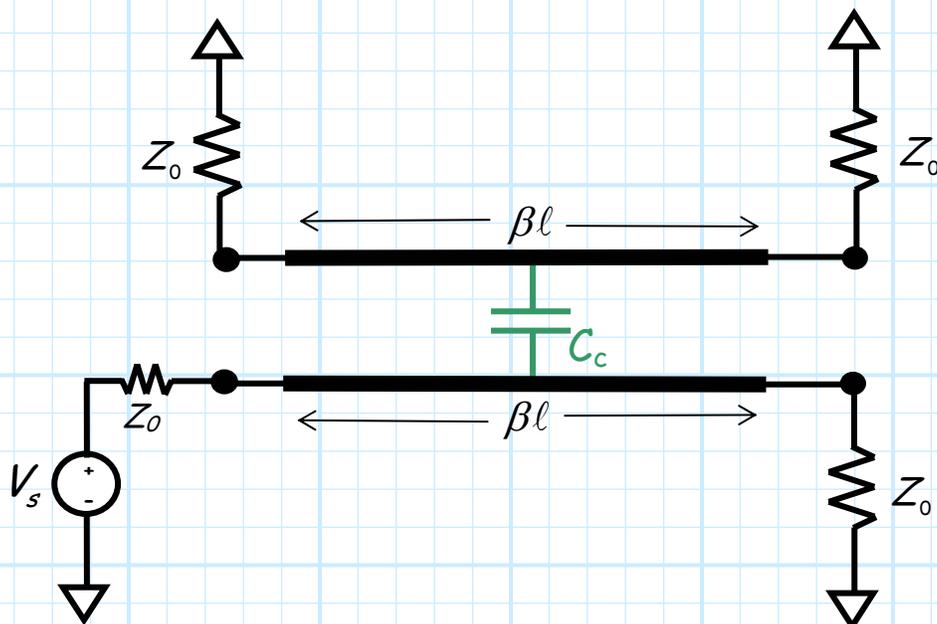Typically, a coupled-line coupler schematic is drawn **without** explicitly showing the **ground conductors** (i.e., without the ground plane):



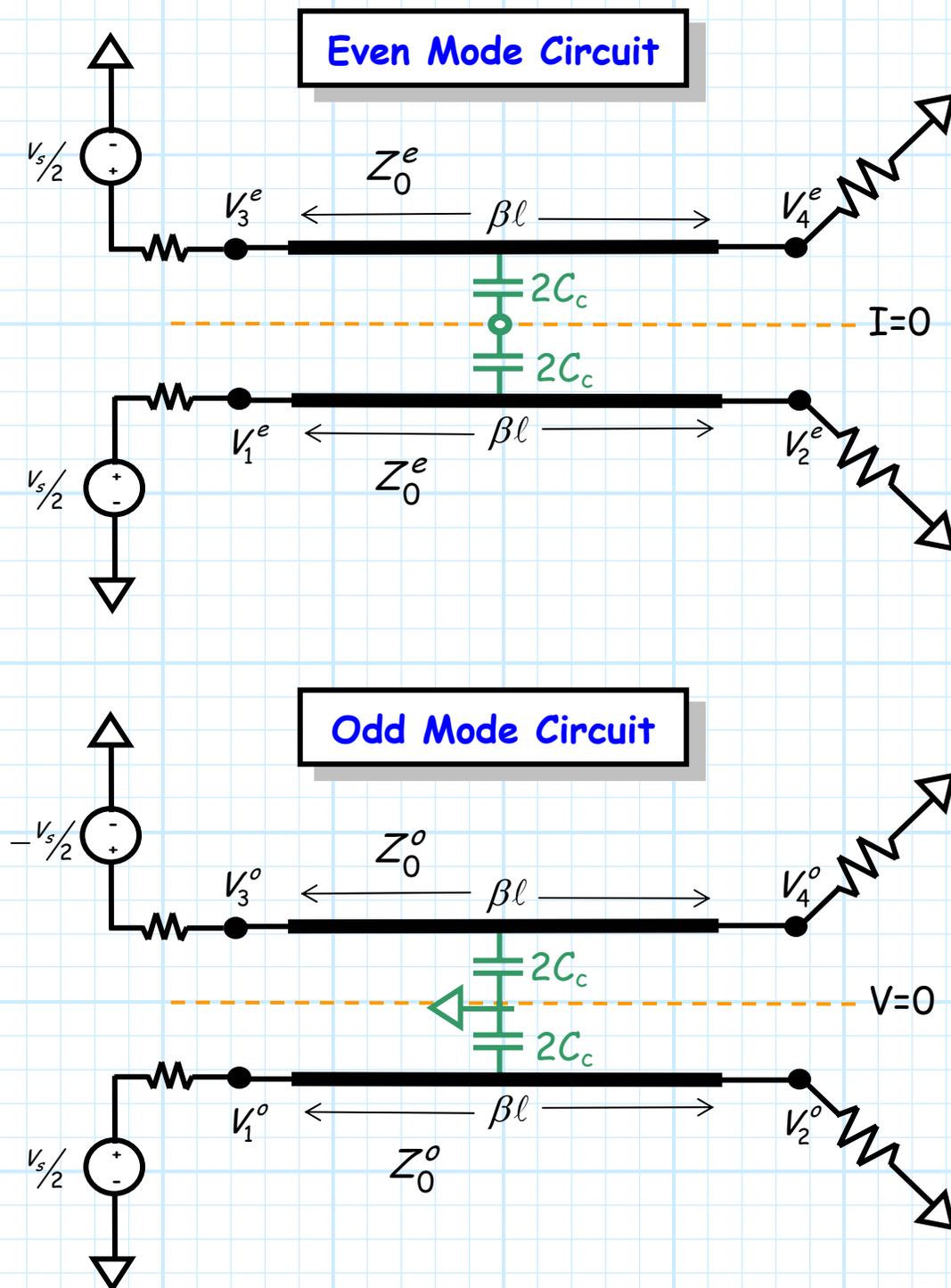To analyze this circuit, we must apply **odd/even mode analysis**. The two circuit analysis modes are:



Note that the **capacitive coupling** associated with these modes are different, resulting in a **different** characteristic impedance of the lines for the two cases (i.e., Z_0^e, Z_0^o).

Q: *So what?*

A: Consider what would happen if the characteristic impedance of each line were **identical** for **each mode**:

$$Z_0^e = Z_0^o = Z_0$$


For this situation we would find that:

$$V_3^e = -V_3^o \quad \text{and} \quad V_4^e = -V_4^o$$

and thus when applying **superposition**:

$$V_3 = V_3^e + V_3^o = 0 \quad \text{and} \quad V_4 = V_4^e + V_4^o = 0$$

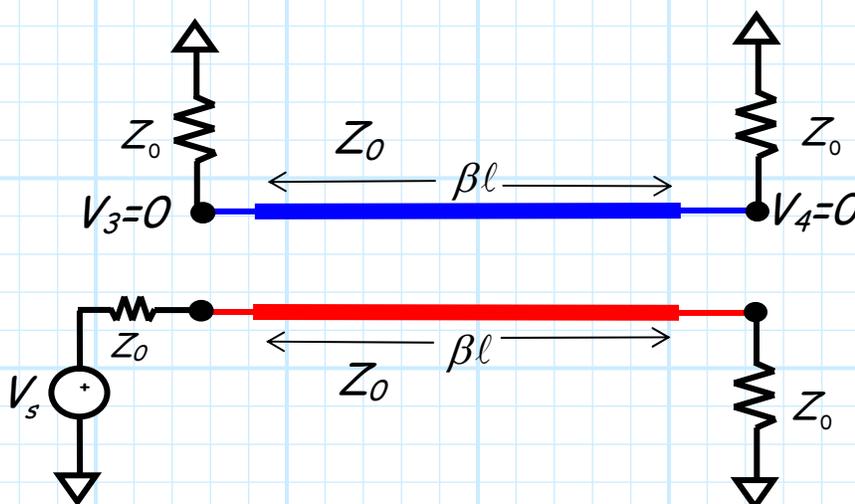indicating that **no power is coupled** from the **"energized"** transmission line onto the **"passive"** transmission line.



This makes sense! After all, if no coupling occurs, then the characteristic impedance of each line is **unaltered** by the presence of the other—their characteristic impedance is Z_0 **regardless** of “mode”.


However, if coupling **does** occur, then $Z_0^e \neq Z_0^o$, meaning in general:

$$V_3^e \neq -V_3^o \quad \text{and} \quad V_4^e \neq -V_4^o$$

and thus in general:

$$V_3 = V_3^e + V_3^o \neq 0 \quad \text{and} \quad V_4 = V_4^e + V_4^o \neq 0$$

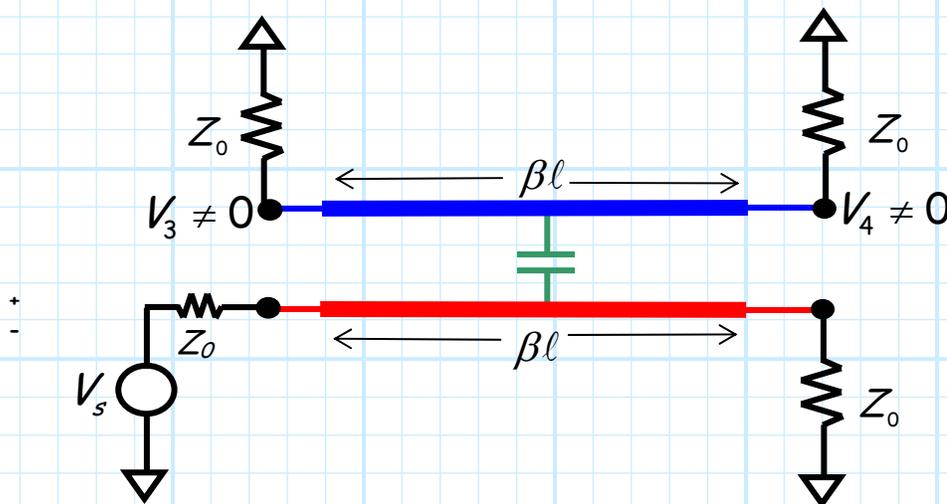The odd/even mode analysis thus reveals the amount of **coupling from the energized section onto the passive section!**



Now, our **first step** in performing the odd/even mode analysis will be to determine scattering parameter S_{11} . To accomplish this, we will need to determine voltage V_1 :

$$V_1 = V_1^e + V_1^o$$

The result is a bit complicated, so it won't be presented here. However, a question we might ask is, what value **should** S_{11} be?

Q: *What value should S_{11} be?*

A: For the device to be a **matched** device, it must be **zero!**

From the value of S_{11} derived from our odd/even analysis, ICBST (it can be shown that) S_{11} will be equal to zero if the odd and even mode characteristic impedances are related as:

$$Z_0^e Z_0^o = Z_0^2$$

In other words, we should design our coupled line coupler such that the **geometric mean** of the even and odd mode impedances is **equal to Z_0** .

Now, assuming this design rule has been implemented, we also find (from odd/even mode analysis) that the scattering parameter S_{31} is:

$$S_{31}(\beta) = \frac{j(Z_0^e - Z_0^o)}{2Z_0 \cot \beta l + j(Z_0^e + Z_0^o)}$$

Thus, we find that **unless** $Z_0^e = Z_0^o$, power must be coupled from port 1 to port 3!

Q: *But what is the value of line **electrical length** βl ?*

A: The **electrical length** of the coupled transmission lines is also a **design parameter**. Assuming that we want to **maximize** the coupling onto port 3 (at design frequency ω_0), we find from the expression above that this is accomplished if we set $\beta_0 l$ such that:

$$\cot \beta_0 l = 0$$

Which occurs when the **line length** is set to:

$$\beta_0 l = \pi/2 \quad \Rightarrow \quad l = \lambda_0/4$$

Once again, our design rule is to set the transmission line length to a value equal to **one-quarter wavelength** (at the design frequency).

$$l = \lambda_0/4$$

Implementing these **two** design rules, we find that at the design frequency:

$$S_{31} = \frac{Z_0^e - Z_0^o}{Z_0^e + Z_0^o}$$

This value is a **very** important one with respect to coupler performance. Specifically, it is the **coupling coefficient** c !

$$c = \frac{Z_0^e - Z_0^o}{Z_0^e + Z_0^o}$$

Given this definition, we can **rewrite** the scattering parameter S_{31} as:

$$S_{31}(\beta) = \frac{jc \tan \beta l}{\sqrt{1-c^2} + j \tan \beta l}$$

Continuing with our odd/even mode analysis, we find (given that $Z_0^e Z_0^o = Z_0^2$):

$$S_{21} = \frac{\sqrt{1-c^2}}{\sqrt{1-c^2} \cos \beta l + j \sin \beta l}$$

and so at our **design frequency**, where $\beta_0 l = \pi/2$, we find:

$$S_{21}(\beta) \Big|_{\beta l = \pi/2} = \frac{\sqrt{1-c^2}}{\sqrt{1-c^2}(0) + j(1)} = -j\sqrt{1-c^2}$$

Finally, our odd/even analysis reveals that at our design frequency:

$$S_{41} = 0$$


Combining these results, we find that at our **design frequency**, the **scattering matrix** of our coupled-line coupler is:

$$S = \begin{bmatrix} 0 & -j\sqrt{1-c^2} & c & 0 \\ -j\sqrt{1-c^2} & 0 & 0 & c \\ c & 0 & 0 & -j\sqrt{1-c^2} \\ 0 & c & -j\sqrt{1-c^2} & 0 \end{bmatrix}$$

Q: Hey! Isn't this the same scattering matrix as the *ideal symmetric directional coupler* we studied in the first section of this chapter?

A: The very same! The coupled-line coupler—if our design rules are followed—results in an “ideal” directional coupler.

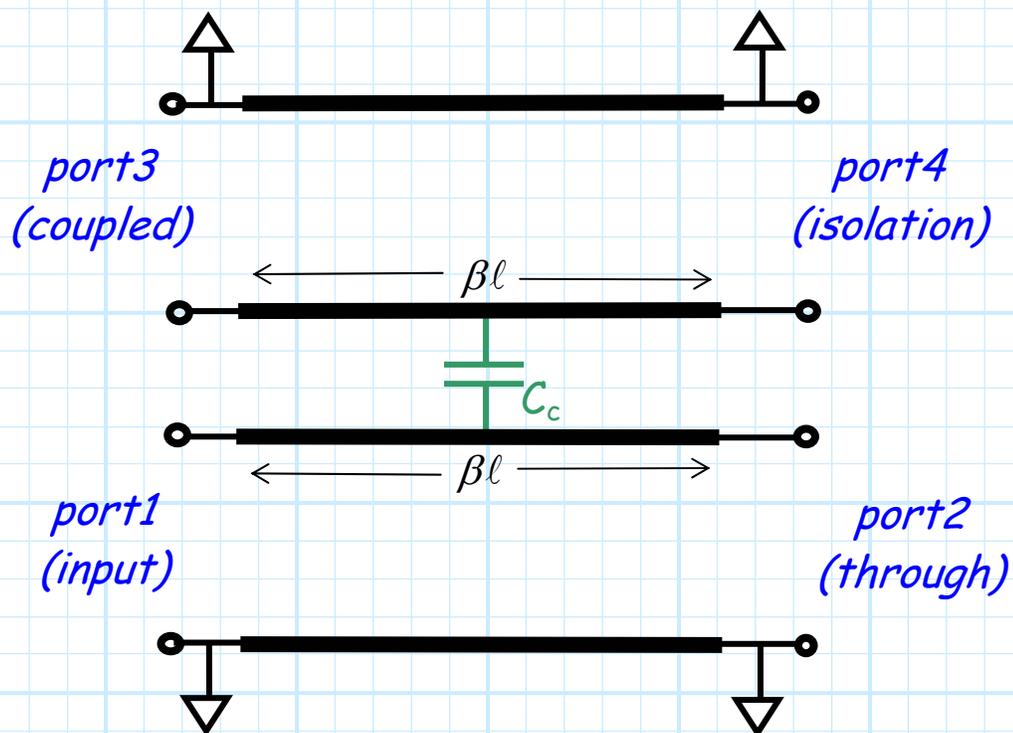If the **input** is port 1, then the **through** port is port 2, the **coupled** port is port 3, and the **isolation** port is port 4!



Q: But, how do we *design* a coupled-line coupler with a *specific* coupling coefficient c ?

A: Given our **two design constraints**, we know that:

$$Z_0^e Z_0^o = Z_0^2 \quad \text{and} \quad c = \frac{Z_0^e - Z_0^o}{Z_0^e + Z_0^o}$$

We can **rearrange** these two expressions to find **solutions** for our odd and even mode impedances:

$$Z_0^e = Z_0 \sqrt{\frac{1+c}{1-c}} \qquad Z_0^o = Z_0 \sqrt{\frac{1-c}{1+c}}$$

Thus, **given** the desired values Z_0 and c , we can determine the proper values of Z_0^e and Z_0^o for an ideal directional coupler.

Q: *Yes, but the odd and even mode impedance depends on the **physical structure** of the coupled lines, such as substrate dielectric ϵ_r , substrate thickness (d or b), conductor width W , and separation distance S .*

*How do we determine **these** physical design parameters for desired values of Z_0^e and Z_0^o ??*

A: That's a much more difficult question to answer! Recall that there is **no** direct formulation relating microstrip and stripline parameters to **characteristic impedance** (we only have numerically derived **approximations**).

* So it's no surprise that there is likewise **no direct formulation** relating odd and even mode characteristic impedances to the specific physical parameters of microstrip and stripline coupled lines.

- * Instead, we again have numerically derived **approximations** that allow us to determine (approximately) the required microstrip and stripline parameters, or we can use a **microwave CAD packages** (like ADS!).
- * For example, **figures 7.29 and 7.30** provide **charts** for selecting the required values of W and S , given some ϵ_r and b (or d).
- * Likewise, example 7.7 on page 345 provides a good **demonstration** of the single-section coupled-line coupler **design synthesis**.