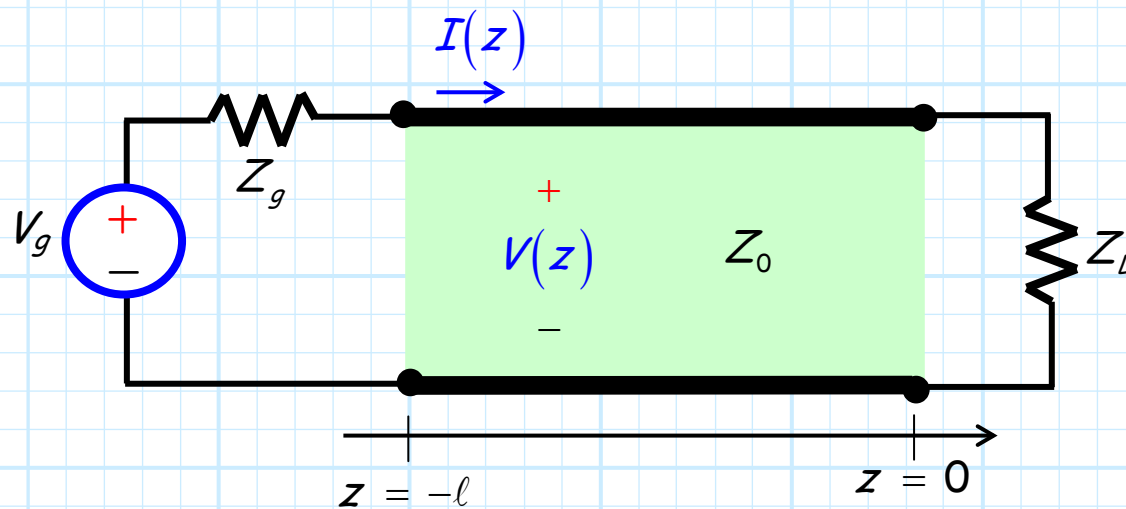


Delivered and Absorbed Power

Q: *If the purpose of a transmission line is to transfer energy from a source to a load, then exactly how at what rate is energy absorbed by load Z_L in the circuit shown below ??*




A: Now that we have a **complete** circuit (with **two** boundary conditions!), we of course can determine the numeric values of wave amplitudes V_0^+ and V_0^- .

$$V_0^+ = V_g e^{-j\beta l} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \quad \text{and} \quad V_0^- = \Gamma_L V_0^+$$

Finally! We can calculate numbers

With knowledge of V_0^+ and V_0^- , we likewise can determine the **total voltage** $V(z)$ (**finally!**) and **total current** $I(z)$ along the transmission line.

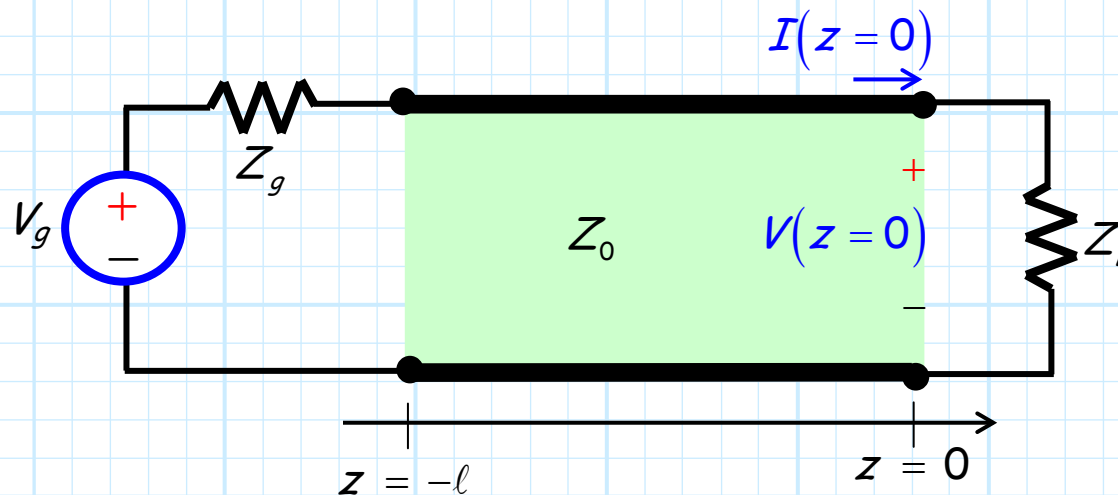Of course, we can **evaluate** this current and voltage at the load (i.e., at $z = 0$), and then directly **compute** the rate at which energy is **absorbed by the load**.



$$P_{abs} = \frac{1}{2} \text{Re} \{ V(z=0) I^*(z=0) \}$$


A truck with 30 cases of bananas...

Alternatively, we could likewise determine the absorbed power via the “wave” viewpoint, where we know that the absorbed power is simply the **difference** between the plus-wave (**incident**) and minus-wave (**reflected**).

$$P_{abs} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

But remember, this simple equation is useful **only** if we first compute the **plus-wave amplitude**:

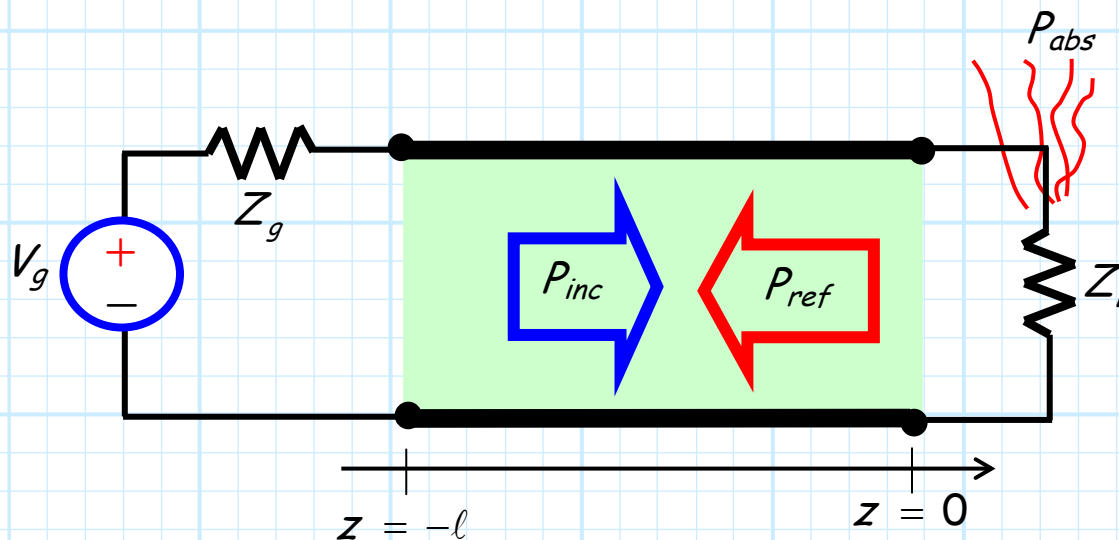
$$V_0^+ = V_g e^{-j\beta l} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})}$$



Move to the beginning of the line

Q: What about the *source*? At what rate does it deliver energy to the circuit?

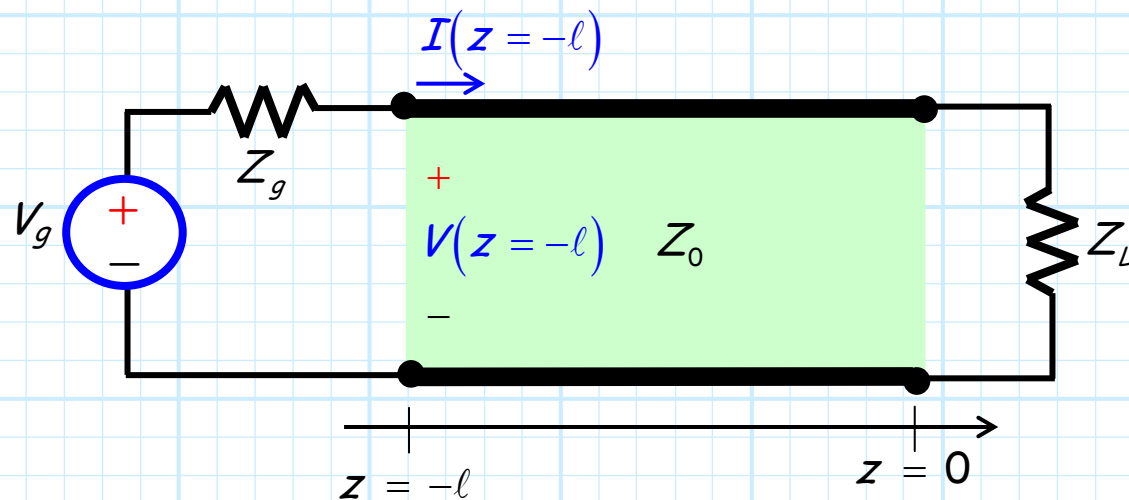A: Well, we could of course (since we know V_0^+ and V_0^-) determine the total voltage and current **at the source** (i.e., at $z = -\ell$), and then directly compute the rate at which energy is delivered **by the source**.



$$P_{del} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \}$$

Conservation of energy— it just makes thing so easy

However, since the transmission line is **lossless**, conservation of energy allows us to correctly conclude that this power **delivered by the source** is likewise the rate at which energy is **absorbed by the load**:

$$P_{abs} = P_{del}$$

Thus, all of the **three** calculations we just discussed will provide the **same correct value** for delivered/absorbed power!

$$P_{del} = \frac{1}{2} \operatorname{Re} \{ V(z = -\ell) I^*(z = -\ell) \} = \frac{|V_0^+|^2}{2 Z_0} (1 - |\Gamma_L|^2) = P_{abs} = \frac{1}{2} \operatorname{Re} \{ V(z = 0) I^*(z = 0) \} = P_{abs}$$


Again, for all three results, we **must** determine V_0^+ and V_0^- .

$$V_0^+ = V_g e^{-j\beta\ell} \frac{Z_0}{Z_0(1 + \Gamma_{in}) + Z_g(1 - \Gamma_{in})} \quad \text{and} \quad V_0^- = \Gamma_L V_0^+$$


A 4th way—a way that is even easier

However, there is one method for determining the delivered/absorbed power that does **not** require the calculation of V_0^+ !

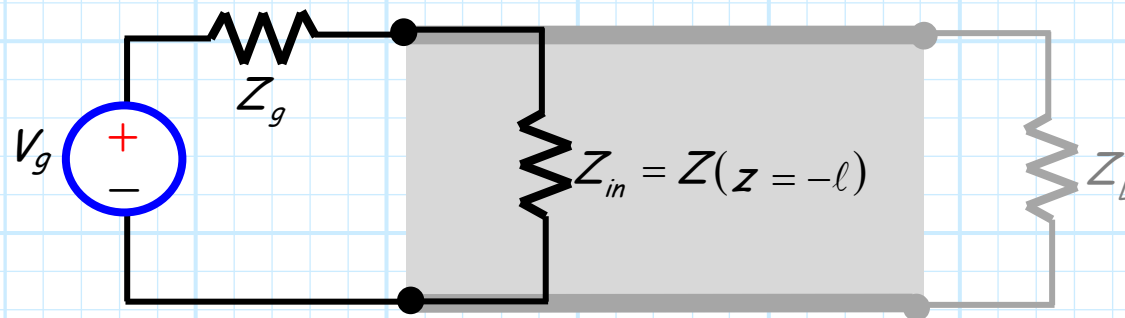Say we replace the transmission line and load with its equivalent circuit—its **input impedance**:



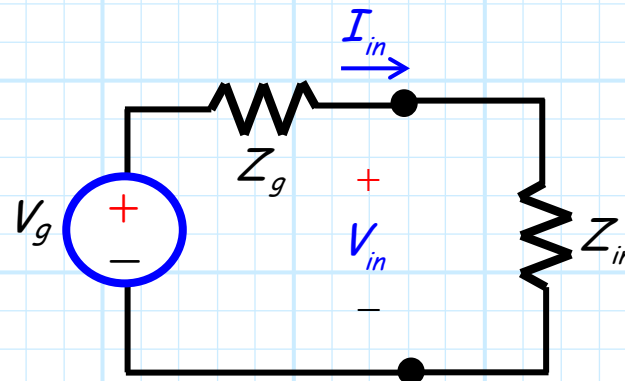Recall that we do **not** need to know V_0^+ to determine input impedance—line impedance $Z(z)$ is independent of either V_0^+ or V_0^- . The **equivalent circuit** is thus:



Dust off you introductory circuits text

Now we can easily find the power **delivered** by the source—it's simply **equal** to the rate at which energy is **absorbed** by the input impedance!


We simply have to apply beginning **circuit theory**.

Note by **voltage division** we can determine:

$$V(z = -\ell) = V_g \frac{Z_{in}}{Z_g + Z_{in}}$$

And from **Ohm's Law** we conclude:
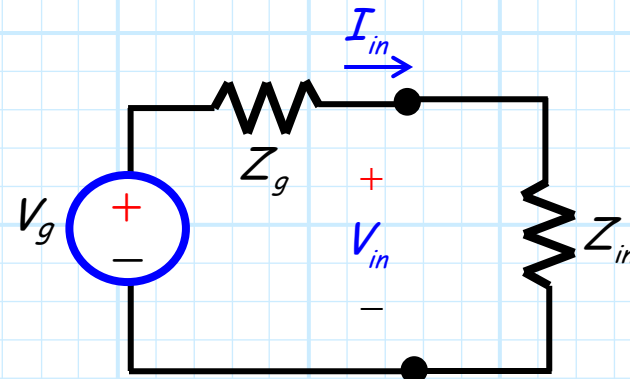
$$I(z = -\ell) = \frac{V_g}{Z_g + Z_{in}}$$



A power equation without V_0^+

And thus, the **power** P_{in} absorbed by Z_{in} (and thus the **power** P_{del} delivered by the source) is:

$$\begin{aligned}
 P_{del} = P_{in} &= \frac{1}{2} \operatorname{Re} \{ V_{in} I_{in}^* \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{V_g^*}{(Z_g + Z_{in})^*} \right\} \\
 &= \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \}
 \end{aligned}$$

By conservation of energy, we know that this is likewise the rate at which the **load** Z_L absorbs energy:

$$P_{del} = \frac{1}{2} \frac{|V_g|^2}{|Z_g + Z_{in}|^2} \operatorname{Re} \{ Z_{in} \} = P_{abs}$$