

# Design for Specified Gain

The **conjugate matched** design of course **maximizes** the transducer gain of an amplifier. But there are times when wish to design an amplifier with **less** than this maximum possible gain!

**Q:** *Why on Earth would we want to design such a **sub-optimal** amplifier?*

**A:** A general characteristic about amplifiers is that we can always trade **gain** for **bandwidth** (the gain-bandwidth product is an approximate **constant!**). Thus, if we desire a **wider** bandwidth, we must **decrease** the amplifier gain.

**Q:** *Just **how** do we go about doing this?*

**A:** We simply design a "matching" network that is actually **mismatched** to the gain element. We know that the **maximum** transducer gain will be achieved if we design a matching network such that:

$$\Gamma_s = \Gamma_{in}^* \quad \text{and} \quad \Gamma_L = \Gamma_{out}^*$$

Thus, a **reduced gain** (and so wider bandwidth) amplifier must have the characteristic that:

$$\Gamma_s \neq \Gamma_{in}^* \quad \text{and} \quad \Gamma_L \neq \Gamma_{out}^*$$

Specifically, we should select  $\Gamma_s$  and  $\Gamma_L$  (and then design the matching network) to provide the **desired** transducer gain  $G_T$ :

$$G_T = \frac{(1 - |\Gamma_s|^2) |S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - \Gamma_L S_{22}|^2} < G_{Tmax}$$

We find that there are **many values** of  $\Gamma_s$  and  $\Gamma_L$  that will provide this sub-optimal gain.

**Q:** *So which of these values do we choose?*

**A:** We choose the values of  $\Gamma_s$  and  $\Gamma_L$  that satisfies the above equation, **and** has the **smallest** of all possible magnitudes of  $|\Gamma_s|$  and  $|\Gamma_L|$ .

→ Remember—**smaller**  $|\Gamma|$  leads to **wider** bandwidth!

This design process is much easier if the gain element is **unilateral**. Recall for that case we find that the transducer gain is:

$$G_{UT} = \frac{(1 - |\Gamma_s|^2) |S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - \Gamma_s S_{11}|^2 |1 - \Gamma_L S_{22}|^2}$$

We can **rewrite** this gain as a product of **three terms**:

$$G_{UT} = G_S G_0 G_L$$

where:

$$G_S = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2}$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

Notice that the value of  $\Gamma_s$  affects  $G_S$  **only**, and the value of  $\Gamma_L$  affects  $G_L$  **only**. Therefore, the unilateral case again decouples into two **independent** problems.

We can compare the values above with their **maximum** values (when  $\Gamma_s = S_{11}^*$  and  $\Gamma_L = S_{22}^*$ ):

$$G_{Smax} = \frac{1}{1 - |S_{11}|^2}$$

$$G_0 = |S_{21}|^2$$

$$G_{Lmax} = \frac{1}{1 - |S_{22}|^2}$$

Thus, to increase the bandwidth of an amplifier, we **select** values of  $G_S$  and  $G_L$  that are **less** (typically by a few dB) than the maximum (i.e., matched) values  $G_{Smax}$  and  $G_{Lmax}$ .

Unlike the values  $G_{Smax}$  and  $G_{Lmax}$ —where there is precisely **one** solution for each ( $\Gamma_s = S_{11}^*$  and  $\Gamma_L = S_{22}^*$ )—there are an **infinite** number of  $\Gamma_s$  ( $\Gamma_L$ ) solutions for a specific value of  $G_s$  ( $G_L$ ).

**Q:** *So which do we choose?*

**A:** We choose the solutions that have the **smallest magnitude!** This will maximize our amplifier **bandwidth**.

**Q:** *How do we determine what these values are?*

**A:** We can solve these equations to determine all  $\Gamma_s$  and  $\Gamma_L$  solutions for **specified** design values of  $G_s$  and  $G_L$ .


$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \qquad G_L = \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

Just as with our stability solutions, the solutions to the equations above form **circles** when plotted on the **complex  $\Gamma$  plane**.

These circles are known as **constant gain circles**, and are defined by two values: a **complex** value  $C_s$  ( $C_L$ ) that denotes the **center** of the circle on the complex  $\Gamma$  plane, and a **real** value  $R_s$  ( $R_L$ ) that specifies the **radius** of that circle.

These solutions are provided on pages 554 and 555 of your text.

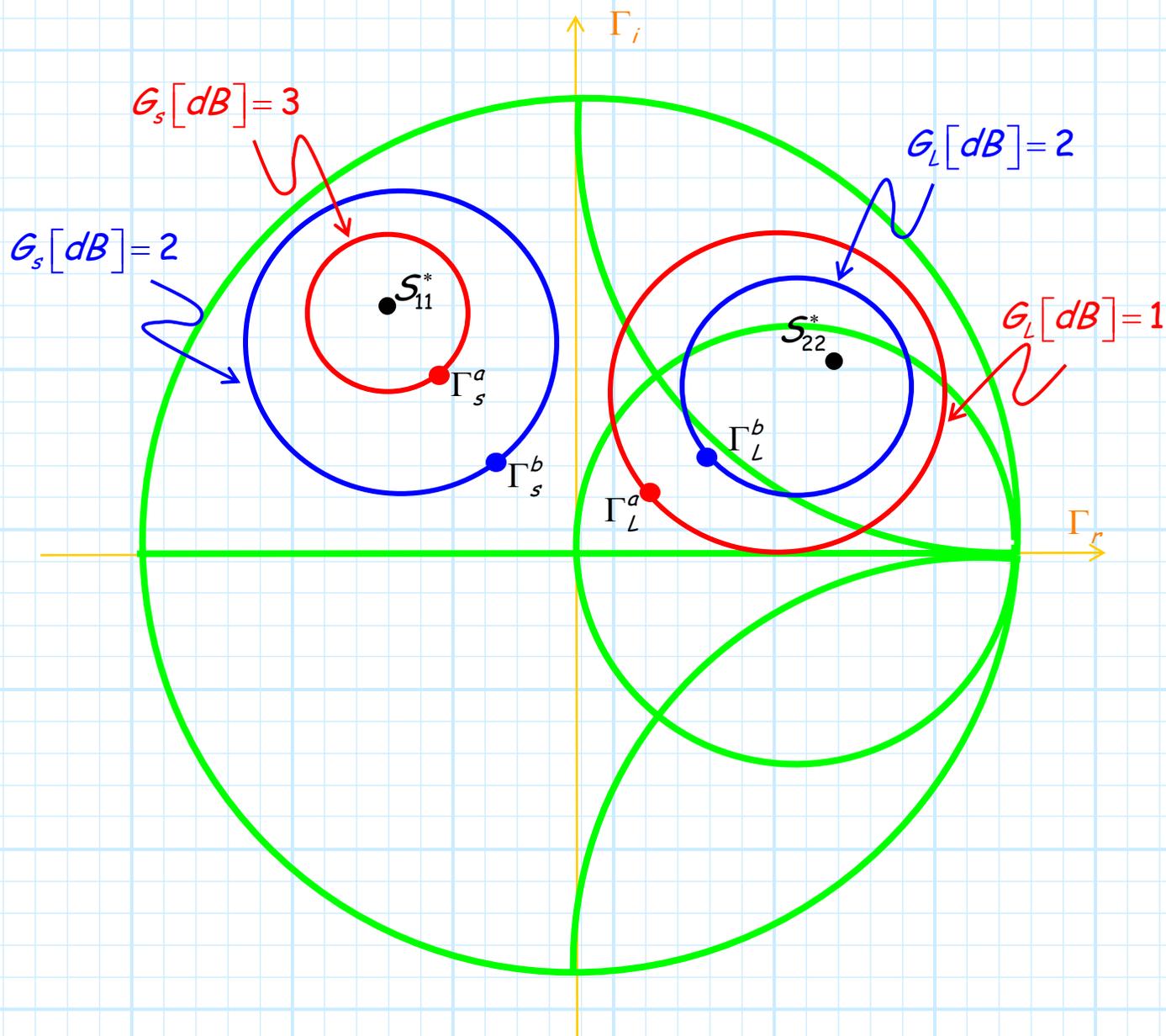Any  $\Gamma$  point on (not inside!) a constant gain circle denotes a value of  $\Gamma$  that will provide the requisite gain. To minimize the bandwidth we should choose the point on the circle that is closest to the center of the complex  $\Gamma$  plane!



For **example**, say we have an amplifier with:

$$G_{Smax} [dB] = 4.0$$

$$G_0 [dB] = 7.0$$

$$G_{Lmax} [dB] = 3.0$$

such that its transducer gain is **14 dB** at its design frequency. To increase the **bandwidth** of this amplifier, we decide to **reduce** the gain to 11 dB.

Thus, we find that our design goal is:

$$G_s [dB] + G_L [dB] = 4.0$$

From the gain circles on the Smith Chart above (assuming they represent the gain circles for this gain element), we find there are **two solutions**; we'll call them **solution a** and **solution b**.

### Solution a

We determine the values  $\Gamma_s^a$  and  $\Gamma_L^a$  from the gain circles:

$$G_s [dB] = 3.0 \quad \text{and} \quad G_L [dB] = 1.0$$

so that  $G_s [dB] + G_L [dB] = 4.0$ .

### Solution b

We determine the values  $\Gamma_s^b$  and  $\Gamma_L^b$  from the gain circles:

$$G_s [dB] = 2.0 \quad \text{and} \quad G_L [dB] = 2.0$$

so that  $G_s [dB] + G_L [dB] = 4.0$ .

There are of course an **infinite** number of possible solutions, as there are an infinite number of solutions to  $G_s [dB] + G_L [dB] = 4.0$ . However, the two solutions provided here are fairly **representative**.

**Q:** *So which solution should we use?*

**A:** That choice is a bit **subjective**.

We note that the point  $\Gamma_L^a$  is **very close** to the center, while the point  $\Gamma_s^a$  is pretty **far away** (i.e.,  $|\Gamma_L^a|$  is small and  $|\Gamma_s^a|$  is large).

In contrast, both  $\Gamma_s^b$  and  $\Gamma_L^b$  are **fairly close** to the center, although neither is as close as  $\Gamma_L^a$ .

To get the widest bandwidth, I would choose **solution b**, but the only way to know for sure is to design and **analyze both solutions**.



Often, the design with the widest bandwidth will depend on how you **define** bandwidth!

**Q:** *So we reduce the transducer gain by designing and constructing a **mismatched** matching network. Won't that result in **return loss**?*

**A:** Absolutely!



We find for these wideband antennas that **neither**  $S_{11}^{amp}$  **nor**  $S_{22}^{amp}$  are equal to **zero**. However, there is a bit of a **silver lining**.

A conjugate matched amplifier is not only narrow band with regard to gain, it is also **narrow band** with regard to **return loss**. **Only** at the design frequency will the amplifier ports be perfectly matched. As we move away from the design frequency, the return loss **quickly degrades!**

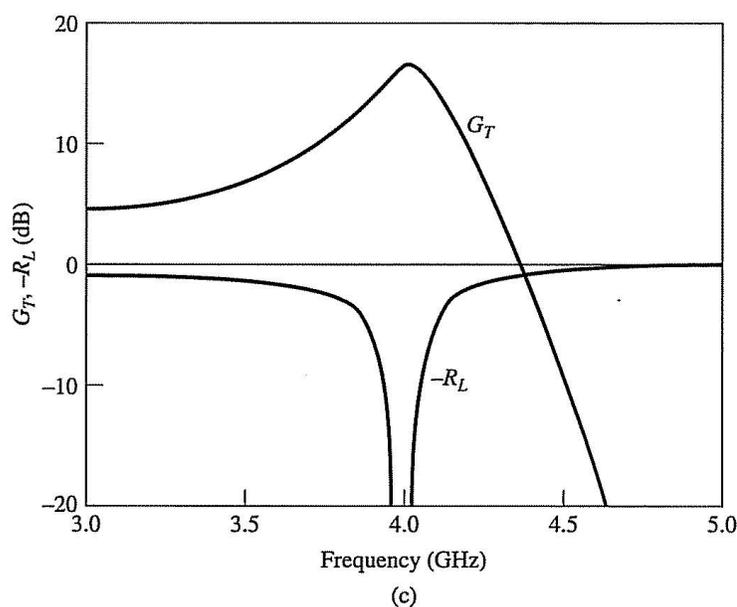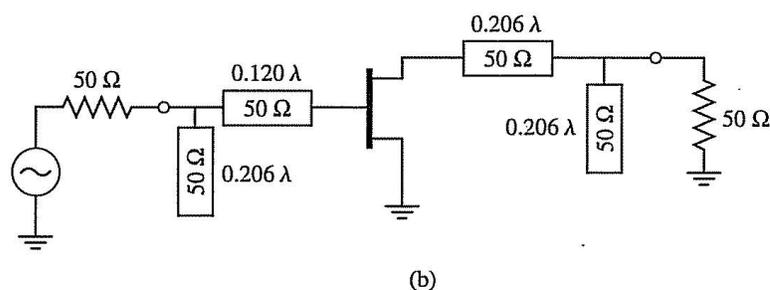

**FIGURE 11.7** Continued. (b) RF circuit. (c) Frequency response.

With the "mismatched" design, we typically find that the return loss is **better** at frequencies away from the design frequency (as compared to the matched design), although at **no frequency** do we achieve a **perfect match** (unlike the matched design).

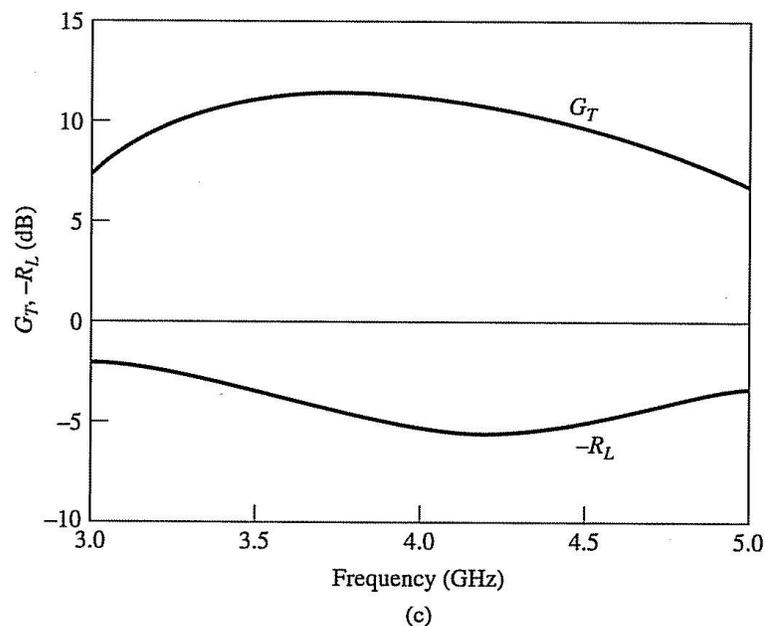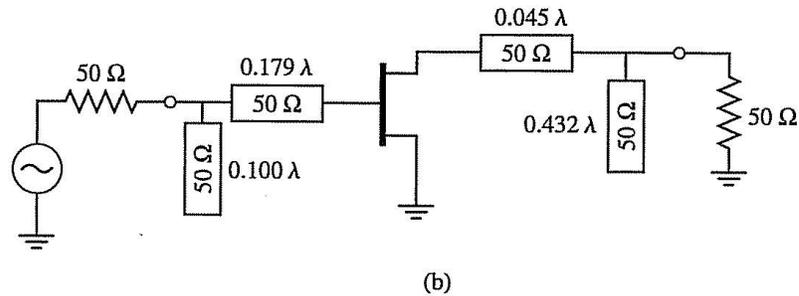

**FIGURE 11.8** Continued. (b) RF circuit. (c) Transducer gain and return loss.

Generally speaking, a good (i.e., **acceptable**) return loss over a wide range of frequencies is **better** than a perfect return loss at one frequency and poor return loss everywhere else!

**Q:** *Won't you **ever** stop talking??*

**A:** Yup. I'm all done.