
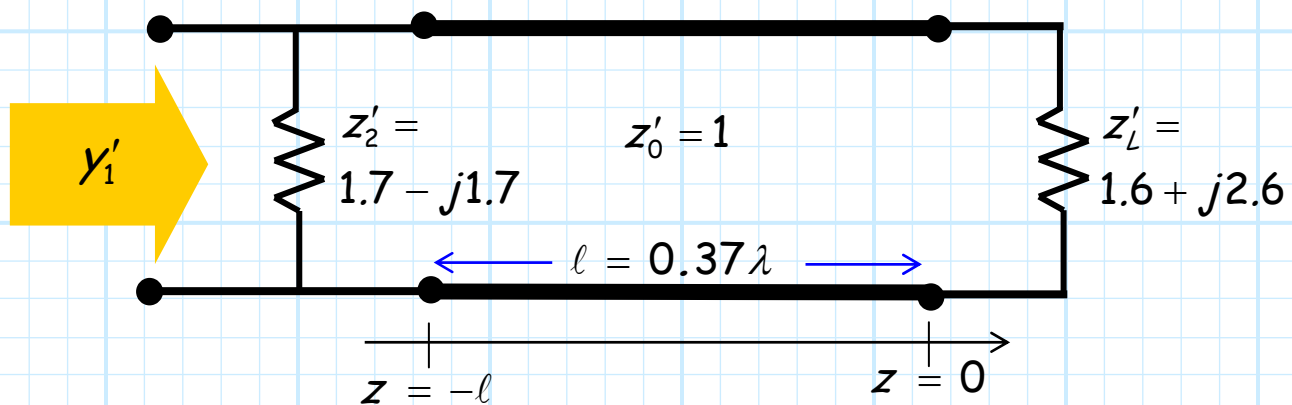

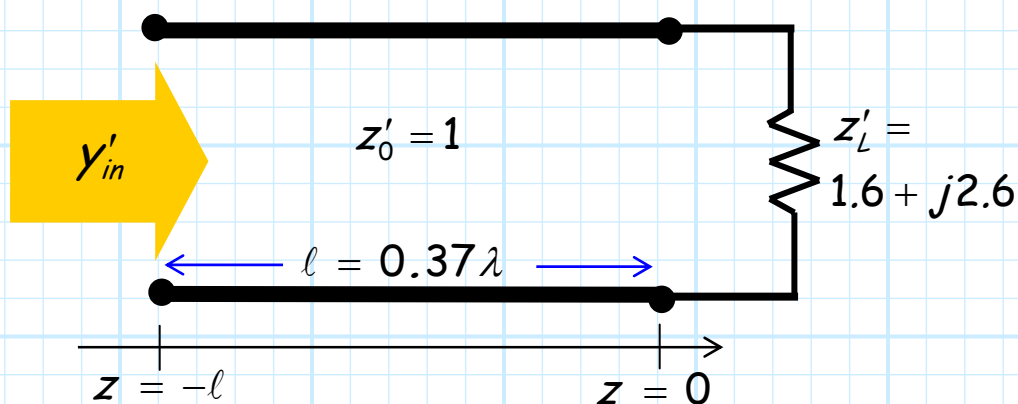
# Example: Admittance Calculations with the Smith Chart

Say we wish to determine the **normalized admittance**  $y'_1$  of the network below:




First, we need to determine the normalized **input** admittance of the transmission line:



There are **two ways** to determine this value!
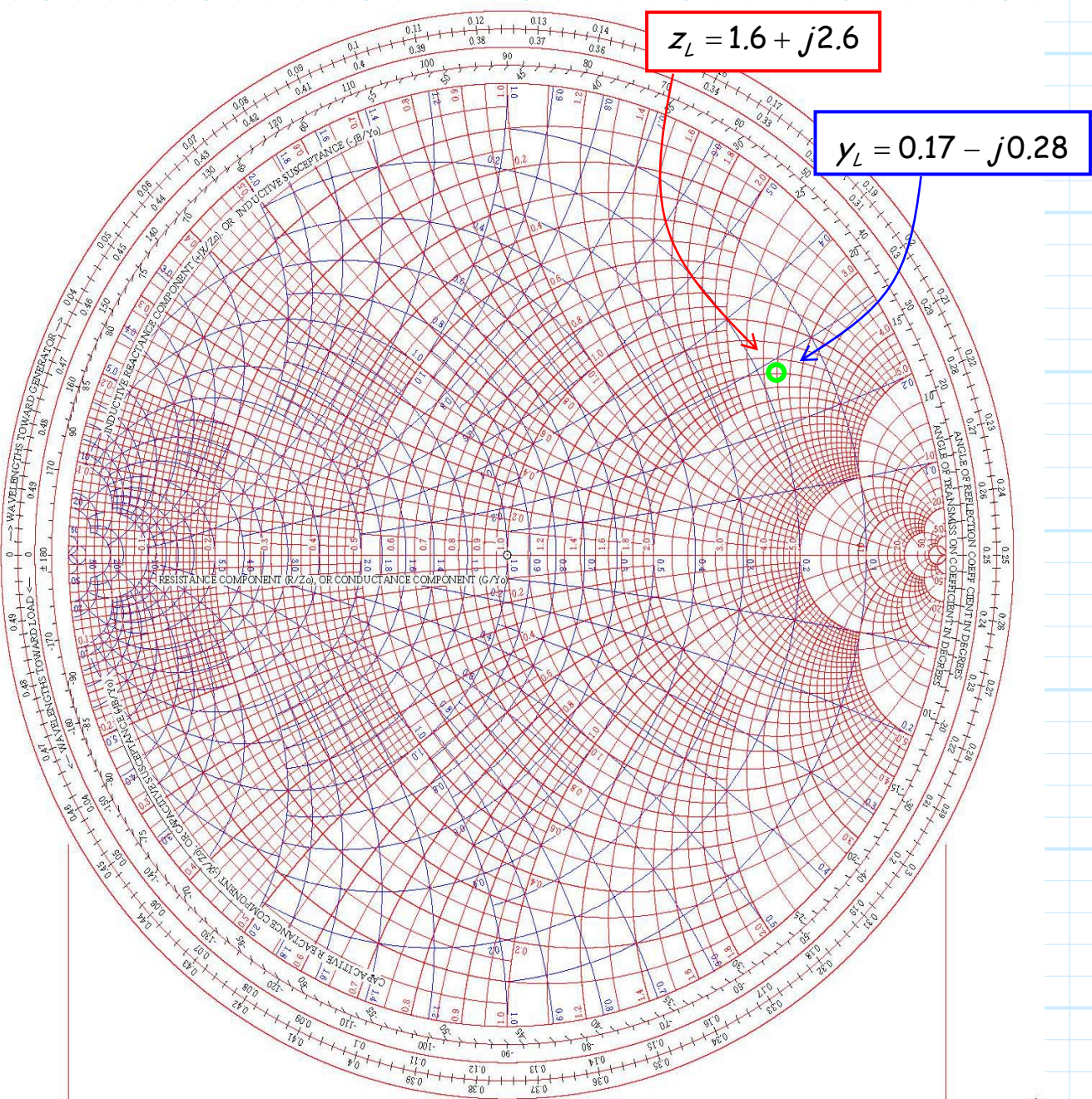
### Method 1

First, we express the load  $z_L = 1.6 + j2.6$  in terms of its **admittance**  $y'_L = 1/z_L$ . We can calculate this complex value—or we can use a **Smith Chart**!






The Smith Chart above shows **both** the **impedance** mapping (red) and **admittance** mapping (blue). Thus, we can locate the impedance  $z_L = 1.6 + j2.6$  on the impedance (red) mapping, and then determine the value of that **same**  $\Gamma_L$  point using the admittance (blue) mapping.


From the chart above, we find this admittance value is **approximately**  $y_L = 0.17 - j0.28$ .

Now, you may have noticed that the Smith Chart above, with both impedance and admittance mappings, is very **busy** and **complicated**. Unless the two mappings are printed in different colors, this Smith Chart can be very **confusing** to use!

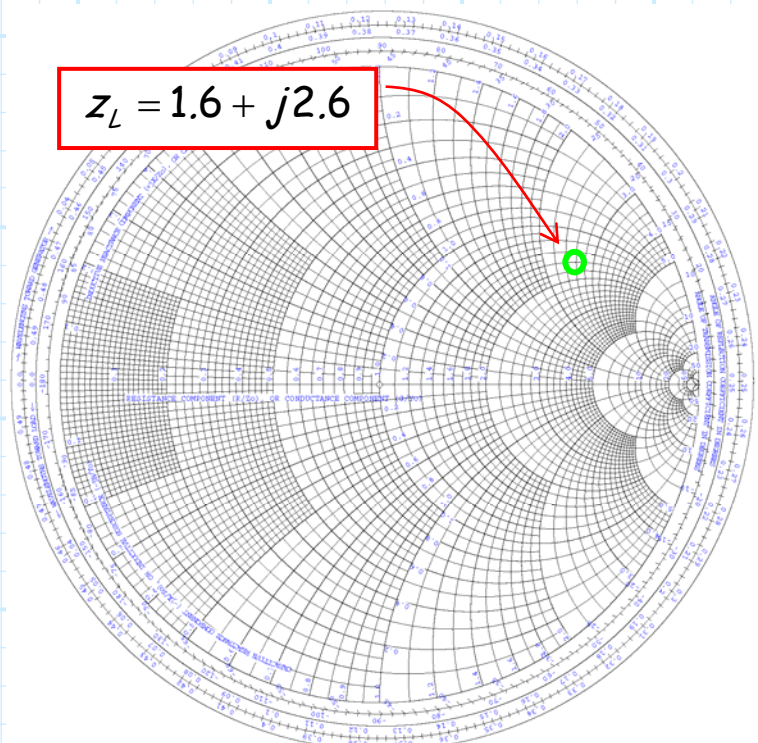But remember, the two mappings are precisely identical—they're just **rotated**  $180^\circ$  with respect to each other. Thus, we can **alternatively** determine  $y_L$  by again first locating  $z_L = 1.6 + j2.6$  on the impedance mapping :



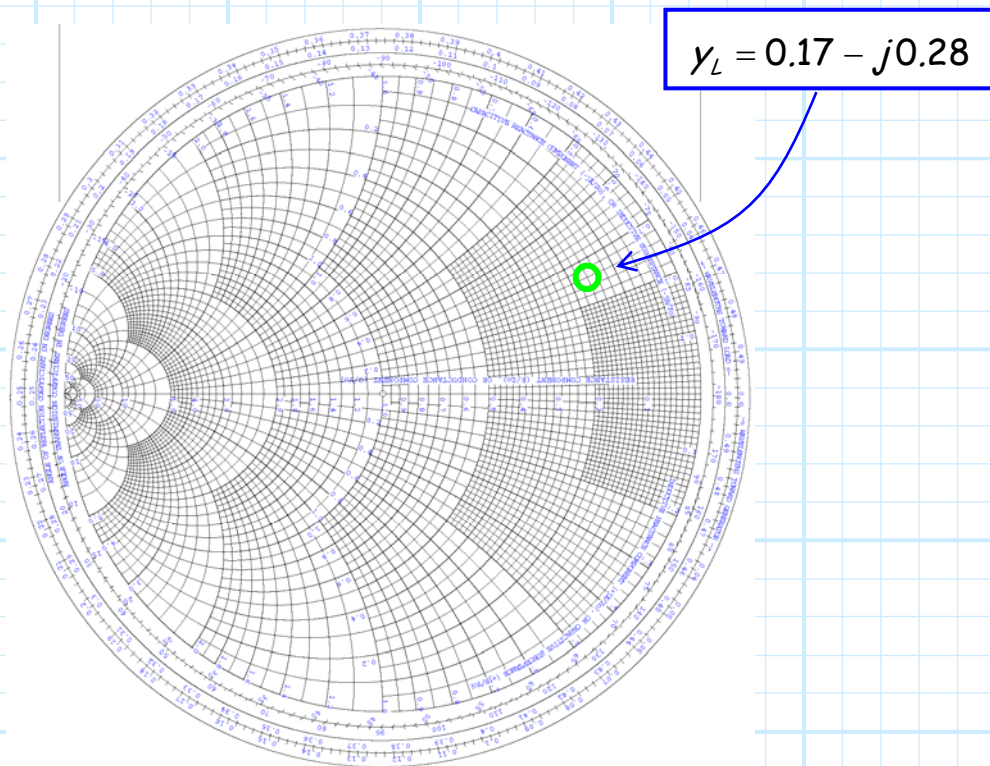Then, we can rotate the **entire** Smith Chart  $180^\circ$ --while keeping the point  $\Gamma_L$  location on the complex  $\Gamma$  plane **fixed**.




Thus, use the **admittance** mapping at that point to determine the admittance value of  $\Gamma_L$ .

Note that rotating the **entire** Smith Chart, while keeping the point  $\Gamma_L$  fixed on the complex  $\Gamma$  plane, is a **difficult** maneuver to successfully—as well as accurately—execute.


But, realize that rotating the entire Smith Chart  $180^\circ$  with respect to point  $\Gamma_L$  is **equivalent** to rotating  $180^\circ$  the **point**  $\Gamma_L$  with respect to the entire Smith Chart!

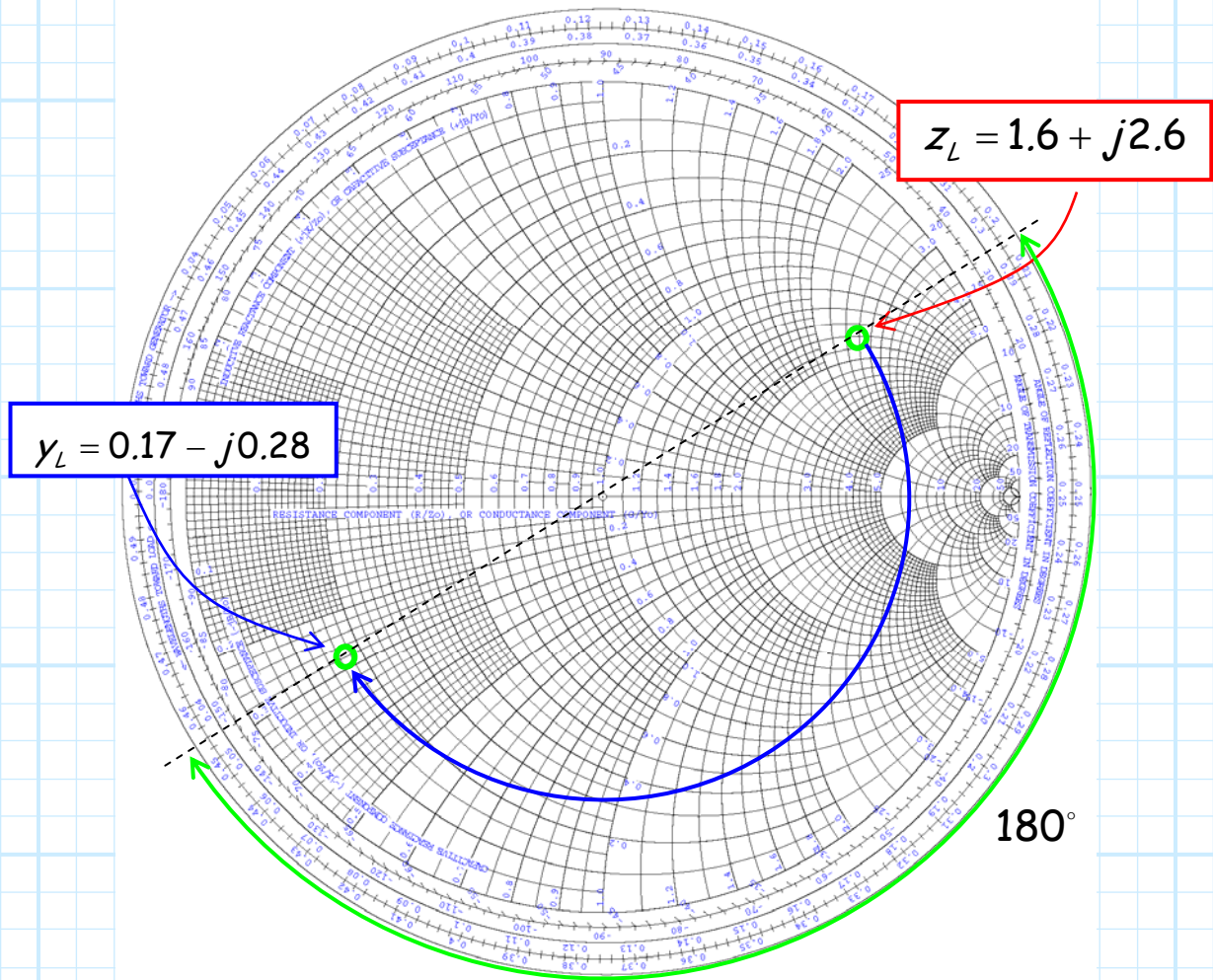This maneuver (rotating the **point**  $\Gamma_L$ ) is **much** simpler, and the **typical** method for determining admittance.



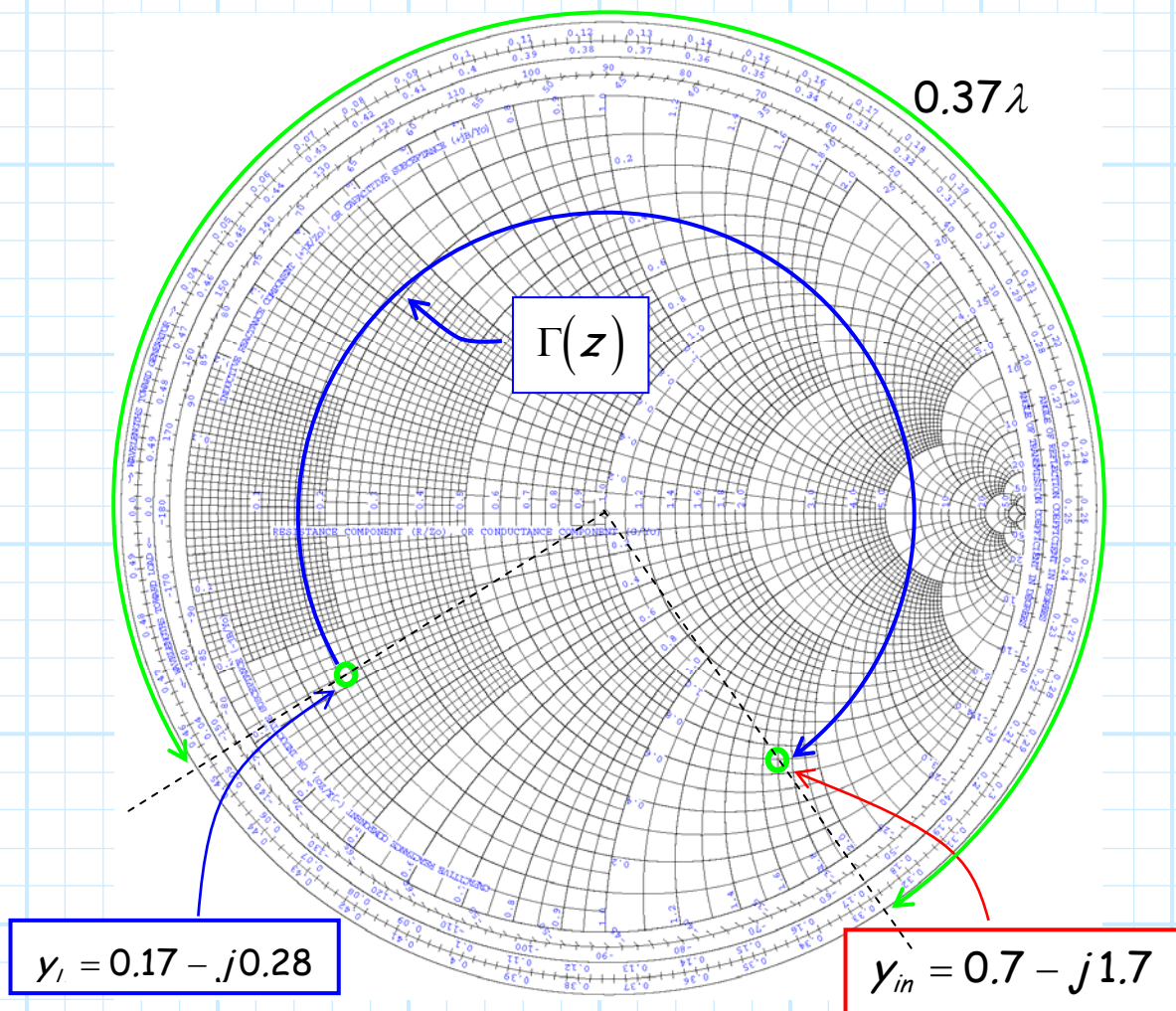Now, we can determine the value of  $y'_{in}$  by simply rotating clockwise  $2\beta\ell$  from  $y'_L$ , where  $\ell = 0.37\lambda$ :






**Transforming** the load admittance to the beginning of the transmission line, we have determined that  $y'_{in} = 0.7 - j1.7$ .

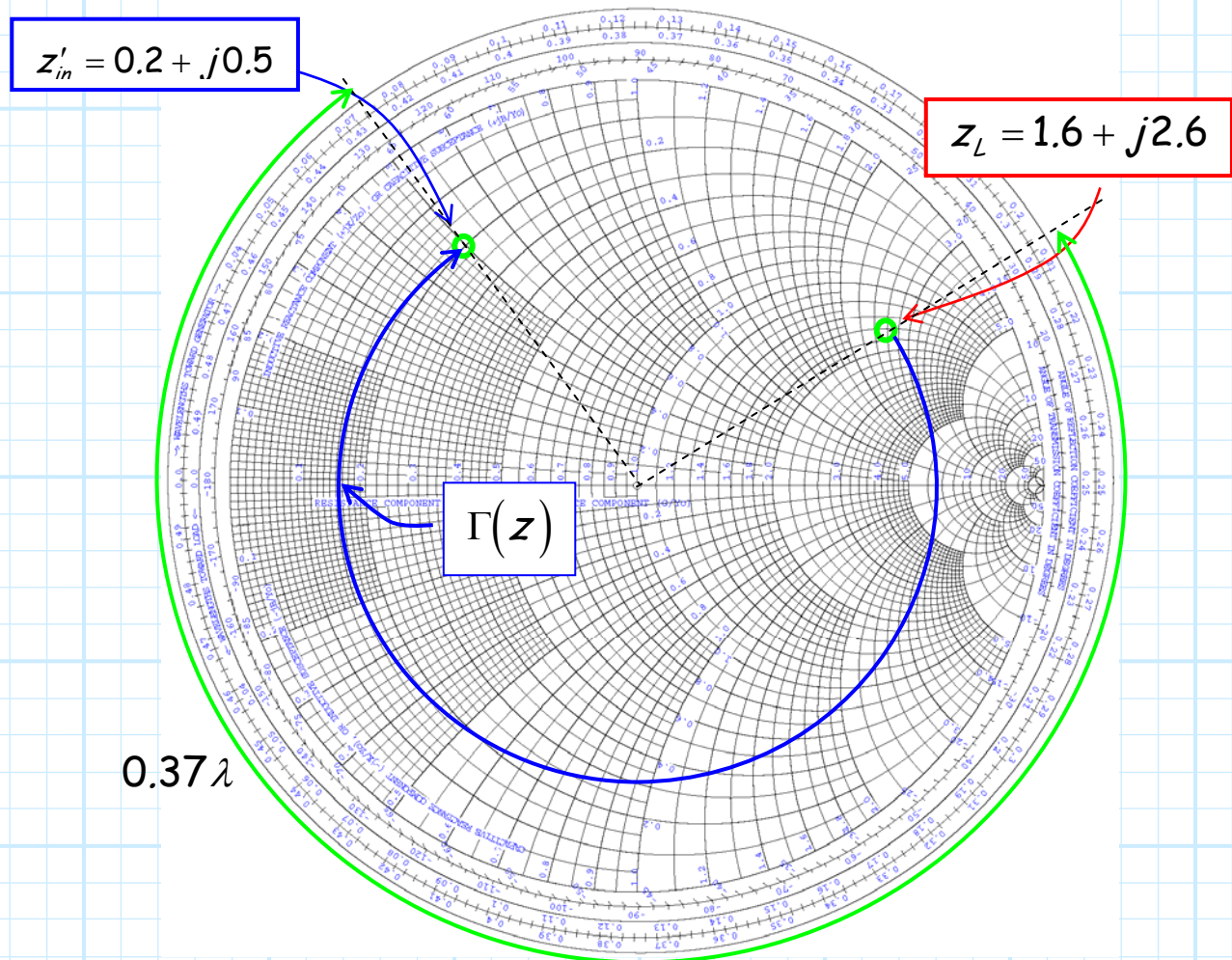
## Method 2

**Alternatively**, we could have **first** transformed impedance  $z'_l$  to the **end** of the line (finding  $z'_{in}$ ), and then determined the value of  $y'_{in}$  from the **admittance** mapping (i.e., rotate  $180^\circ$  around the Smith Chart).



The **input impedance** is determined after rotating clockwise  $2\beta l$ , and is  $z'_{in} = 0.2 + j0.5$ .

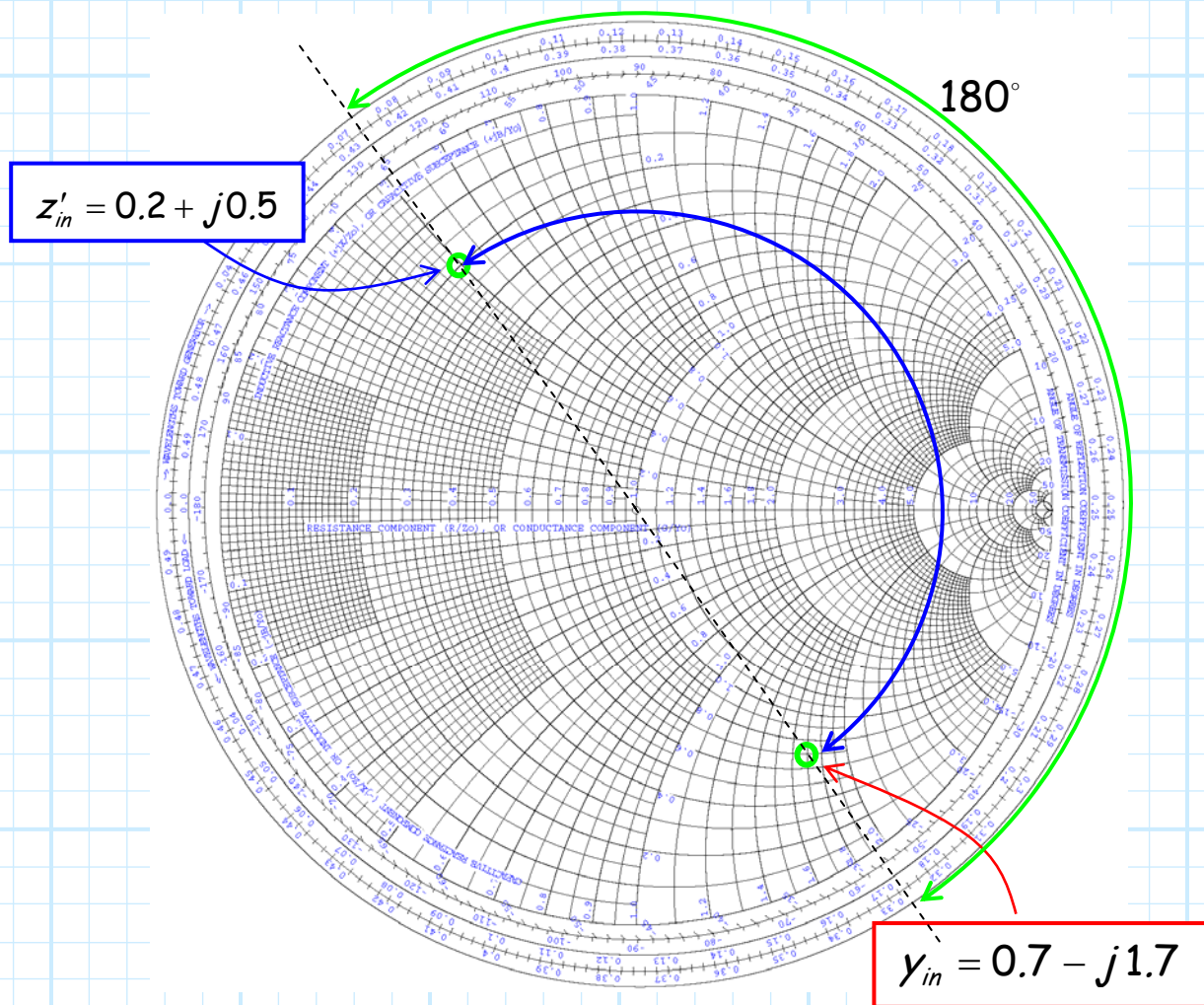Now, we can rotate this point  $180^\circ$  to determine the **input admittance** value  $y'_{in}$ :




The result is the **same** as with the earlier method--  
 $y'_{in} = 0.7 - j1.7$ .

Hopefully it is **evident** that the two methods are equivalent. In method 1 we **first** rotate 180°, and **then** rotate  $2\beta l$ . In the second method we **first** rotate  $2\beta l$ , and **then** rotate 180°--the result is thus the **same**!

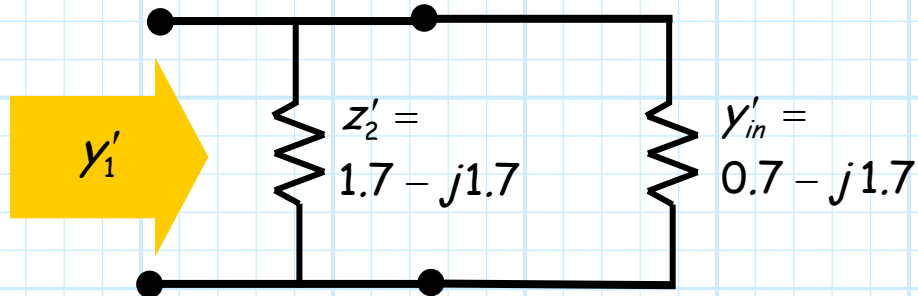
Now, the remaining **equivalent** circuit is:





Determining  $y'_1$  is just **basic circuit theory**. We first express  $z'_2$  in terms of its admittance  $y'_2 = 1/z'_2$ .

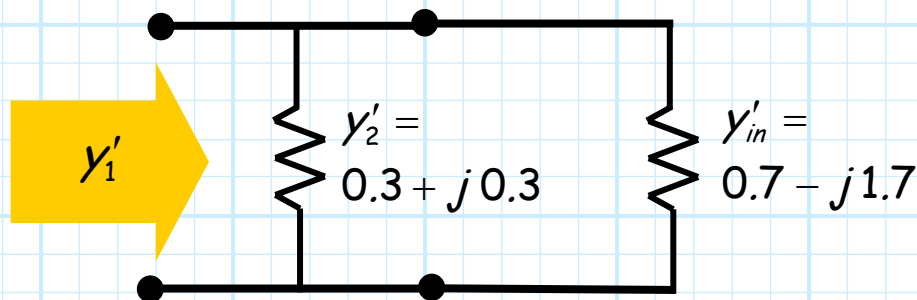Note that we could do this using a **calculator**, but could likewise use a **Smith Chart** (locate  $z'_2$  and then rotate  $180^\circ$ ) to accomplish this calculation! Either way, we find that  $y'_2 = 0.3 + j0.3$ .



Thus,  $y'_1$  is simply:

$$\begin{aligned} y'_1 &= y'_2 + y'_{in} \\ &= (0.3 + j0.3) + (0.7 - j1.7) \\ &= 1.0 - j1.4 \end{aligned}$$