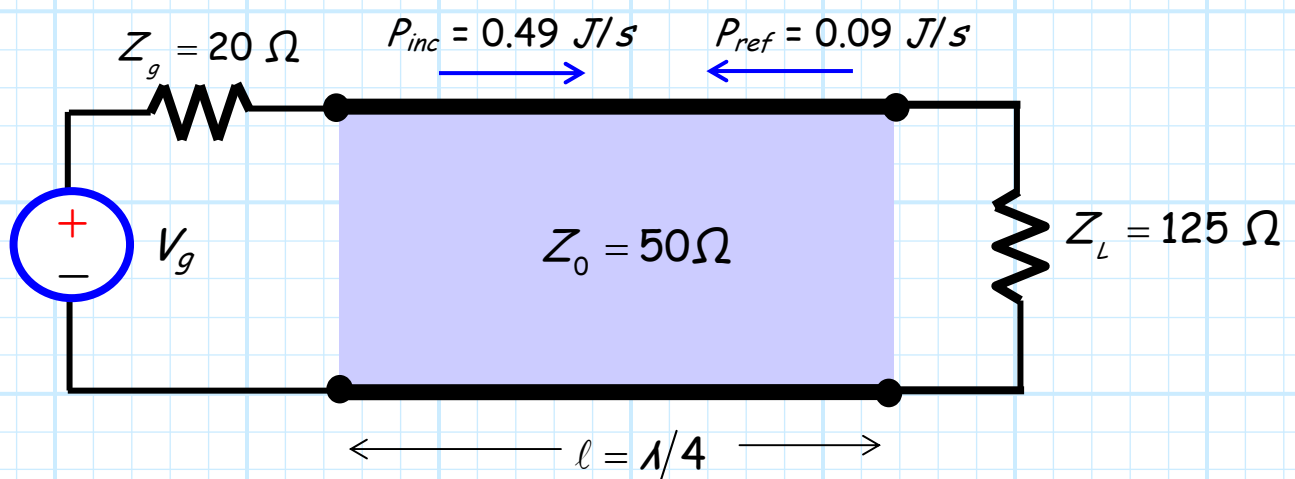


Example: Conservation of Energy and You

Consider this circuit, where the transmission line is **lossless** and has length $\ell = \lambda/4$:



The wave **incident** on the load Z_L has power of $P_{inc} = 0.49 \text{ J/s}$.

The wave **reflected** from the load Z_L has power of $P_{ref} = 0.09 \text{ J/s}$.

Determine the **magnitude** of source voltage V_g (i.e., determine $|V_g|$).


Hint: This is **not** a boundary condition problem. Do **not** attempt to find $V(z)$ and/or $I(z)$!

Solution

From **conservation of energy**, we find the load absorbs energy at a rate of:

$$\begin{aligned} P_{abs} &= P_{inc} - P_{ref} \\ &= 0.49 - 0.09 \\ &= 0.4 \text{ W} \end{aligned}$$

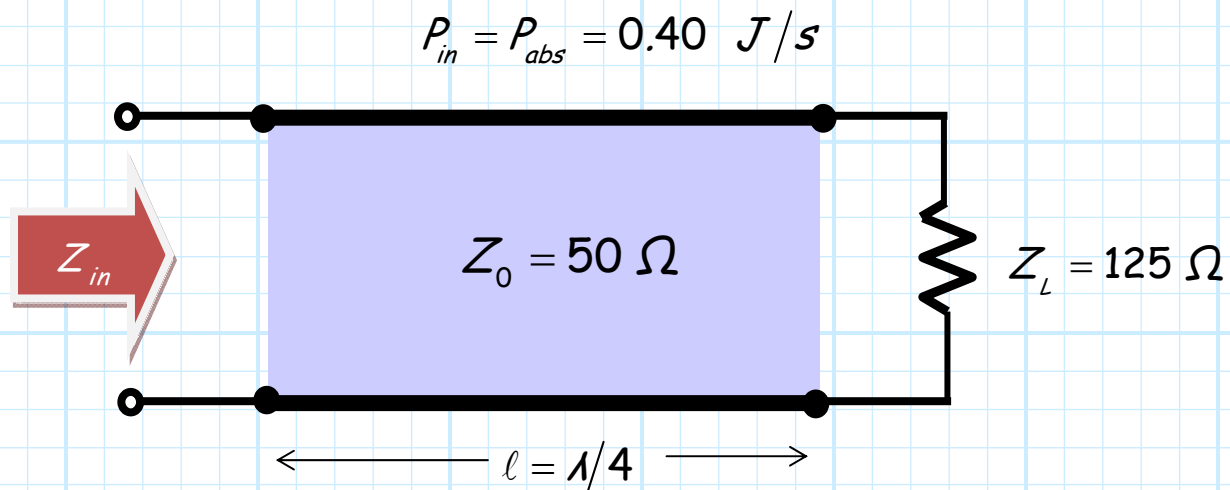Since the transmission line is **lossless**, this absorbed power **must** likewise be the power **delivered** by the source to the input of the transmission line (i.e., the power absorbed by input impedance Z_{in}).




Note the transmission line length has the **special case** $\ell = \lambda/4$, therefore the input impedance is easily computed:

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{50^2}{125} = 20 \Omega = Z_g$$

A conjugate match ($Z_{in} = Z_g^*$)!

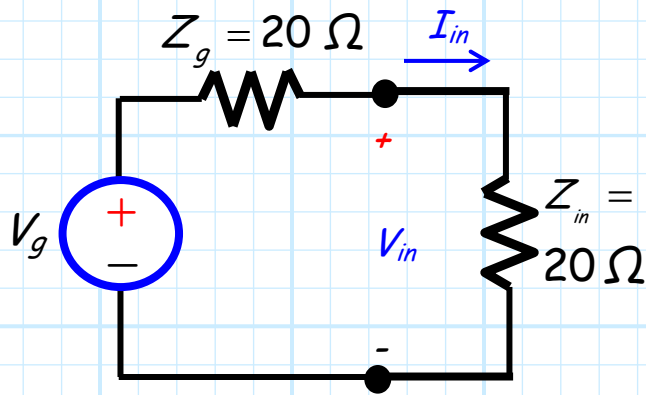Thus, the power **delivered** by the source is:



$$\begin{aligned}
 P_{del} &= \frac{1}{2} \operatorname{Re} \{ V_{in} I_{in}^* \} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ \left(\frac{V_g}{2} \right) \left(\frac{V_g^*}{20 + 20} \right) \right\} \\
 &= \frac{1}{8} \operatorname{Re} \left\{ |V_g|^2 \right\} \frac{1}{20} \\
 &= \frac{|V_g|^2}{160}
 \end{aligned}$$

And since we know that $P_{abs} = P_{del} = 0.4 \text{ W}$, we can conclude:

$$P_{del} = 0.4 = \frac{|V_g|^2}{160} \quad \Rightarrow \quad \underline{\underline{|V_g| = \sqrt{160(0.4)} = 8.0 \text{ V}}}$$