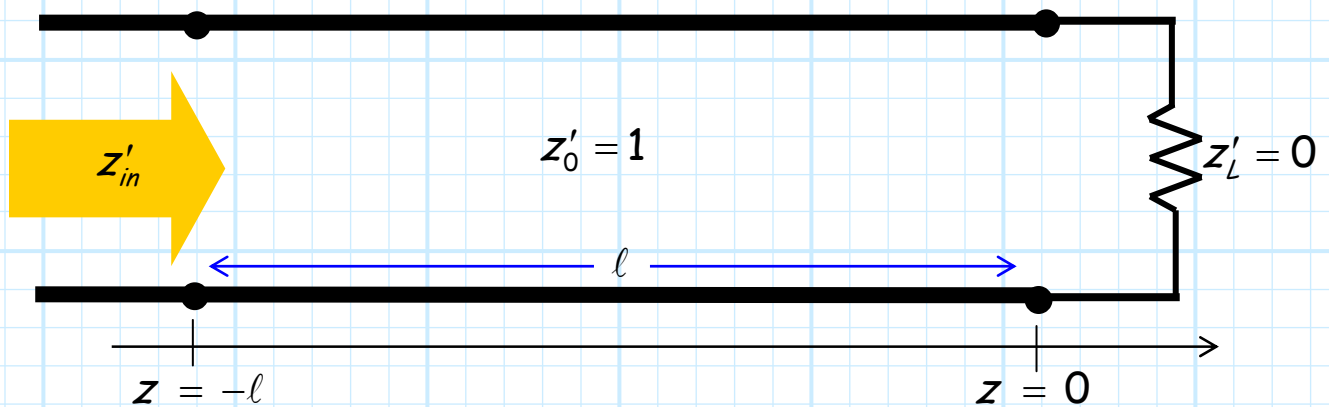


Example: The Input Impedance of a Shorted Transmission Line

Let's determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:


a) $l = \lambda/8 = 0.125\lambda \Rightarrow 2\beta l = 90^\circ$

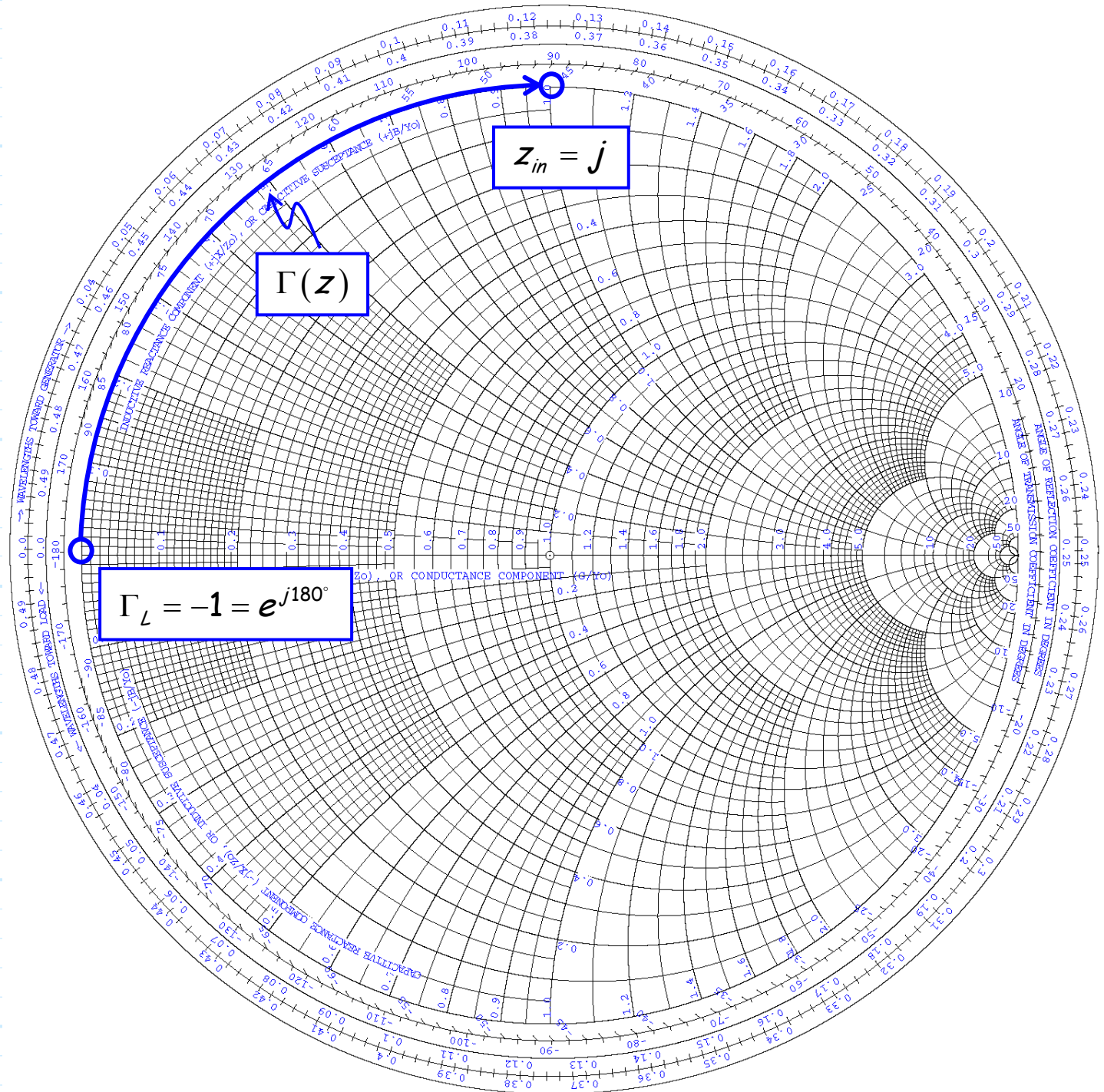b) $l = 3\lambda/8 = 0.375\lambda \Rightarrow 2\beta l = 270^\circ$



$$a) \ell = \lambda/8 = 0.125\lambda \Rightarrow 2\beta\ell = 90^\circ$$

Rotate clockwise 90° from $\Gamma = -1.0 = e^{j180^\circ}$ and find $z'_{in} = j$.



$$\text{b) } l = 3\lambda/8 = 0.375\lambda \Rightarrow 2\beta l = 270^\circ$$

Rotate clockwise 270° from $\Gamma = -1.0 = e^{j180^\circ}$ and find $z'_{in} = -j$.

