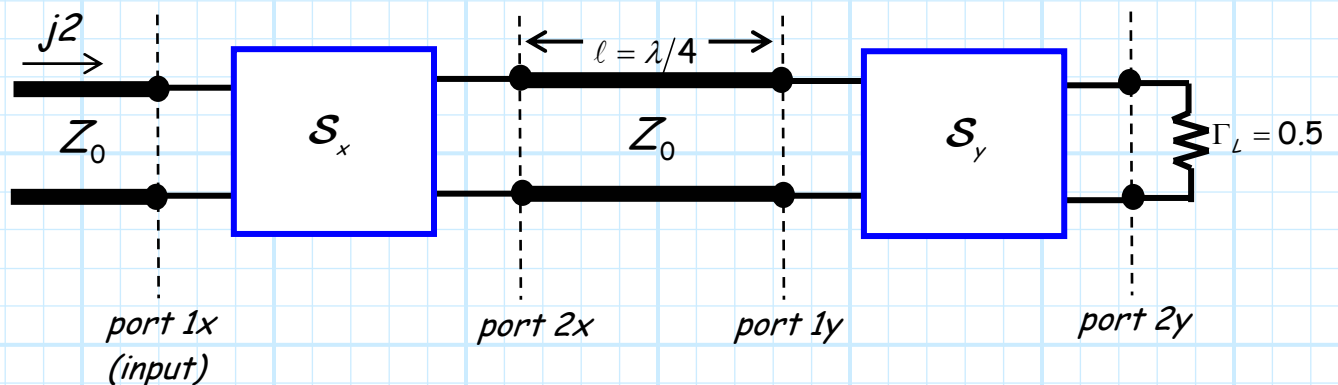


Example: Analysis Using Signal Flow Graphs

Below is a single-port device (with input at port 1a) constructed with two two-port devices (S_x and S_y), a quarter wavelength transmission line, and a load impedance.



Where $Z_0 = 50\Omega$.

The scattering matrices of the two-port devices are:

$$S_x = \begin{bmatrix} 0.35 & 0.5 \\ 0.5 & 0 \end{bmatrix} \quad S_y = \begin{bmatrix} 0 & 0.8 \\ 0.8 & 0.4 \end{bmatrix}$$


Likewise, we know that the value of the voltage wave incident on port 1 of device S_x is:

$$a_{1x} = \frac{V_{01x}^+ (z_{1x} = z_{1xp})}{\sqrt{Z_0}} = \frac{j2}{\sqrt{50}} = \frac{j\sqrt{2}}{5} \text{ V}$$


Now, let's draw the complete **signal flow graph** of this circuit, and then reduce the graph to determine:

- The total current through load Γ_L .
- The power delivered to (i.e., absorbed by) port $1x$.

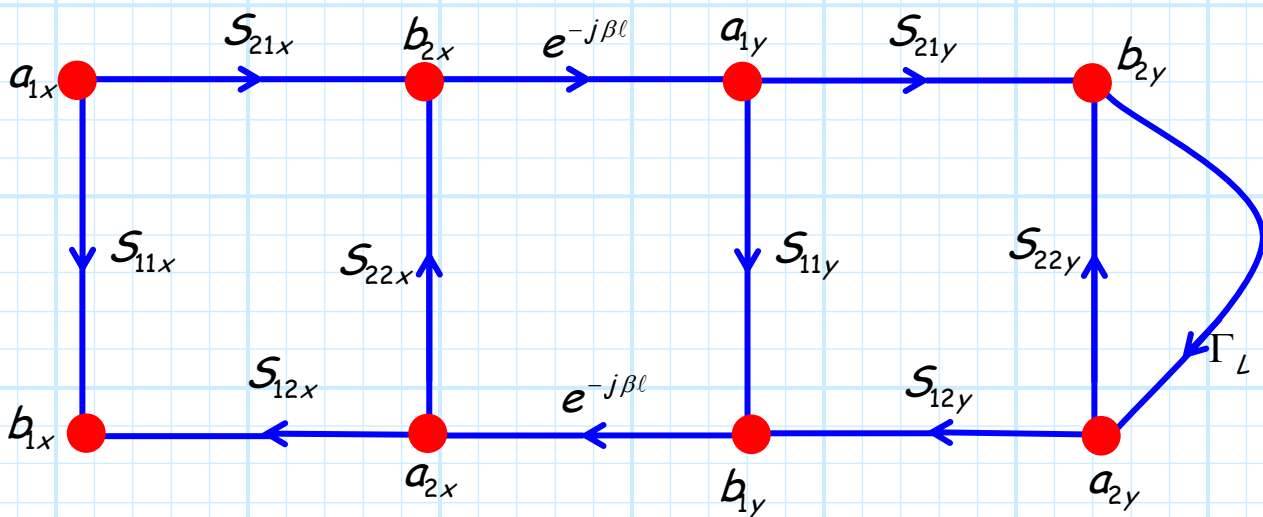
The signal flow graph describing this network is:



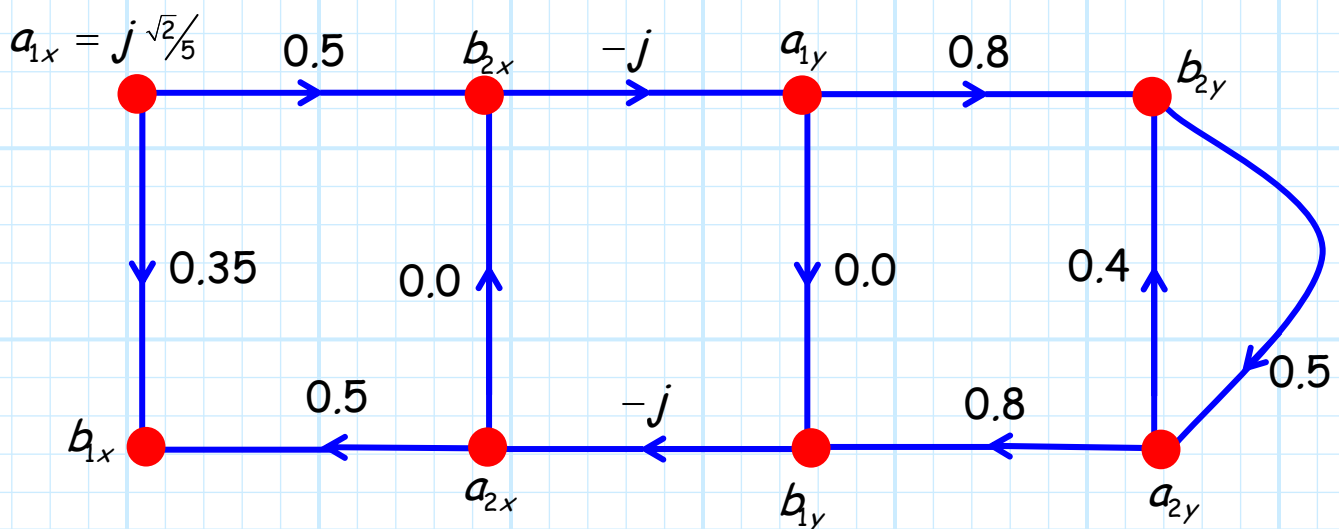
Inserting the numeric values of branches:




Removing the zero valued branches:

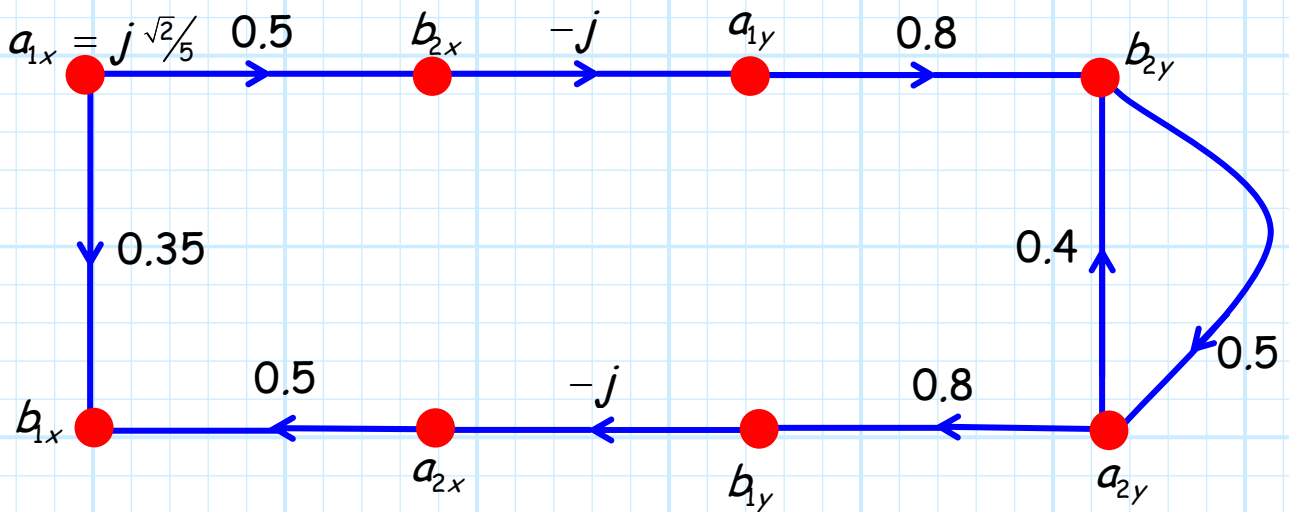

And now applying "splitting" rule 4:

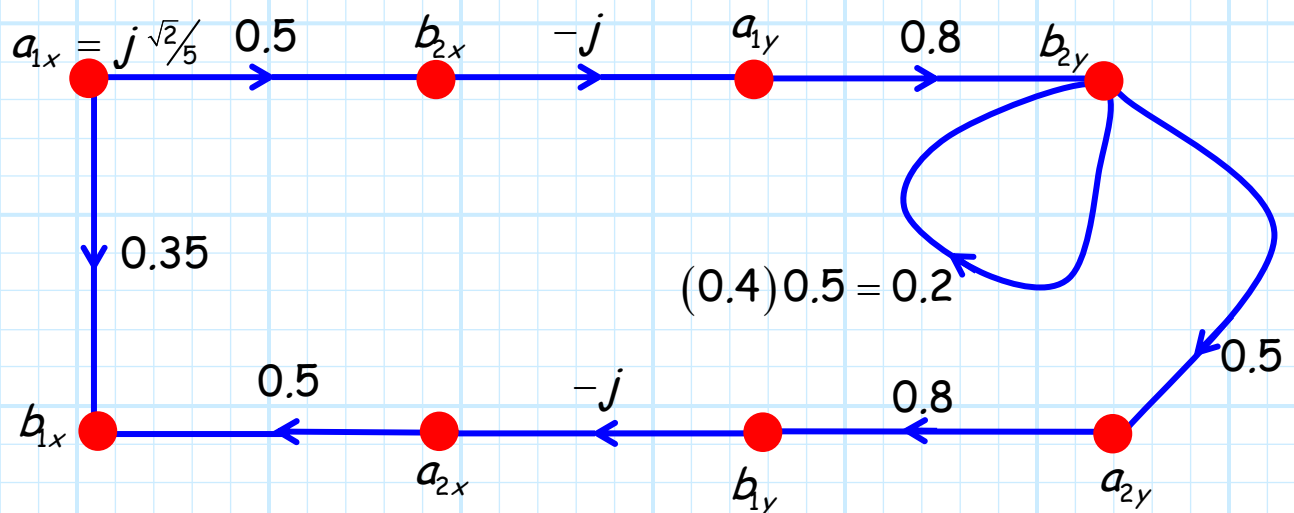

Followed by the "self-loop" rule 3:

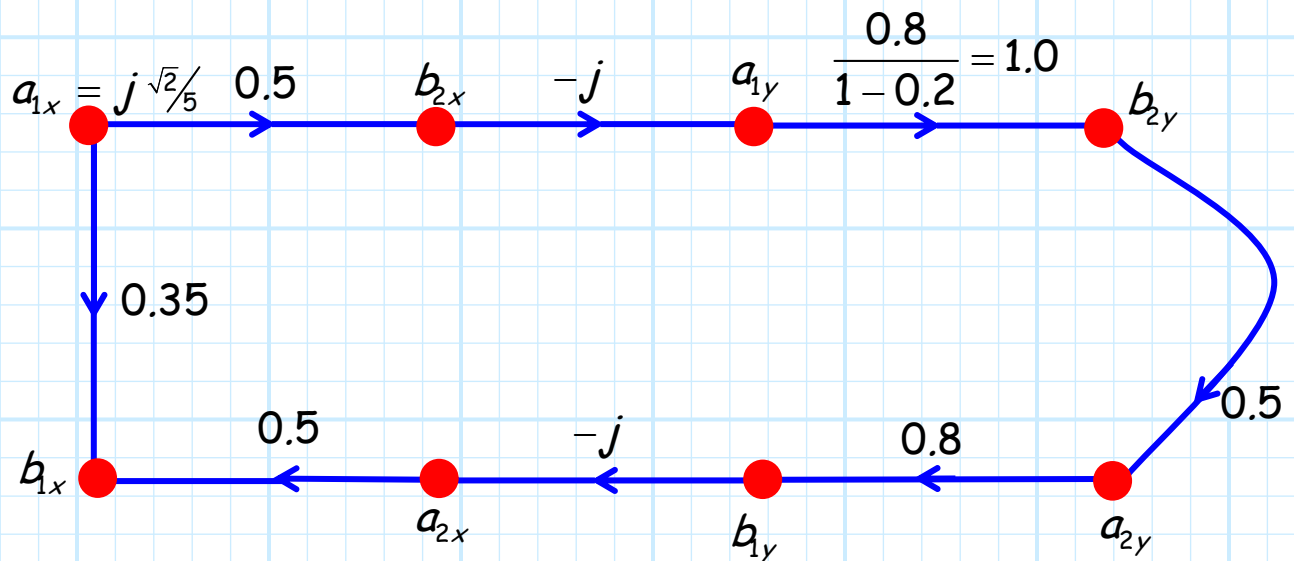


Now, let's use this simplified signal flow graph to find the solutions to our questions!

a) The total current through load Γ_L .

The total current through the load is:

$$\begin{aligned} I_L &= -I(z_{2y} = z_{2yP}) \\ &= -\frac{V_{02y}^+(z_{2y} = z_{2yP}) - V_{02y}^-(z_{2y} = z_{2yP})}{Z_0} \\ &= -\frac{a_{2y} - b_{2y}}{\sqrt{Z_0}} \\ &= \frac{b_{2y} - a_{2y}}{\sqrt{50}} \end{aligned}$$

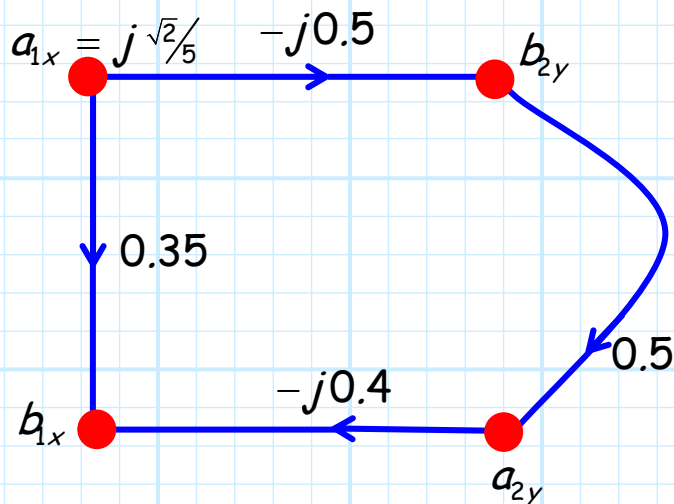Thus, we need to determine the value of nodes a_{2y} and b_{2y} . Using the "series" rule 1 on our signal flow graph:



Note we've simply **ignored** (i.e., neglected to plot) the node for which we have **no interest!**

From this graph we can conclude:

$$b_{2y} = -j0.5 a_{1x} = -j0.5 \left(\frac{j\sqrt{2}}{5} \right) = 0.1\sqrt{2}$$

and:

$$a_{2y} = 0.5 b_{2y} = 0.5(0.1\sqrt{2}) = 0.05\sqrt{2}$$

Therefore:


$$I_L = \frac{b_{2y} - a_{2y}}{\sqrt{50}} = \frac{(0.1 - 0.05)\sqrt{2}}{\sqrt{50}} = \frac{0.05}{5} = 10.0 \text{ mA}$$

b) The **power** delivered to (i.e., absorbed by) port 1x.

The power delivered to port 1x is:


$$\begin{aligned} P_{abs} &= P^+ - P^- \\ &= \frac{|V_{1x}^+(z_{1x} = z_{1xp})|^2}{2Z_0} - \frac{|V_{1x}^-(z_{1x} = z_{1xp})|^2}{2Z_0} \\ &= \frac{|a_{1x}|^2 - |b_{1x}|^2}{2} \end{aligned}$$

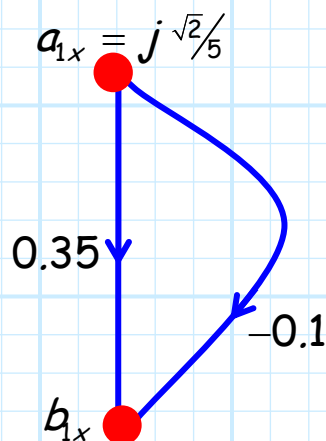Thus, we need determine the values of nodes a_{1x} and b_{1x} . Again using the series rule 1 on our signal flow graph:



Again we've simply **ignored** (i.e., neglected to plot) the node for which we have **no interest!**

And then using the "parallel" rule 2:

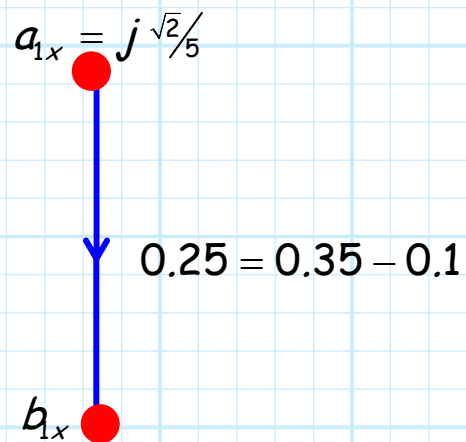

Therefore:

$$b_{1x} = 0.25 a_{1x} = 0.25 (j\sqrt{2}/5) = j0.05\sqrt{2}$$

and:

$$P_{abs} = \frac{|j\sqrt{2}/5|^2 - |j0.05\sqrt{2}|^2}{2} = \frac{0.08 - 0.005}{2} = 37.5 \text{ mW}$$