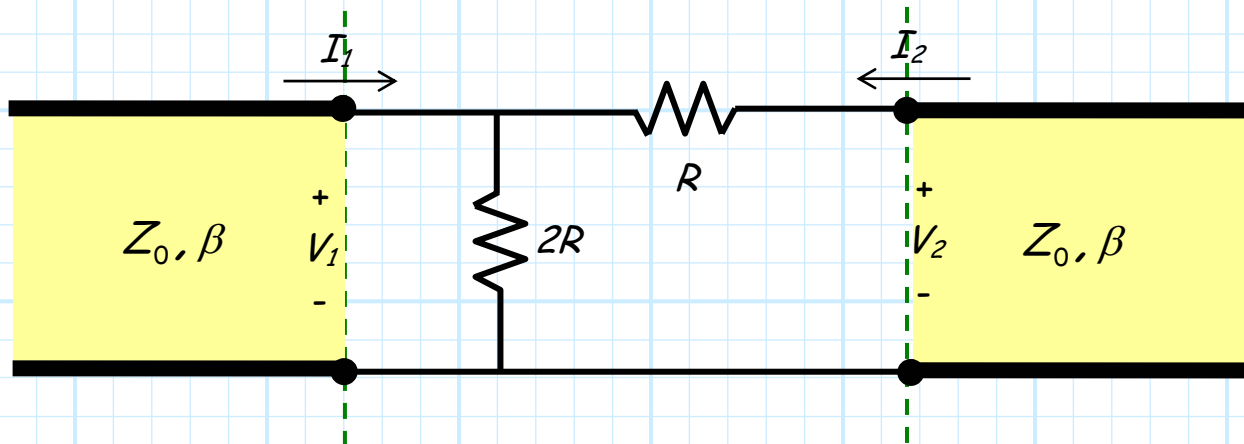



# Example: Evaluating the Admittance Matrix

Consider the following two-port device:



Let's determine the **admittance matrix** of this device!

**Step 1:** Place a **short** at port 2.

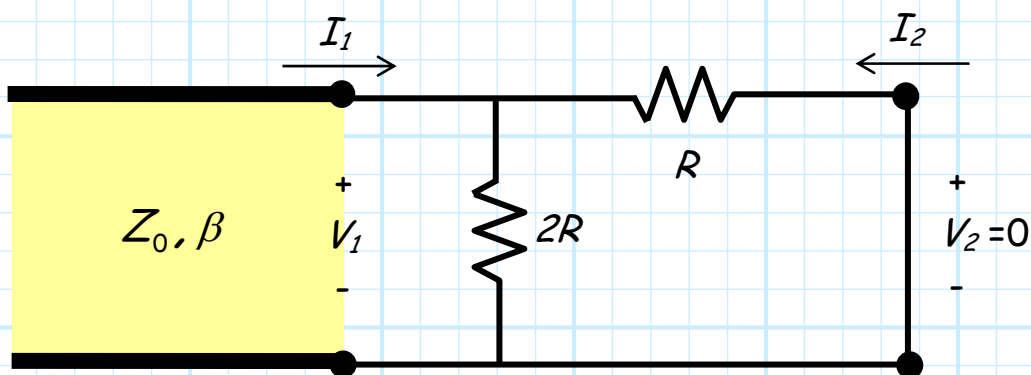

**Step 2:** Determine currents  $I_1$  and  $I_2$ .

Note that **after** the short was placed at port 2, both resistors are in **parallel**, with a potential  $V_2$  across each.

The current  $I_1$  is thus simply the **sum** of the two currents through **each** resistor:

$$I_1 = \frac{V_1}{2R} + \frac{V_1}{R} = \frac{3V_1}{2R}$$

The current  $I_2$  is simply the **opposite** of the current through  $R$ :

$$I_2 = -\frac{V_1}{R}$$

**Step 3:** Determine trans-admittance  $Y_{11}$  and  $Y_{21}$ .

$$Y_{11} = \frac{I_1}{V_1} = \frac{3}{2R}$$

$$Y_{21} = \frac{I_2}{V_1} = -\frac{1}{R}$$




Note that  $Y_{21}$  is **real**—but **negative**!

This is **still** a valid physical result, **although** you will find that the **diagonal** terms of an impedance or admittance matrix (e.g.,  $Y_{22}$ ,  $Z_{11}$ ,  $Y_{44}$ ) will **always** have a real component that is **positive**.

To find the **other two** trans-admittance parameters, we must **move** the short and then **repeat** each of our previous steps!

**Step 1:** Place a short at port 1.

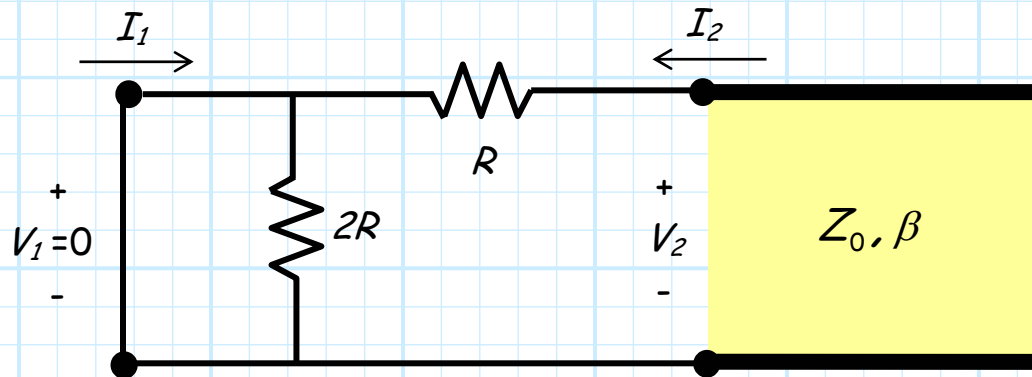

**Step 2:** Determine currents  $I_1$  and  $I_2$ .

Note that **after** a short was placed at port 1, resistor  $2R$  has **zero** voltage across it—and thus **zero** current through it!

Likewise, from KVL we find that the **voltage** across resistor  $R$  is equal to  $V_2$ .

Finally, we see from KCL that  $I_1 = I_2$ .

The current  $I_2$  thus:

$$I_2 = \frac{V_2}{R}$$

and thus:

$$I_1 = -\frac{V_2}{R}$$

**Step 3:** Determine trans-admittance  $Y_{12}$  and  $Y_{22}$ .

$$Y_{12} = \frac{I_1}{V_2} = -\frac{1}{R}$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{1}{R}$$

The **admittance** matrix of this two-port device is therefore:

$$\mathbf{y} = \frac{1}{R} \begin{bmatrix} 1.5 & -1 \\ -1 & 1 \end{bmatrix}$$

Note this device (as **you** may have suspected) is **lossy** and **reciprocal**.

**Q:** *What about the **impedance** matrix? How can we determine that?*

**A:** One way is simply determine the **inverse** of the admittance matrix above.

$$\begin{aligned} \mathbf{z} &= \mathbf{y}^{-1} \\ &= R \begin{bmatrix} 1.5 & -1 \\ -1 & 1 \end{bmatrix}^{-1} \\ &= R \begin{bmatrix} 2 & 2 \\ 2 & 3 \end{bmatrix} \end{aligned}$$



**Q:** *But I don't know how to **invert** a matrix! How can I **possibly** pass one of your long, scary, evil exams?*

**A:** **Another** way to determine the impedance matrix is simply to apply the **definition** of trans-impedance to **directly** determine the elements of the impedance matrix—**similar** to how we just determined the admittance matrix!

Specifically, follow these **steps**:

**Step 1:** Place an **open** at port 2 (or 1)

**Step 2:** Determine **voltages**  $V_1$  and  $V_2$ .

**Step 3:** Determine trans-**impedance**  $Z_{11}$  and  $Z_{21}$  (or  $Z_{12}$  and  $Z_{22}$  ).

You try this procedure on the circuit of this example, and make sure **you** get the **same** result for  $\mathcal{Z}$  as we determined on the previous page (from matrix inversion)—after all, **you** want to do **well** on my long, scary, evil **exam**!